

Chapter 3

Voltage and current laws

NODES, PATHS, LOOPS, AND BRANCHES

A node is a place where two or more elements connect

Path: a route from one node to another


Loop : closed path

Branch: a path that contains an element

No of nodes = 3

No of branches = 5

No of loops = 6

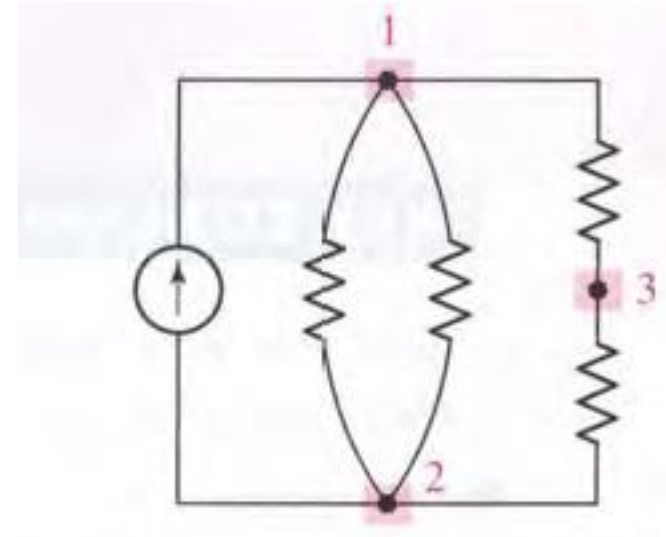

KIRCHHOFF'S CURRENT LAW


KCL

The algebraic sum of currents entering a node is equal to algebraic sum of currents leaving the same node

For any node

$$\sum i_{in} = \sum i_{out}$$

$$i_A + i_B = i_C + i_D$$

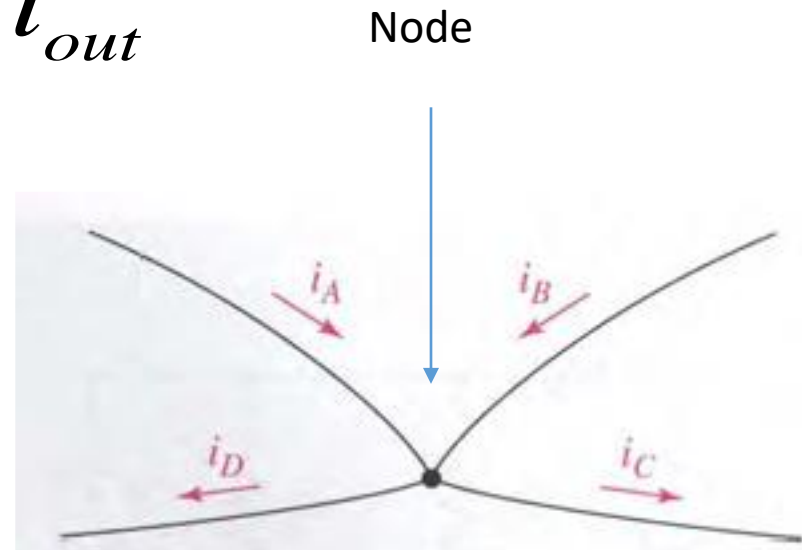


KIRCHHOFF'S VOLTAGE LAW

KVL

The algebraic sum of the voltages around any closed path is zero.

$$\sum_{n=1}^N v_n = 0$$

$$-v_1 + v_2 - v_3 = 0$$

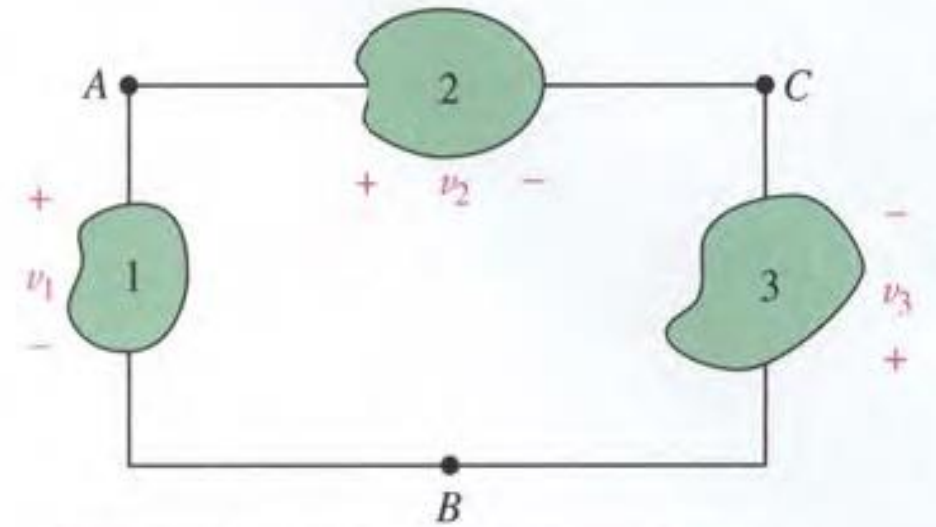


Example : Find V_x and I_x

KVL

$$-5 - 7 + v_x = 0$$

Ohms Law
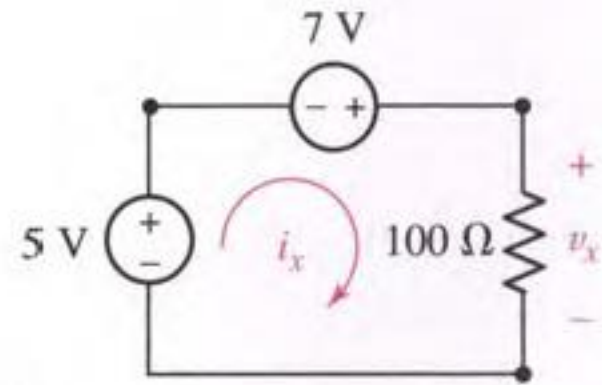
$$i_x = \frac{v_x}{100} = \frac{12}{100} \text{ A} = 120 \text{ mA}$$



Example : find V_{R2} , V_x ?

KVL at loop 1

$$4 - 36 + V_{R2} = 0$$

$$V_{R2} = 32\text{V}$$


KVL at loop 2

$$-v_{R2} + 12 + 14 + v_x = 0$$

$$-32 + 12 + 14 + v_x = 0$$

$$-6 + v_x = 0$$

$$v_x = 6\text{V}$$

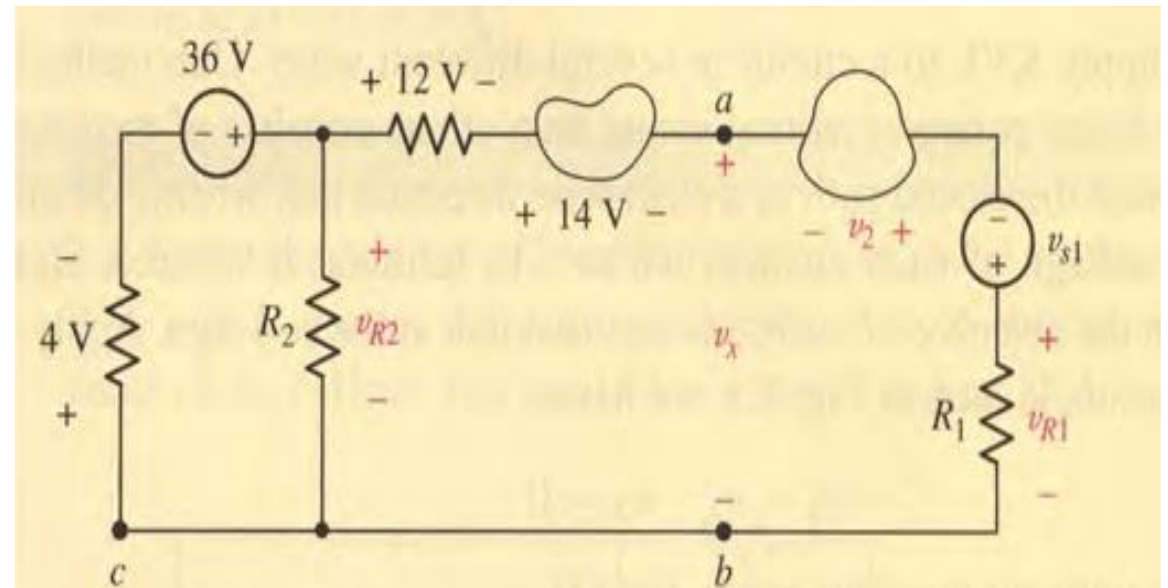

Find V_x in the following circuit

KVL at loop 1

$$-60 + v_8 + v_{10} = 0$$

$$-60 + 5(8) + v_{10} = 0$$

$$-60 + 40 + v_{10} = 0$$

$$v_{10} = 20v$$

KCL at node 1

$$5 = i_4 + i_{10}$$

$$i_{10} = \frac{v_{10}}{10} = \frac{20}{10} = 2A$$

$$5 = i_4 + 2$$

$$i_4 = 3A$$



KVL at loop 2

$$-v_{10} + v_4 + v_x = 0$$


$$v_4 = i_4(4) = 3(4) = 12v$$

$$-20 + 12 + v_x = 0$$

$$v_x = 8v$$

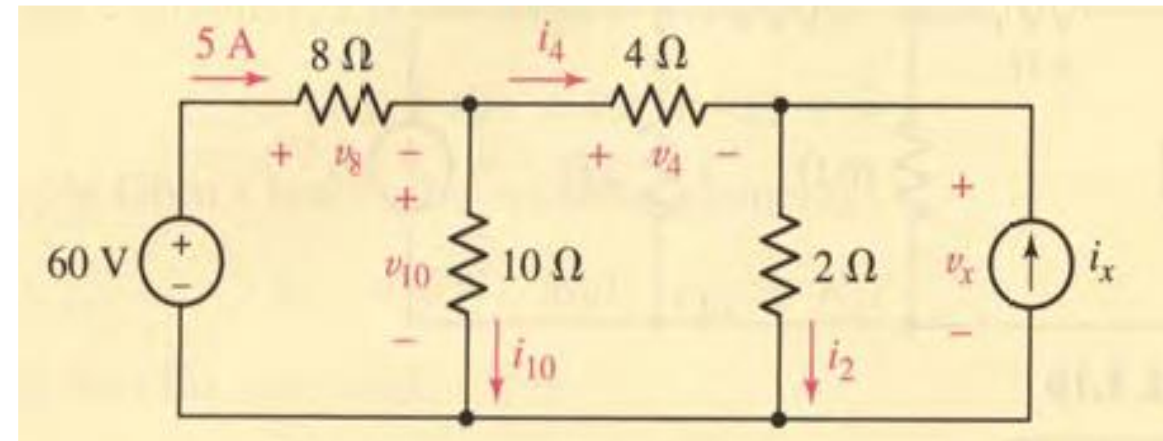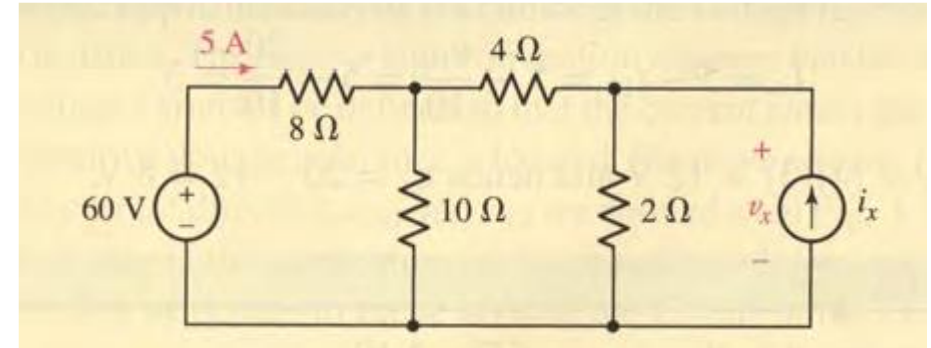

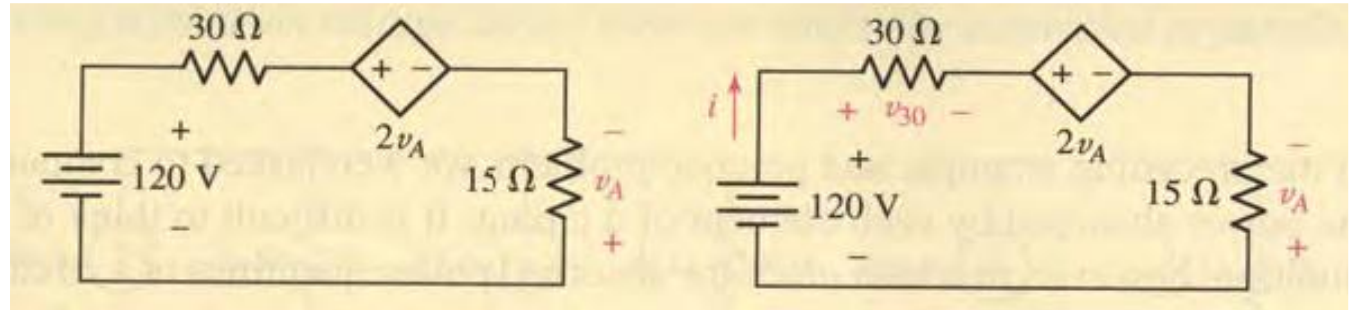Find power of each element in the following circuit



applying KVL around the loop:

$$-120 + v_{30} + 2v_A - v_A = 0$$

Using Ohm's law to introduce the known resistor values:

$$v_{30} = 30i \quad \text{and} \quad v_A = -15i$$

Note that the negative sign is required since i flows into the negative terminal of v_A .

Substituting into Eq. [7] yields

$$-120 + 30i - 30i + 15i = 0$$

and so we find that

$$i = 8 \text{ A}$$

Computing the power *absorbed* by each element:



$$p_{120\text{V}} = (120)(-8) = -960 \text{ W}$$

$$p_{30\Omega} = (8)^2(30) = 1920 \text{ W}$$

$$\begin{aligned} p_{\text{dep}} &= (2v_A)(8) = 2[(-15)(8)](8) \\ &= -1920 \text{ W} \end{aligned}$$

$$p_{15\Omega} = (8)^2(15) = 960 \text{ W}$$

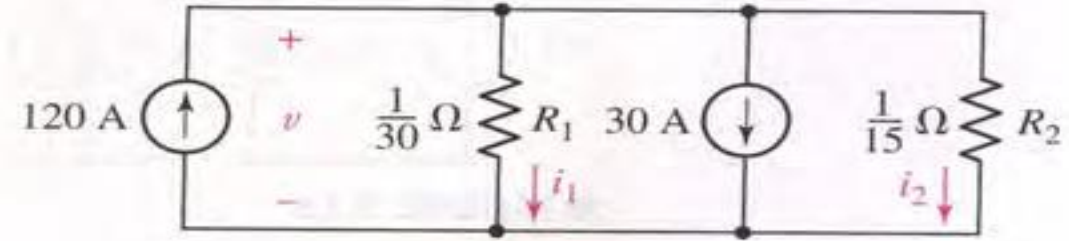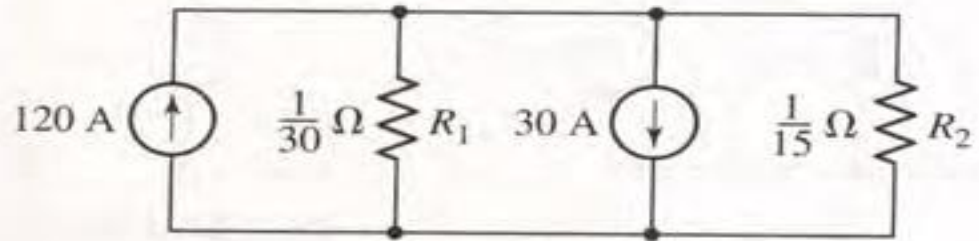Find power of each element in the following circuit



$$-120 + i_1 + 30 + i_2 = 0$$

Writing both currents in terms of the voltage v using Ohm's law,

$$i_1 = 30v \quad \text{and} \quad i_2 = 15v$$

we obtain

$$-120 + 30v + 30 + 15v = 0$$

Solving this equation for v results in

$$v = 2 \text{ V}$$

and invoking Ohm's law then gives

$$i_1 = 60 \text{ A} \quad \text{and} \quad i_2 = 30 \text{ A}$$

The absorbed power in each element can now be computed. In the two resistors,


$$p_{R1} = 30(2)^2 = 120 \text{ W} \quad \text{and} \quad p_{R2} = 15(2)^2 = 60 \text{ W}$$

and for the two sources,

$$p_{120\text{A}} = 120(-2) = -240 \text{ W} \quad \text{and} \quad p_{30\text{A}} = 30(2) = 60 \text{ W}$$


Since the 120 A source absorbs negative 240 W, it is actually *supplying* power to the other elements in the circuit. In a similar fashion, we find that the 30 A source is actually *absorbing* power rather than *supplying* it.

SERIES AND PARALLEL CONNECTED SOURCES

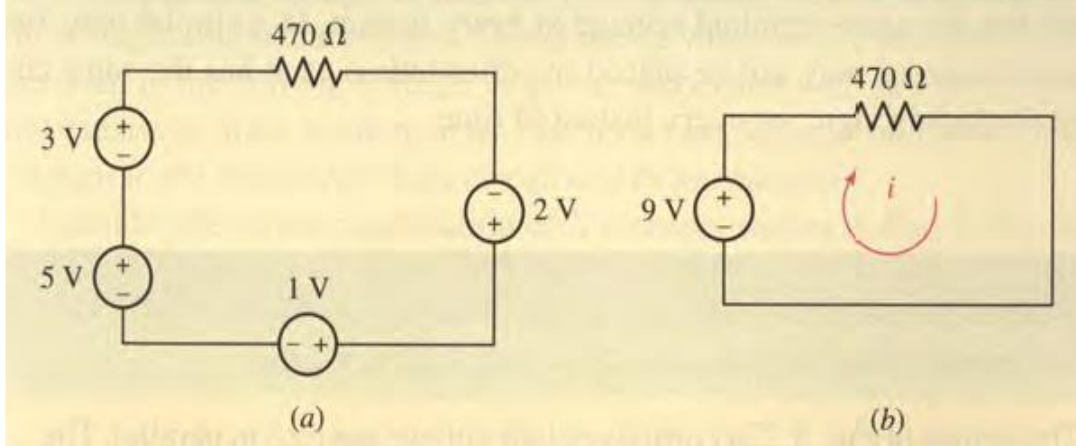

$$+3 + 5 - 1 + 2 = 9\text{ V}$$

$$i = \frac{9}{470} = 19.15\text{ mA}$$

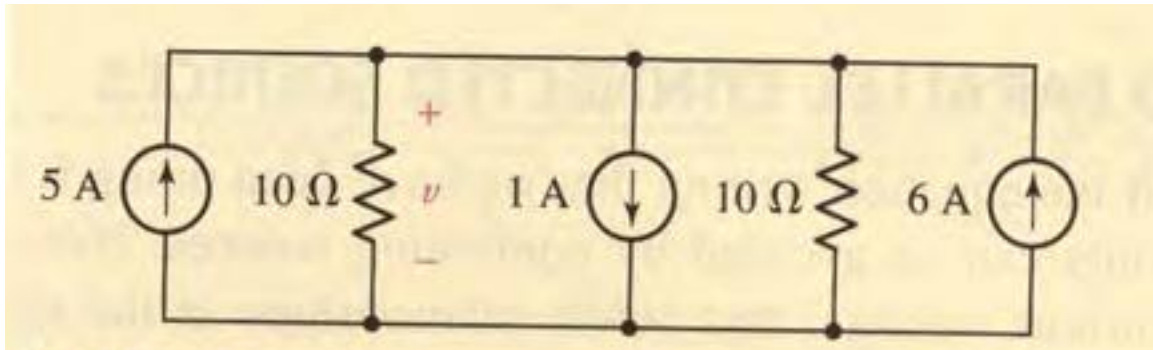

$$I_T = 5 - 1 + 6 = 10\text{ A}$$

$$R_t = 5\ \Omega$$

$$V = I_T \cdot R_t = 10 * 5 = 50\text{ v}$$

