
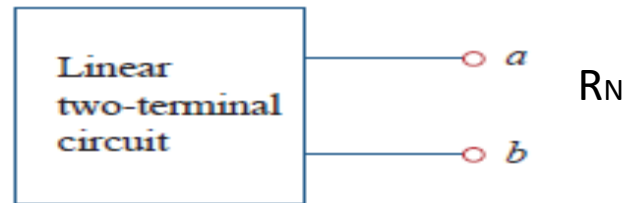
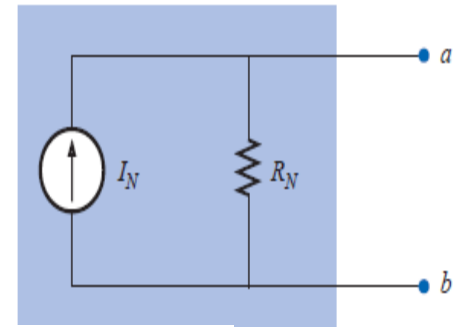



Chapter 5

Circuit Analysis Techniques **Norton Theorem**

NORTON'S THEOREM


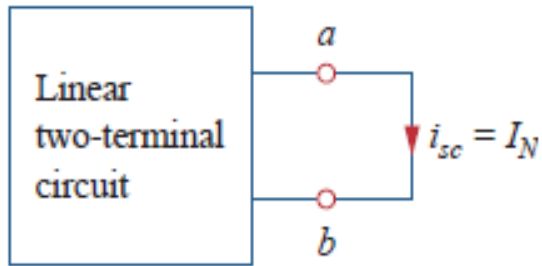


Source transformation

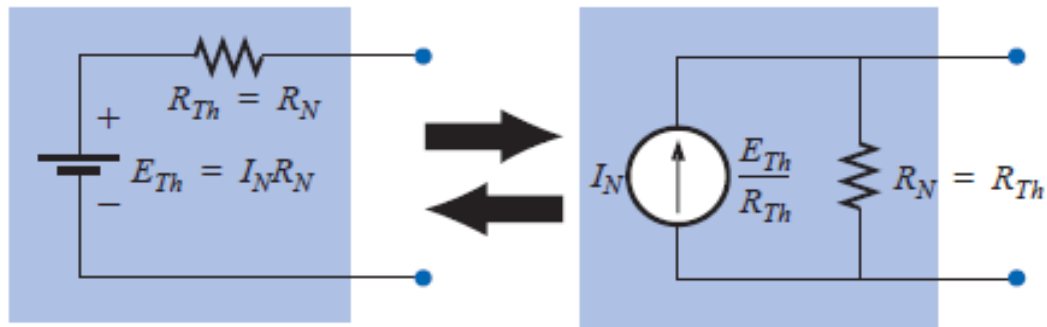

If we have dependent source


Find Norton equivalent seen by R_L

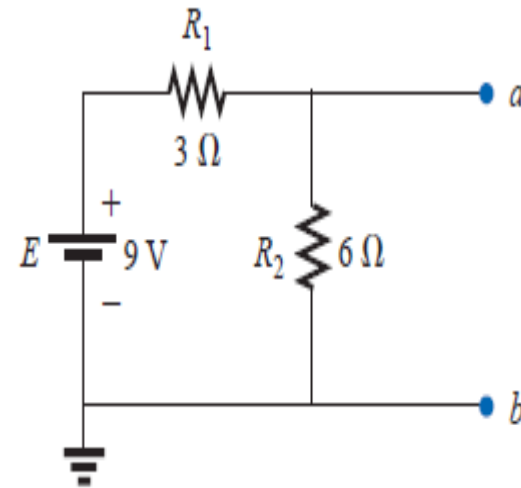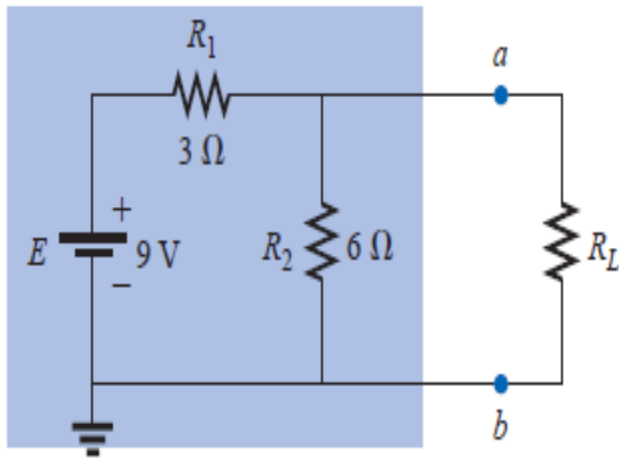


$$V_{Th} = U_{oc}$$

$$I_N = i_{sc}$$


$$R_{Th} = \frac{U_{oc}}{i_{sc}} = R_N$$

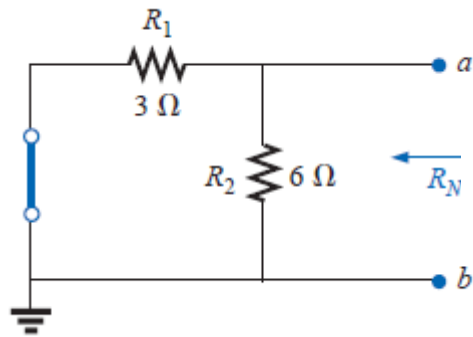



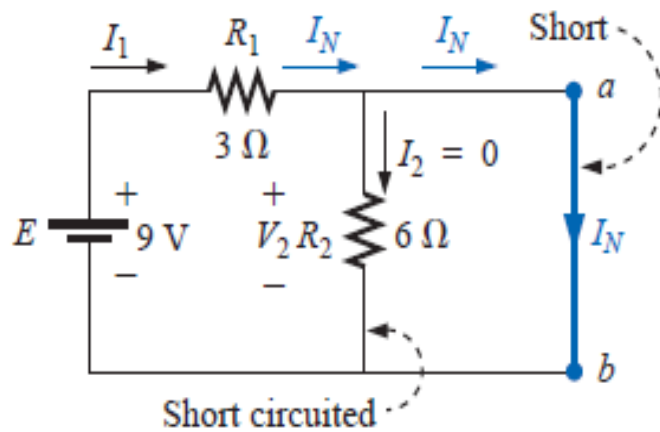
$$R_N = R_1 \parallel R_2 = 3 \Omega \parallel 6 \Omega = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 6 \Omega} = \frac{18 \Omega}{9} = 2 \Omega$$


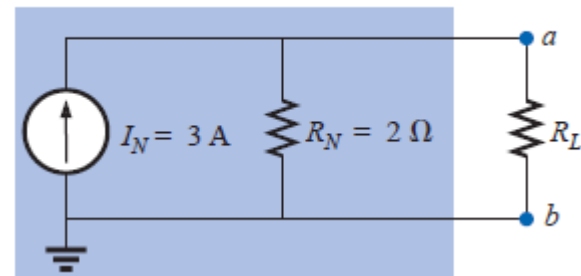
$$I_N = \frac{E}{R_1} = \frac{9 \text{ V}}{3 \Omega} = 3 \text{ A}$$




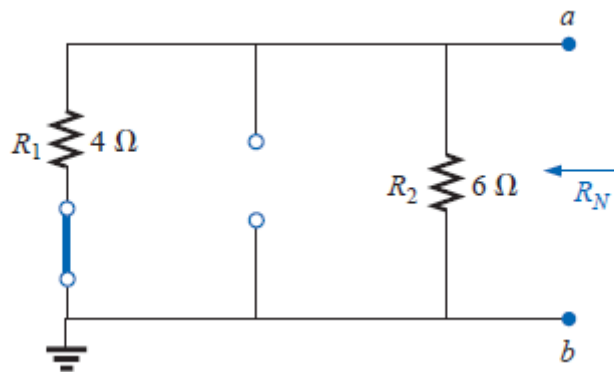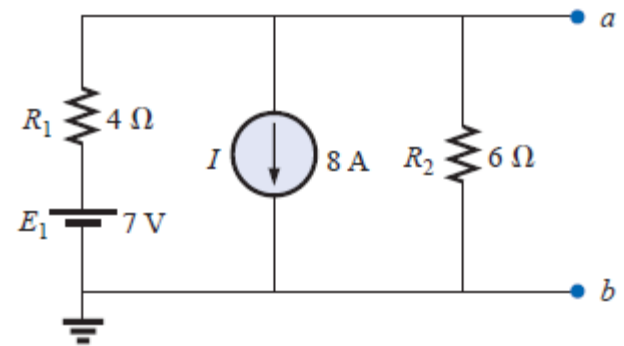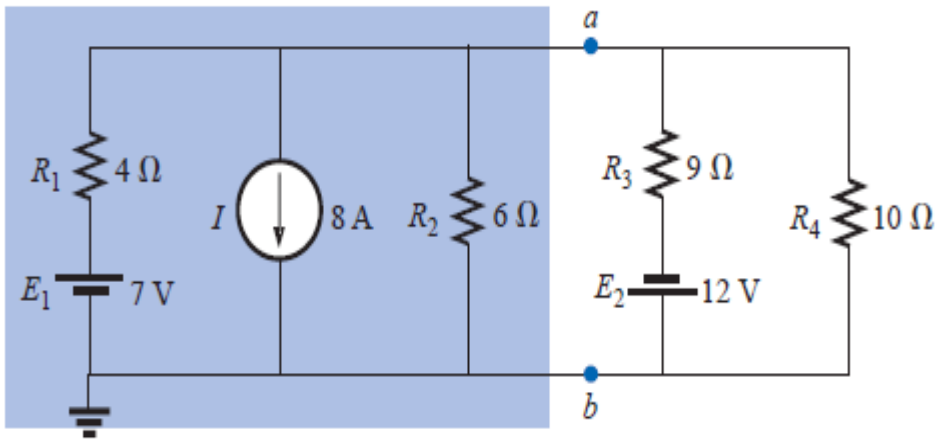Find Norton equivalent seen by a and b to the left



$$R_N = R_1 \parallel R_2 = 4 \Omega \parallel 6 \Omega = \frac{(4 \Omega)(6 \Omega)}{4 \Omega + 6 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$



Using superposition

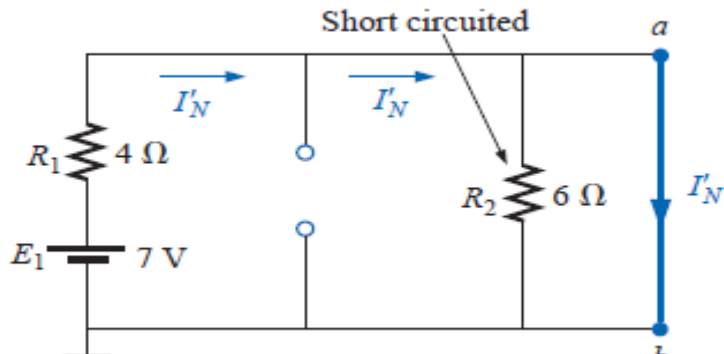


$$I'_N = \frac{E_1}{R_1} = \frac{7 \text{ V}}{4 \Omega} = 1.75 \text{ A}$$

$$I''_N = I = 8 \text{ A}$$
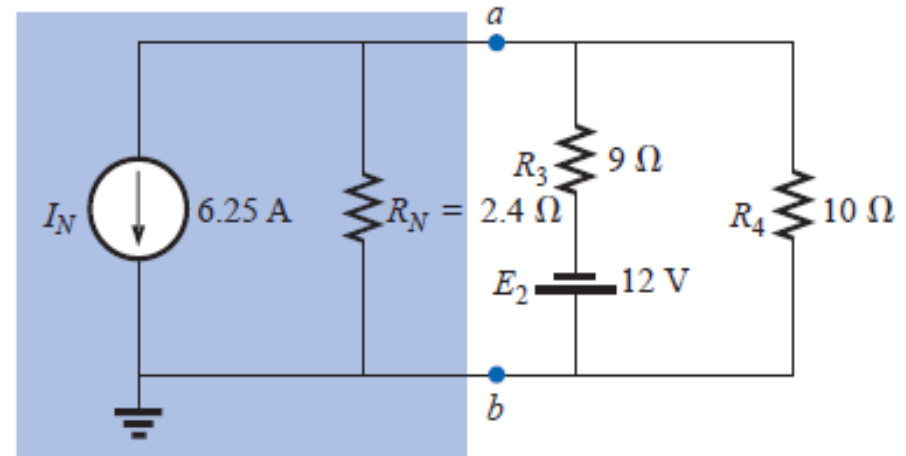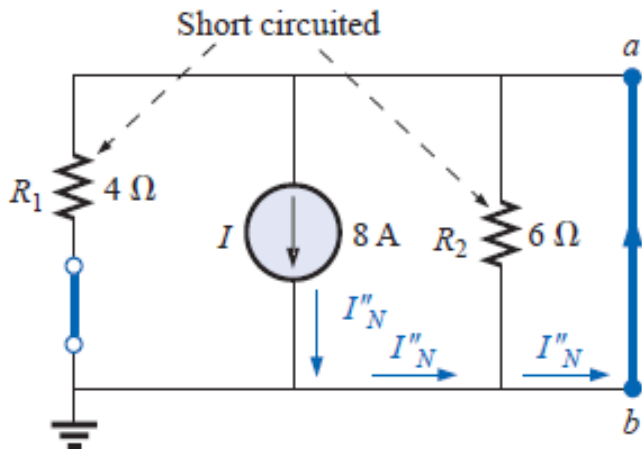
$$I_N = I''_N - I'_N = 8 \text{ A} - 1.75 \text{ A} = 6.25 \text{ A}$$




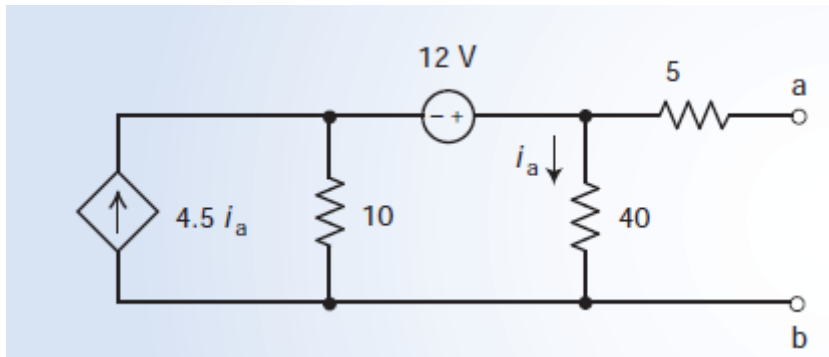Find thevenin equivalent seen by terminals a and b



Solution : Since we have dependent source

$$R_{th} = \frac{V_{o.c}}{I_{s.c}}$$

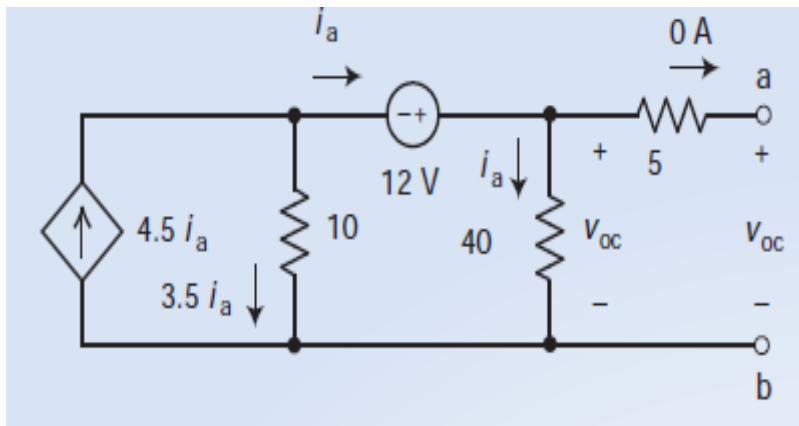


$$i_a = \frac{V_{oc}}{40}$$

KVL

$$0 = -12 + v_{oc} - 10(3.5i_a)$$

$$v_{oc} = 96 \text{ V}$$

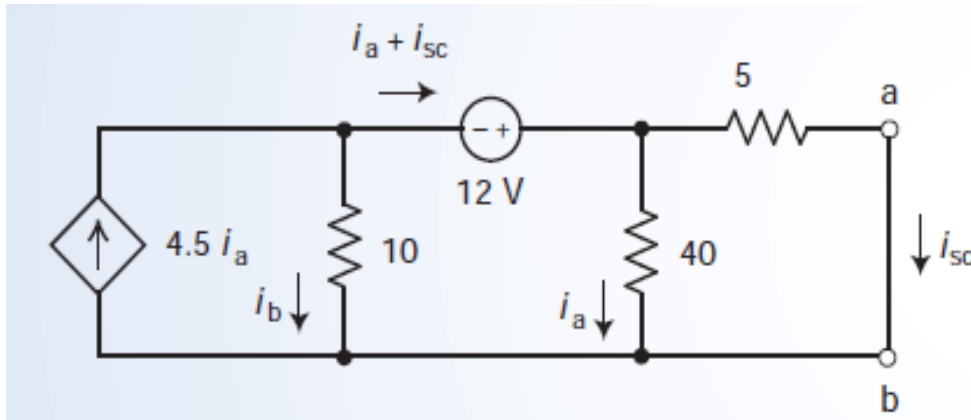

$$R_{th} = \frac{V_{o.c}}{I_{s.c}} = \frac{96}{1.1294} = 85\ \Omega$$

KVL at loop 1

$$5i_{sc} - 40i_a = 0 \Rightarrow i_a = \frac{i_{sc}}{8}$$

KCL at Node 1

$$4.5i_a = i_b + (i_a + i_{sc}) \Rightarrow i_b = 3.5i_a - i_{sc} = -\frac{9}{16}i_{sc}$$

KVL at loop2

$$-12 + 5i_{sc} - 10\left(-\frac{9}{16}i_{sc}\right) = 0$$

$$i_{sc} = \frac{12}{5 + \frac{90}{16}} = 1.1294 \text{ A}$$

