

Chapter 5

**Circuit Analysis Techniques
Maximum power transfer
And delta wye conversion**

Maximum Power Transfer


Applicable on Thevenin or Norton circuits

Maximum power occurs for R if

$$R = R_{th} = R_N$$

$$i = \frac{V_{th}}{R_{th} + R} = \frac{V_{th}}{R_{th} + R_{th}} = \frac{V_{th}}{2 \cdot R_{th}}$$


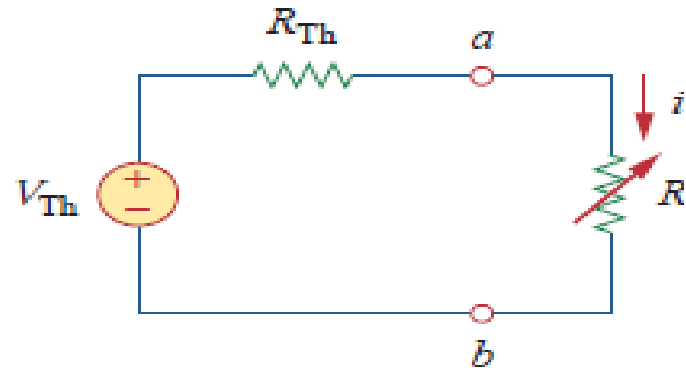
$$P_{\max} = i^2 \cdot R = \left(\frac{V_{th}}{2 \cdot R_{th}} \right)^2 \cdot R_{th} = \frac{V_{th}^2}{4 \cdot R_{th}}$$




For Norton when $R_L = R_N$

$$i = \frac{i_s}{2}$$
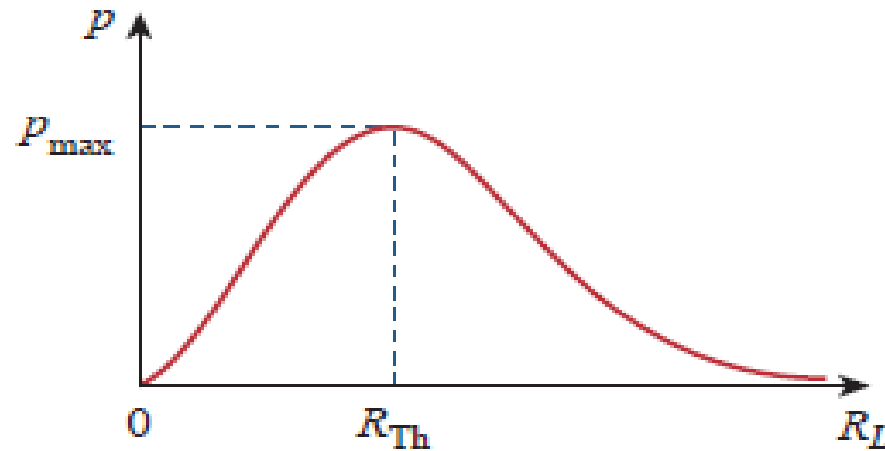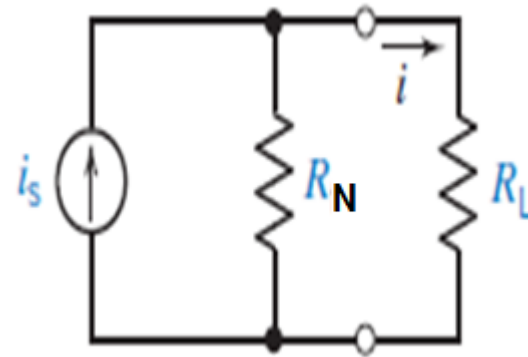
$$P_{\max} = i^2 \cdot R_L = \left(\frac{i_s}{2}\right)^2 R_N = \frac{i_s^2 \cdot R_N}{4}$$




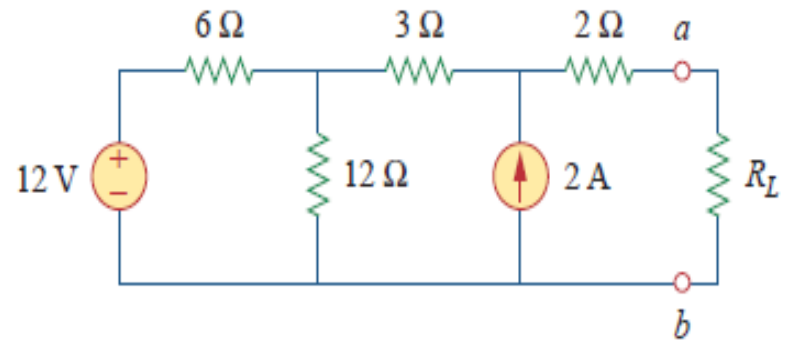Find the value of R_L for maximum power and find value of maximum power




First we have to find Thevenin
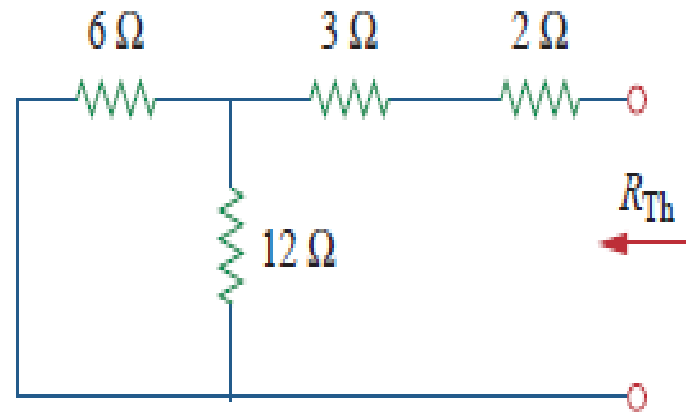
$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



Mesh Analysis

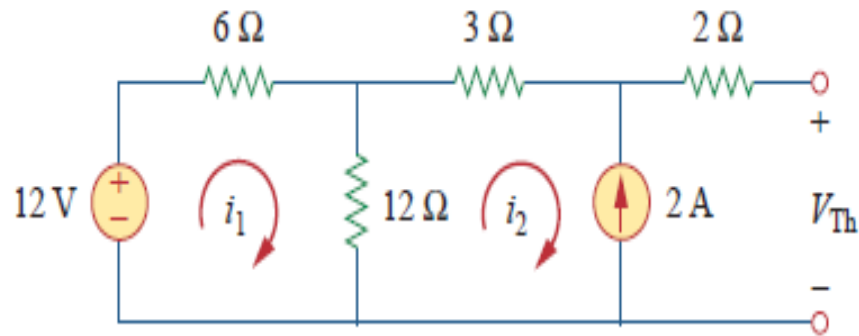

$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A}$$

$$\therefore i_1 = -2/3.$$

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0$$

$$\Rightarrow V_{Th} = 22 \text{ V}$$


For maximum power transfer,

$$R_L = R_{Th} = 9 \Omega$$


and the maximum power is

$$P_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

Y- Δ (T- π) AND Δ -Y (π -T) CONVERSIONS

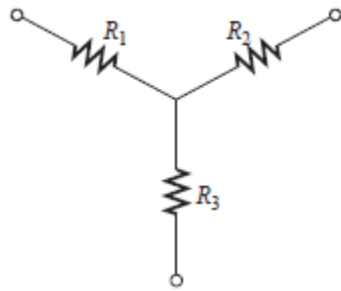


“ Y ”

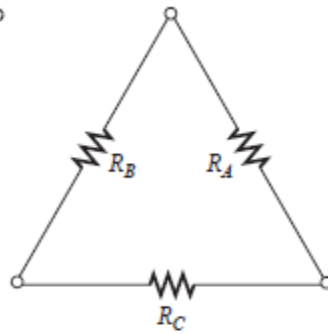


“ Δ ”

(a)

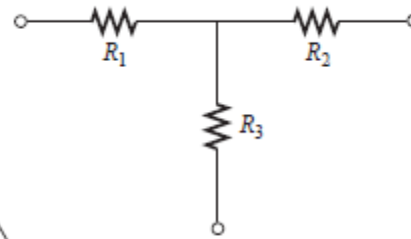


“ T ”

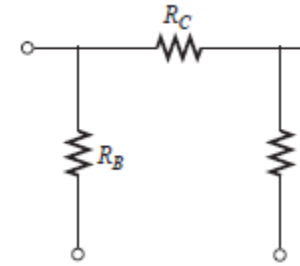

“ π ”

(b)

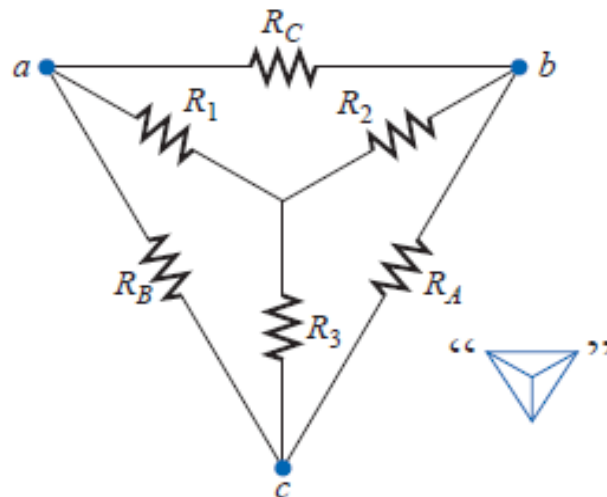

“ Y ”


From delta to Y

$$\Delta = R_A + R_B + R_C$$

$$R_1 = \frac{R_B \cdot R_C}{\Delta}$$

$$R_2 = \frac{R_A \cdot R_C}{\Delta}$$

$$R_3 = \frac{R_A \cdot R_B}{\Delta}$$

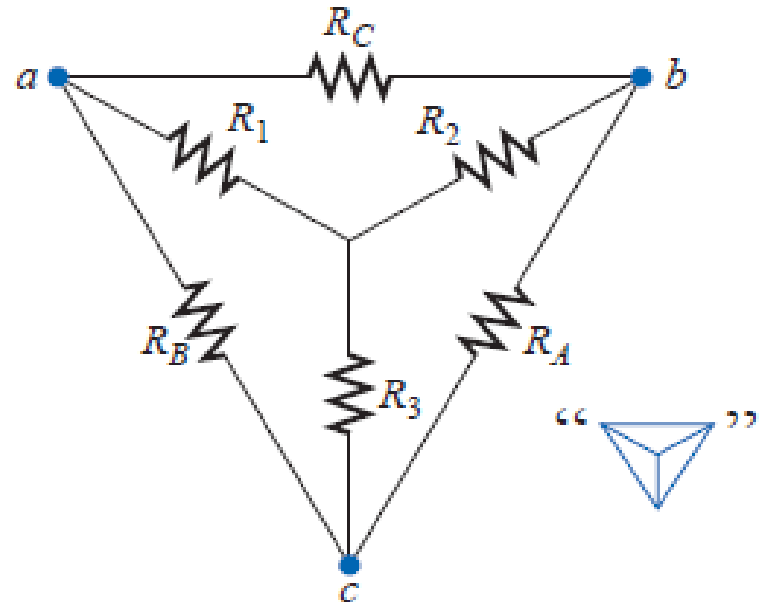


From Y to Delta

$$Y = R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1$$

$$R_A = \frac{Y}{R_1}$$

$$R_B = \frac{Y}{R_2}$$

$$R_c = \frac{Y}{R_3}$$


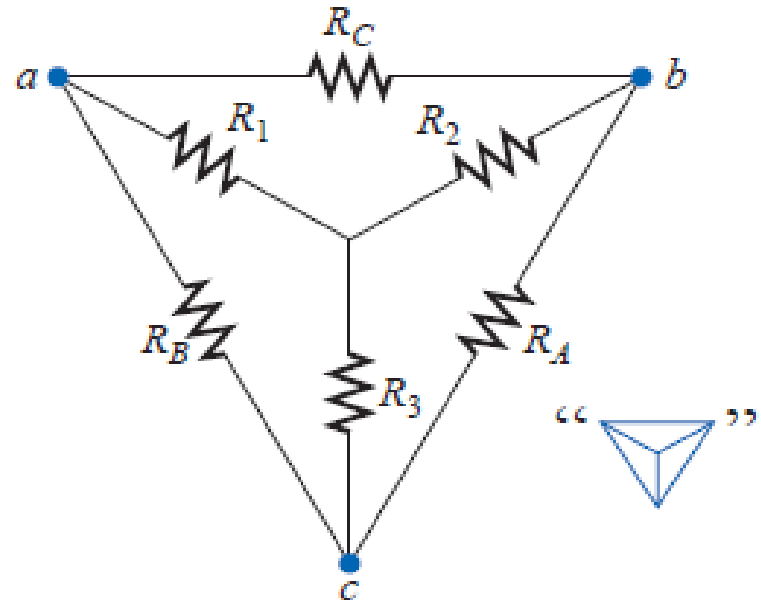


$$\Delta = 6 + 3 + 3 = 12$$

$$R_1 = \frac{6(3)}{12} = \frac{18}{12} = 1.5\Omega$$

$$R_2 = \frac{6(3)}{12} = \frac{18}{12} = 1.5\Omega$$
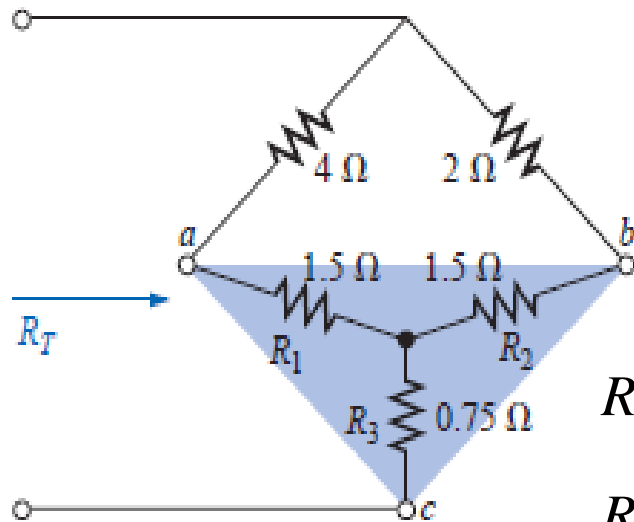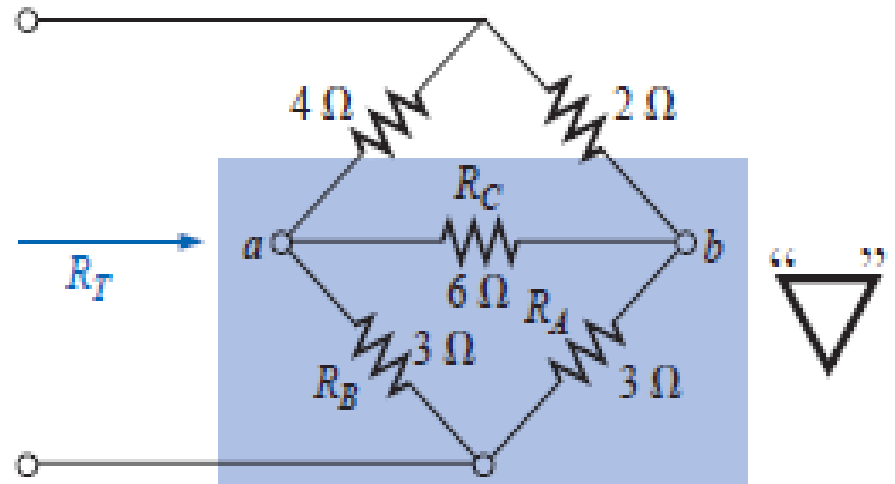
$$R_3 = \frac{3(3)}{12} = \frac{9}{12} = 0.75\Omega$$




$$R_T = \frac{3.5(5.5)}{3.5 + 5.5} + 0.75$$

$$R_T = 2.889\Omega$$

Balanced case

$$R_Y = \frac{R_\Delta}{3}$$

$$R_\Delta = 3R_Y$$

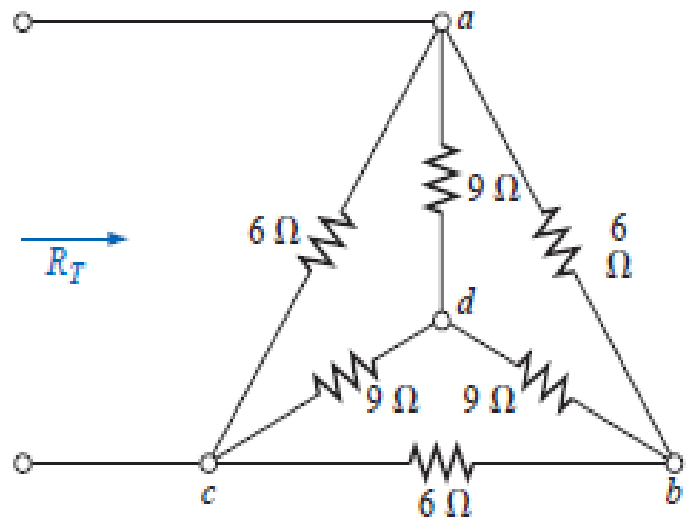

$$R_Y = \frac{R_\Delta}{3} = \frac{6\ \Omega}{3} = 2\ \Omega$$

