

Chapter 8

Basic RL and RC circuits

The Source-Free RC Circuit


This is a circuit without source

We assume that the capacitor is fully charged to V_0

$$v(t) = v_0 \cdot e^{\frac{-t}{\tau}}$$

$$v_0 = v(0) \quad \text{Initial voltage}$$
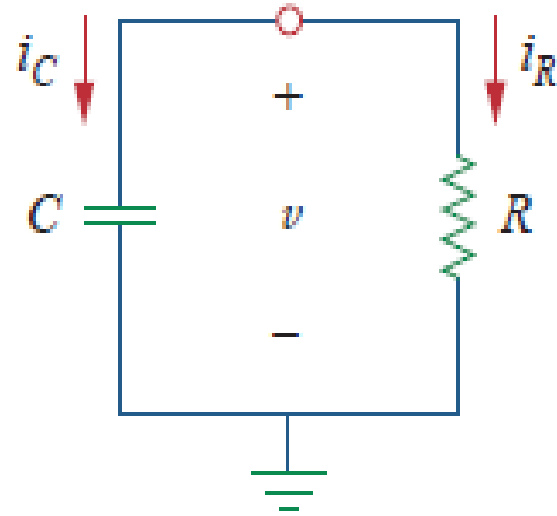
$$\tau = R.C \quad \text{Time constant}$$



$$i_c(t) = C \frac{dv(t)}{dt} = C \frac{d(v_o \cdot e^{\frac{-t}{\tau}})}{dt}$$

$$i_c(t) = C \cdot v_o \cdot \frac{-1}{\tau} \cdot e^{\frac{-t}{\tau}} = -C \cdot v_o \frac{1}{R \cdot C} \cdot e^{\frac{-t}{\tau}} = -\frac{v_o}{R} \cdot e^{\frac{-t}{\tau}}$$

$$i_c(t) = I_o \cdot e^{\frac{-t}{\tau}}$$


$$i_R(t) = -i_c(t) = \frac{v(t)}{R} = \frac{v_o}{R} \cdot e^{\frac{-t}{\tau}}$$


The **natural response** of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.

The **time constant** of a circuit is the time required for the response to decay to a factor of $1/e$ or 36.8 percent of its initial value.¹

Response after τ
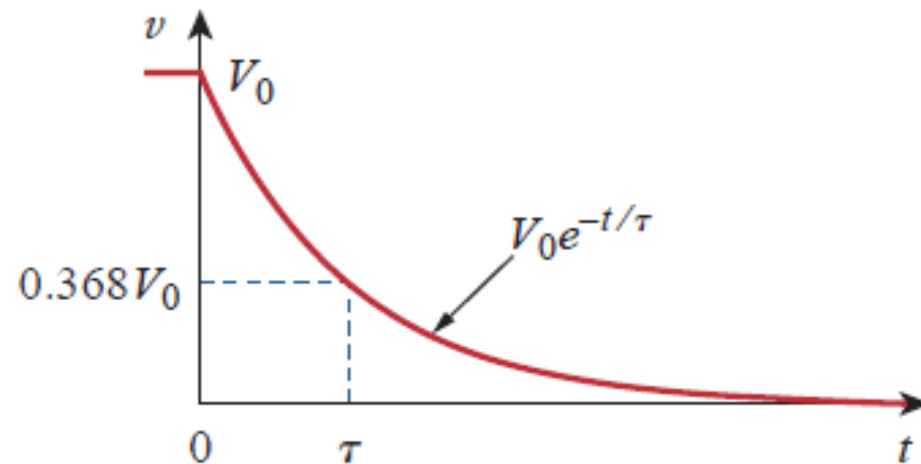
$$V_0 e^{-\tau/RC} = V_0 e^{-1} = 0.368V_0$$



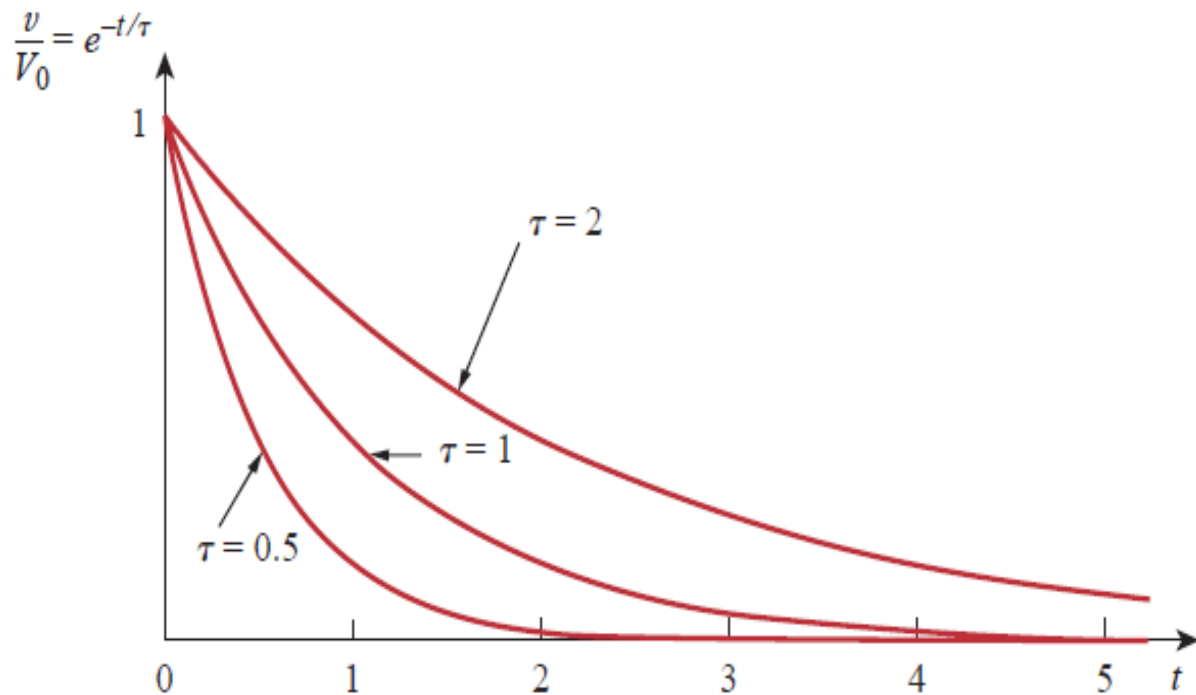

The Key to Working with a Source-free *RC* Circuit Is Finding:



1. The initial voltage $v(0) = V_0$ across the capacitor.
2. The time constant τ .

R: is the thevenin resistance computed at the terminals of the capacitor

let $v_C(0) = 15$ V. Find v_C , v_x , and i_x for $t > 0$.

$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$
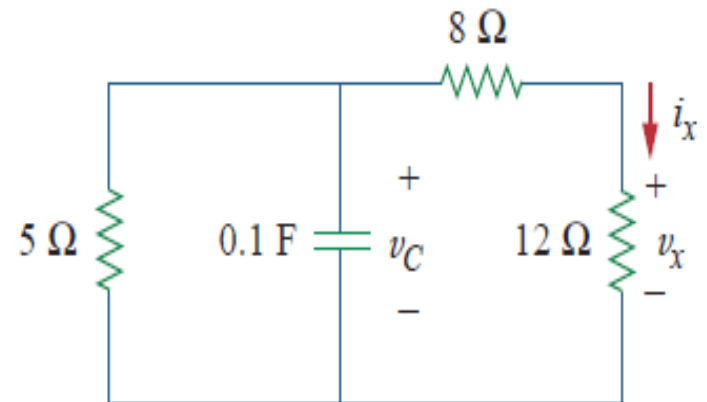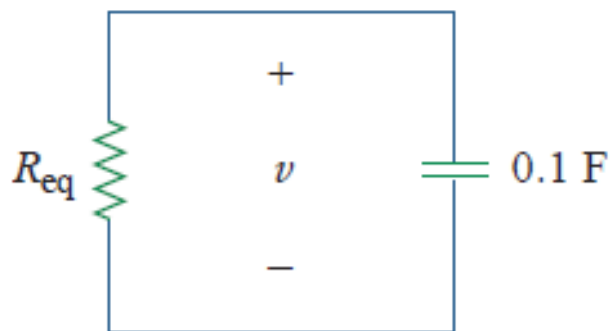
$$\tau = R_{\text{eq}}C = 4(0.1) = 0.4 \text{ s}$$



$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}, \quad v_C = v = 15e^{-2.5t} \text{ V}$$

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$

The Source-Free RL Circuit

$$i(t) = I_0 e^{-t/\tau}$$



$$\tau = \frac{L}{R}$$

$$v_R(t) = iR = I_0 R e^{-t/\tau}$$

$$V_L(t) = -V_R(t) = -I_0 R e^{-t/\tau}$$

$$V_L(t) = V_0 e^{-t/\tau}$$

$$V_0 = -I_0 R$$

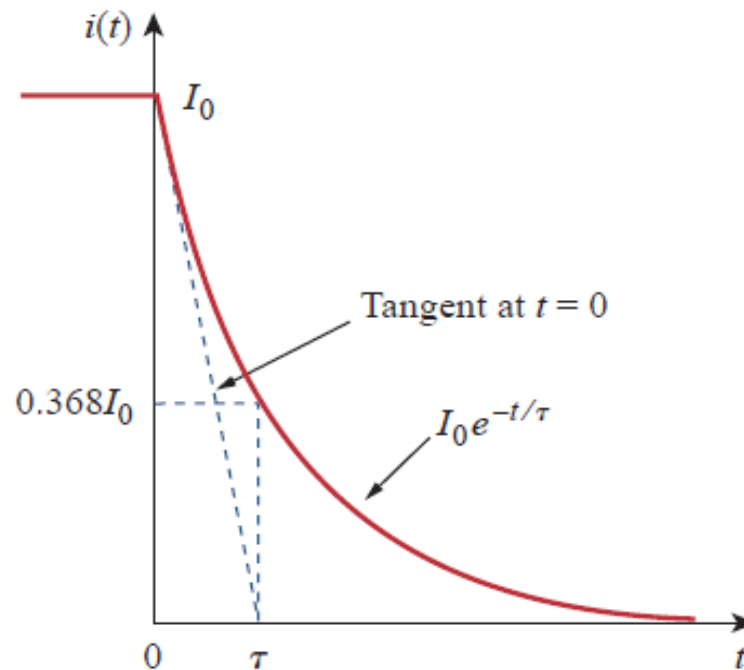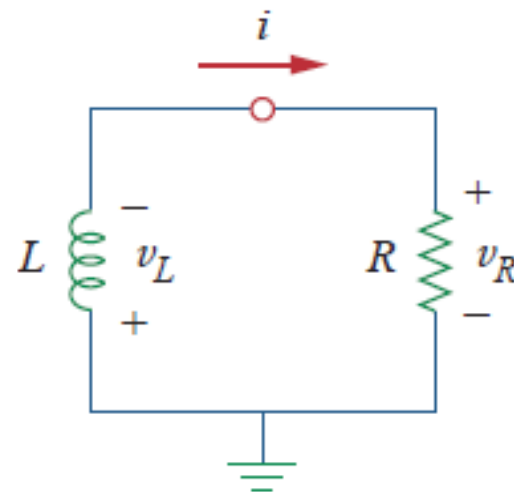

The Key to Working with a Source-free RL Circuit Is to Find:


1. The initial current $i(0) = I_0$ through the inductor.
2. The time constant τ of the circuit.

Find V , \dot{I}_L for $t \geq 0$

$$R_T = 10 + 40 = 50\Omega \rightarrow \tau = \frac{L}{R_T} = \frac{5}{50} = \frac{1}{10} \text{ s}$$

$$I_L(t) = 2.4e^{\frac{-t}{\tau}} = 2.4e^{-10t}$$

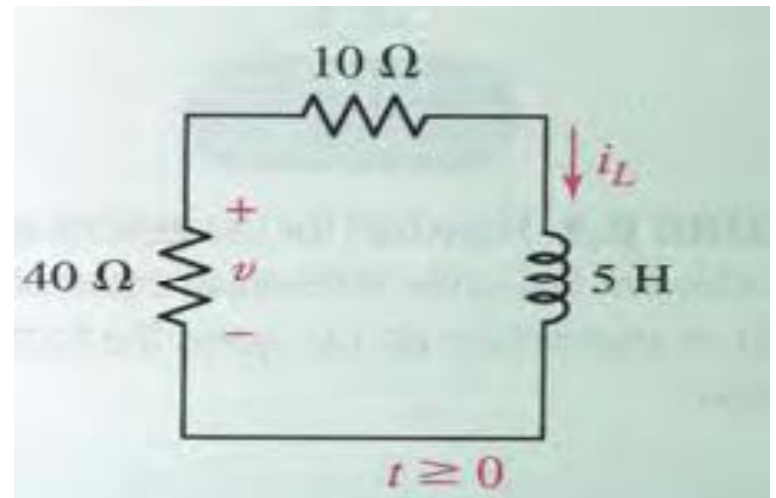
$$V_{40\Omega} = -2.4(40).e^{-10t} = -96.e^{-10t}$$




$$I_0 = 2.4 \text{ A}$$

Switches

2-port switch

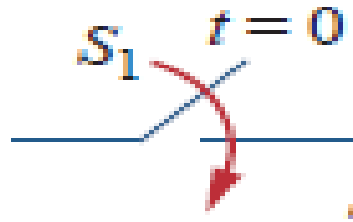


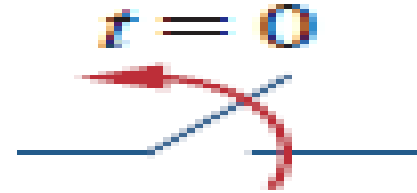$t > 0$ switch is closed
 $t < 0$ switch is open



$t > 0$ switch is open
 $t < 0$ switch is closed

3-port switch

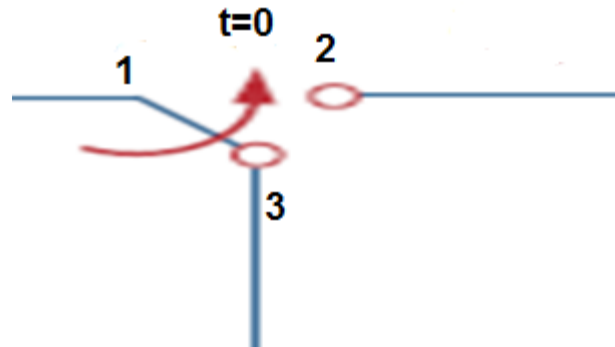

$t < 0$ select 3

$t > 0$ select 2