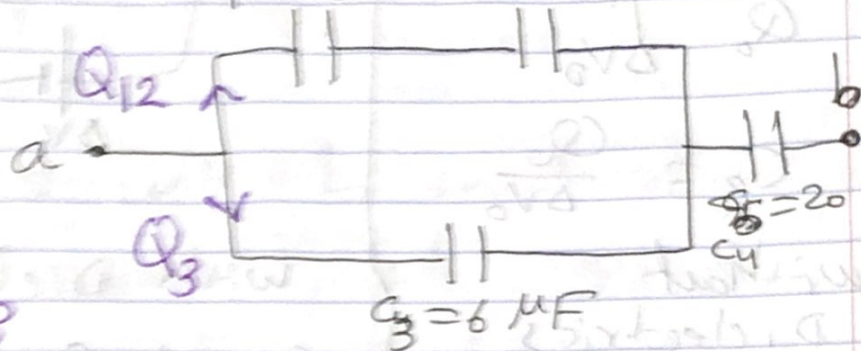


problems on ch 26

- 23 Four capacitors are connected as shown in Figure
- 802 (a) Find the equivalent capacitance between a and b
- (b) calculate the charge on each capacitor taking $\Delta V_{ab} = 15 \text{ V}$

$$C_1 = 15 \mu\text{F} \quad C_2 = 3 \mu\text{F}$$



① $C_{eq} = ?$

$$(15, 3) \xrightarrow{S} \frac{15 \times 3}{15 + 3} = 2.5 \mu\text{F} = C_{12}$$

$$(2.5, 6) \xrightarrow{P} C_{eq} = 2.5 + 6 = 8.5 \mu\text{F}$$

$$C_{eq} = 8.5 \mu\text{F}$$

② $V_3 = V_{ab} = 15 \text{ volt}$

$$\rightarrow Q_3 = V_3 \cdot C_3$$

$$= 15 \times 6 = 90 \mu\text{C}$$

$$\rightarrow V_{12} = V_{ab} = 15 \text{ Volt}$$

$$\rightarrow Q_{12} = V_{12} \cdot C_{12}$$

①

$$Q_{12} = 2.5 \times 15 \\ = 37.5 \mu\text{C}$$

$$\rightarrow Q_1 = Q_2 = 37.5 \mu\text{C}$$

$$\rightarrow V_1 = \frac{Q_1}{C_1} = \frac{37.5}{15} = 2.5 \text{ Volt}$$

$$\rightarrow V_2 = \frac{Q_2}{C_2} = \frac{37.5}{3} = 12.5 \text{ Volt}$$

21 | A group of N identical capacitors
802 | is connected first in series and
then in parallel. The combined
capacitance in parallel is 100 times
larger than for the series connection.
How many capacitors are in the group.

Series

$$C_{eq} = \frac{C}{N}$$

Parallel

$$C_{eq} = NC$$

$$C_{eq \text{ parallel}} = 100 C_{eq \text{ series}}$$

$$NC = 100 \left(\frac{C}{N} \right)$$

$$N^2 = 100$$

$$N = 10$$


②

26

802

Find

- ① C_{eq}
- ② Q on each
- ③ ΔV on each

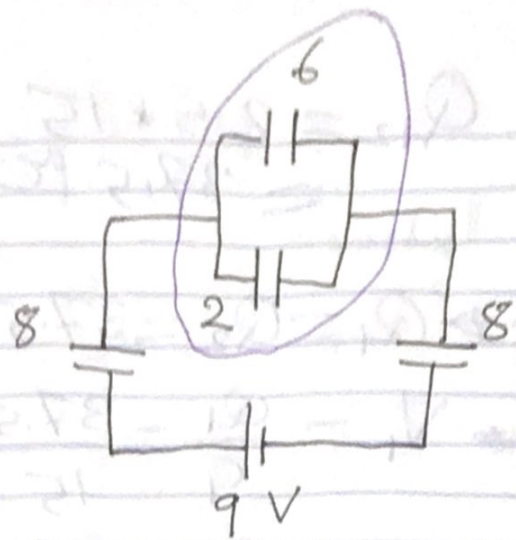

1] $(6, 2) \rightarrow P \quad 6+2=8$

$(8, 8, 8) \rightarrow S \quad \frac{1}{C_{eq}} = \frac{1}{8} + \frac{1}{8} + \frac{1}{8}$

$\rightarrow C_{eq} = \frac{8}{3} \text{ MF}$

2] $Q_T = C_{eq} \cdot \Delta V$
 $= \frac{8}{3} \times 9 = 24 \text{ } \mu\text{E}$

$Q_8 = 24 \text{ } \mu\text{E}$

$\Delta V_8 = \frac{Q}{C} = \frac{24}{8} = 3\text{V}$

$\Delta V_2 = \Delta V_6 = 3 \text{ Volts}$

$Q_2 = (\Delta V)(C)$
 $= 3 \times 2 = 6 \text{ } \mu\text{E}$

$Q_6 = (\Delta V)(C)$
 $= 3 \times 6 = 18 \text{ } \mu\text{E}$

③ ⑤

31) A 12 volt battery is connected to a capacitor resulting in $54 \mu\text{C}$ of charge stored on the capacitor.

- (a) How much energy stored in the capacitor
 (b) What is the capacitance

$$\Delta V = 12 \quad Q = 54 \mu\text{C}$$

~~$$U = \frac{1}{2} \cdot \frac{Q^2}{\Delta V} = \frac{1}{2} \cdot \frac{(54 \times 10^{-6})^2}{12}$$

$$U = \frac{1}{2} \cdot \frac{Q}{\Delta V} \Delta V^2$$~~

$$\begin{aligned}
 1) \quad U &= \frac{1}{2} \cdot Q \cdot \Delta V \\
 &= \frac{1}{2} \cdot 54 \times 10^{-6} \times 12 \\
 &= 324 \times 10^{-6} \text{ J} = 324 \mu\text{J}
 \end{aligned}$$

$$2) \quad C = \frac{Q}{\Delta V} = \frac{54 \times 10^{-6}}{12} = 4.5 \text{ } \mu\text{F}$$

3) If the battery is removed and dielectric constant of $K=5$ is inserted between the plates

Calculate

$$① \quad C = K C_0 = 5 \times 4.5 = 22.5 \mu\text{F}$$

$$② \quad Q = Q_0 = 54 \mu\text{C}$$

$$③ \quad \Delta V = \frac{\Delta V_0}{K} = \frac{12}{5} = 2.4 \text{ volt}$$


$$④ \quad U = \frac{U_0}{K} = \frac{324}{5} = 64.8 \mu\text{J}$$

4

EX 26
788

Two 9. V
capacitors

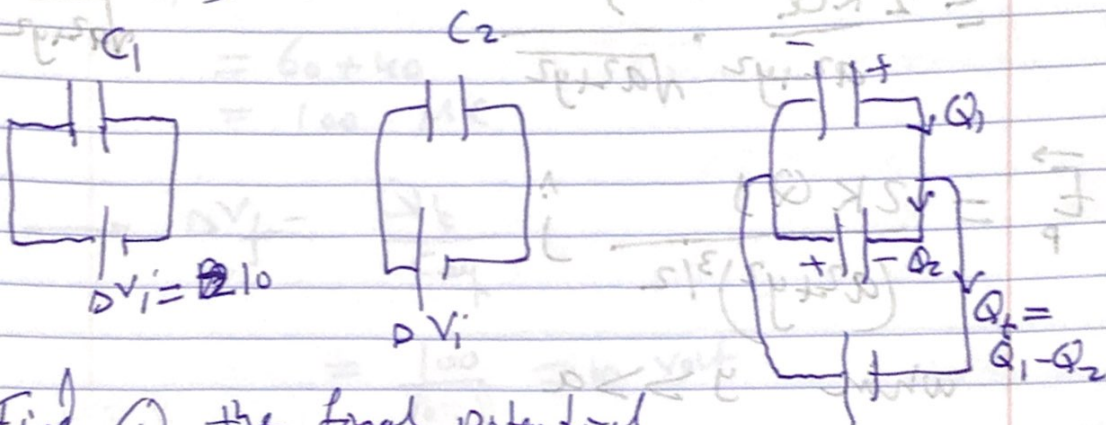Two capacitors C_1 and C_2 where $C_1 = 6 \mu F$, $C_2 = 4 \mu F$ are charged to the same initial potential difference $\Delta V_i = 10$ volt. The charged capacitors are removed from the battery and their plates are connected with opposite polarity, find as in Figure



Find (1) the final potential difference $\Delta V_f = ??$ $\Delta V_f = ??$

$$Q_1 = C_1 \cdot \Delta V_i = 6 \times 10 = 60 \mu C$$

$$Q_2 = C_2 \cdot \Delta V_i = 4 \times 10 = 40 \mu C$$

$$C_{eq} = C_1 + C_2 = 6 + 4 = 10 \mu F$$

$$Q_t = Q_1 - Q_2 = 60 - 40 = 20 \mu C$$

$$\Delta V_f = \frac{Q_t}{C_{eq}} = \frac{20}{10} = 2 \text{ volt.}$$

$$Q_1' = \Delta V_f \cdot C_1 = 2 \times 6 = 12 \mu C$$

$$Q_2' = \Delta V_f \cdot C_2 = 2 \times 4 = 8 \mu C$$

(5)