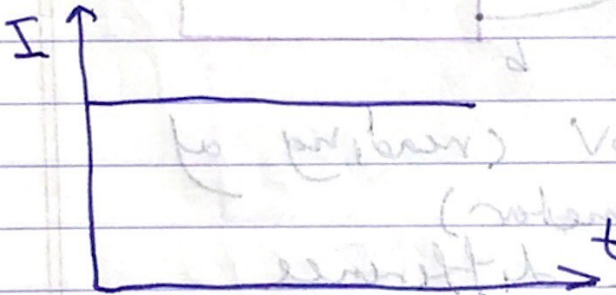


Chapter 28

Direct-Current Circuits

Electromotive Force (E)

DC - current
Direct current



source of DC current is Battery
conservation of Energy in Battery
Chemical Energy \rightarrow Electrical Energy
Battery in circuit is

OR $\frac{r}{E}$
E: electromotive force (V)




r: internal Resistance (Ω)



Electromotive force (\mathcal{E}): Maximum potential difference between the terminals of the battery

القوة الدافعة الكهربائية هي أقصى فرق جهد بين طرفي البطارية

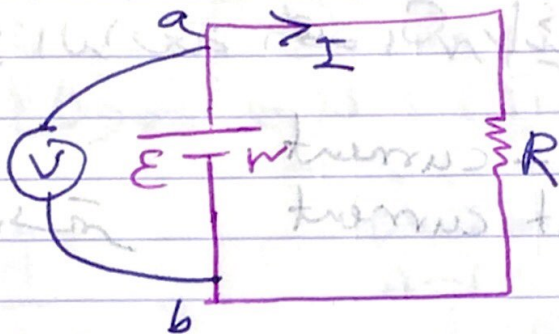unit of \mathcal{E} is
volt = $\frac{J}{C}$



$V_a - V_b = \Delta V$ (reading of
voltmeter)
= potential difference

$$\Delta V = \mathcal{E} - Ir$$

when $I = 0$ (open circuit)

$$\rightarrow \Delta V = \mathcal{E}$$



when $r = 0 \rightarrow$

$$\Delta V = \mathcal{E}$$

$\mathcal{E} = 12$ volt means the battery delivers 12 J to move 1 C from a \rightarrow b

(2)

Simple current - circuit

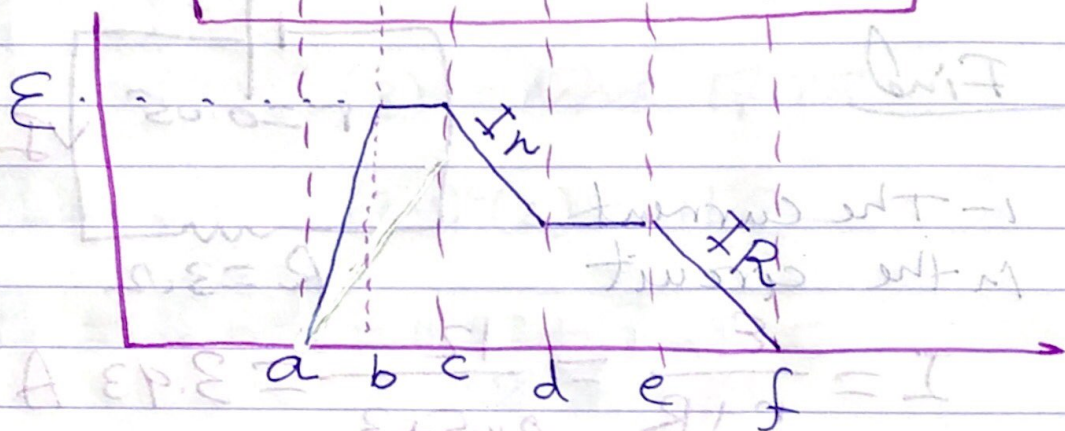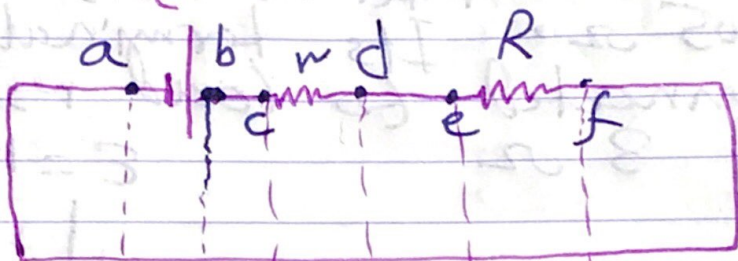

$$\mathcal{E} = I r + I R$$

$$I = \frac{\mathcal{E}}{r + R} \quad \text{simple circuit equation}$$

$$I(\mathcal{E} = I r + I R)$$

$$I \mathcal{E} = I^2 r + I^2 R \quad \text{conservation of energy}$$

$$P_{\mathcal{E}} = I \mathcal{E}$$

power from battery

$$P_r = I^2 r$$

power delivered to internal

$$P_R = I^2 R$$

resistance = = load resistance


3

Ex 28.1
834

A battery has emf of $\mathcal{E} = 12$ volt and an internal resistance of 0.05Ω . Its terminals are connected to load resistance of 3Ω .

$\mathcal{E} = 12V$

Find

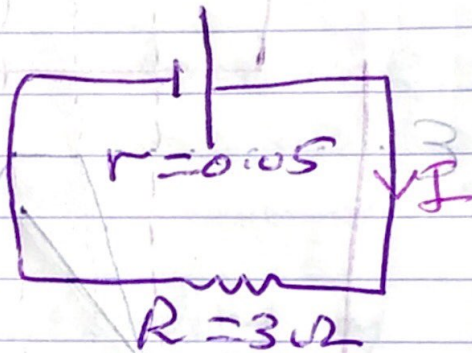

- 1- The current in the circuit

$$I = \frac{\mathcal{E}}{r + R} = \frac{12}{0.05 + 3} = 3.93 \text{ A}$$

- 2- The terminal voltage of the battery

$$\Delta V = \mathcal{E} - Ir = 12 - 3.93 \times 0.05 = 11.8 \text{ volt}$$

- 3- Power delivered to load resistance

$$P_R = I^2 R = (3.93)^2 (3) = 46.3 \text{ watt}$$

- 4- Power delivered to internal resistance

$$P_r = I^2 r = (3.93)^2 (0.05) = 0.772 \text{ W}$$

- 5- Power delivered by the battery

$$P_{\mathcal{E}} = I \mathcal{E} = 3.93 \times 12 = 47.16$$

on

$$P_{\mathcal{E}} = P_r + P_R =$$

(47)


$P_{\mathcal{E}} = 47.16$	$P_r = 0.772$	$P_R = 46.3$
$P_{\mathcal{E}} = I \mathcal{E}$	$P_r = I^2 r$	$P_R = I^2 R$

قوة
 Suppose the battery ages its internal
 resistance $r = 2 \Omega$ $\mathcal{E} = 12$

①

$$I = \frac{\mathcal{E}}{r+R} = \frac{12}{2+3}$$

$$= \frac{12}{5} = 2.4 \text{ A}$$

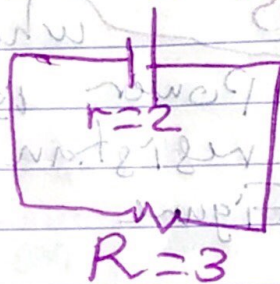

②

$$P_R = I^2 R$$

$$= (2.4)^2 (3) = 17.28$$

$$P_r = I^2 r = (2.4)^2 (2) = 11.52$$

$$P_{\mathcal{E}} = P_r + P_R = 11.52 + 17.28$$

$$= 28.8 \text{ watt}$$

or

$$P_{\mathcal{E}} = I \mathcal{E}$$

$$= (2.4)(12) = 28.8 \text{ W}$$

terminal voltage of the battery

$$\Delta V = \mathcal{E} - I r$$


$$= 12 - 2.4(2)$$

$$= 7.2 \text{ volt.}$$

5

EX (28.2)
835

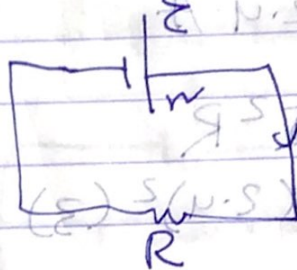Find the load Resistance R for which the maximum Power is delivered to the load resistance is maximum in Figure



$$P = I^2 R$$


$$= \frac{\epsilon^2 R}{(r+R)^2}$$

$$\frac{dP}{dR} = \frac{d}{dR} \left(\frac{\epsilon^2 R}{(r+R)^2} \right) = 0$$

$$= \frac{d}{dR} (\epsilon^2 R (R+r)^{-2}) = 0$$

→ $R = r$


$$P_{\max} = \frac{\epsilon^2}{4r}$$

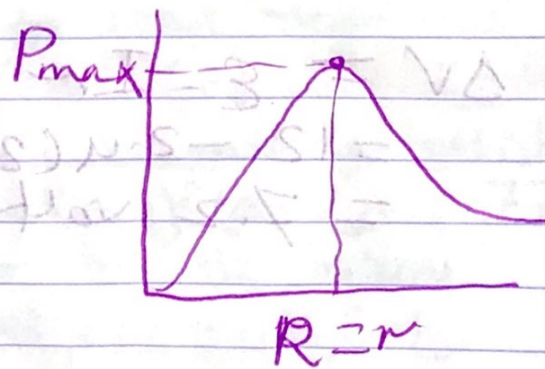

①

28.2 Resistors in series and parallel

→ Series combination

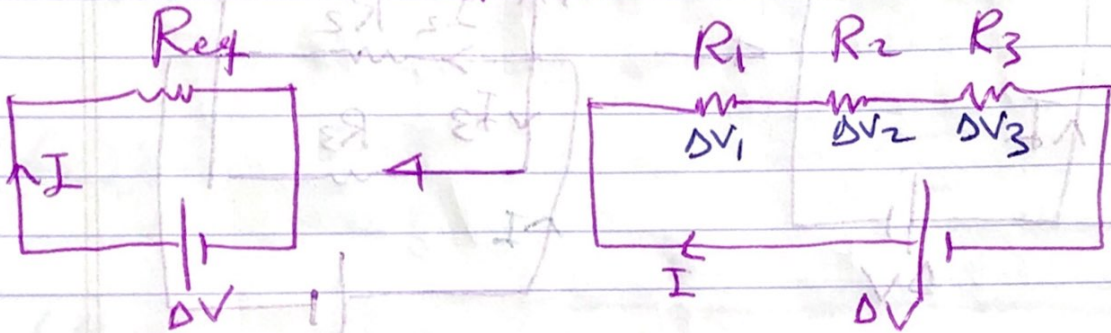

I : the same

ΔV : divided


$$\Delta V = \Delta V_1 + \Delta V_2 + \Delta V_3$$

$$R_{eq} = ??$$

$$\Delta V = \Delta V_1 + \Delta V_2 + \Delta V_3$$

$$I R_{eq} = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

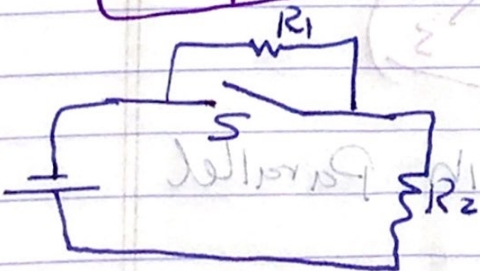

S : open


$$R_{eq} = R_2 + R_1$$

S : closed

$$R_{eq} = R_2 \text{ only}$$

7

Resistors In Parallel

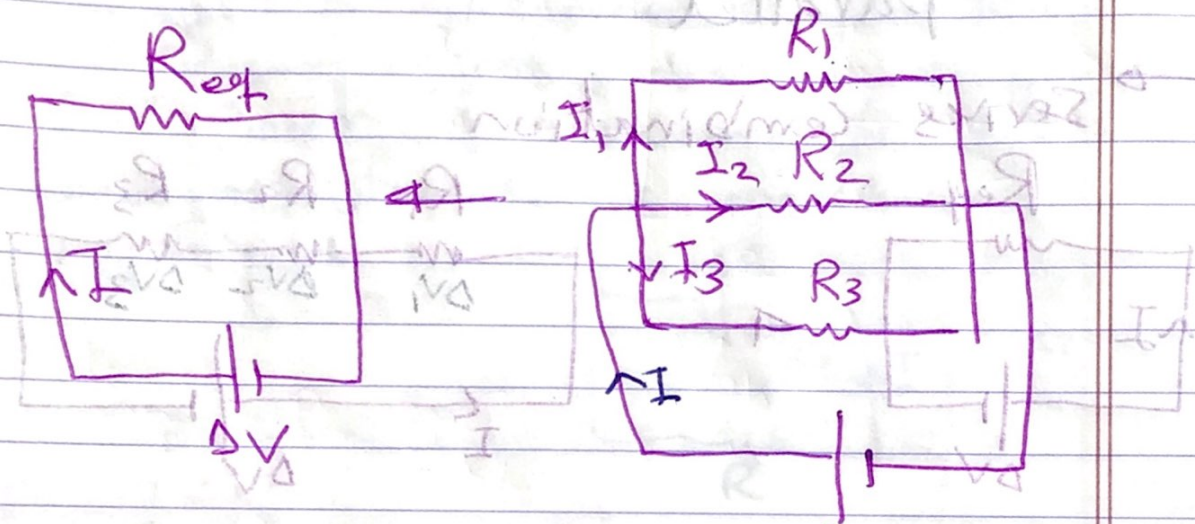

ΔV : the same
 I : divided

$$I = I_1 + I_2 + I_3$$

but $I = \frac{\Delta V}{R}$


$$\frac{\Delta V}{R_{eq}} = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} + \frac{\Delta V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

For R_1, R_2 only in Parallel


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

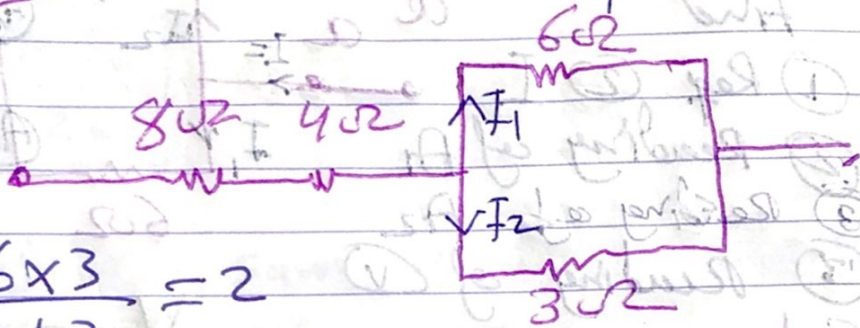① EX (28.4)
841 Find the equivalent Resistance R_{eq}



$$(6, 3) \xrightarrow{P} \frac{6 \times 3}{6 + 3} = 2$$

$$(8, 4, 2) \xrightarrow{S}$$

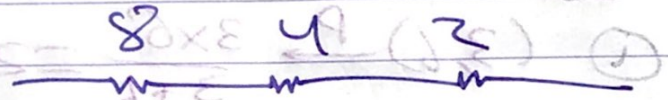

$$R_{eq} = 8 + 4 + 2 = 14 \Omega$$

② $\Delta V = 42 \text{ volt}$
what is the current in each Resistor

$$I = \frac{\Delta V}{R_{eq}} = \frac{42}{14} = 3 \text{ A}$$

$$I_1 = I_2 = I = 3 \text{ A}$$

$$\Delta V_1 = \Delta V_2$$

$$6 I_1 = 3 I_2$$

$$I_2 = 2 I_1 \quad \text{--- (1)}$$

$$I_1 + I_2 = 3 \quad \text{--- (2)}$$

$$I_1 = 1 \text{ A}$$

$$I_2 = 2 \text{ A}$$

9

EX

Find

- Req
- Reading of A_1
- Reading of A_2
- Reading of V

Sol.

$$\textcircled{1} (3, 6) \rightarrow \frac{3 \times 6}{3 + 6} = 2$$

$$(2, 5) \rightarrow \text{Req} = 2 + 5 = 7 \Omega$$

$$\textcircled{2} + \textcircled{3} \quad V_1 = V_2$$

$$I_1 R_1 = I_2 R_2$$

$$6 I_1 = 3 I_2$$

$$I_2 = 2 I_1 \quad \textcircled{1}$$

$$I_1 + I_2 = I \quad \textcircled{2}$$

$$I_1 + I_2 = 3 \quad \textcircled{2}$$

Substitute $\textcircled{1}$ in $\textcircled{2}$

$$I_1 + 2 I_1 = 3 \rightarrow I_1 = 1 \text{ A} = I$$

$$I_2 = 2 \text{ A}$$

$\textcircled{3}$ Reading of V

$$V = I R = 3 \times 5 = 15 \text{ volt}$$

10

General Circuit Equation

$$I = \frac{\sum \mathcal{E}}{\sum R}$$

$\sum \mathcal{E}$: algebraic sum of Electromotive forces of all batteries

$$\sum \mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2 + \dots \text{ (algebraic sum)}$$

$$\sum R = R_{eq} + \sum r$$

I : current passes through batteries

I : main current

EX Find I_p
(24, 12, 8) \rightarrow

$$\frac{1}{R} = \frac{1}{24} + \frac{1}{12} + \frac{1}{8}$$

$$= \frac{1+2+3}{24}$$

$$R = 4$$


$$(4, 7) \rightarrow R_{eq} = 11 \Omega$$

$$\sum r = 1$$

$$\rightarrow \sum R = 11 + 1 = 12 \Omega$$

$$\rightarrow I = \frac{\sum \mathcal{E}}{\sum R} = \frac{36}{12} = 3 \text{ A}$$

11

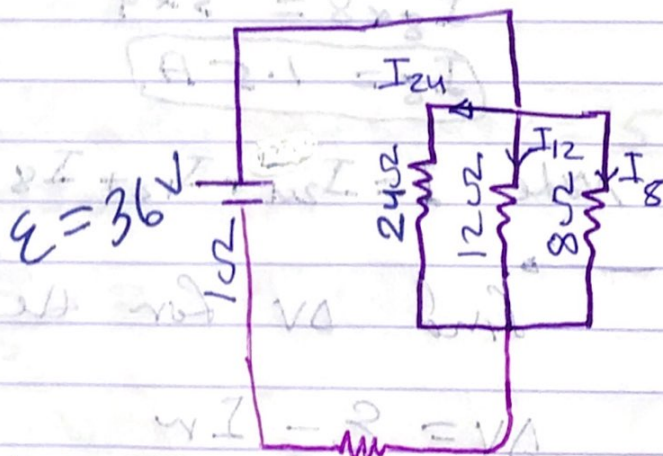

Find current of each Resistance

$$I_{2\Omega} \times 2\Omega = I \times R_P \quad (V_{2\Omega} = V_P)$$

$$I_{2\Omega} \times 2\Omega = 3 \times 4 \frac{3\Omega}{5\Omega} = I$$

$$I_{2\Omega} = 0.5 \text{ A}$$

$$I_{12} \times 12 = I \times R_P$$

$$I_{12} \times 12 = 3 \times 4 \frac{3\Omega}{5\Omega} = I$$

$$I_{12} = 1 \text{ A}$$

$$I_8 \times 8 = I \times R_P$$

$$I_8 \times 8 = 3 \times 4$$

$$I_8 = 1.5 \text{ A}$$

$$I = I_{2\Omega} + I_{12} + I_8$$

Find ΔV for the battery


$$\Delta V = \mathcal{E} - I r$$

$$= 36 - 3 \times 1 = 33 \text{ Volt}$$

Find Power delivered to 12Ω

$$P = I^2 R = (1)^2 (12) = 12 \text{ watt}$$

12

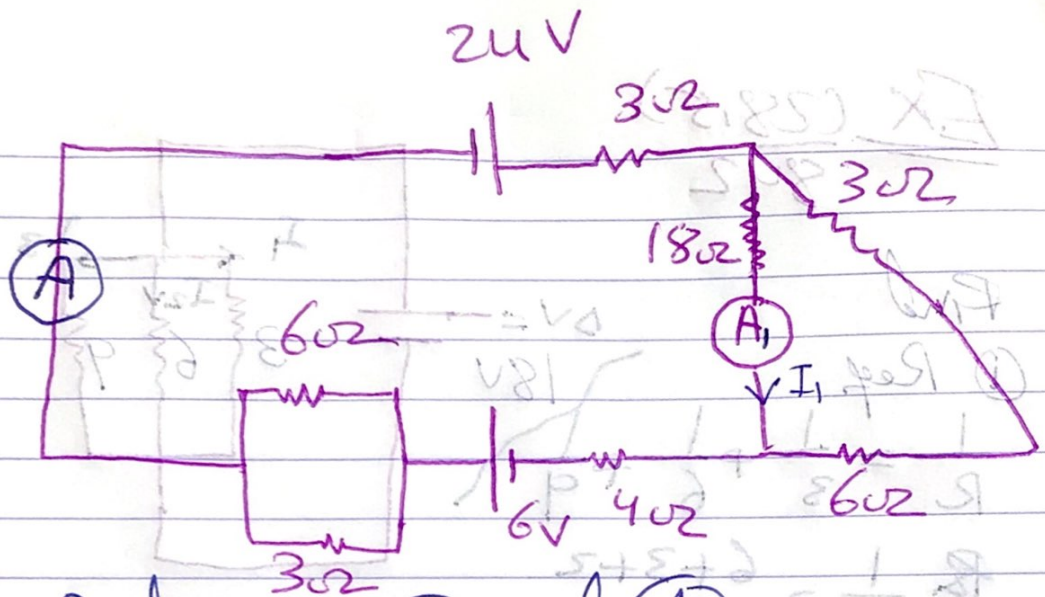

Find Reading of (A) and (A_1)

$$(3, 6) \xrightarrow{S} 3 + 6 = 9$$

$$(9, 18) \xrightarrow{P} \frac{9 \times 18}{9 + 18} = 6$$

$$(6, 3) \xrightarrow{P} \frac{6 \times 3}{6 + 3} = 2$$

$$(3, 6, 4, 2) \xrightarrow{S} R_{eq} = 3 + 6 + 4 + 2 = 15$$

$$\sum \mathcal{E} = 6 + 24 = 30 \text{ volt}$$

$$I = \frac{\sum \mathcal{E}}{\sum R} = \frac{30}{15} = 2 \text{ A } (A)$$

$$V = 2 \text{ V} = V_p = I_1 \times 18 = 2 \times 6 = 12 \text{ V}$$

$$I_1 \times 18 = 2 \times 6 = 12 \text{ V}$$

$$I_1 = \frac{2}{3} \text{ A}$$

13

EX (28.5)
842


Find

① Req

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{6} + \frac{1}{9}$$

$$\frac{1}{R} = \frac{6+3+2}{18}$$

$$R = \frac{18}{11} \Omega$$

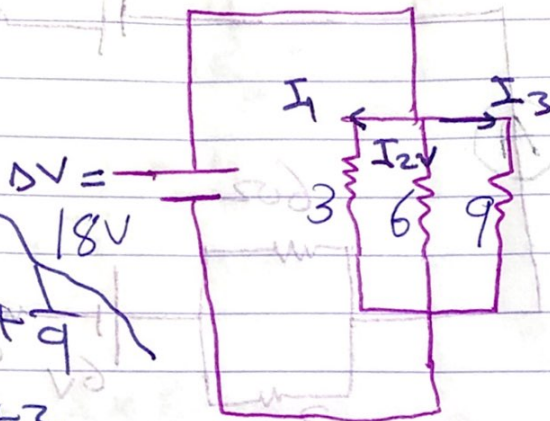

② Current of each Resistance

$$I_1 = \frac{\Delta V}{R_1} = \frac{18}{3} = 6 A$$

$$I_2 = \frac{\Delta V}{R_2} = \frac{18}{6} = 3 A$$

$$I_3 = \frac{\Delta V}{R_3} = \frac{18}{9} = 2 A$$

③ Power delivered to each Resistance

$$P_3 = I^2 R = (6)^2 (3) = 108 W$$

$$P_6 = (3)^2 (6) = 54 W$$

$$P_9 = (2)^2 (9) = 36 W$$

④ Power delivered to the combination

$$P_{\text{comb}} = \frac{(\Delta V)^2}{R_{\text{eq}}} = \frac{(18)^2}{\frac{18}{11}} = 198 W$$

or $P_{\text{comb}} = P_1 + P_2 + P_3$

14