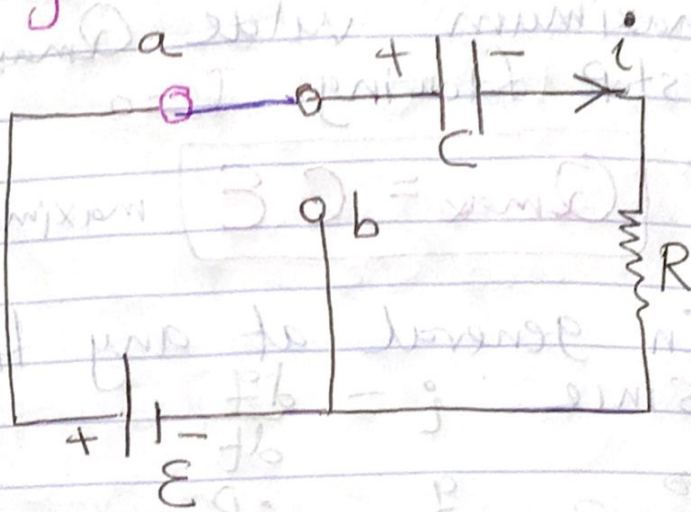


RC - Circuits - Part 3

A circuit containing a series combination of a resistor and a capacitor is called an RC circuit.

Charging a Capacitor:

When the switch is thrown to position a the capacitor begins to charge up.



Initially the capacitor is uncharged the switch is thrown at position (a).

Applying Kirchhoff's voltage loop (Loop Rule)

$$\mathcal{E} - V_c - iR = 0$$

$$\mathcal{E} - \left(\frac{q}{C}\right) - iR = 0$$

potential diff across resistor

potential diff across capacitor

①

at $t=0$ the charge on the capacitor is zero

$$Q_i = 0$$

Thus

$$I_i = \frac{\mathcal{E}}{R}$$

after some long time the charge on the capacitor reaches its maximum value Q_{\max} So I stop flowing $I=0$

$$Q_{\max} = C\mathcal{E} \quad \text{maximum charge}$$

In general at any time (t)

$$\text{since } i = \frac{dq}{dt}$$

$$\rightarrow \mathcal{E} - \frac{q}{C} - iR = 0$$

$$i = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{C\mathcal{E}}{RC} - \frac{q}{RC}$$

$$= \frac{(C\mathcal{E} - q)}{RC}$$

(2)

$$\int \frac{dq}{q - CE} = -\frac{1}{RC} \int dt$$

Integrate the expression ($q=0$ at $t=0$)

$$\ln(q - CE) \Big|_0^q = -\frac{t}{RC}$$

$$Q(t) = CE \left(1 - e^{-\frac{t}{RC}} \right)$$

$$Q(t) = Q_{\max} \left(1 - e^{-\frac{t}{RC}} \right)$$

$$Q_{\max} = CE$$

let $\tau = RC$ τ : time constant


derive $Q(t)$ ($i(t) = \frac{dq}{dt}$)

$$i(t) = CE \left(0 - \left(-\frac{1}{RC} \right) e^{-\frac{t}{RC}} \right)$$

$$i(t) = \frac{E}{R} \cdot e^{-t/RC}$$

3

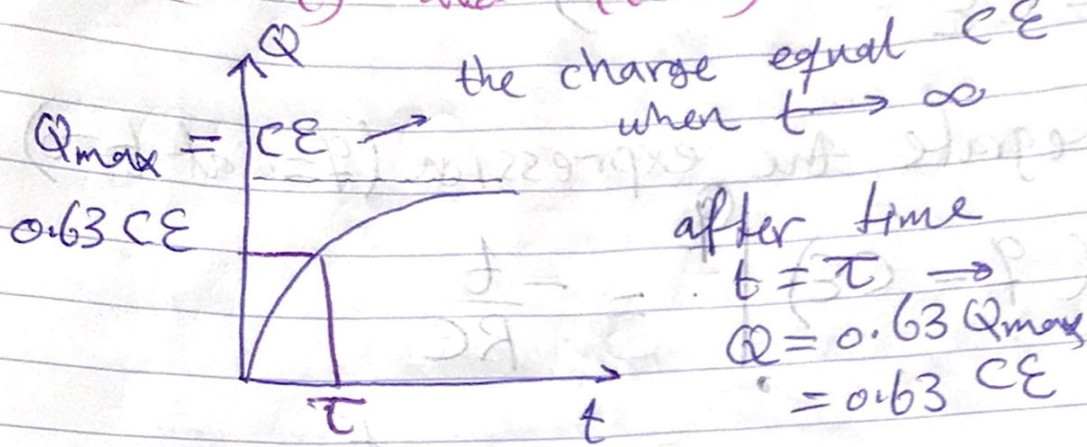Graphical Representation of $(Q-t)$ and $(i-t)$ and V_c




when $t = \tau$


$\rightarrow Q = 0.63 Q_{max}$

$Q = 0.63 CE$

$(V_c - t)$

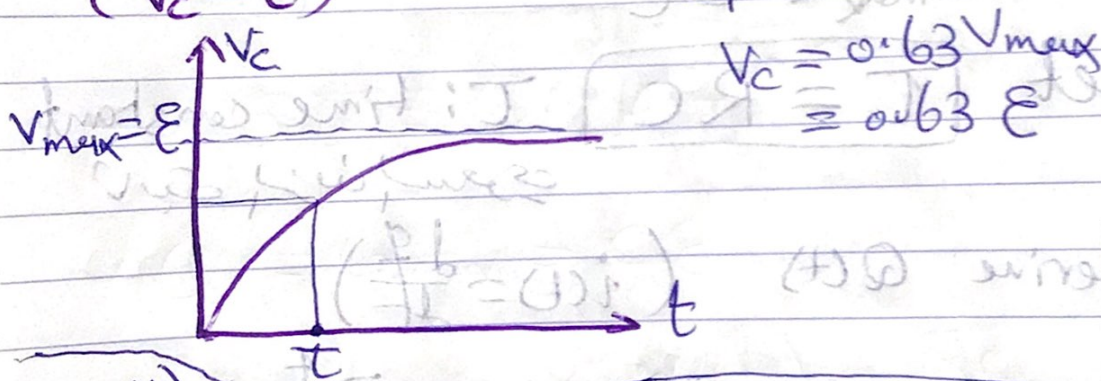


$I(t)$

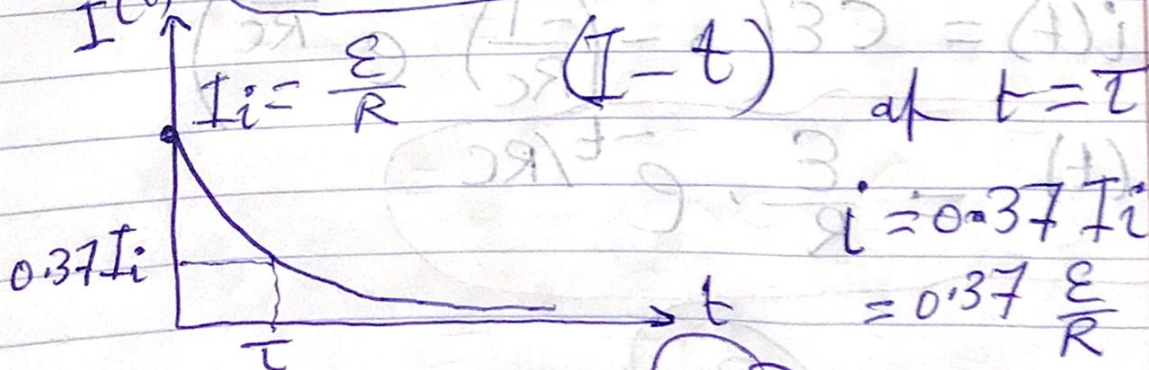

(4)

discharging a capacitor

The capacitor is initially fully charged

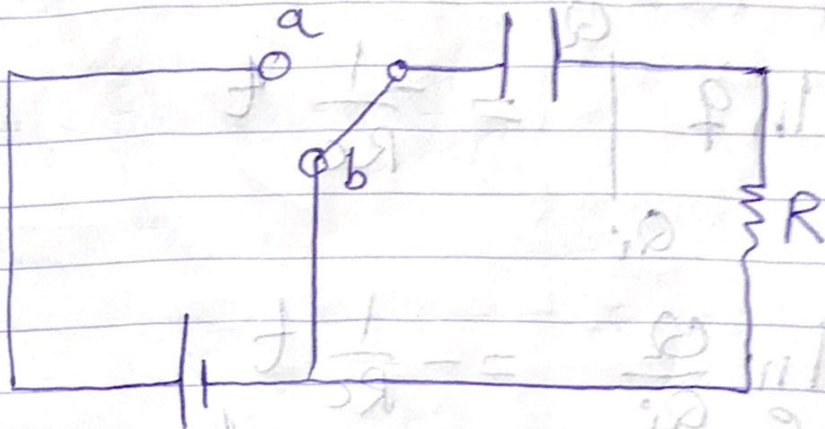

When the switch is thrown to position b the capacitor discharges

$$-\frac{q}{C} - iR = 0$$

$$i = \frac{dq}{dt}$$

$$-R \frac{dq}{dt} = \frac{q}{C}$$

$$\frac{dq}{q} = -\frac{1}{RC} dt$$

Integrating the expression using

$$q = Q_i = CE \text{ at } (t=0)$$

$$Q_i \int \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$

(5)

$$\ln\left(\frac{q}{Q_i}\right) = -\frac{t}{RC}$$

$$Q(t) = Q$$

$$\ln \frac{Q}{Q_i} = -\frac{1}{RC} t$$

$$\ln \frac{Q}{Q_i} = -\frac{1}{RC} t$$

$$\rightarrow \frac{Q}{Q_i} = e^{-\frac{t}{RC}}$$

$$\rightarrow Q(t) = Q_i e^{-\frac{t}{RC}}$$

$$Q_i = Q_{\max} = CE$$

$$i(t) = \frac{dQ}{dt} = Q_i \left(-\frac{1}{RC}\right) e^{-\frac{t}{RC}}$$




$$= -\frac{CE}{RC} e^{-\frac{t}{RC}}$$

$$i(t) = -\frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}$$

$$V_c(t) = \frac{Q(t)}{C}$$

$$\rightarrow V_c(t) = \mathcal{E} e^{-\frac{t}{RC}}$$



Graphical Representation

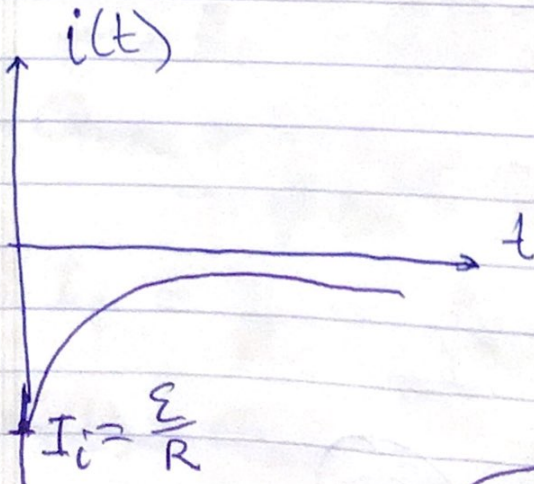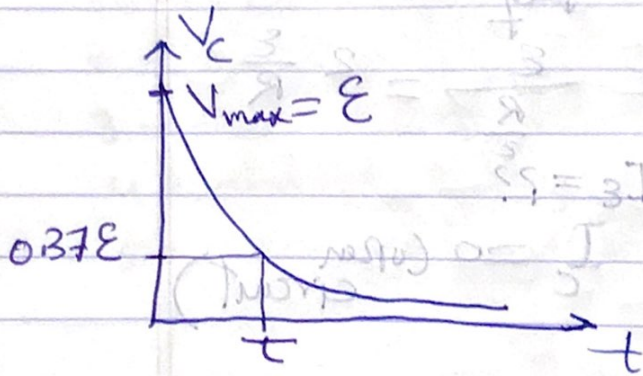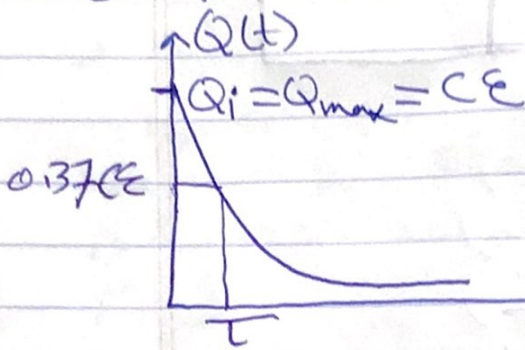

7

Quiz
 Consider

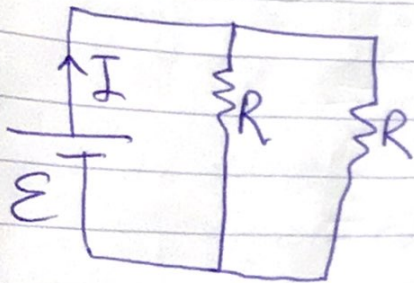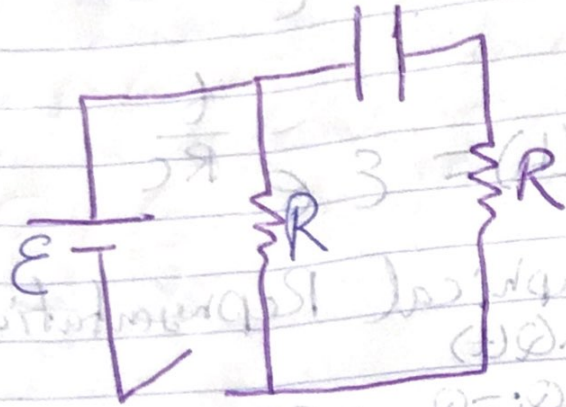
(a)
 at $t=0$
 the beginning
 what is
 I through
 battery



$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{\frac{R}{2}} = 2 \frac{\mathcal{E}}{R}$$

(b) after long time $I_{\mathcal{E}} = ??$

after long time $I_C = 0$ (open circuit)

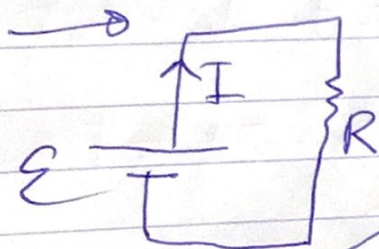


$$I = \frac{\mathcal{E}}{R}$$

8

EX (28.9)

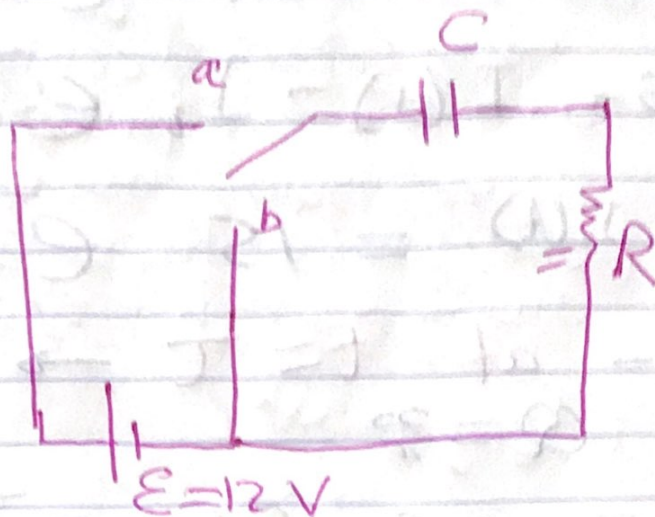An uncharged capacitor and resistor are connected in series to a battery as shown in fig. when the switch is thrown at (a)



Find

- 1 - time constant
- 2 - maximum charge
- 3 - the initial (maximum) current
- 4 - charge as function of time
- 5 - current as function of time

$$E = 12\text{ V}$$

$$R = 8 \times 10^5\ \Omega$$

$$C = 5\ \mu\text{F}$$

$$1 - \tau = RC = 8 \times 10^5 \times 5 \times 10^{-6} = 4\ \text{sec}$$

$$2 - Q_{\text{max}} = CE = 5 \times 10^{-6} \times 12 = 60\ \mu\text{C}$$

$$3 - I_i = \frac{E}{R} = \frac{12}{8 \times 10^5} = 15\ \mu\text{A}$$

$$4 - Q(t) = Q_{\text{max}} \left(1 - e^{-\frac{t}{\tau}} \right)$$

(9)

$$Q(t) = 60(1 - e^{-\frac{t}{\tau}}) \quad (\text{p. 85}) \times 1$$

$$5 - I(t) = I_0 e^{-\frac{t}{\tau}}$$

$$I(t) = 15 e^{-\frac{t}{\tau}}$$

6 - at $t = \tau \rightarrow$

$Q = ?$

$$Q \text{ at } Q = 60(1 - e^{-1})$$

$$= 60(1 - \frac{1}{e})$$

$$= 60(1 - \frac{1}{2.72})$$

$$= 0.63 \times 60$$

$$Q = 37.8 \text{ Me}$$

7 - at $t = 1 \text{ sec} \rightarrow I = ?$

$$I = 15 e^{-\frac{1}{\tau}}$$

$$= 15 e^{-0.25}$$

$$= (15)(0.778)$$

$$= 11.68 \text{ MA}$$

10

EX 28.10 Discharging
the last example
when the switch is at (b)

(A) After how many time constants
($t = ?$) is the charge on the
capacitor equal one-fourth
its initial (max) value

$$Q(t) = Q_i e^{-\frac{t}{\tau}} \quad (Q_i = Q_{\max} = CE)$$

when $Q = \frac{Q_i}{4}$

$$\rightarrow \frac{Q_i}{4} = Q_i e^{-\frac{t}{\tau}}$$

$$\ln\left(\frac{1}{4}\right) = \ln\left(e^{-\frac{t}{\tau}}\right)$$

$$-\ln 4 = -\frac{t}{\tau}$$

$$t = (\ln 4)\tau$$

$$t = 1.39\tau$$

$$= 1.39 \times 4$$

$$t = 5.56 \text{ sec}$$

(B) The energy stored in the capacitor decreases with time as the capacitor discharges.

After how many time constants ($t = ?$) is this stored energy one-fourth its initial value?

$$U(t) = \frac{Q^2}{2C}$$

$$= \frac{1}{2C} \left(Q_i e^{-\frac{t}{\tau}} \right)^2$$

$$U(t) = \frac{Q_i^2}{2C} e^{-\frac{2t}{\tau}}$$

$$U_i = \frac{Q_i^2}{2C}$$

when $U = \frac{1}{4} U_i \rightarrow$

$$\frac{1}{4} U_i = U_i e^{-\frac{2t}{\tau}}$$

$$-\ln 4 = -\frac{2t}{\tau}$$

$$\rightarrow t = \frac{\tau \ln 4}{2}$$

$$t = 0.69 \tau$$

(12)