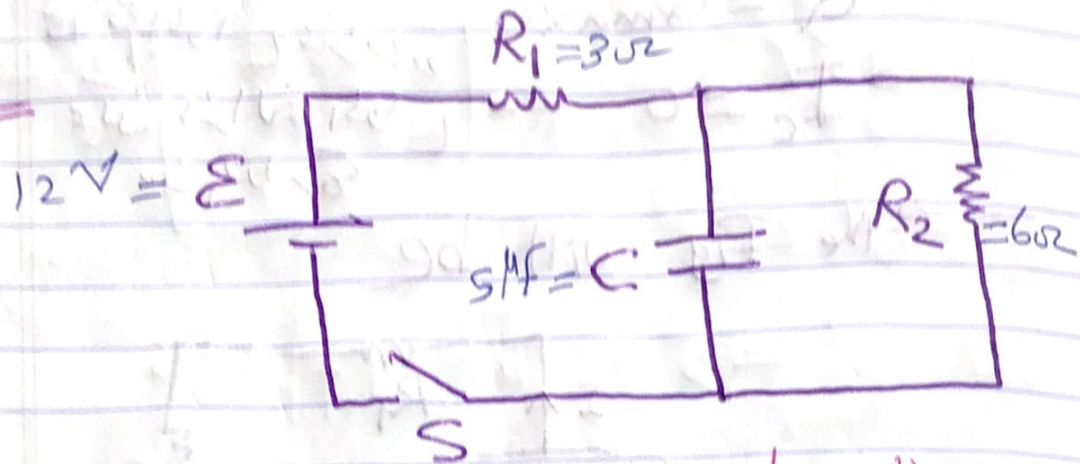


RC-circuit

Q1



In the Figure calculate the current in the capacitor
A) when the switch is closed ($t=0$)
B) after very long time


(A) at $t=0$

$$Q_i = 0$$
$$V_c = \frac{Q_i}{C} = 0$$

Since R_2 in parallel with $C \rightarrow V_{R_2} = 0$

$$\rightarrow I_{R_2} = 0$$

\rightarrow the 2nd fig

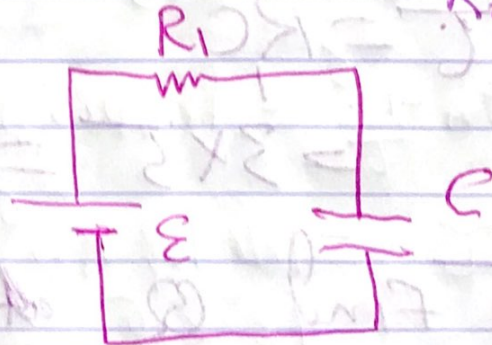

$$I_c = \frac{E}{R_1} = \frac{12}{3}$$
$$= 4 \text{ A}$$

\leftarrow

①

(B) after long time


$$Q = Q_{\max}$$

$$I_c = 0$$

$$I_c = 0$$

كل ما في الـ capacitor
على حالة الاتزان
في حالة الاتزان

the Fig will be

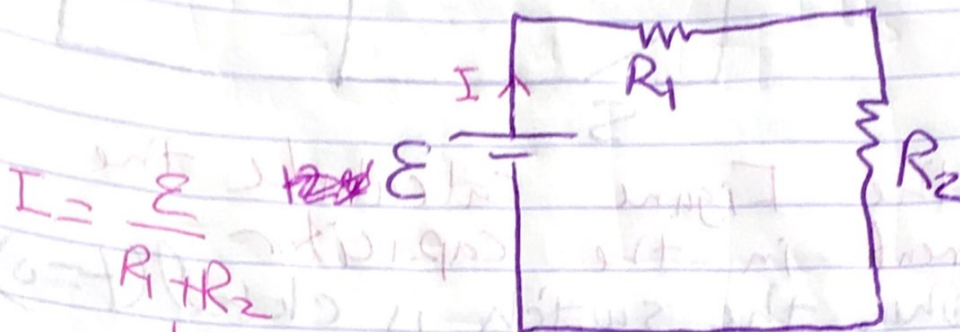

$$I = \frac{E}{R_1 + R_2}$$
$$= \frac{12}{3 + 6}$$
$$= \frac{12}{9} \text{ A}$$

(C) Find τ (time constant)

$$\tau = RC$$

$$= 3 \times 5 = 15 \text{ Ms}$$

(D) Find Q_{\max} at $t = \frac{RC}{2}$

$$Q_{\max} = CE = 5 \times 12 = 60 \text{ Mc}$$

(2)

E) Find V_c at $t = 5 \text{ Ms}$

$$V_c = \varepsilon \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$= 12 \left(1 - e^{-\frac{5}{15}}\right)$$

$$= 12(1 - 0.716)$$

$$V_c = 3.4 \text{ volt}$$

F) Find V_{R_2} at $t = 5 \text{ Ms}$

$$\rightarrow V_{R_2} = V_c = 3.4 \text{ volt (Parallel)}$$

E) Find V_{R_1} at $t = 5 \text{ Ms}$

$$V_{R_1} = 12 - 3.4 = 8.6 \text{ volt}$$

G) Find I , I_c , I_{R_2}
at $t = 5 \text{ Ms}$

$$I = \frac{V_{R_1}}{R_1} = \frac{8.6}{3} = 2.87 \text{ A}$$


$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{3.4}{6} = 0.57 \text{ A}$$

$$I_c = I - I_{R_2} = 2.87 - 0.57 = 2.3 \text{ A}$$

on $I = I_i e^{-\frac{t}{\tau}} = 4 e^{-\frac{5}{15}} = 2.87$

3

4

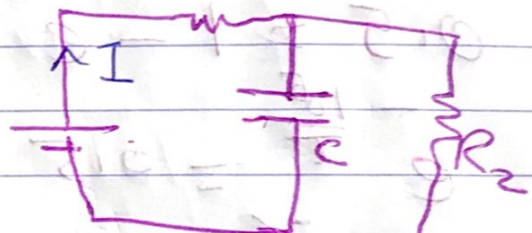

charging capacitor

Ex / In Figure


Given

$$\mathcal{E} = 10 \text{ V}$$

$$C = ??$$

$$R = 10^4 \Omega$$

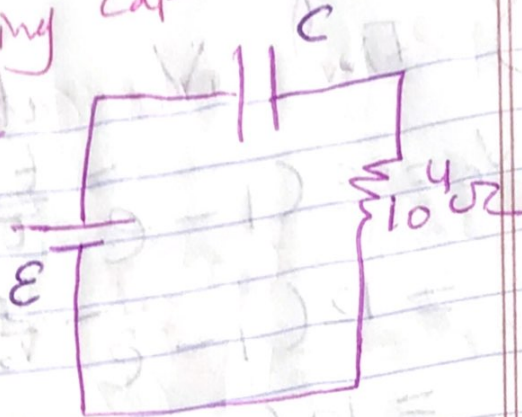if $V_c = 5 \text{ V}$ at $t = 1 \mu\text{s}$



$$\tau = RC =$$

$$V_c = \mathcal{E} \left(1 - e^{-\frac{t}{\tau}} \right)$$

$$5 = 10 \left(1 - e^{-\frac{10^{-6}}{\tau}} \right)$$

$$0.5 = 1 - e^{-\frac{10^{-6}}{\tau}}$$

$$e^{-\frac{10^{-6}}{\tau}} = 0.5$$

$$-\frac{10^{-6}}{\tau} = \ln(0.5) \rightarrow \tau = \frac{10^{-6}}{\ln 0.5}$$

$$\tau = 1.44 \times 10^{-6} = 1.44 \times 10^{-6}$$

$$RC = 1.44 \times 10^{-6}$$

$$10^4 \times C = 1.44 \times 10^{-6} \rightarrow C = 1.44 \times 10^{-10}$$

4

3

= 144 pF

EX Find time needed for a capacitor to have a charge equal 99% from its max charge

$$Q = 99\% Q_{\max} \rightarrow t = ?? \tau$$

$$Q = Q_{\max} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$0.99 Q_{\max} = Q_{\max} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$e^{-\frac{t}{\tau}} = 0.01$$

$$\ln(0.01) = -\frac{t}{\tau}$$

$$t = 4.6 \tau$$

$$t = 4.6 R C$$

5

2

Ex During Discharging capacitor

if $V_{c \text{ max}} = 100 \text{ volt}$

and $V_c = 1 \text{ volt}$ after $t = 10 \text{ sec}$

Find V_c at $t = 20 \text{ sec}$


① V_c at $t = 10 \text{ sec}$

$$V_c = V_{\text{max}} e^{-\frac{t}{\tau}}$$

$$1 = 100 e^{-\frac{10}{\tau}}$$

$$\ln(0.01) = -\frac{10}{\tau}$$

$$\tau = 2.17 \text{ sec}$$

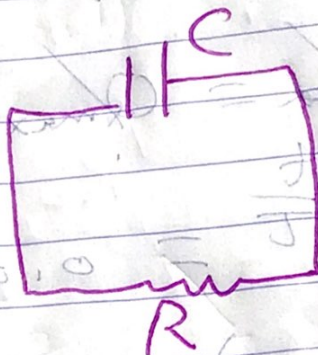

②

$$V_c = V_{\text{max}} e^{-\frac{t}{\tau}}$$

$$= 100 e^{-\frac{20}{2.17}}$$


$$= 0.01 \text{ volt}$$

⑥

43

862

The

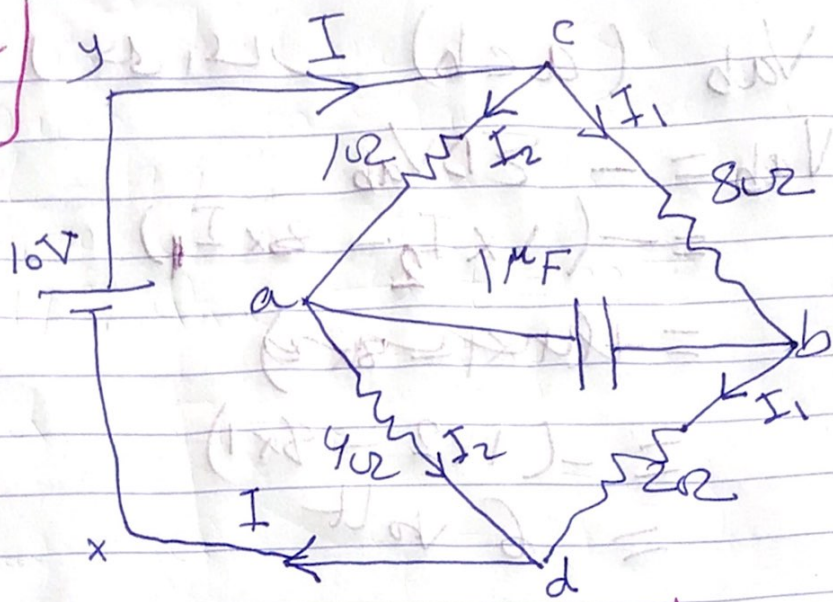

The circuit in Fig has been connected for a long time
 (a) what is the potential difference across the capacitor
 (b) If the battery is disconnected from the circuit over what time interval does the capacitor discharge to one-tenth its initial voltage

(a) $V_{ab} = ??$

$I_2 = 6 I_1$ is $\frac{1}{2} \times 1.8 =$

xycbdx

$\sum \Delta V = 0$

$10 - 8I_1 - 2I_1 = 0 \rightarrow I_1 = 1A$

$\sum \Delta V = 0$ (xycadx)

$10 - 1 \times I_2 - 4 \times I_2 = 0 \Rightarrow I_2 = 2A$

7

8

$$V_{ab} \text{ (acb)}$$

$$V_{ab} = - \sum \Delta V_{ab}$$

$$= - (1 \times I_2 - 8 \times I_1)$$

$$= - (1 \times 2 - 8 \times 1)$$

$$= - (1 \times 2 - 8 \times 1)$$

$$= 6 \text{ volt}$$

after long time


$$(1, 8) \xrightarrow{S} 9$$

$$(4, 2) \xrightarrow{S} 6$$

$$(6, 9) \xrightarrow{P}$$

$$\frac{6 \times 9}{6 + 9} =$$


$$= 3.6$$

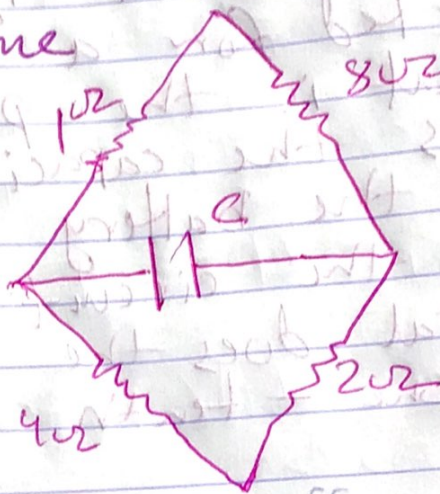

$$V_{ab} = 6 \text{ V (1)}$$

at $t = 0$

$$\Delta V_1 = 3.6$$

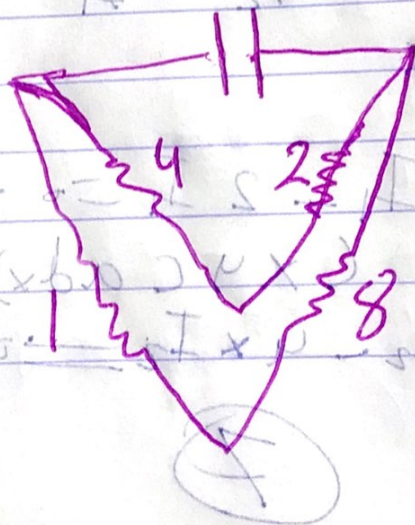

$$\textcircled{8}$$

$$\textcircled{7}$$

$$\Delta V = \Delta V_i e^{-\frac{t}{\tau}}$$

$$\frac{I}{I_0} \Delta V_i = \Delta V_i e^{-\frac{t}{\tau}}$$

$$-\ln \frac{I}{I_0} = -\frac{t}{\tau}$$

$$\rightarrow t = \tau \times \ln \frac{I_0}{I}$$

$$= 8.29 \mu s$$