

CHAPTER 4 / PART B

AC

INDICATING INSTRUMENTS MEASUREMENTS

1


AC METERS

AC electromechanical meter movements come in two basic arrangements:


- based on DC movement designs, and
- engineered specifically for AC use (measure **RMS** value)

Permanent-magnet moving coil (PMMC) meter movements will not work correctly if it **directly connected to alternating current**

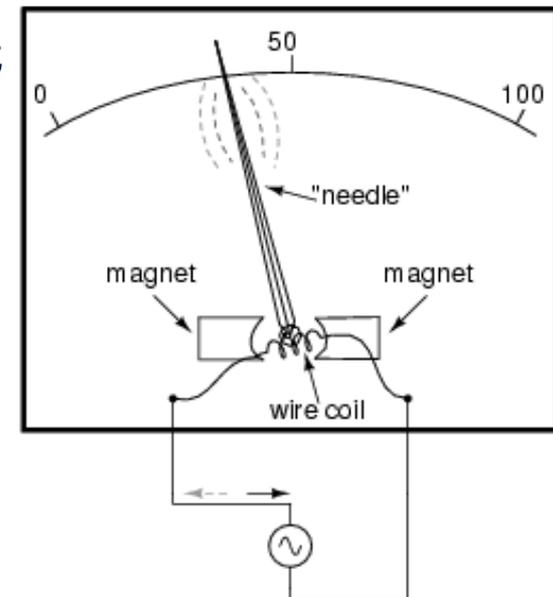because the **direction** of needle movement will **change** with each half-cycle of the AC.





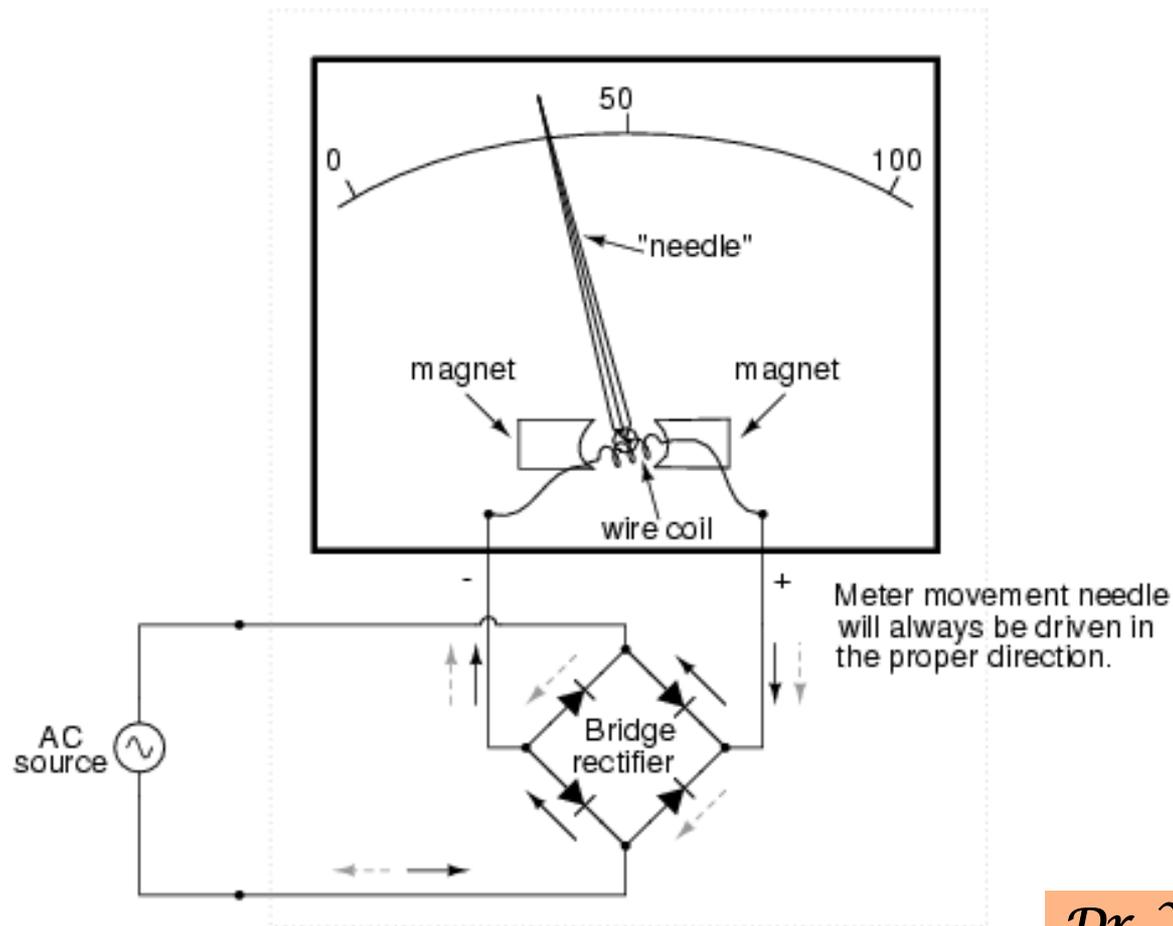- In order to use a **DC-style meter** movement such as the D'Arsonval design, the alternating current must be **rectified into DC**.
- This is most easily accomplished through the use of devices called **diodes**.




RECTIFIER-TYPE AC METERS

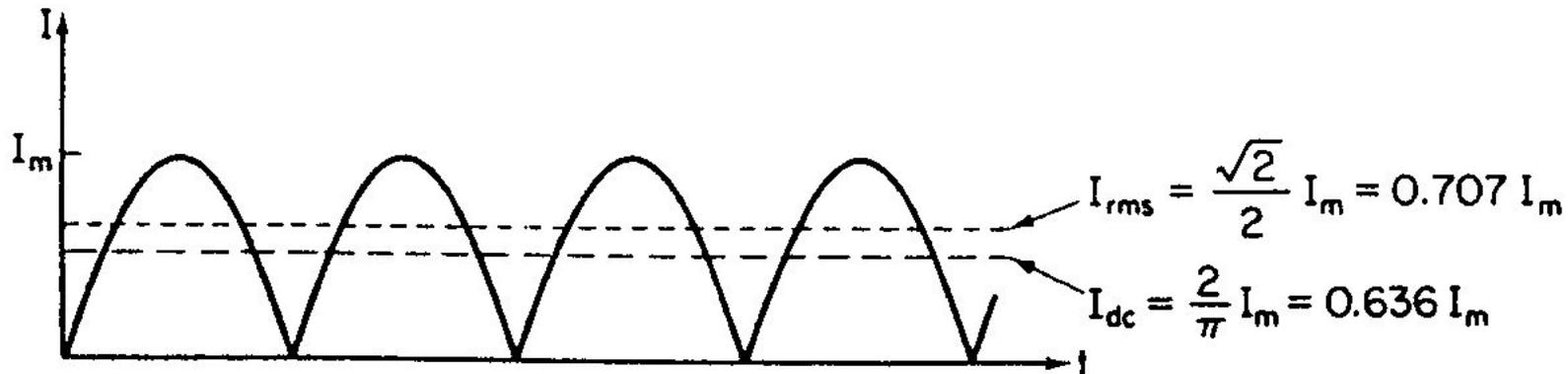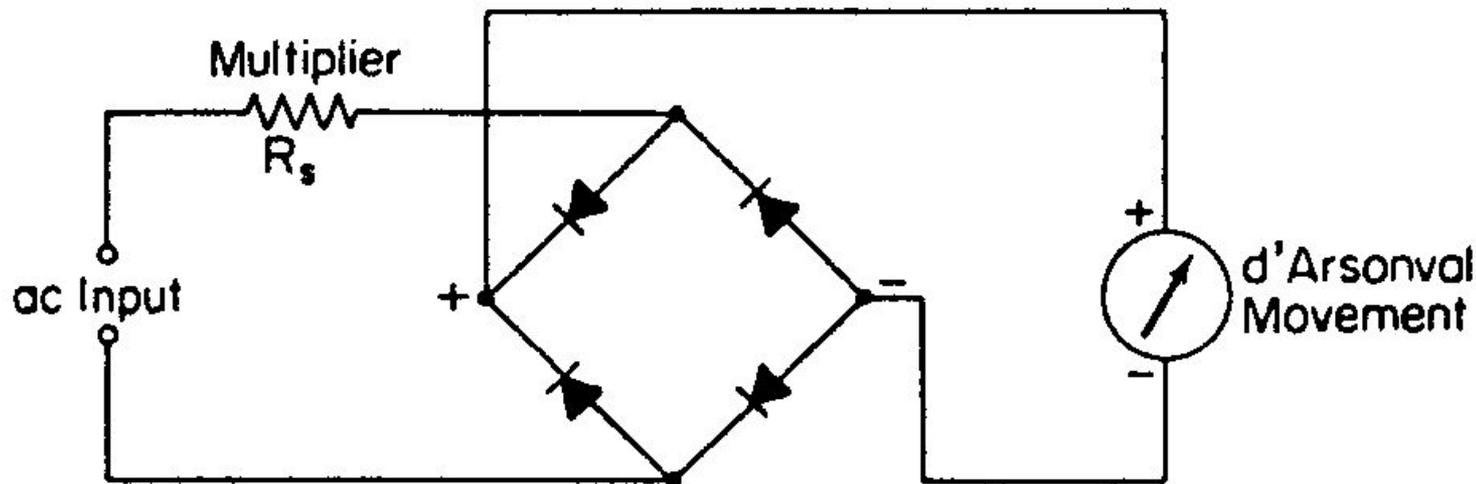The meter deflection is proportional to the **average** current
ac measurement expressed usually in **r.m.s** scale is used



RMS AN AVERAGE VALUES (*AFTER RECTIFIER*)

	Half-wave Rectifier	Bridge Rectifier
Average voltage	$V_{dc} = \frac{V_m}{\pi}$	$V_{dc} = \frac{2V_m}{\pi}$
rms voltage	$V_{rms} = \frac{V_m}{2}$	$V_{rms} = \frac{V_m}{\sqrt{2}}$

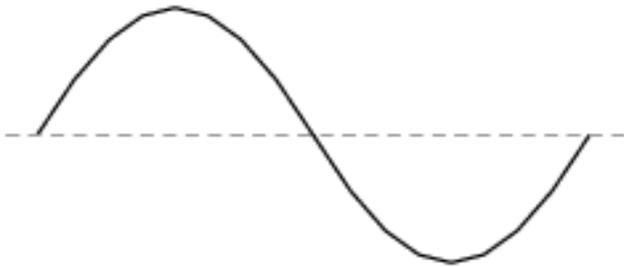


RMS = 0.707 (Peak)
 AVG = 0.637 (Peak)
 P-P = 2 (Peak)



RMS = Peak
 AVG = Peak
 P-P = 2 (Peak)
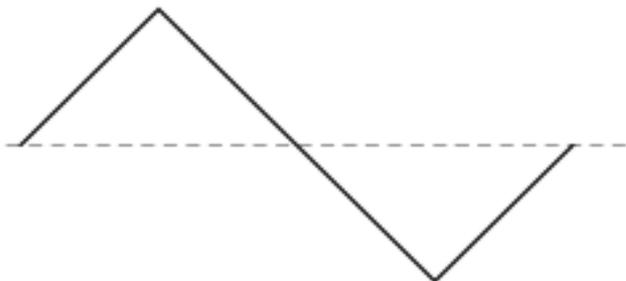
$$V_{dc} = \frac{2(\sqrt{2}V_{rms})}{\pi} \cong 0.9V_{rms}$$




RMS = 0.577 (Peak)
 AVG = 0.5 (Peak)
 P-P = 2 (Peak)

VOLTMETER CIRCUIT

R_{sh} is placed in order **D_1** to draw more current to move its operating mode into **linear** portion.

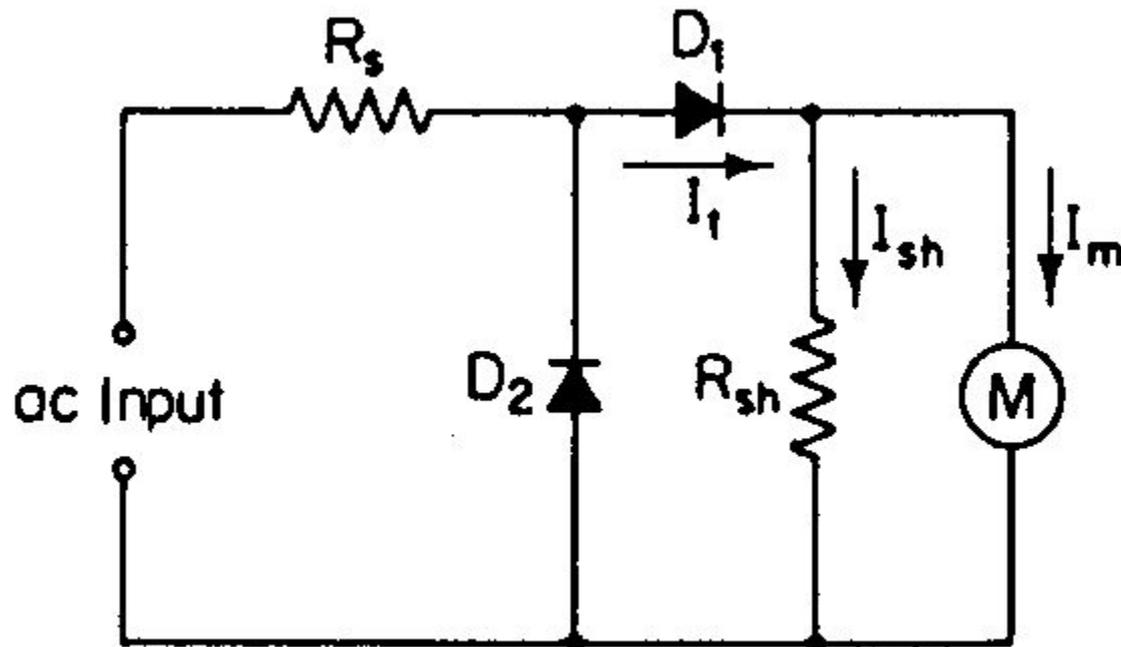Diode **D_2** is placed to protect the meter from the **reverse current** during the **-ve** half cycle.



VOLTMETER CIRCUIT (MULTIRANGE)

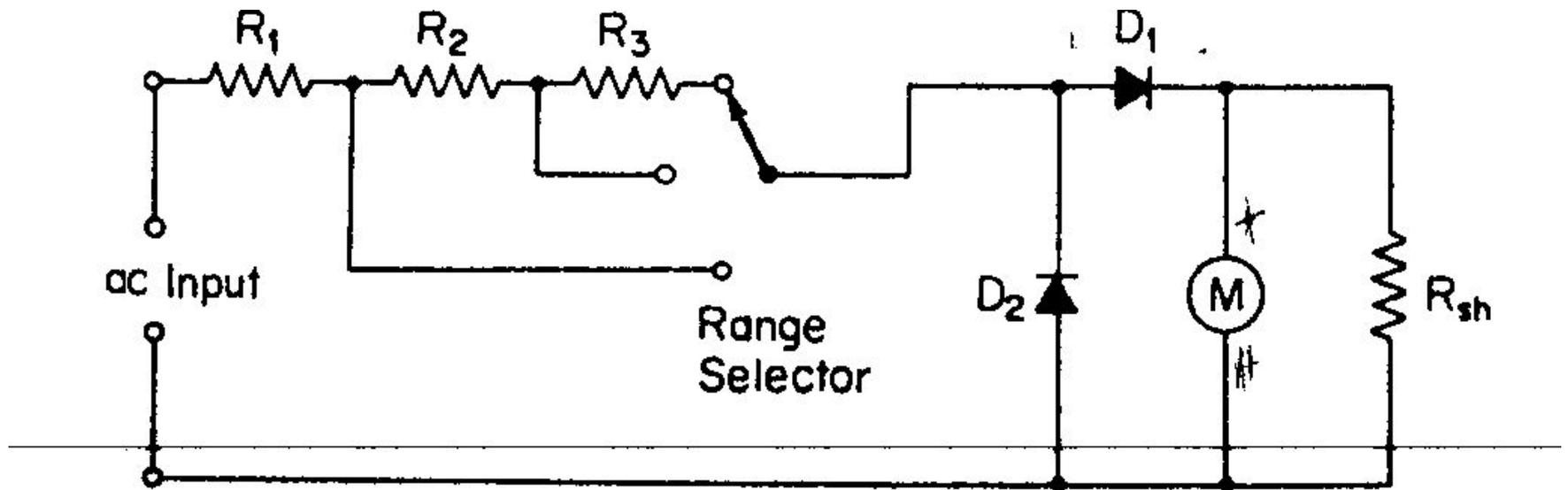


Figure 4-34 Typical ac voltmeter section of a commercial multimeter.

Example [4-10]: A meter has internal resistance of 100Ω requires 1mA DC for f.s.d. A shunt resistor with value of 100Ω is placed across the meter. The diodes forward resistance is 400Ω . For **10V** ac range calculate the value of **R_s** and the *sensitivity* of the voltmeter.

Solution

10V ac – rms

(a) Since R_m and R_{sh} are both 100Ω , the total current the source must supply for full-scale deflection is $I_f = 2\text{mA}$. For half-wave rectification the equivalent dc value of the rectified ac voltage will be

$$E_{dc} = 0.45 E_{rms} = 0.45 \times 10\text{V} = 4.5\text{V}$$

The total resistance of the instrument circuit then is

$$R_t = \frac{E_{dc}}{I_f} = \frac{4.5\text{V}}{2\text{mA}} = 2,250\Omega$$

This total resistance is made up of several parts. Since we are interested only in the resistance of the circuit during the half-cycle that the movement receives current, we can eliminate the infinite resistance of reverse-biased diode D_2 from the circuit. Therefore

$$R_t = R_s + R_{D_1} + \frac{R_m R_{sh}}{R_m + R_{sh}}$$

and

$$R_t = R_s + 400 + \frac{100 \times 100}{200} = R_s + 450\Omega$$

The value of the multiplier therefore is


$$R_s = 2,250 - 450 = 1,800\Omega$$

(b) The sensitivity of the voltmeter on this 10-V ac range is

$$S = \frac{2,250\Omega}{10\text{V}} = 225\Omega/\text{V}$$

For FW

$E_{dc} = 0.9 E_{rms}$

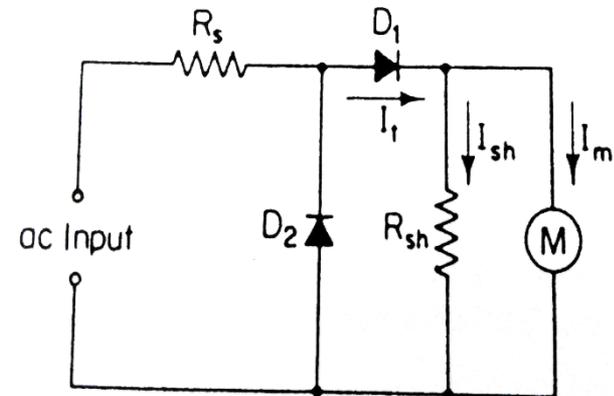

MULTIRANGE VOLTMETER CIRCUIT EXAMPLE


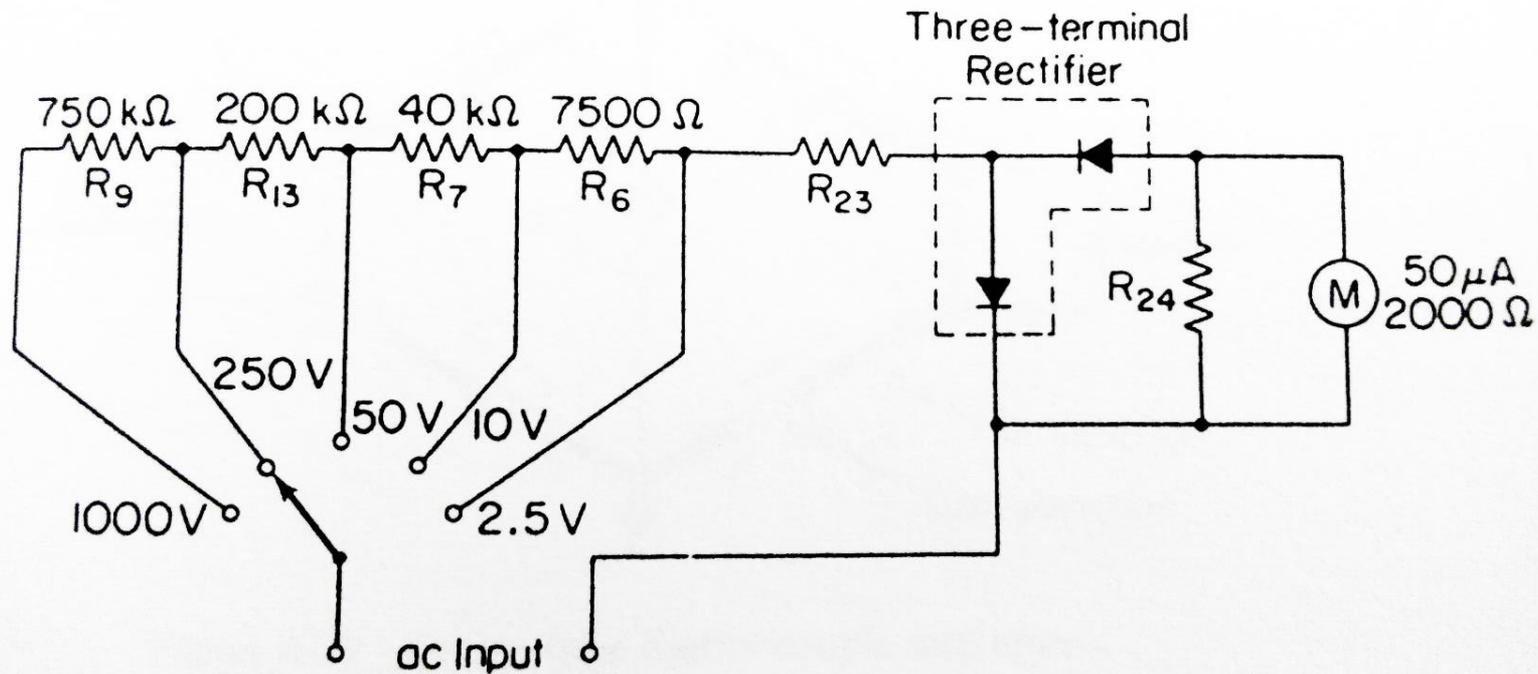



Figure 4-36 Multirange ac voltmeter circuit of the Simpson Model 260 multimeter (courtesy of the Simpson Electric Company).

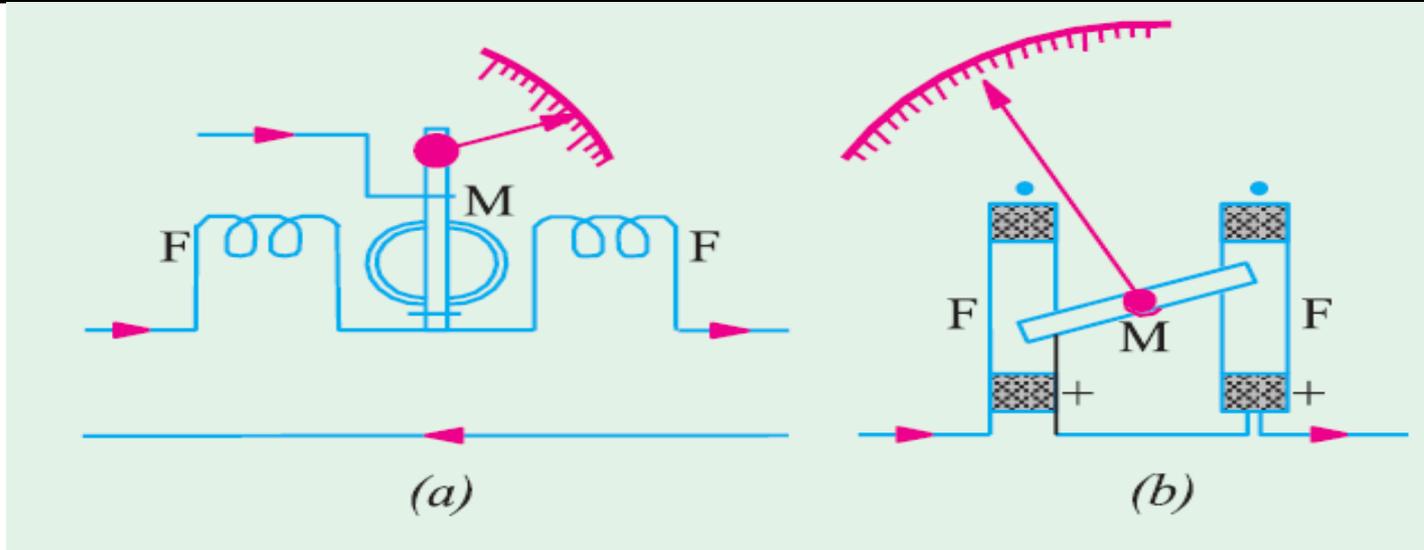Dynamometer or Electrodynamamic Instrument




- **Operating magnetic field** is produced by a pair of fixed coils (field coils)
- Fixed coils are placed closed together, parallel to each other & air-cored
- Air core: to avoid *hysteresis* effects and to provide magnetic field for moving coil to move more uniformly
- *Used in low freq.*

ElectroDynamometer

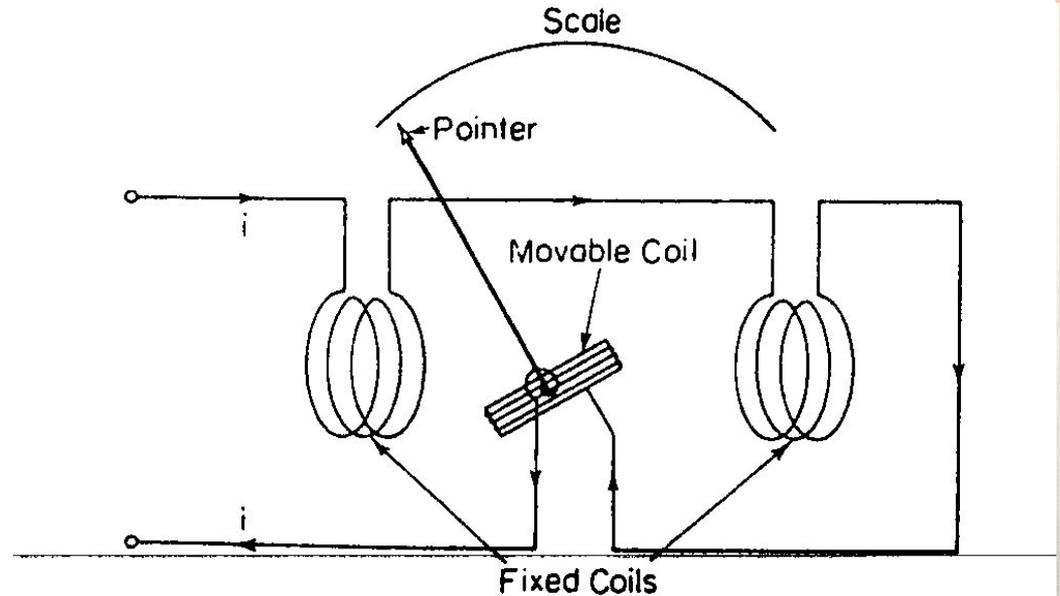

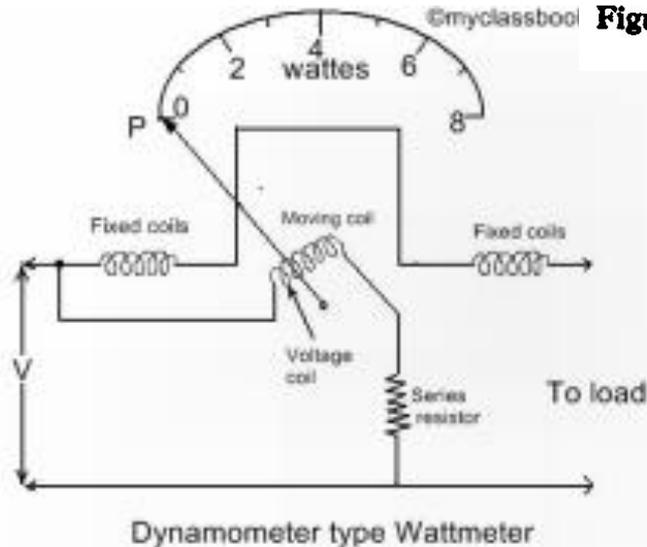©myclassbook **Figure 4-30** Schematic diagram of an electro-dynamometer movement.



➤ Generally used as *wattmeter*


ELECTRODYNAMOMETER

- The working principle of a basic electrodynameometer instrument is same as the PMMC instrument.
- The only difference in this case is that the permanent magnet is **replaced with two fixed coils** connected in series.
- The **moving coil** is also connected in **series** with the fixed coils.
- The **two fixed coils** are connected to electromagnets in such a manner that they form poles of **opposite polarity**.
- As the moving coil **carries** current through it and it being **placed** in the field of fixed coils, it experience a **force** due to which the **moving coil rotates**.

ELECTRODYNAMOMETER


$$I = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\text{average } i^2}$$

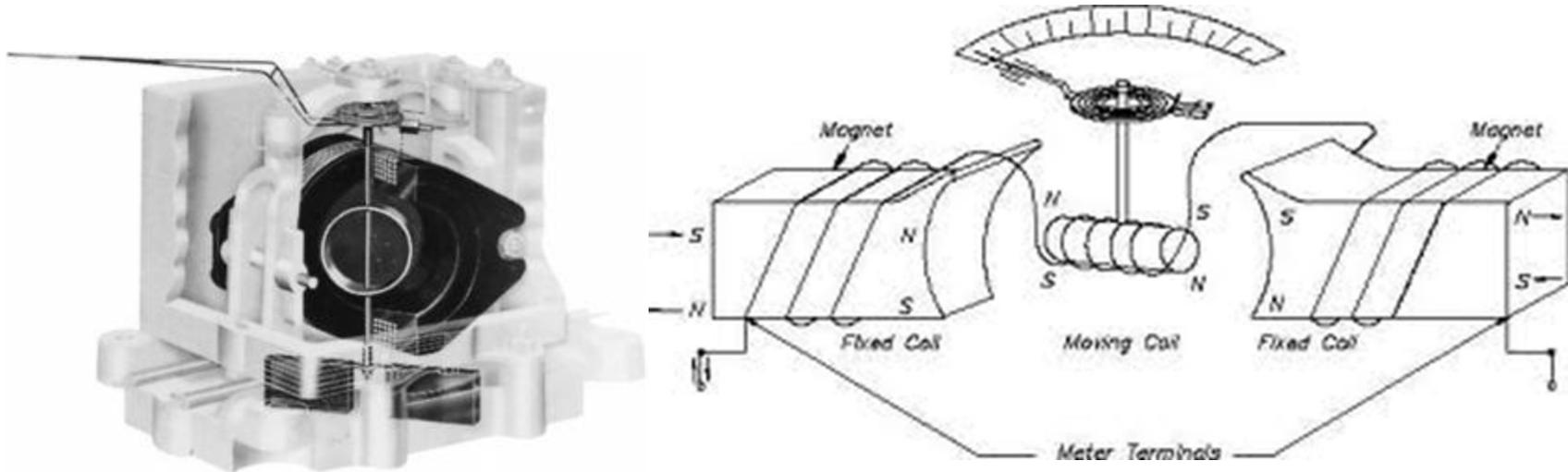The Electrodynamometer reads the current ***I*** (the *root mean square*) which equivalent to **DC value.**




ELECTRODYNAMOMETER

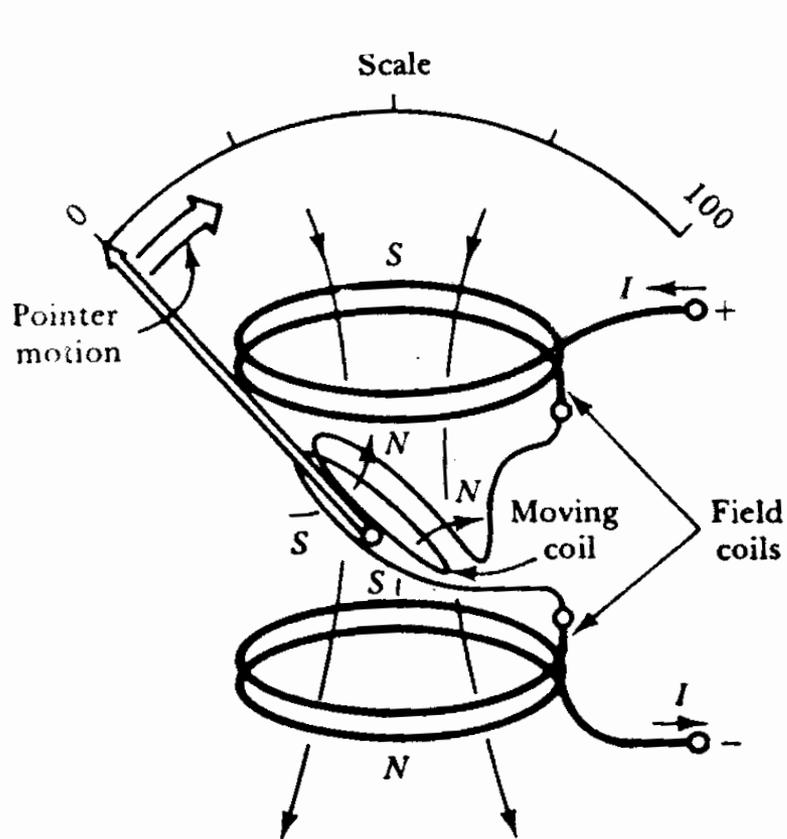Positive deflection of pointer occurs in an electrodynamic instrument regardless of current direction. The instrument can be used directly for both ac and dc measurements.



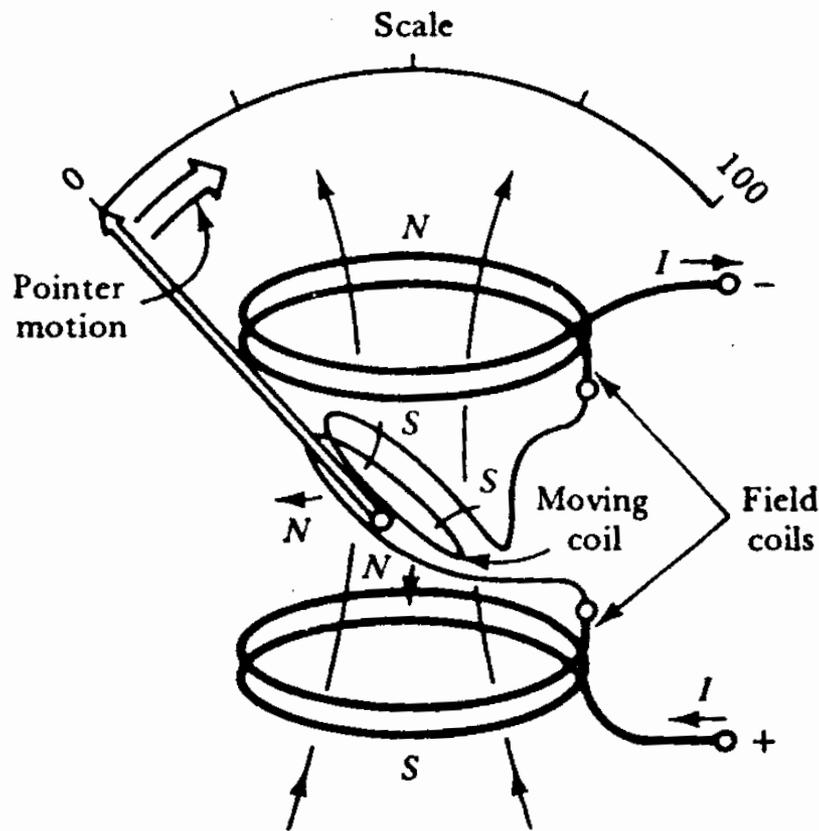
(a) Current flowing from top to bottom produces positive deflection



(b) Current flowing from bottom to top also produces positive deflection


Electrodynamometer as Ammeter

Without shunt

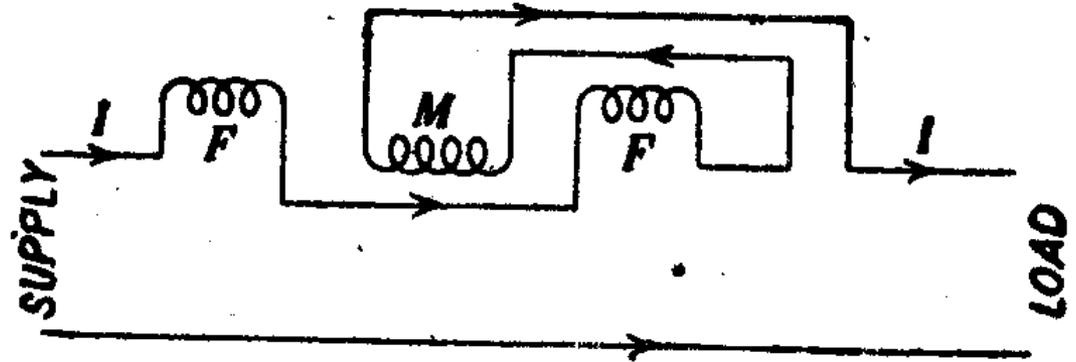


$I_1 =$ fixed coil I , $I_2 =$ moving coil I

With a shunt

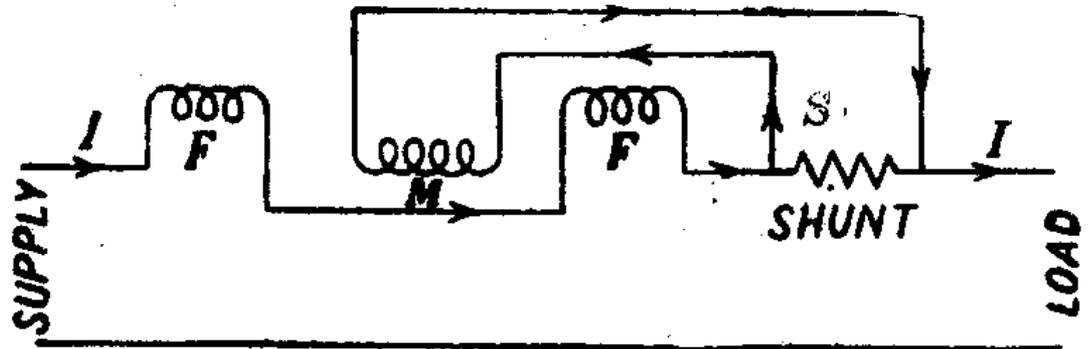

Electrodynamometer as Voltmeter

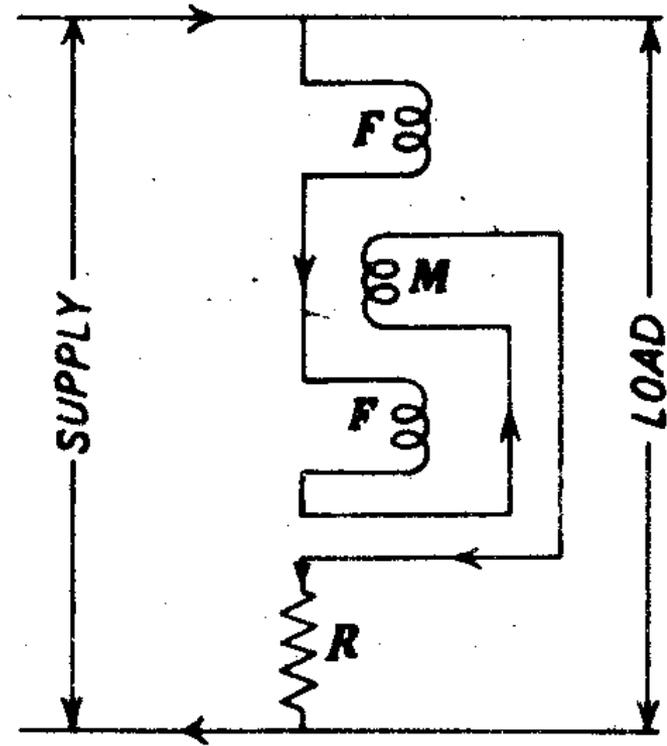


Damping :

- Pneumatic (air chamber or vanes)
- Eddy current damping is not efficient due to weak operating magnetic field.

ELECTRODYNAMOMETER POWER MEASUREMENTS

Wattmeter

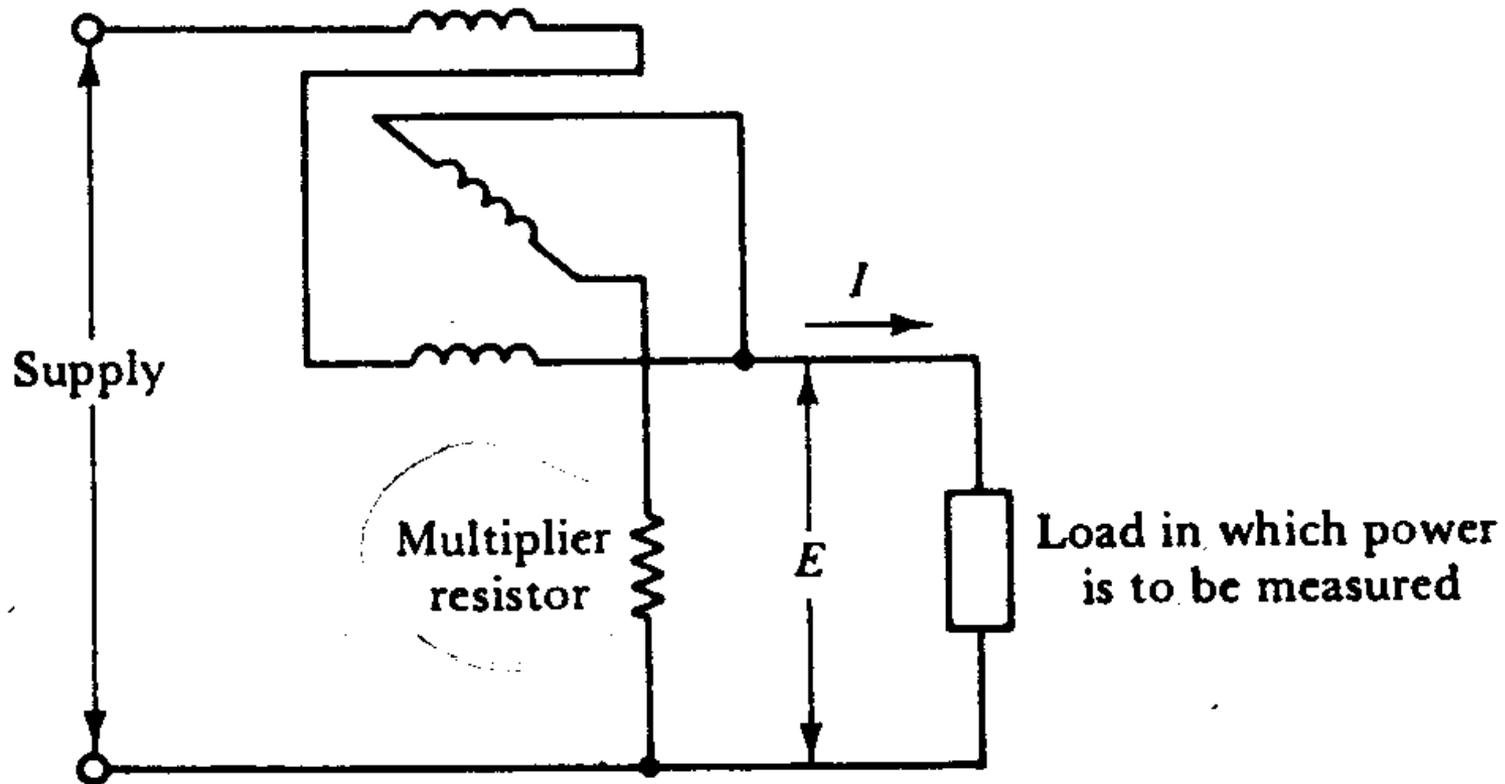


(a) Electrodynamic wattmeter circuit

The deflection of the moving coil is proportional to the **product of the i_p and i_c**

The **average deflection** over a period:

$$i_p = e / R_p$$

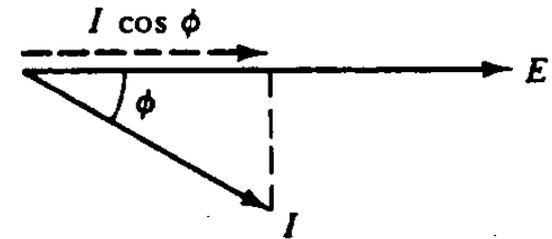
$$\theta_{av} = K \frac{1}{T} \int_0^T i_c i_p dt = K_2 \frac{1}{T} \int_0^T ei dt$$



$$P_{av} = \frac{1}{T} \int_0^T ei dt$$

$$\theta_{av} = K_3 EI \cos \theta$$

(c) Wattmeter measures $EI \cos \phi$

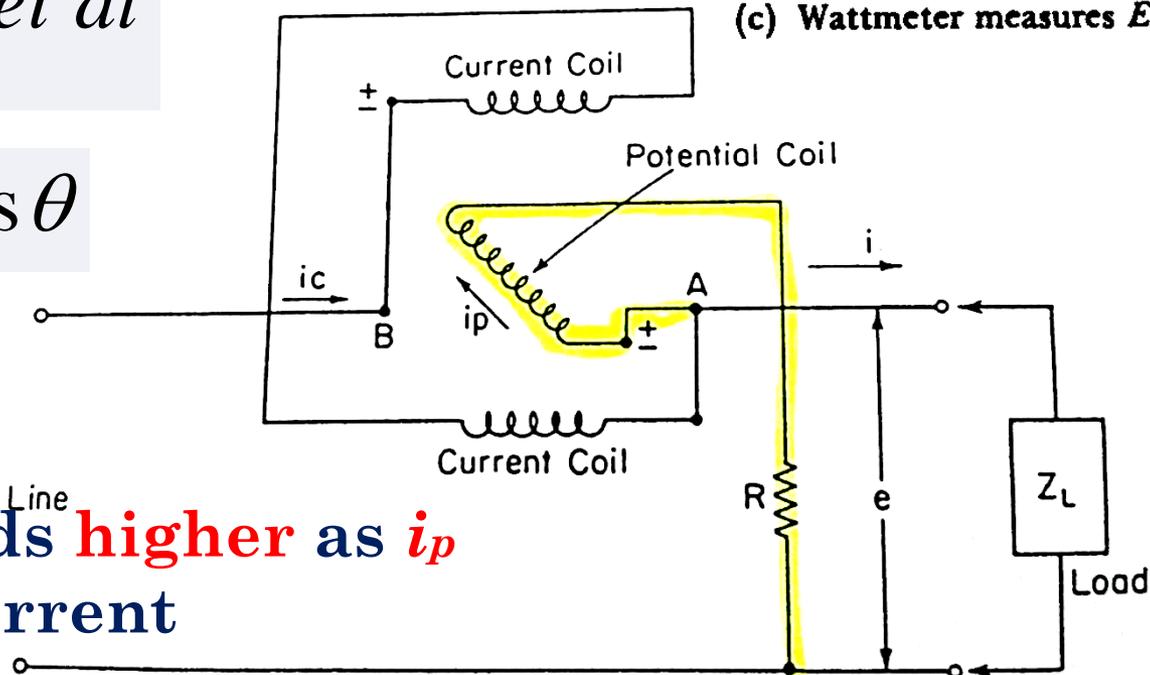

Wattmeter reads **higher** as i_p is not a load current

WATTMETERS

To compensate the current i_p to get more accurate reading of the power.

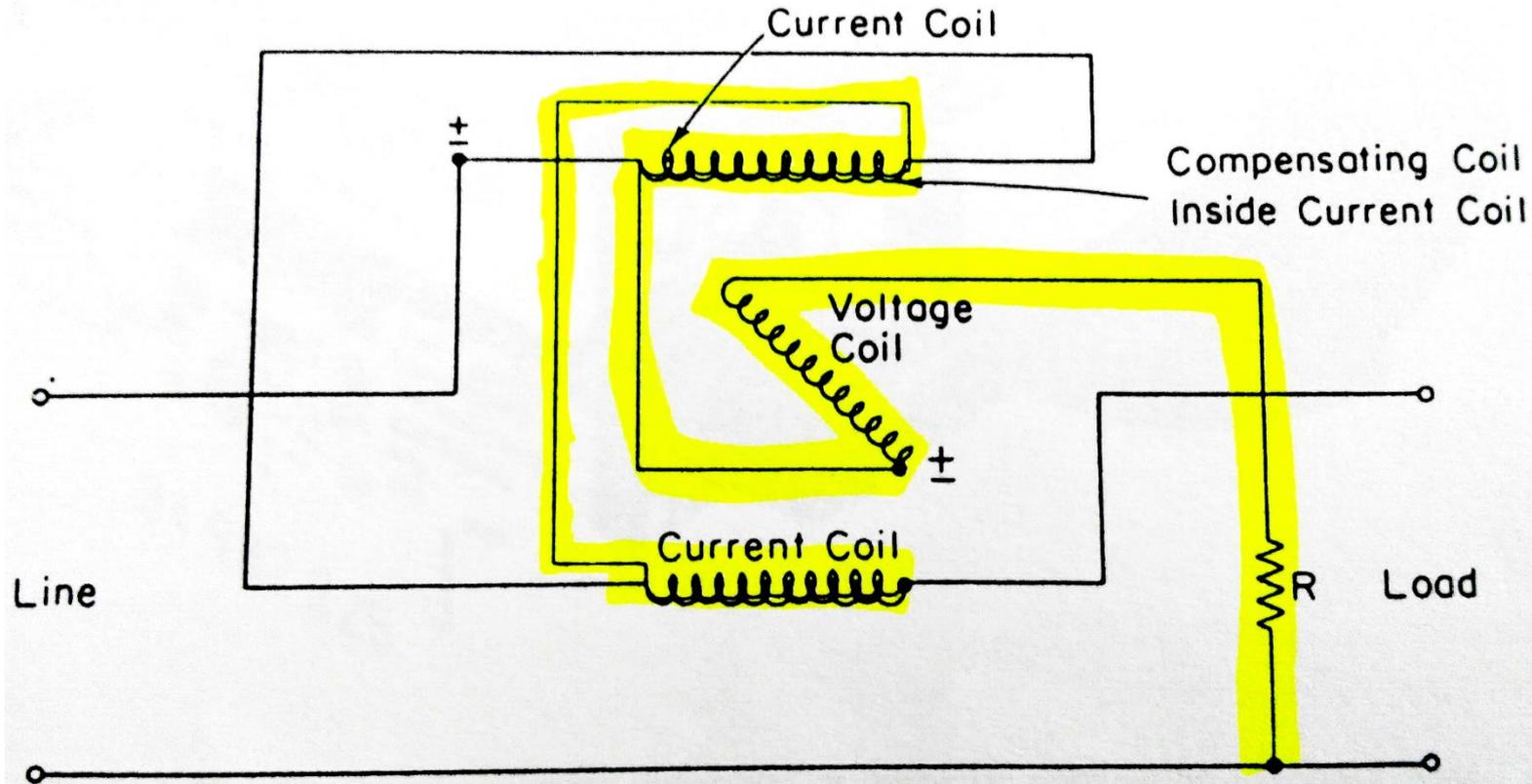


Figure 4-41 Diagram of a compensated wattmeter in which the effect of the current in the potential coil is canceled by the current in the compensating winding.

ELECTRONIC WATTMETERS

Why using the Electronic Watt-Meters:

- ✓ Small power measurements.
- ✓ Power measurements at frequencies beyond the range of electro-dynamometer type instruments.
- ✓ It has a higher accuracy than the analog meters.



WATTHOUR METERS

Current coil in series with line

Voltage coil connected across the line

Eddy currents flow in the disk

Reaction of Eddy currents creates a torque (**rotates**)

The number of rotations is proportional to the energy consumed (**KWh**)



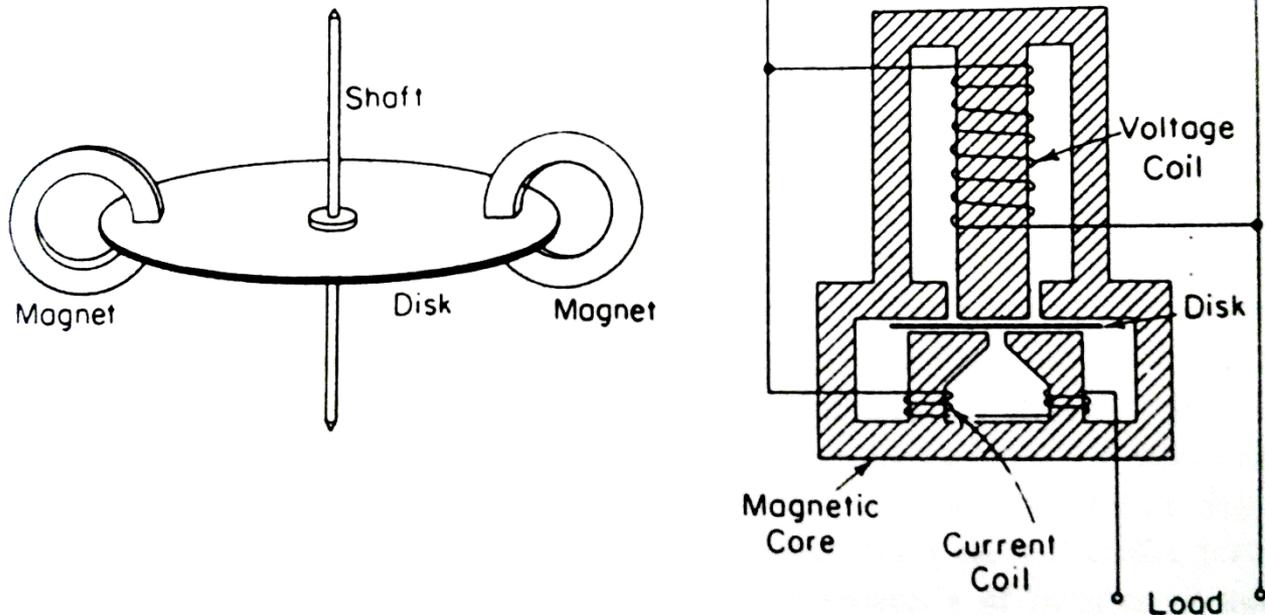


Figure 4-42 Elements of a single-phase watt-hour meter.


WATTHOUR METERS

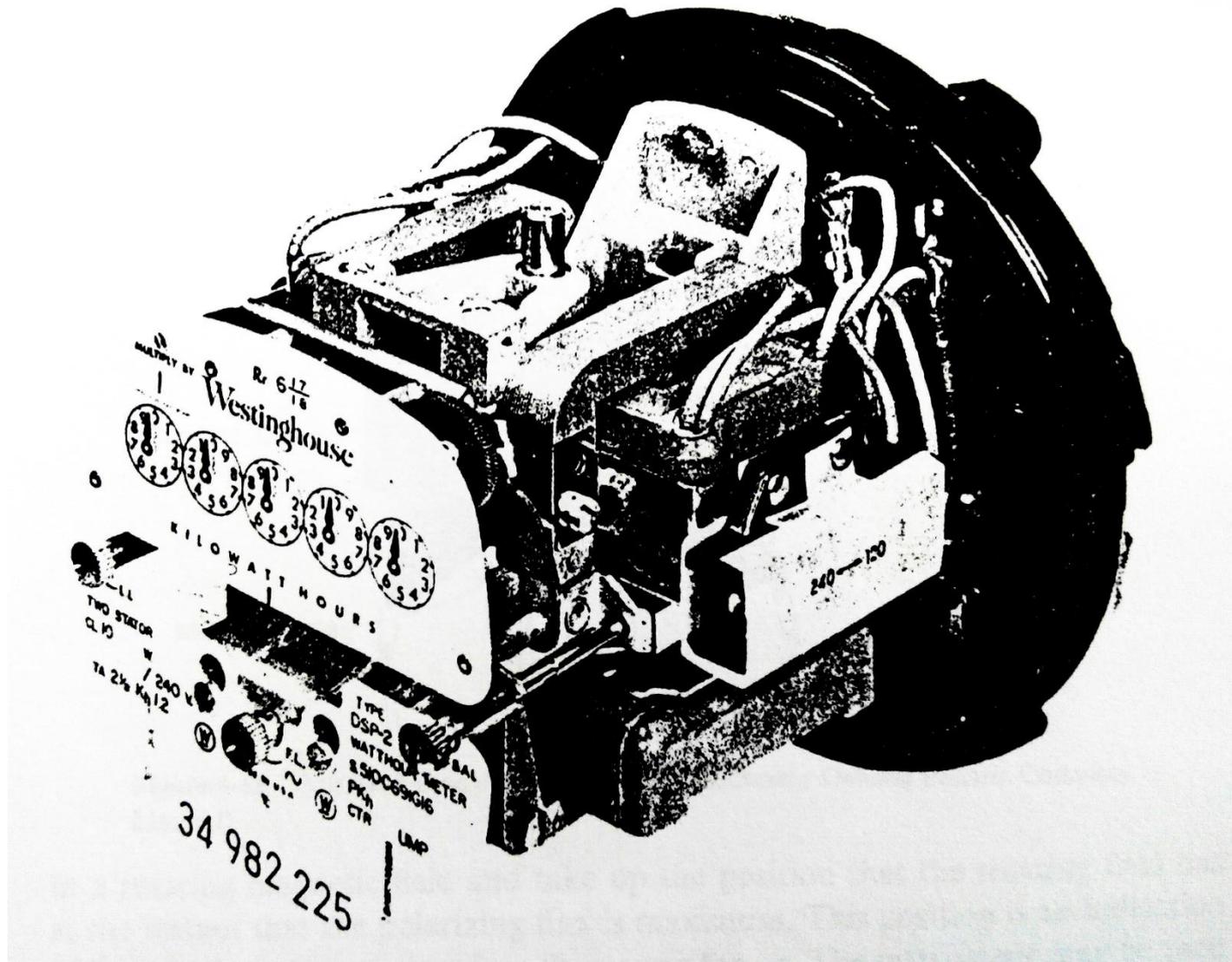

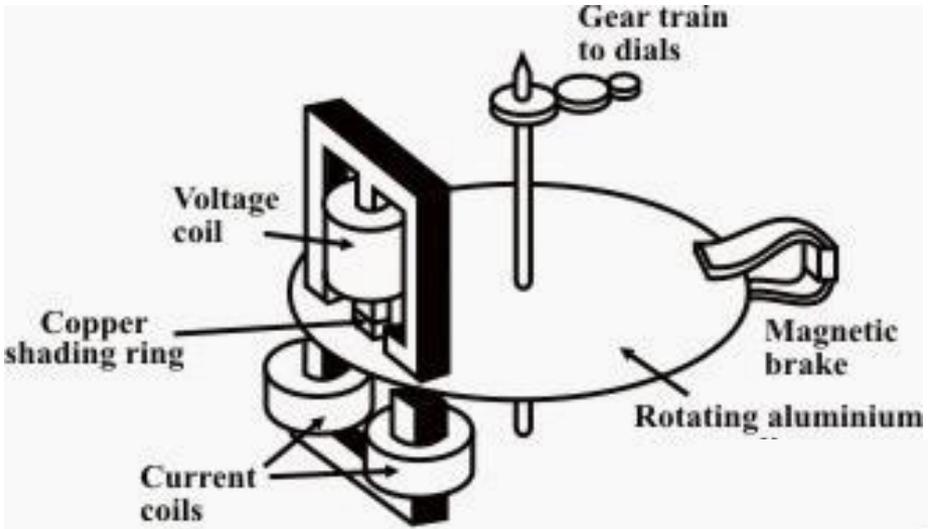Overview of Single Phase Induction Type Energy Meter



Watt-hour mete

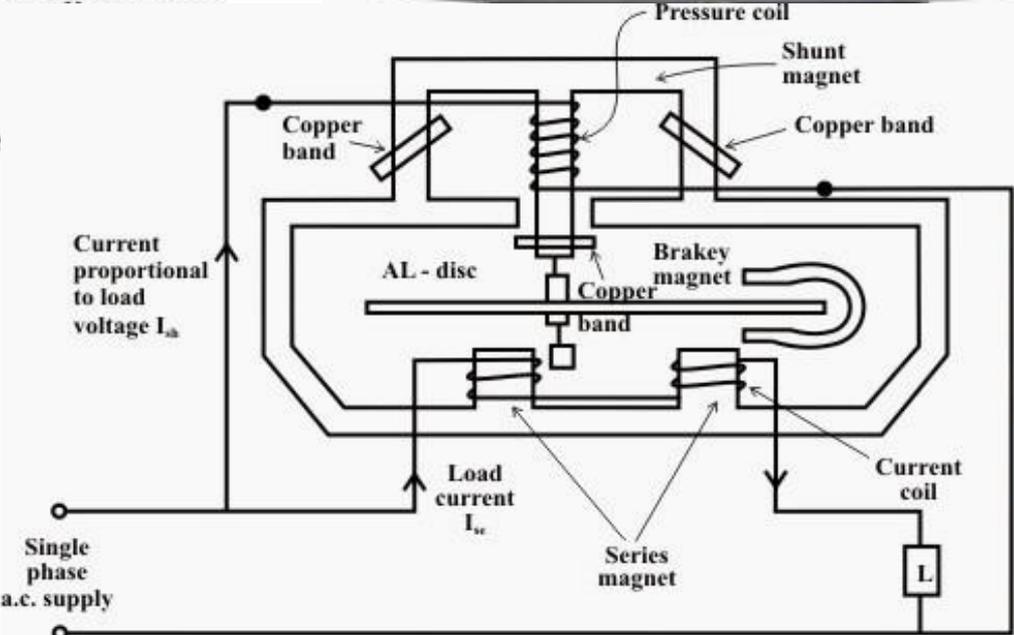


POWER - FACTOR METERS

Power Factor Meters are meant for measuring power factor of a circuit as the ratio between the effective true power & the apparent power.

$$P.F = \cos \phi = \frac{\text{True Power}}{\text{Apparent Power}} = \frac{V.I.\cos \phi}{V.I}$$

The power factor is **indirectly** determined by measuring the **phase angle** (ϕ) between **current** and **voltage**.

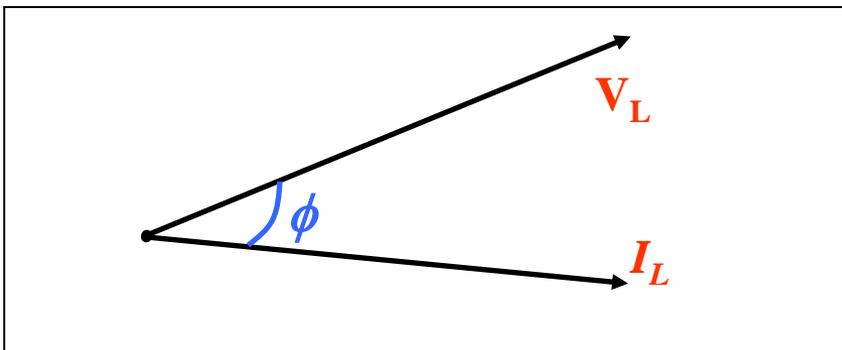However, the **indicators** are calibrated in values of **cos** (ϕ)



POWER-FACTOR METERS

The torque is also proportional to the mutual inductance between each part of the crossed coil and the stationary field coil. This mutual inductance depends on the angular position of the crossed-coil elements with respect to the position of the stationary field coil. When the movable element is at balance, it can be shown that its angular displacement is a function of the phase angle between line current (field coil) and line voltage (crossed coils). The indication of the pointer, which is connected to the movable element, is calibrated directly in terms of the phase angle or power factor.


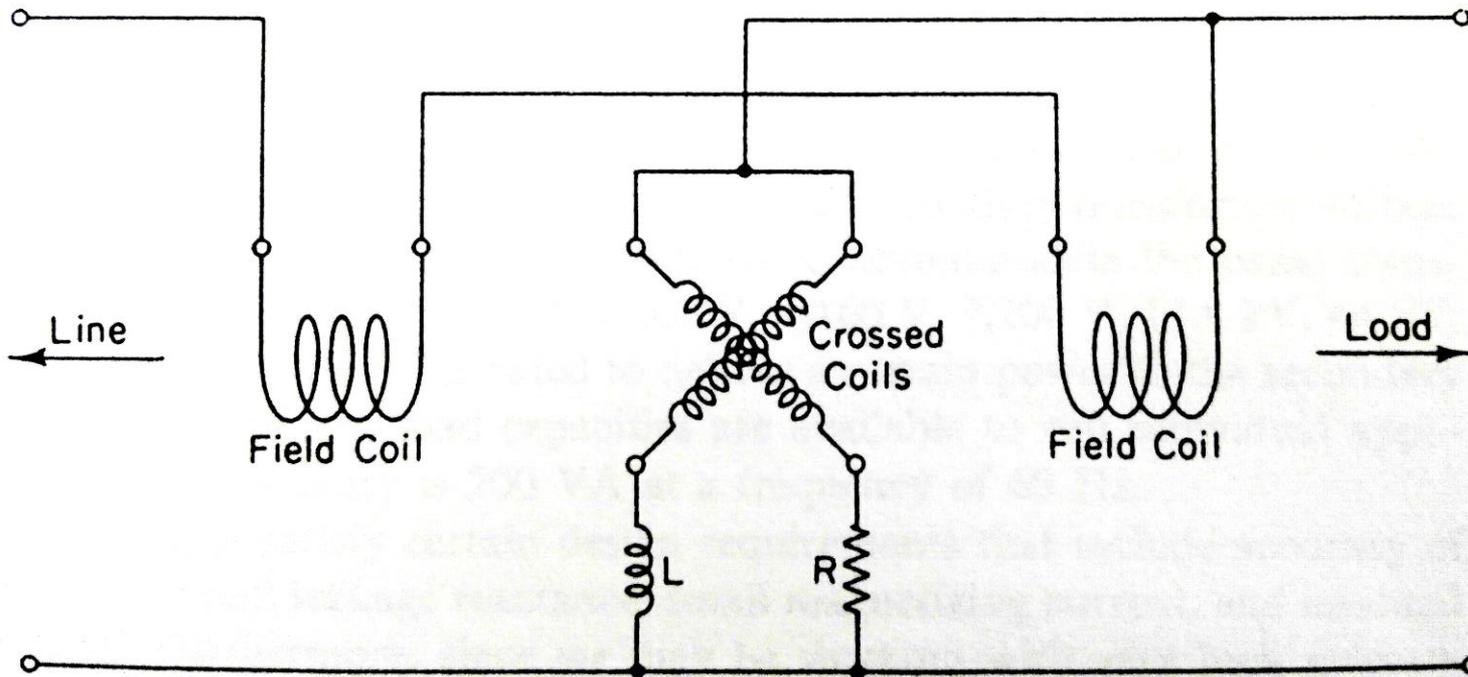


Figure 4-44 Connections for a single-phase crossed-coil power-factor meter.

POWER-FACTOR METERS

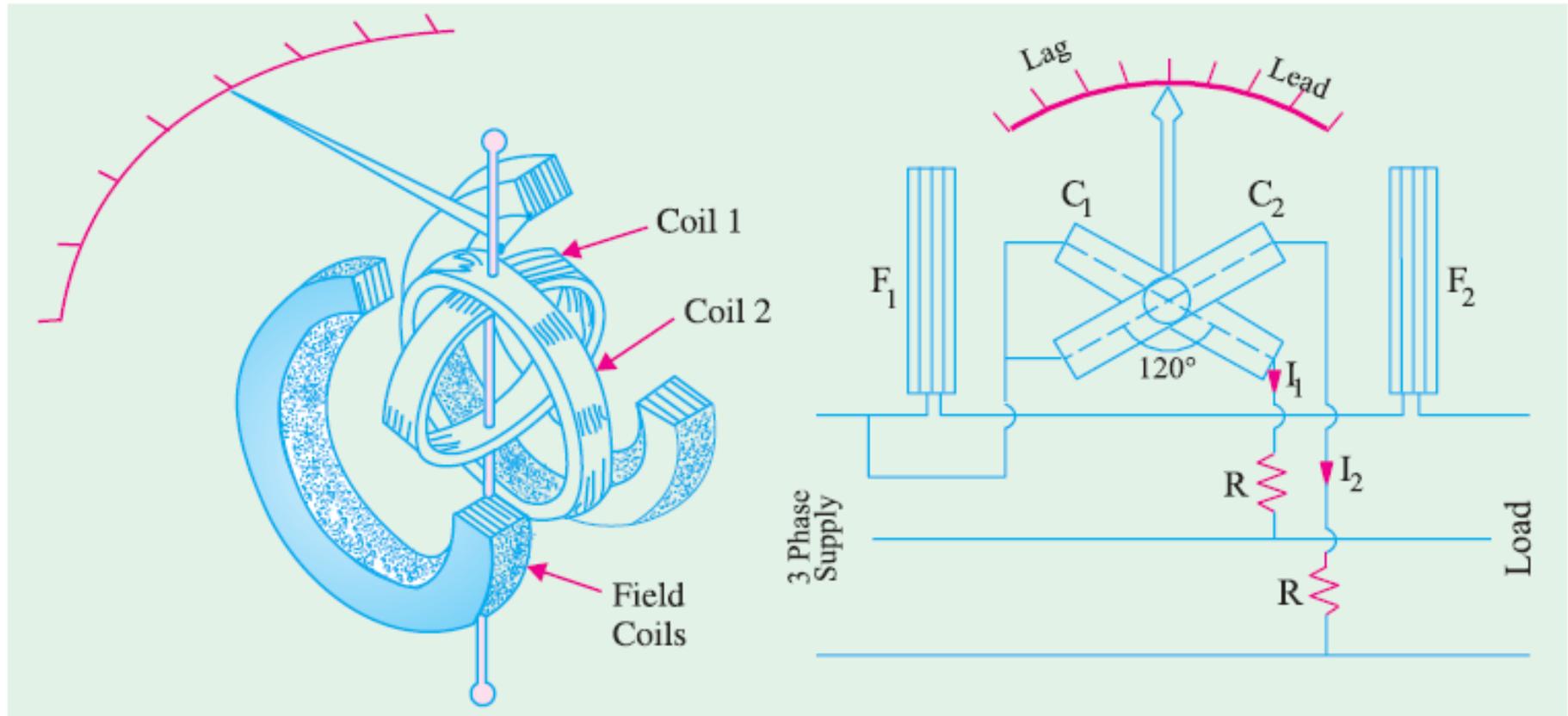

For reliable readings, the instrument has to be calibrated at the frequency of the supply on which it is to be used. At any other frequency (or when harmonics are present), the reactance of L will change so that the magnitude and phase of current through C_2 will be incorrect and that will lead to serious errors in the instrument readings.

POWER-FACTOR METER

called a *cross coil power factor meter*.


It has two moving coils (**A** and **B**), mounted on the same shaft.

The currents in the two coils are equal in magnitude but **displaced** in time by **90**. This is achieved by **setting** ($R = \omega L$).

For **unity** power factor ($\phi=0$), the current in coil (**A**) will be in phase with the I_L , while the current coil (**B**) will be out of phase by 90.

Thus, there will be a torque T_A acting on coil (**A**) alone, the other coil experiencing **zero torque**.

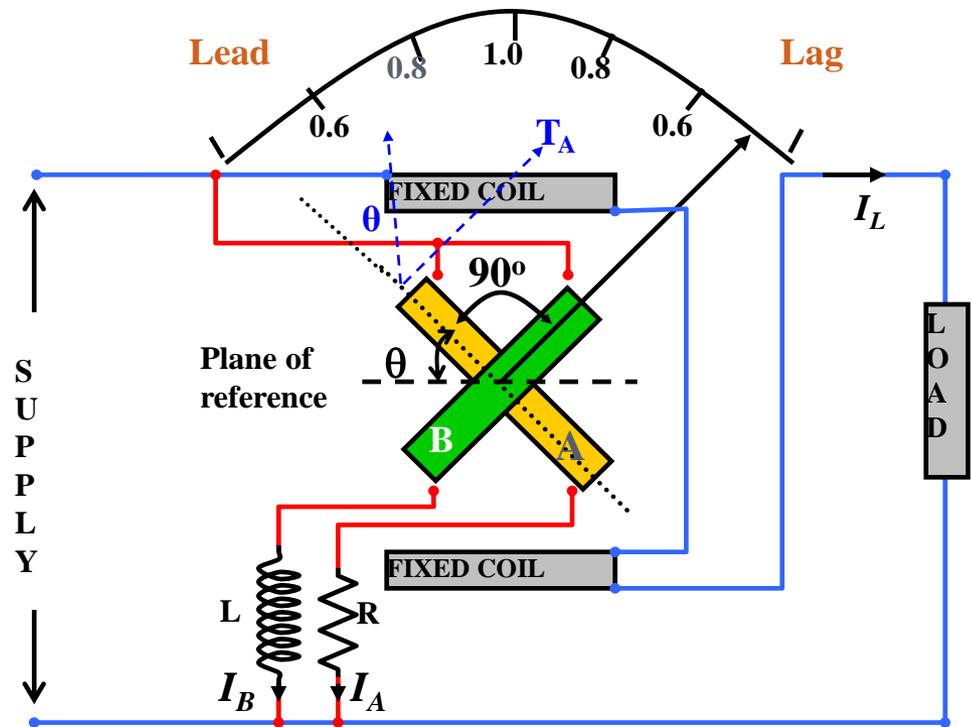Consequently coil (**A**) will rotate until it is perpendicular with the fixed coils. Under this condition, the pointer **shows a reading equal to '1'**




$$T_A = K * V_L * I_L * \cos \phi * \sin \theta.$$

$$T_B = K * V_L * I_L * \cos (90^\circ - \phi) * \sin (90^\circ + \theta).$$

FOR A **P.F.** EQUAL TO ZERO ($\phi=90$),
THE CURRENT IN THE COIL (**B**) IN
PHASE WITH THE I_L .

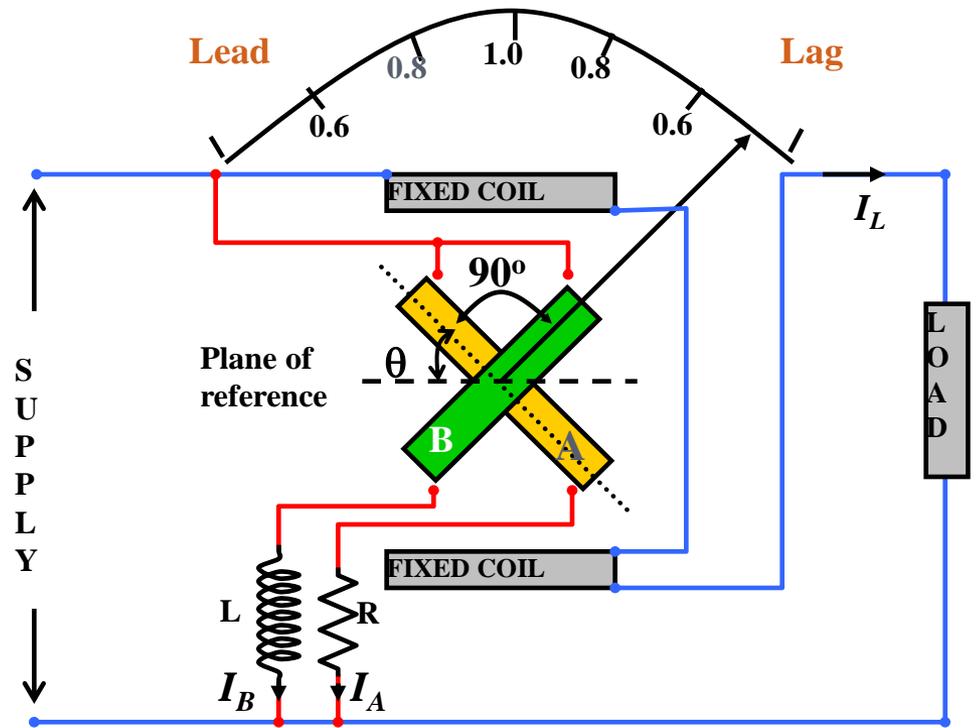THUS, COIL (**B**) WILL NOW ROTATE
UNTIL IT IS PERPENDICULAR WITH
THE FIXED COILS.




$$T_A = K * V_L * I_L * \cos \phi * \sin \theta. \quad (\text{equal to } \rightarrow 0)$$

$$T_B = K * V_L * I_L * \cos (90^\circ - \phi) * \sin (90^\circ + \theta).$$

$$\therefore T_B = K * V_L * I_L * \sin (\phi) * \cos (\theta).$$

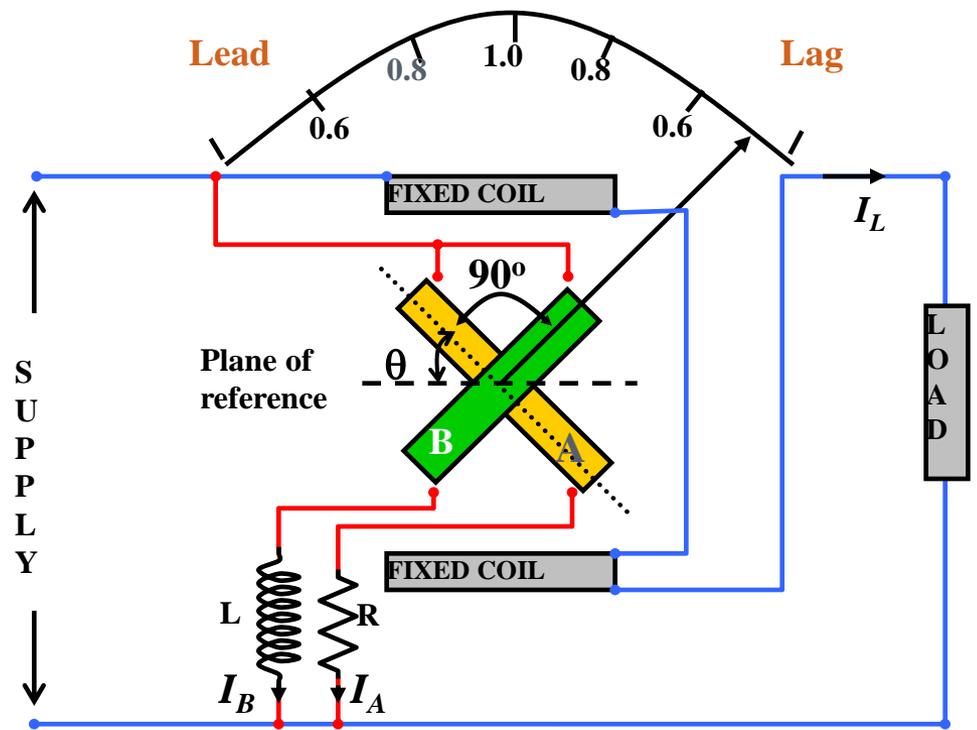FOR OTHER P.F. LYING BETWEEN 0 AND 1, THE DEFLECTION OF THE COILS WILL BE TO SOME INTERMEDIATE POSITION DEPENDING ON THE VALUE OF THE P.F. THE DIRECTION DEPEND ON THE NATURE OF THE POWER FACTOR : LAG OR LEAD.



$$T_A = K * V_L * I_L * \cos \phi * \sin \theta.$$

$$\text{and } T_B = K * V_L * I_L * \cos (90^\circ - \phi) * \sin (90^\circ + \theta).$$

$$\therefore T_B = K * V_L * I_L * \sin (\phi) * \cos (\theta).$$

in the **resting position**, the two torque forces T_A and T_B have to balance themselves.

$$K * V_L * I_L * \cos \phi * \sin \theta = K * V_L * I_L * \sin (\phi) * \cos (\theta)$$

$$\therefore \phi = \theta$$

Thus, the scale is calibrated to automatically reflect the power factor.

POWER-FACTOR METERS

Sec. 4-17 Instrument Transformers

103

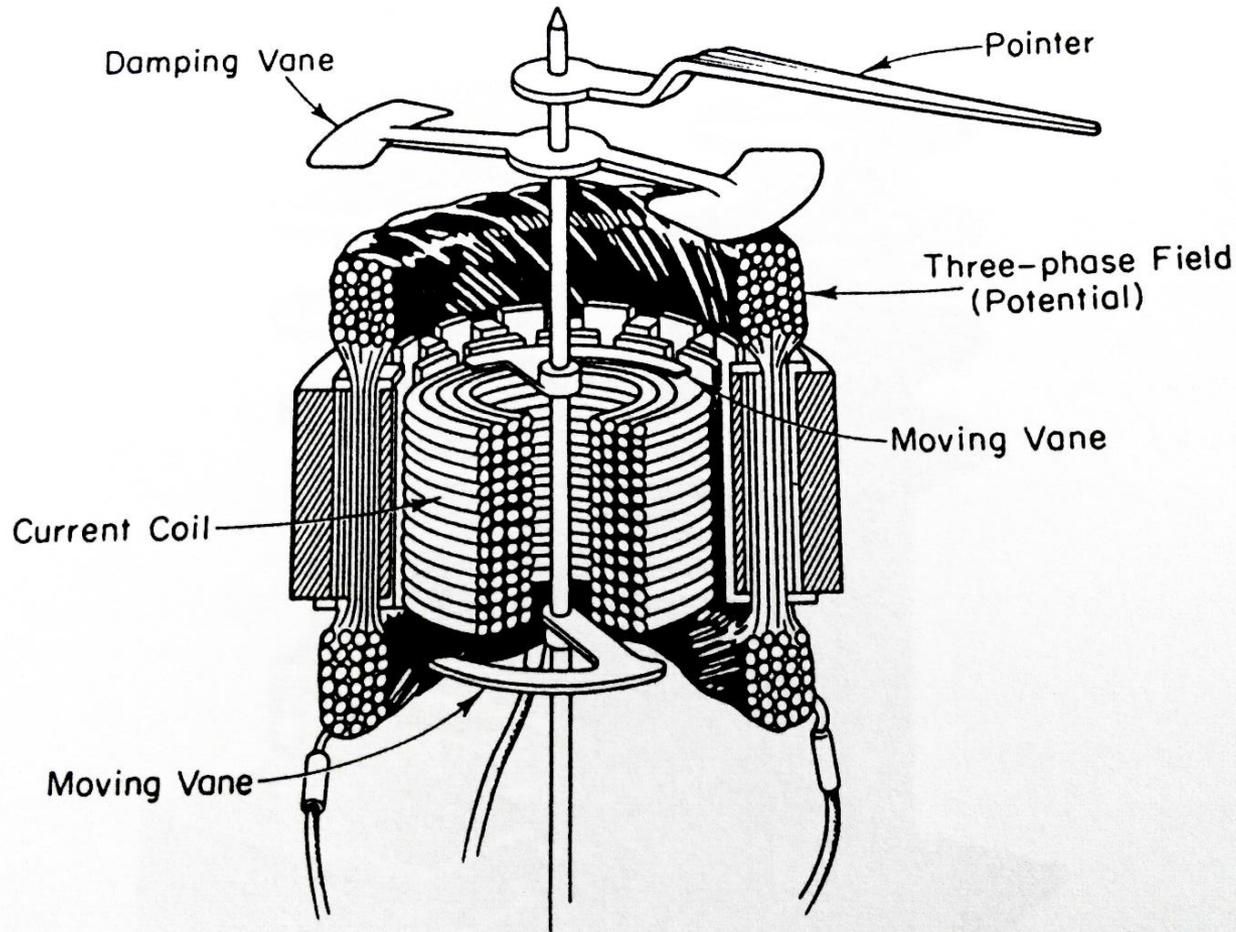


Figure 4-45 Polarized-vane power-factor meter (courtesy General Electric Company Limited).

INSTRUMENT TRANSFORMER

Function:

1. Extend the range ac measurement
2. Isolate the measuring instrument from high voltage power line.

Types

1. Current Transformer (CT)
2. Potential Transformer (PT)



Figure 4-47 Current transformer (courtesy Westinghouse Electric Corporation).



Potential transformer

INSTRUMENT TRANSFORMER

1. Extend the range ac measurement using resistors is more **suitable** for DC measurement.
2. In ac measurements the circuits **reactance** is frequency dependent, so to get more accurate measurement over a range of freq. Transformers.
3. The **range** of extension depends of the transformer ratio.

The Isolation of the measuring instrument from high voltage power line is **important due to**:

- safety hazards and
- insulation difficulties of high voltage lines.

INSTRUMENT TRANSFORMER

voltmeters, and two ammeters. The potential transformers are connected across phase lines *A* and *B*, and phase lines *C* and *B*; the current transformers are in

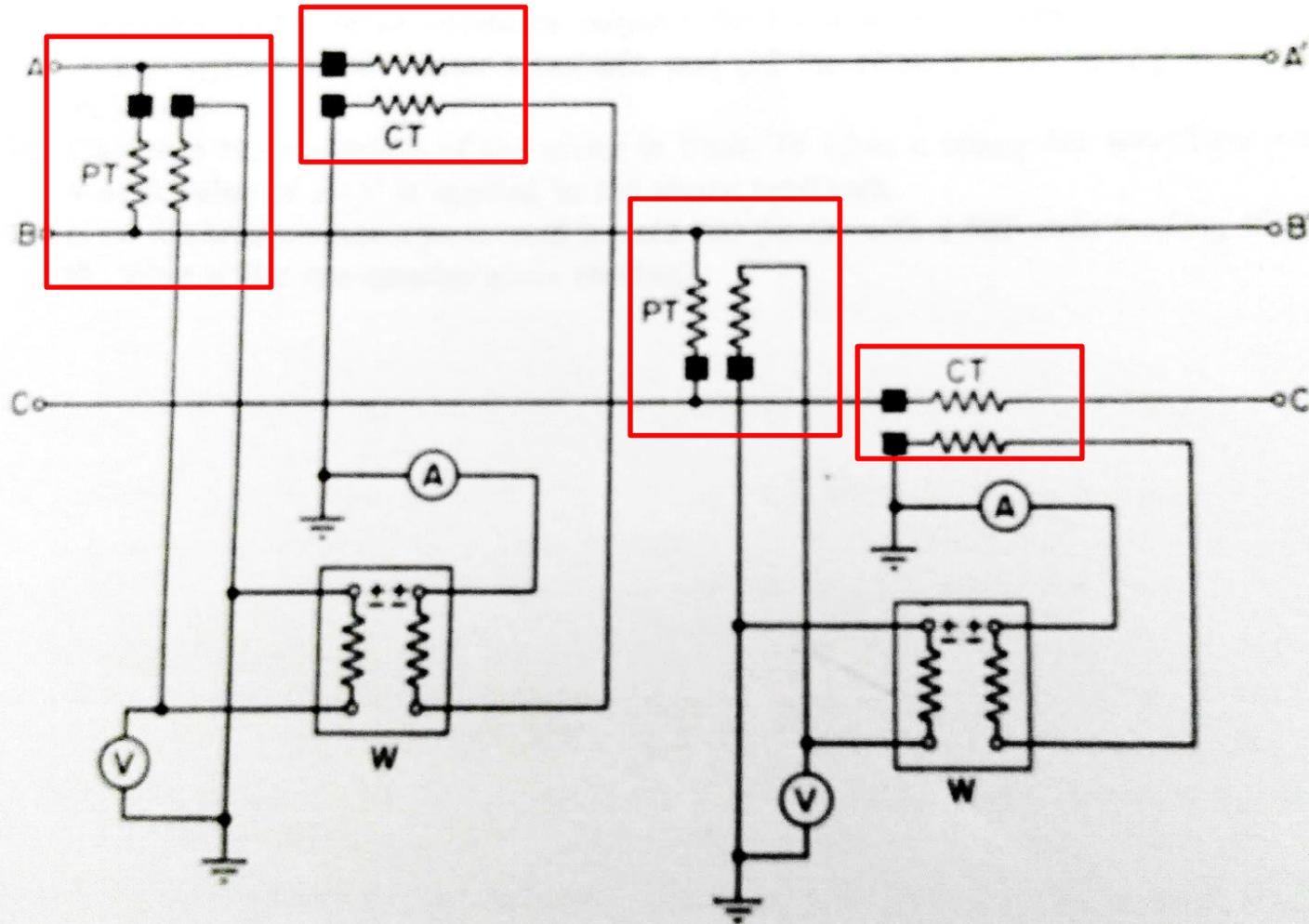


Figure 4-48 Instrument transformers in a three-phase measurement application. Polarity markings of the potential and current transformers are indicated by black

