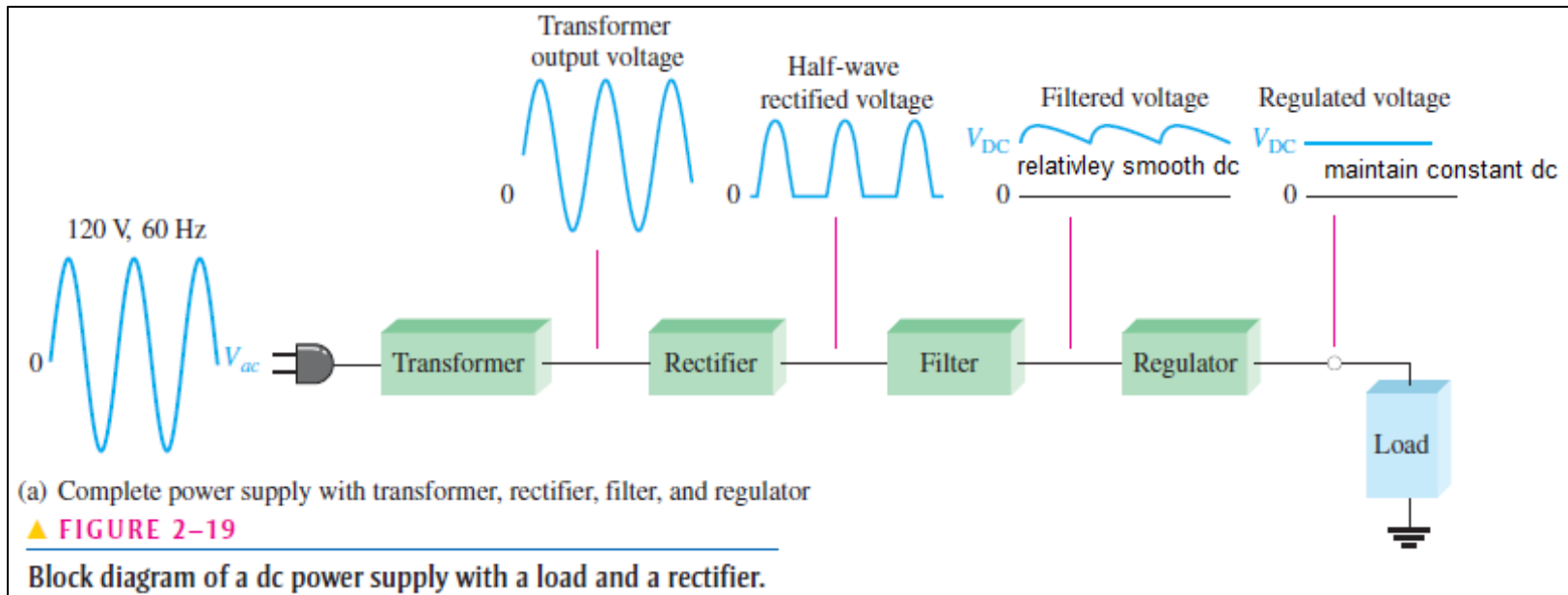


## 2-4 Half-Wave Rectifiers

- ▶ Because of their ability to conduct current in one direction and block current in the other direction, diodes are used in circuits called **rectifiers** that **convert ac voltage into dc voltage**.
- ▶ Rectifiers are found in all **dc power supplies** that operate from an ac voltage source. A power supply is an essential part of each electronic system from the simplest to the most complex.

### The Basic DC Power Supply




## 2-4 Half-Wave Rectifiers

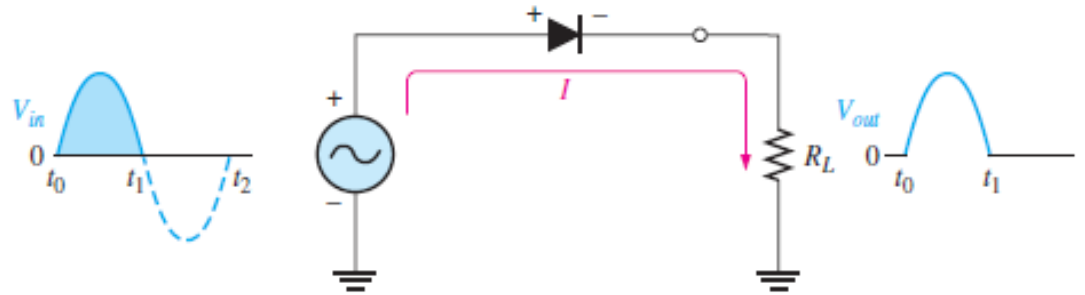
### Operation:

► Assume ideal diode ( neglect barrier potential 0.7)


□ During the positive half-cycle of the input voltage, the output voltage looks like the positive half of the input voltage. The current path is through ground back to the source.



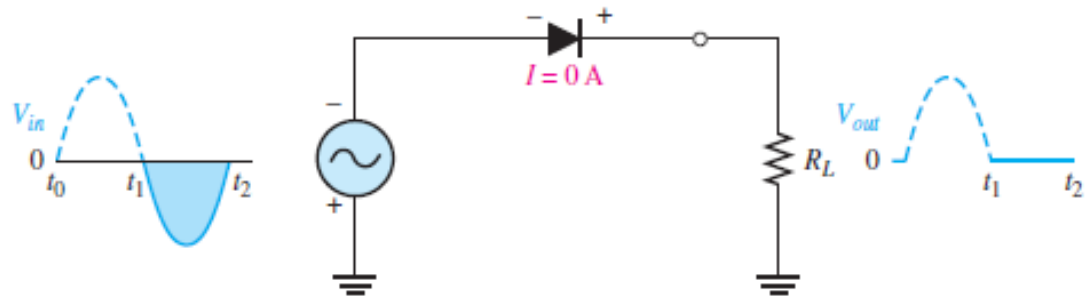□ During the negative half-cycle of the input voltage, the current is 0, so the output voltage is also 0.



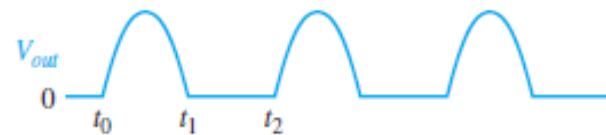□ The half-wave output voltage for three input cycles ►




## 2-4 Half-Wave Rectifiers

### Average Value of the Half-Wave Output Voltage

(measured on a dc voltmeter).

- assume ideal diode, neglect barrier potential 0.7
- **Mathematically:** the area under a full cycle divided by  $2\pi$  (the number of radians in a full cycle)

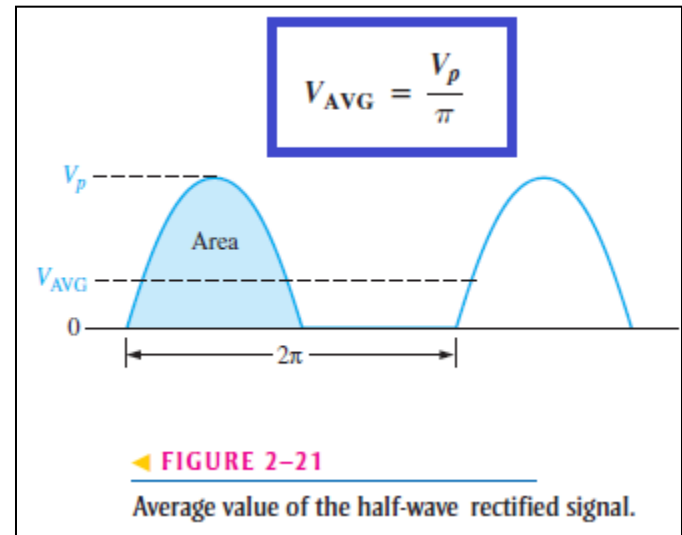
**V<sub>p</sub>**: peak value of the rectified voltage



#### EXAMPLE 2-2

What is the average value of the half-wave rectified voltage in Figure 2-22?


#### ▶ **FIGURE 2-22**

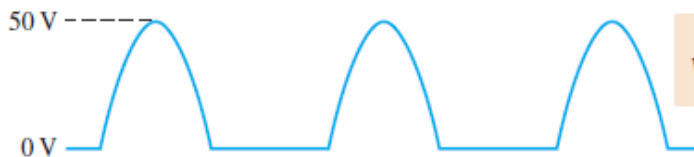

$$V_{AVG} = \frac{V_p}{\pi} = \frac{50 \text{ V}}{\pi} = 15.9 \text{ V}$$

## 2-4 Half-Wave Rectifiers

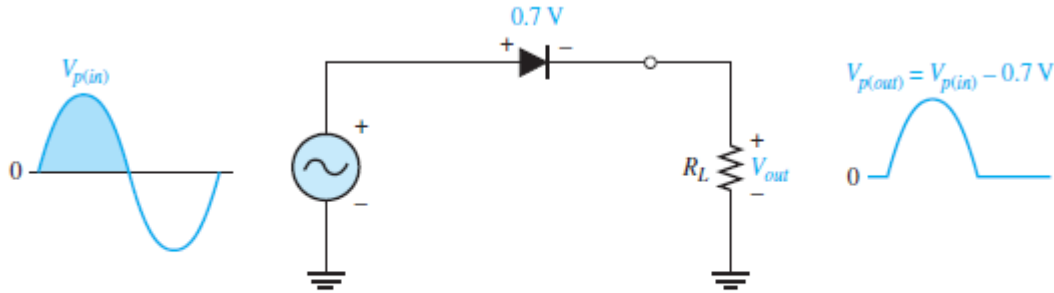
### ► Effect of the Barrier Potential on the Half-Wave Rectifier Output



▲ FIGURE 2-23

The effect of the barrier potential on the half-wave rectified output voltage is to reduce the peak value of the input by about  $0.7\text{ V}$ .

### ► Peak Inverse Voltage (PIV)

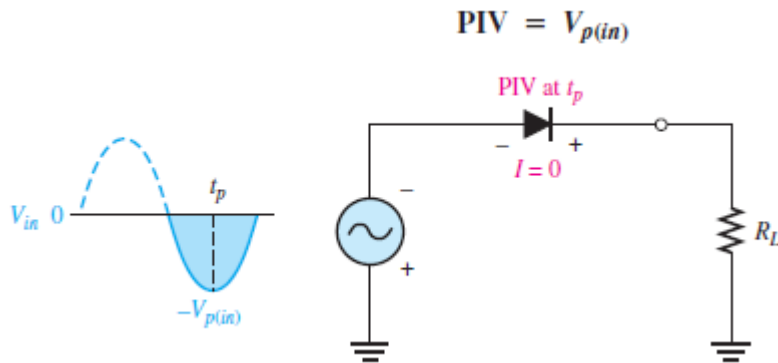



The PIV occurs at the peak of each half-cycle of the input voltage when the diode is reverse-biased. In this circuit, the PIV occurs at the peak of each negative half-cycle.

## 2-4 Half-Wave Rectifiers

### Example
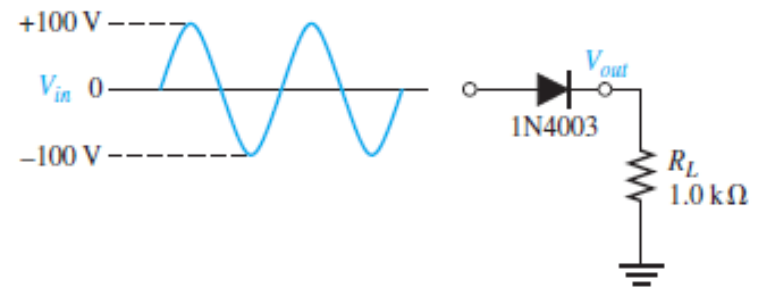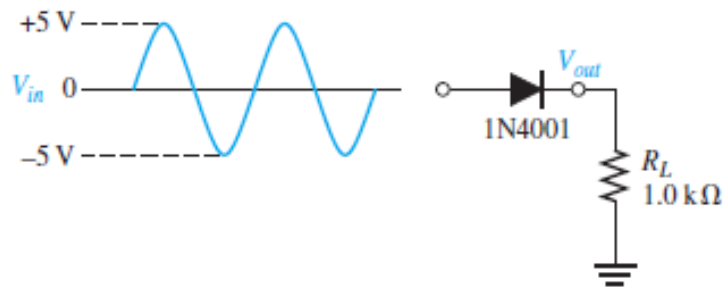
#### EXAMPLE 2-3

Draw the output voltages of each rectifier for the indicated input voltages, as shown in Figure 2-24. The 1N4001 and 1N4003 are specific rectifier diodes.



▲ FIGURE 2-24

*Solution*

$$(a) V_{p(out)} = V_{p(in)} - 0.7 \text{ V} = 5 \text{ V} - 0.7 \text{ V} = 4.30 \text{ V}$$

$$(b) V_{p(out)} = V_{p(in)} - 0.7 \text{ V} = 100 \text{ V} - 0.7 \text{ V} = 99.3 \text{ V}$$




## 2-4 Half-Wave Rectifiers

### Transformer Coupling

Transformer coupling provides two advantages:


- It allows the source voltage to be stepped down as needed.
- The ac source is electrically isolated, thus preventing a shock hazard in the secondary circuit.

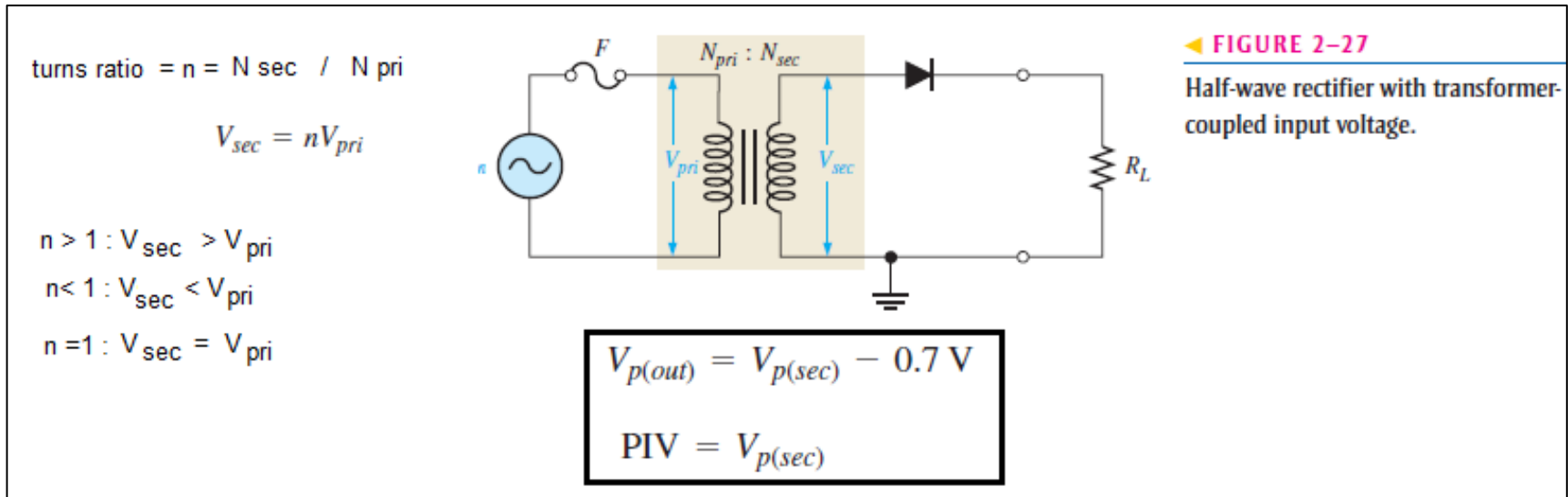

**EXAMPLE 2–4**

Determine the peak value of the output voltage for Figure 2–28 if the turns ratio is 0.5.

► **FIGURE 2–28**

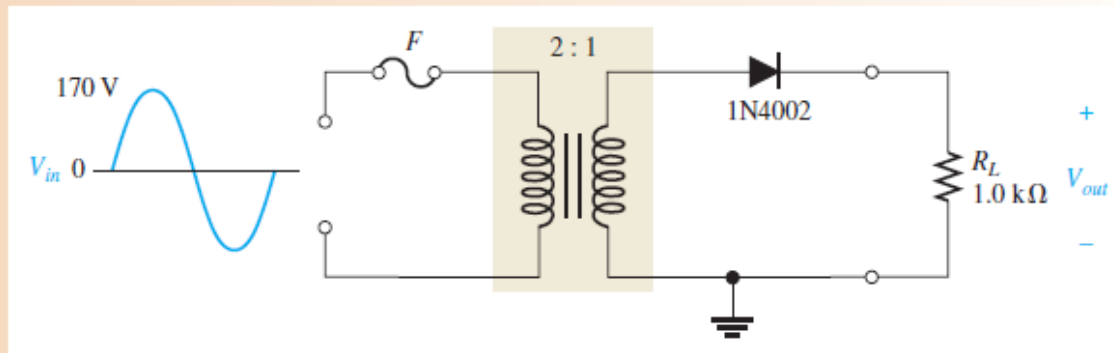

**Solution**

$$V_{p(\text{pri})} = V_{p(\text{in})} = 170 \text{ V}$$

The peak secondary voltage is

$$V_{p(\text{sec})} = nV_{p(\text{pri})} = 0.5(170 \text{ V}) = 85 \text{ V}$$

The rectified peak output voltage is

$$V_{p(\text{out})} = V_{p(\text{sec})} - 0.7 \text{ V} = 85 \text{ V} - 0.7 \text{ V} = 84.3 \text{ V}$$


where  $V_{p(\text{sec})}$  is the input to the rectifier.

**Related Problem**

- Determine the peak value of the output voltage for Figure 2–28 if  $n = 2$  and  $V_{p(\text{in})} = 312 \text{ V}$ .
- What is the PIV across the diode?
- Describe the output voltage if the diode is turned around.
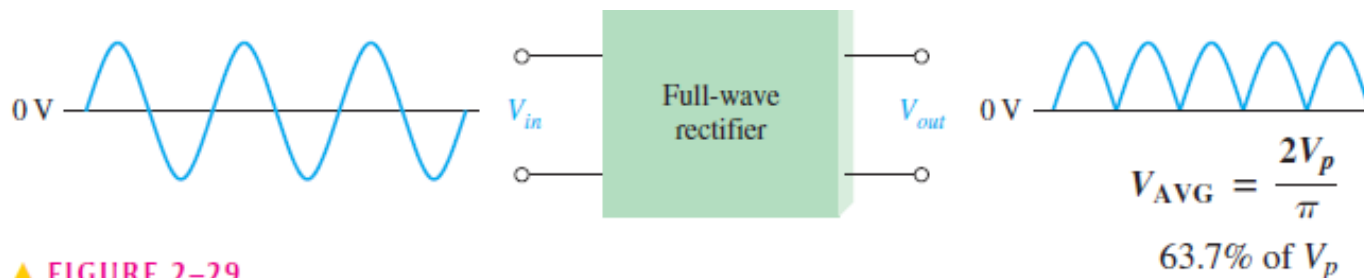
## 2-5 Full-Wave Rectifiers


- ▶ Allows unidirectional (one-way) **current through the load** during the entire 360° of the input cycle



▲ FIGURE 2-29

Full-wave rectification.


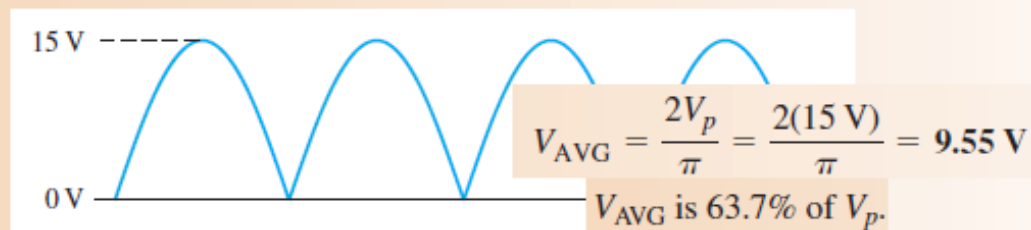
Find the average value of the full-wave rectified voltage in Figure 2-30.





## 2-5 Full-Wave Rectifiers

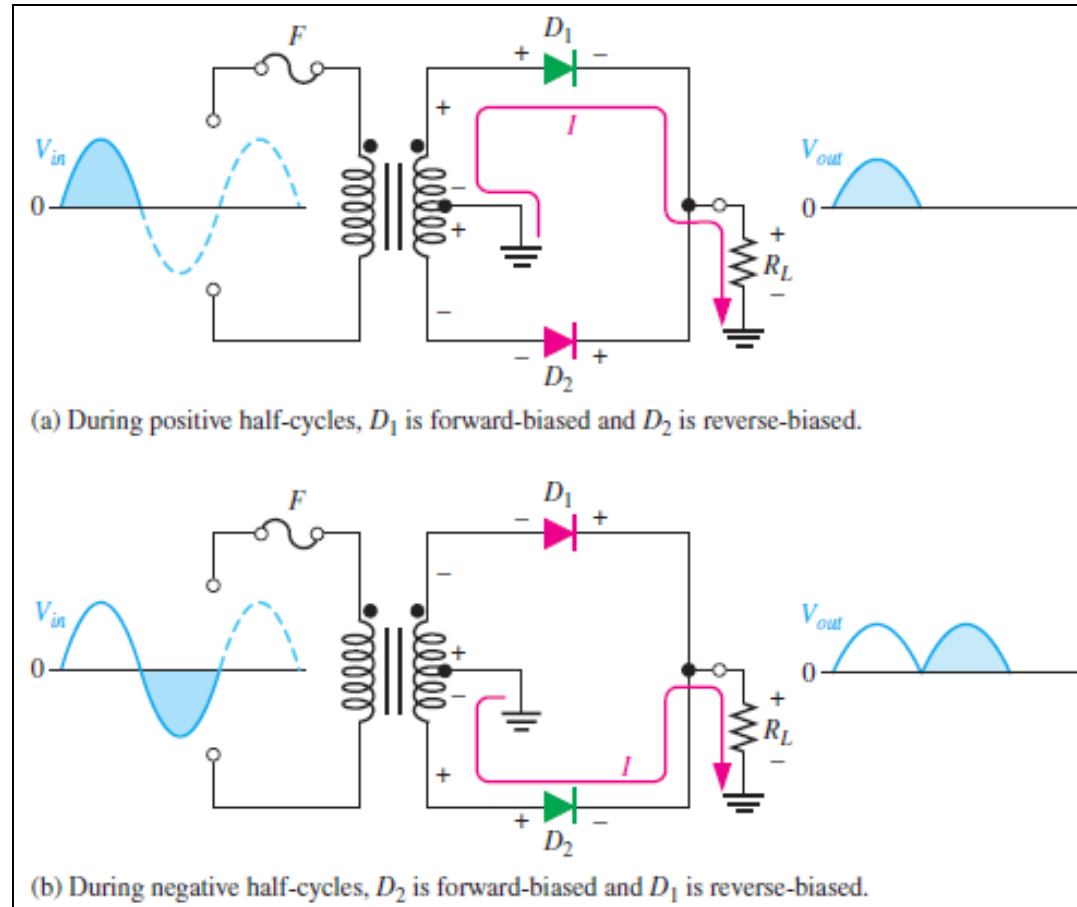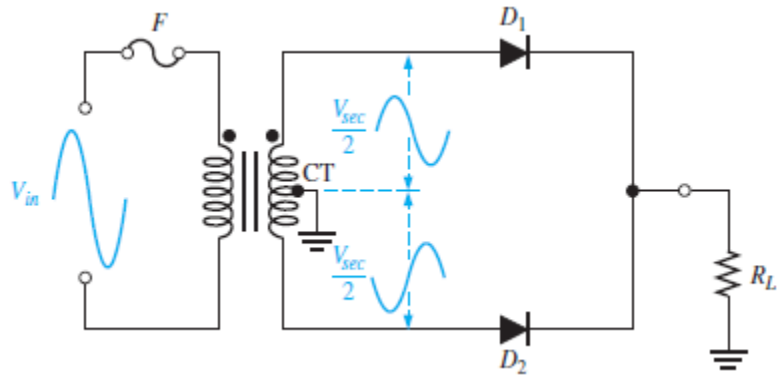
### a) Center-Tapped Full-Wave Rectifier Operation:



## 2-5 Full-Wave Rectifiers (Center-Tapped)
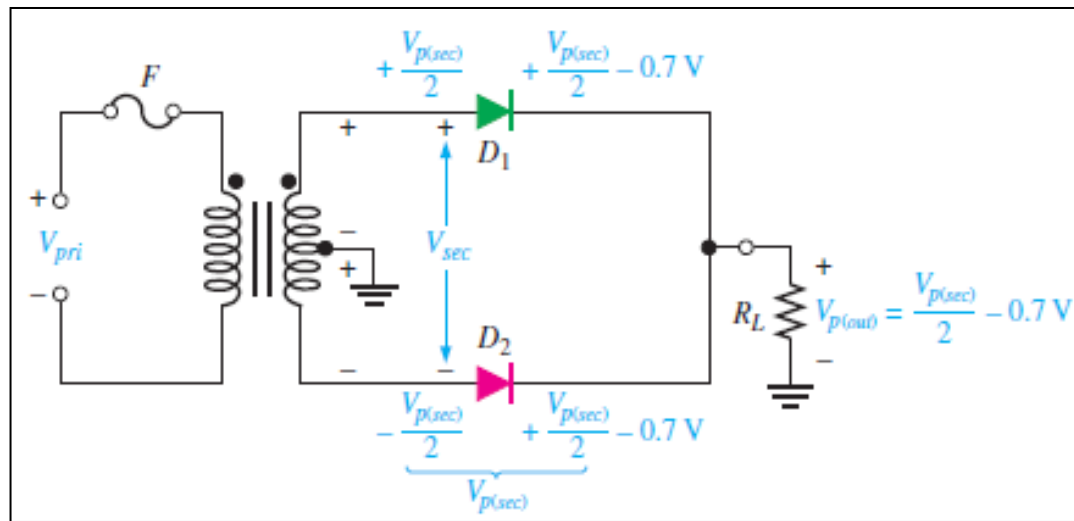
### Peak Inverse Voltage (PIV)

- ▶ if this voltage is exceeded the diode may be destroyed



The peak inverse voltage across  $D_2$  is

$$\begin{aligned} \text{PIV} &= \left( \frac{V_{p(sec)}}{2} - 0.7\text{ V} \right) - \left( -\frac{V_{p(sec)}}{2} \right) = \frac{V_{p(sec)}}{2} + \frac{V_{p(sec)}}{2} - 0.7\text{ V} \\ &= V_{p(sec)} - 0.7\text{ V} \end{aligned}$$

Since  $V_{p(out)} = V_{p(sec)}/2 - 0.7\text{ V}$ , then by multiplying each term by 2 and transposing,


$$V_{p(sec)} = 2V_{p(out)} + 1.4\text{ V}$$

Therefore, by substitution, the peak inverse voltage across either diode in a full-wave center-tapped rectifier is

$$\text{PIV} = 2V_{p(out)} + 0.7\text{ V}$$

**EXAMPLE 2–6**

- (a) Show the voltage waveforms across each half of the secondary winding and across  $R_L$  when a 100 V peak sine wave is applied to the primary winding in Figure 2–36.
- (b) What minimum PIV rating must the diodes have?

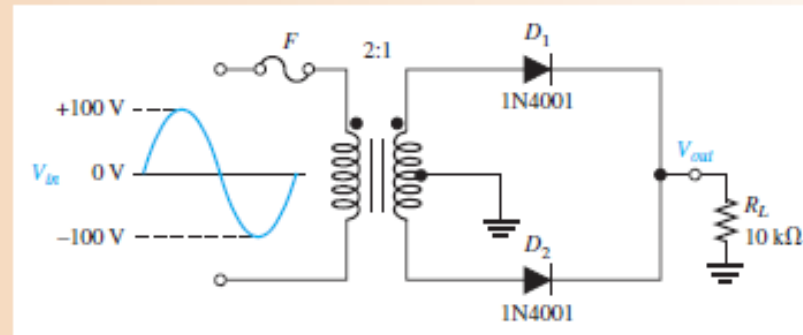▶ **FIGURE 2–36**

**Solution** (a) The transformer turns ratio  $n = 0.5$ . The total peak secondary voltage is

$$V_{p(sec)} = nV_{p(prim)} = 0.5(100 \text{ V}) = 50 \text{ V}$$

There is a 25 V peak across each half of the secondary with respect to ground. The output load voltage has a peak value of 25 V, less the 0.7 V drop across the diode. The waveforms are shown in Figure 2–37.

- (b) Each diode must have a minimum PIV rating of

$$\text{PIV} = 2V_{p(out)} + 0.7 \text{ V} = 2(24.3 \text{ V}) + 0.7 \text{ V} = 49.3 \text{ V}$$

▶ **FIGURE 2–37**