
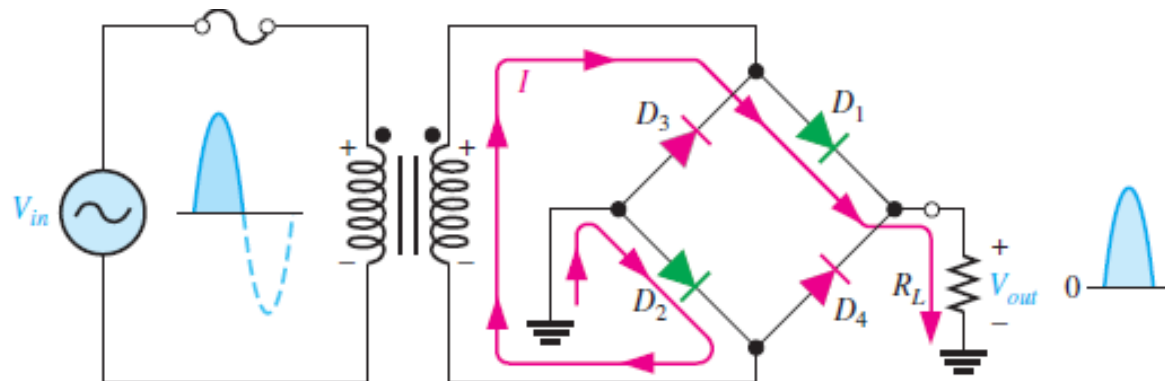


2-5 Full-Wave Rectifiers

b) Bridge Full-Wave Rectifier Operation

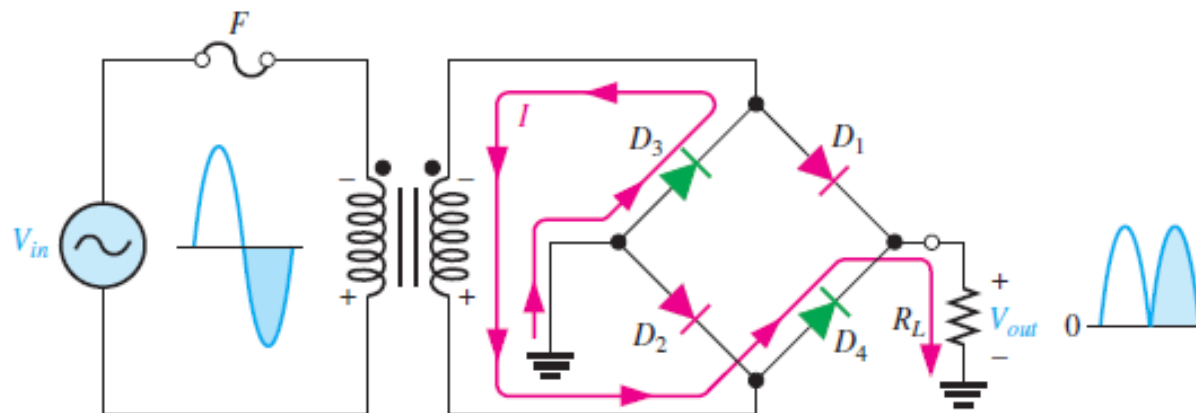

(a) During the positive half-cycle of the input, D_1 and D_2 are forward-biased and conduct current. D_3 and D_4 are reverse-biased.




(b) During the negative half-cycle of the input, D_3 and D_4 are forward-biased and conduct current. D_1 and D_2 are reverse-biased.

Ideally	$V_{p(out)} = V_{p(sec)}$
Practically	$V_{p(out)} = V_{p(sec)} - 1.4 \text{ V}$

2-5 Full-Wave Rectifiers (Bridge)


Peak Inverse Voltage (PIV)

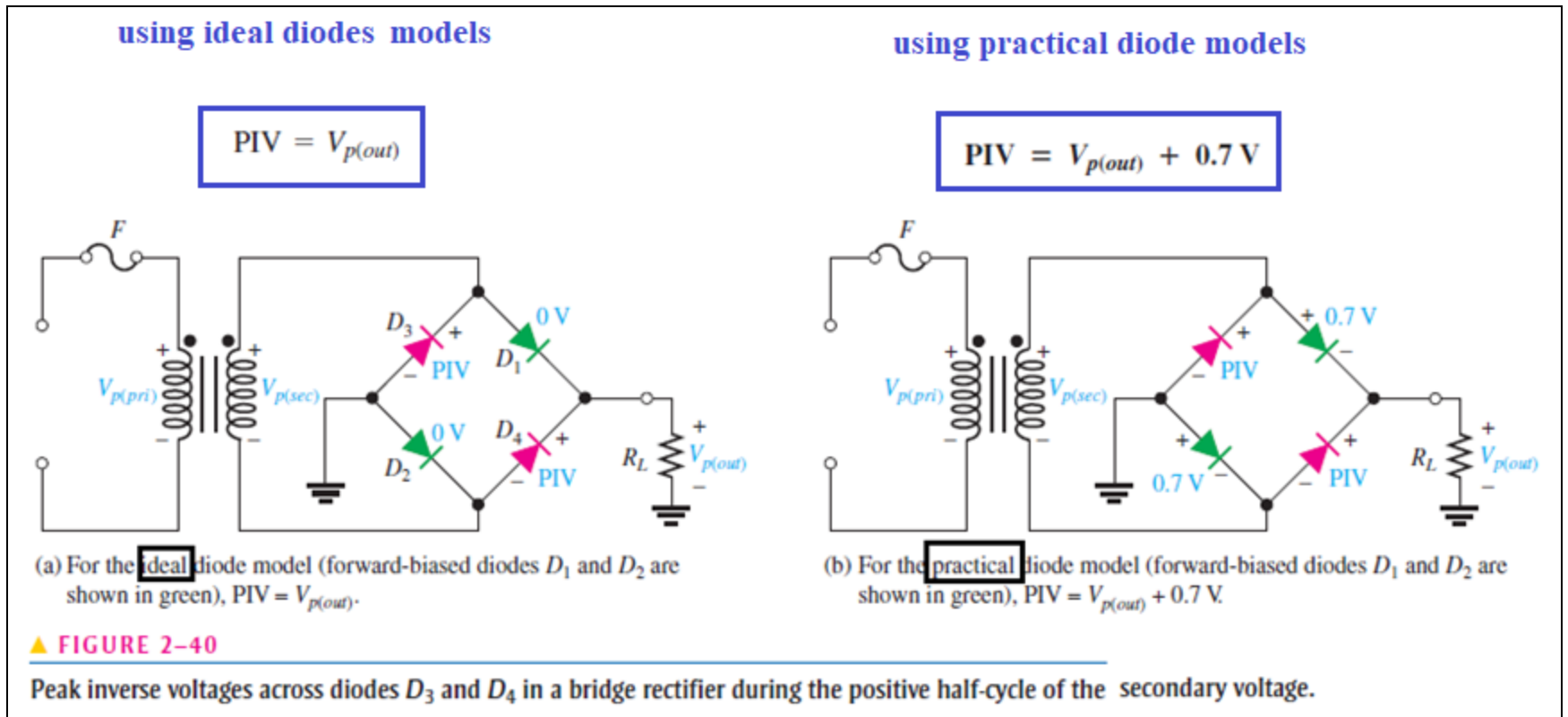

EXAMPLE 2-7

Determine the peak output voltage for the bridge rectifier in Figure 2-41. Assuming the practical model, what PIV rating is required for the diodes? The transformer is specified to have a 12 V rms secondary voltage for the standard 120 V across the primary.

► **FIGURE 2-41**

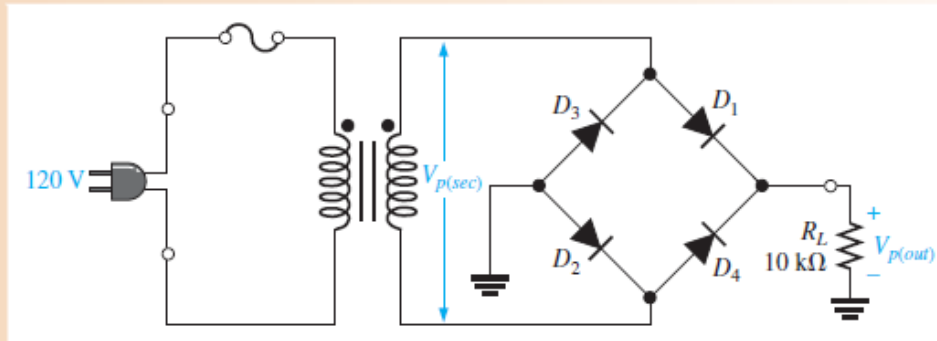

Solution The peak output voltage (taking into account the two diode drops) is

$$V_{p(sec)} = 1.414V_{rms} = 1.414(12\text{ V}) \cong 17\text{ V}$$

$$V_{p(out)} = V_{p(sec)} - 1.4\text{ V} = 17\text{ V} - 1.4\text{ V} = 15.6\text{ V}$$

The PIV rating for each diode is

$$\text{PIV} = V_{p(out)} + 0.7\text{ V} = 15.6\text{ V} + 0.7\text{ V} = 16.3\text{ V}$$

2-6 Power Supply Filters & Regulators


Filter: ideally eliminates the fluctuations in the output voltage of a half wave or full-wave rectifier and produces a constant-level dc voltage.




Power supply filtering. Rectifier with a filter

Capacitor-Input Filter

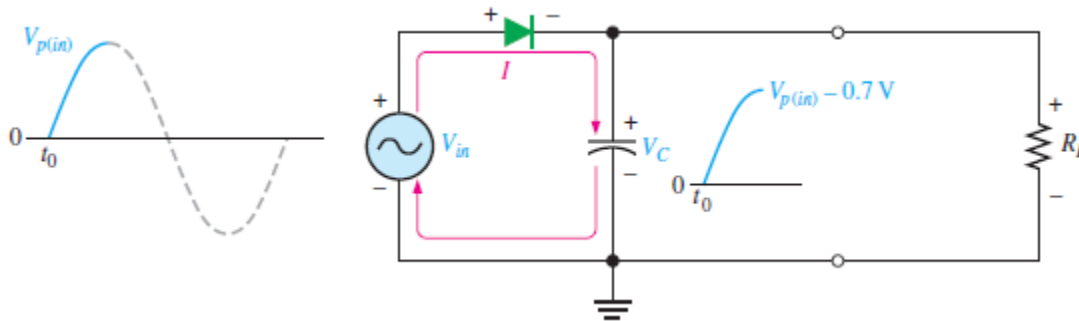
► Operation of a half-wave rectifier with a capacitor-input filter.



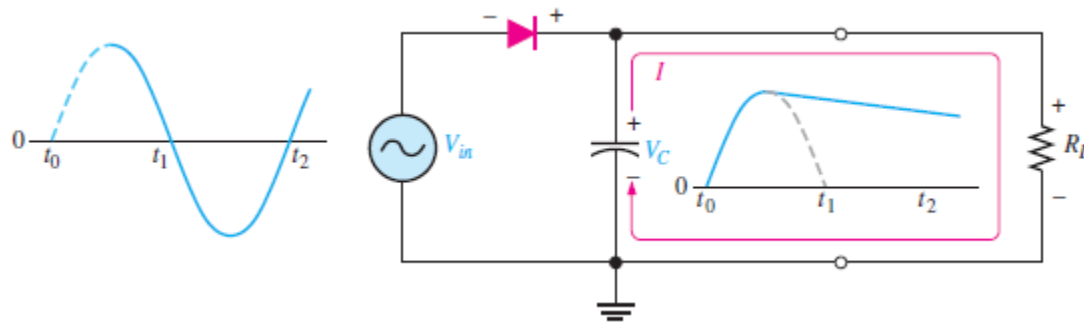Initial charging of the capacitor (diode is forward-biased) happens only once when power is turned on.





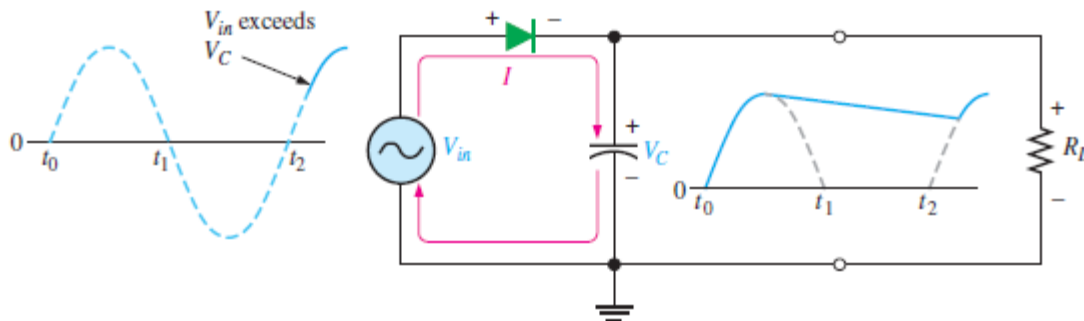
The capacitor discharges through R_L after peak of positive half-cycle when the diode is reverse-biased. This discharging occurs during the portion of the input voltage indicated by the solid dark blue curve.



The capacitor charges back to peak of input when the diode becomes forward-biased. This charging occurs during the portion of the input voltage indicated by the solid dark blue curve.

Capacitor-Input Filter

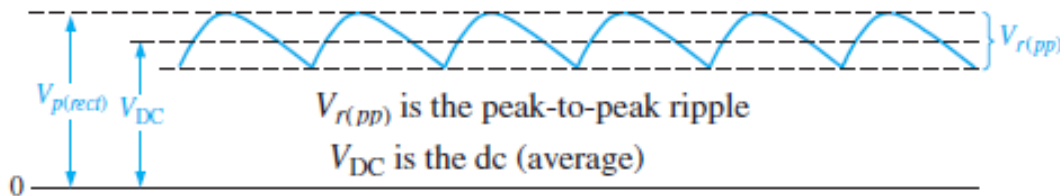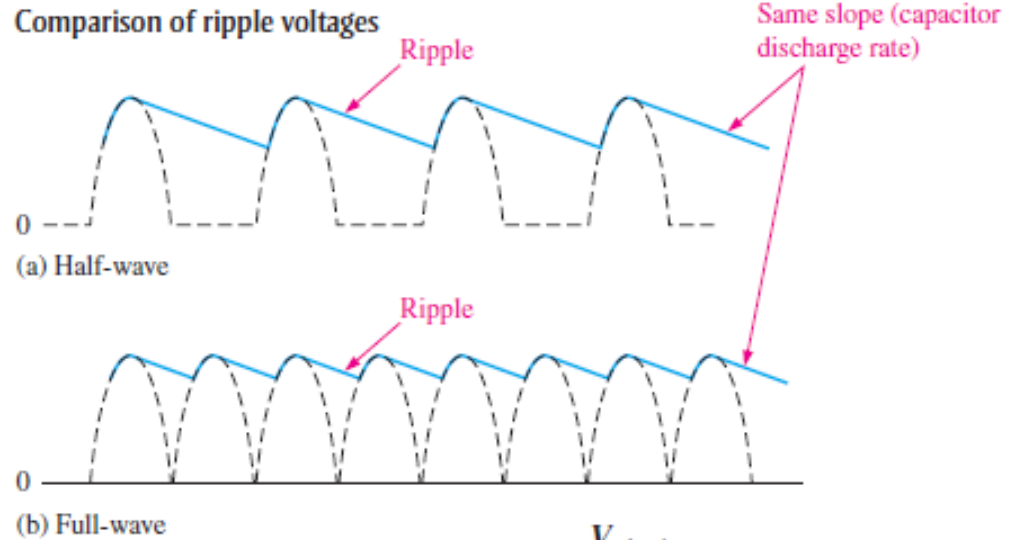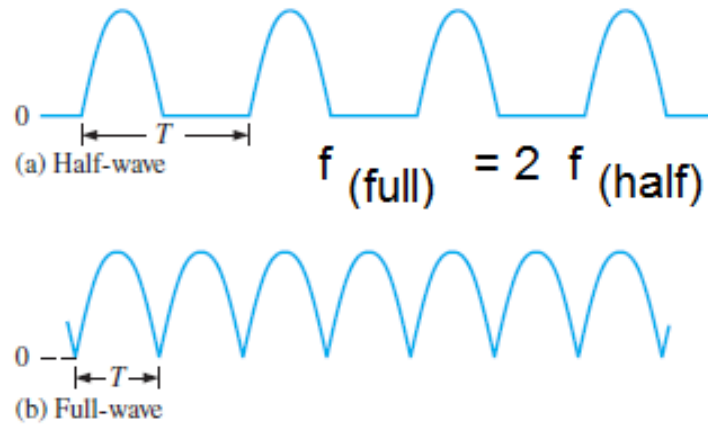► **Ripple Factor (r)** is an indication of the effectiveness of the filter



$$\text{ripple factor } r = \frac{V_{r(pp)}}{V_{DC}}$$

$$V_{r(pp)} \cong \left(\frac{1}{fR_L C} \right) V_{p(rect)}$$


$$V_{DC} \cong \left(1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

Note: the above equations are derived for **full-wave rectifier**

EXAMPLE 2-8

Determine the ripple factor for the filtered bridge rectifier with a load as indicated in Figure 2-48.

▶ **FIGURE 2-48**

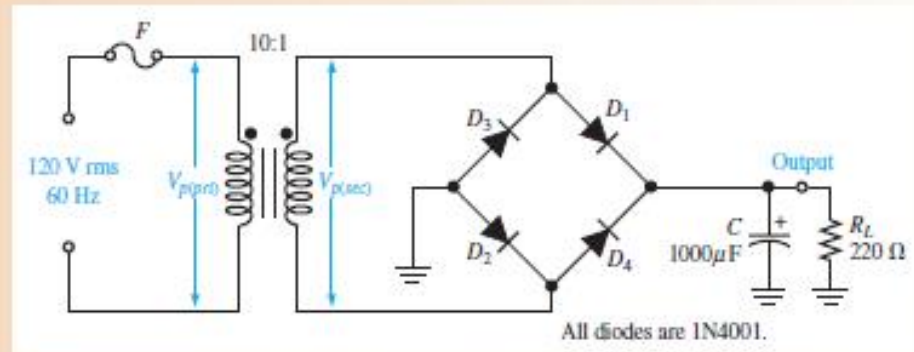

Solution The transformer turns ratio is $n = 0.1$. The peak primary voltage is

$$V_{p(prim)} = 1.414V_{rms} = 1.414(120 \text{ V}) = 170 \text{ V}$$

The peak secondary voltage is

$$V_{p(sec)} = nV_{p(prim)} = 0.1(170 \text{ V}) = 17.0 \text{ V}$$

The unfiltered peak full-wave rectified voltage is

$$V_{p(rect)} = V_{p(sec)} - 1.4 \text{ V} = 17.0 \text{ V} - 1.4 \text{ V} = 15.6 \text{ V}$$

The frequency of a full-wave rectified voltage is 120 Hz. The approximate peak-to-peak ripple voltage at the output is

$$V_{r(pp)} \cong \left(\frac{1}{fR_L C} \right) V_{p(rect)} = \left(\frac{1}{(120 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 0.591 \text{ V}$$

The approximate dc value of the output voltage is determined as follows:

$$V_{DC} = \left(1 - \frac{1}{2fR_L C} \right) V_{p(rect)} = \left(1 - \frac{1}{(240 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 15.3 \text{ V}$$


The resulting ripple factor is

$$r = \frac{V_{r(pp)}}{V_{DC}} = \frac{0.591 \text{ V}}{15.3 \text{ V}} = \mathbf{0.039}$$

The percent ripple is 3.9%.

Power Supply Regulators

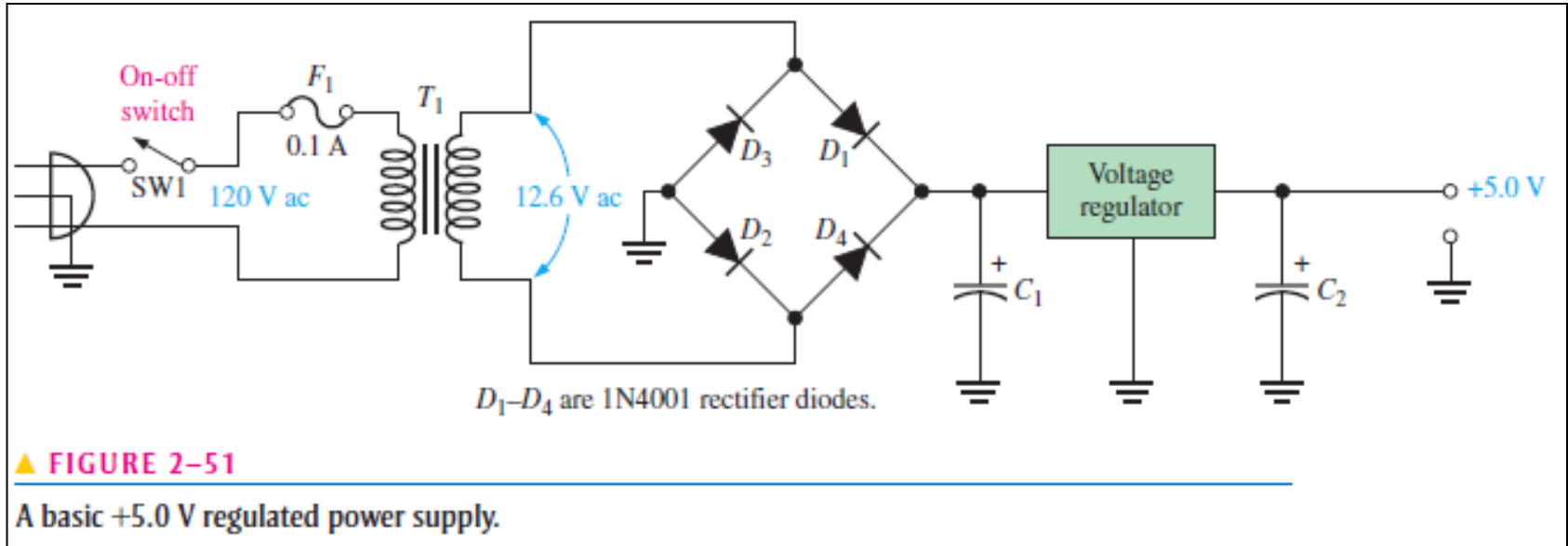- **Voltage regulation:** prevents changes in the filtered dc voltage due to variations in **input voltage** or **load**.
- Connected to the output of a filtered rectifier and maintains a constant output voltage (or current) despite changes in the input, the load current, or the temperature.



Example: Three-terminal regulators IC: designed for fixed output voltages require only external capacitors to complete the regulation portion of the power supply. Filtering is accomplished by a large-value capacitor between the input voltage and ground. An output capacitor is connected from the output to ground to improve the transient response.

Power Supply Regulators

Percent Regulation:

- Specify the performance of a voltage regulator.
- It can be in terms of input (line) regulation or load regulation.

a) Line Regulation: specifies how much change occurs in the **output voltage** for a given change in the **input voltage**.

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\%$$

b) Load Regulation: specifies how much change occurs in the **output voltage** over a certain range of **load current** values, usually from minimum current (no load, NL) to maximum current (full load, FL).

$$\text{Load regulation} = \left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) 100\%$$

EXAMPLE 2-9

A certain 7805 regulator has a measured no-load output voltage of 5.18 V and a full-load output of 5.15 V. What is the load regulation expressed as a percentage?

Solution Load regulation = $\left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) 100\% = \left(\frac{5.18 \text{ V} - 5.15 \text{ V}}{5.15 \text{ V}} \right) 100\% = 0.58\%$