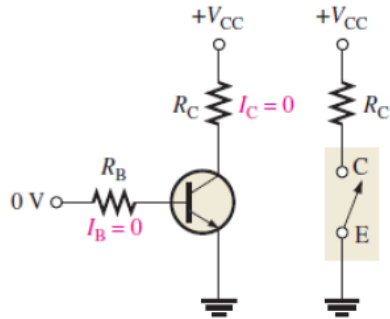


Chapter.5


Transistor Bias Circuits

BJT as a Switch


(a) Cutoff - open switch



(b) Saturation - closed switch

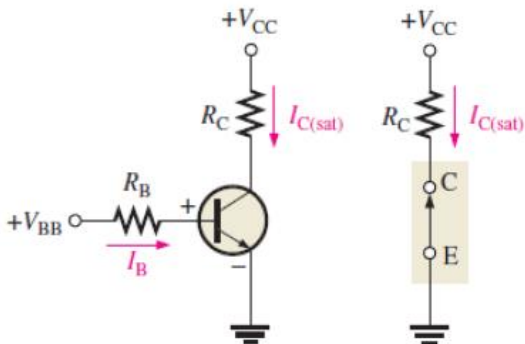


BJT as an Amplifier

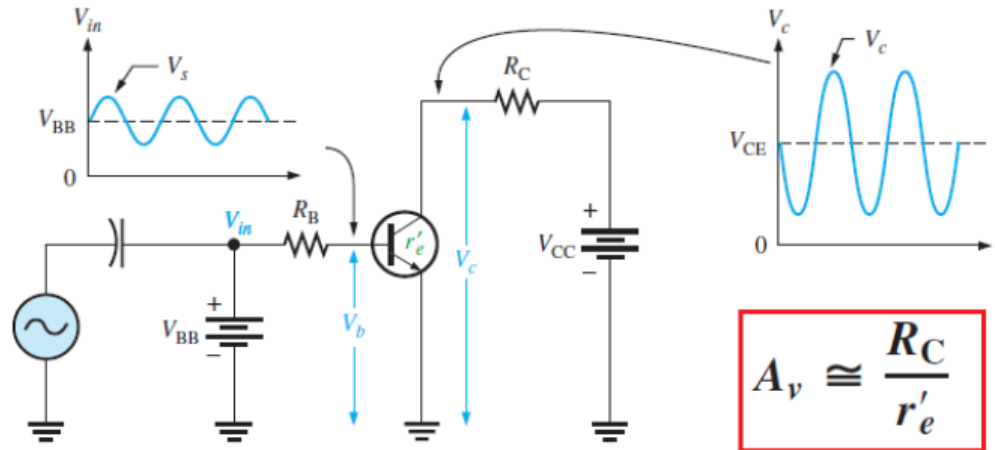

DC Bias


- ❑ A transistor must be properly biased with a dc voltage in order to operate as a linear amplifier.
- ❑ The purpose of biasing a circuit is to establish a proper stable dc operating point **Q-point** (V_{CE} , I_C).
- ❑ A dc operating point must be set so that signal variations at the input terminal are amplified and accurately reproduced at the output terminal.

DC biased circuit

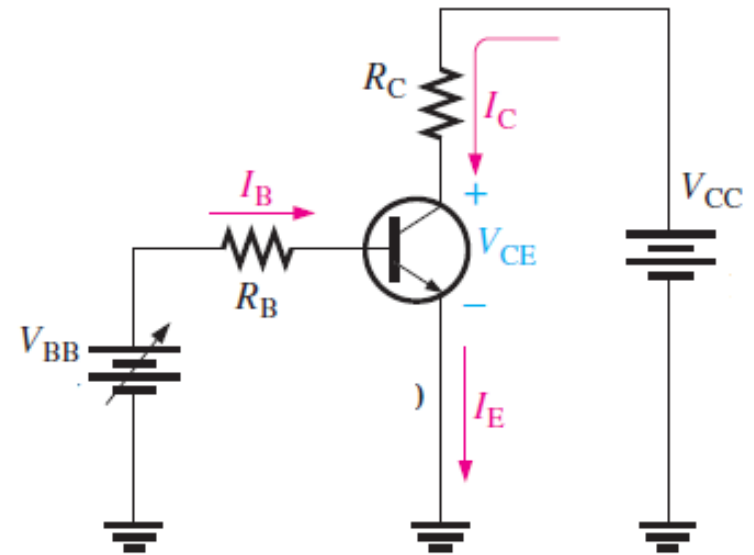

Graphical Analysis of DC Biasing

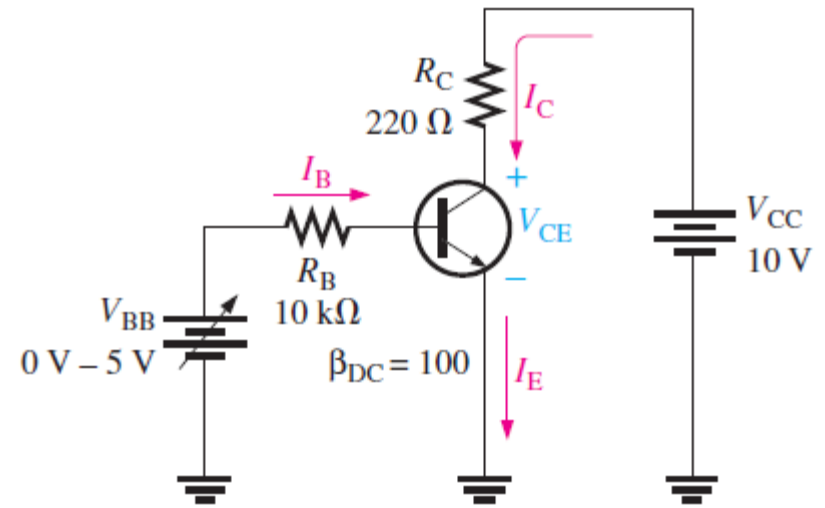- ❑ The transistor is biased with V_{CC} and V_{BB} to obtain certain values of I_B , I_C , I_E , and V_{CE} .
- ❑ The **collector characteristic curves** are shown to illustrate the effects of dc bias.
- ❑ By varying I_B , we can obtain several Q-points.




(a) DC biased circuit

- ❑ **DC load line** passes through the Q-point on a transistor's collector curves intersecting the vertical axis at approximately $I_{C(sat)}$ and the horizontal axis at $V_{CE(off)}$.

$$I_{C(sat)} = (V_{CC} - V_{CE(sat)}) / R_C = 45.5 \text{ mA}$$


	$I_B (\mu A)$	$I_C (mA)$	$V_{CE} (V)$
Q_1	200	20	5.6
Q_2	300	30	3.4
Q_3	400	40	1.2

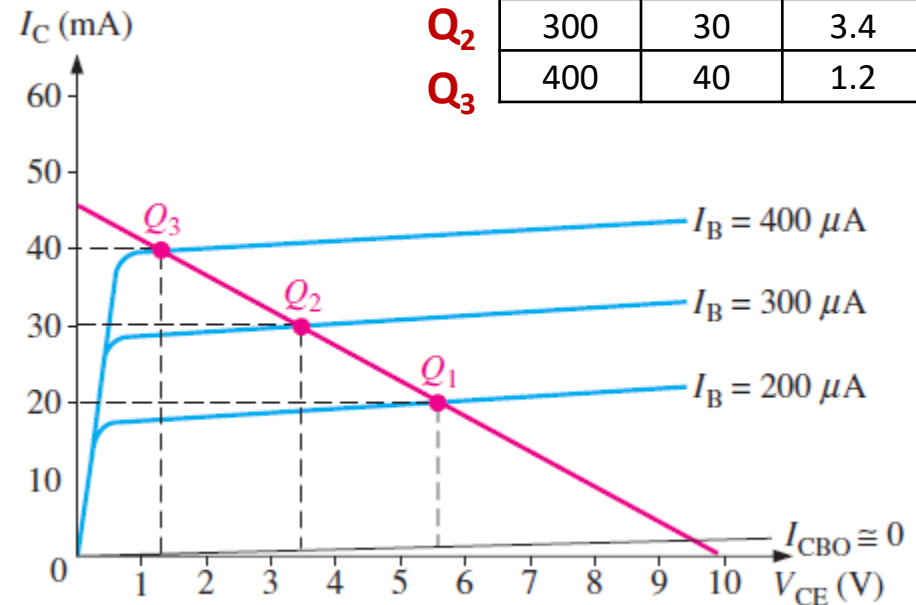

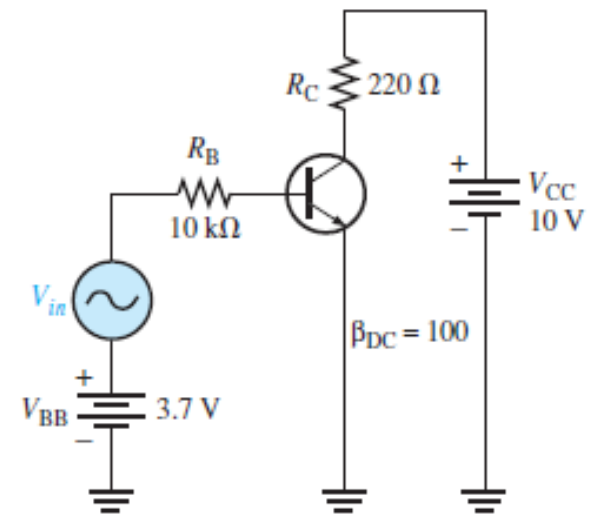(b) The dc load line.

Linear Operation

- ❑ The region along the load line including all points between saturation and cutoff is generally known as the **linear region** of the transistor's operation.
- ❑ The output voltage is ideally a linear reproduction of the input.
- ❑ **Q-Point:** ($V_{CEQ} = 3.4 \text{ V}$, $I_{CQ} = 30 \text{ mA}$)
- ❑ Assume sinusoidal voltage, V_{IN} , is superimposed on V_{BB} , causing the base current to vary sinusoidally **100 μA** above and below its Q-point value of **300 μA** .
- ❑ This causes the collector current to vary **10 mA** above and below its Q-point value of **30 mA**.
- ❑ The collector to-emitter voltage varies **2.2 V** above and below its Q-point value of **3.4 V**.



$$I_{BQ} = \frac{V_{BB} - 0.7 \text{ V}}{R_B} = \frac{3.7 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 300 \mu\text{A}$$

$$I_{CQ} = \beta_{DC} I_{BQ} = (100)(300 \mu\text{A}) = 30 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10 \text{ V} - (30 \text{ mA})(220 \Omega) = 3.4 \text{ V}$$

