
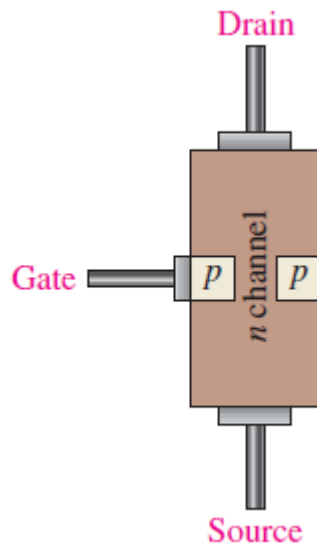


Chapter 8

Field-Effect Transistors (FETs)

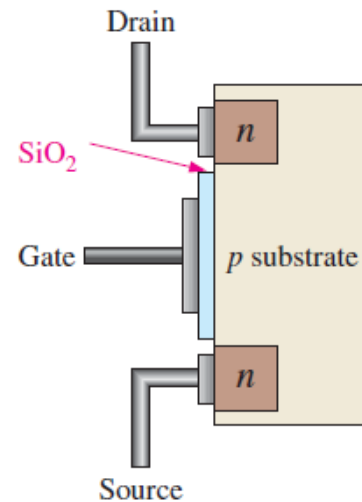

n-channel JFET



n-channel E-MOSFET

Comparison between BJT and FET

Bipolar Junction Transistor (BJT)	Field Effect Transistor (FET)
Bipolar: use both electron and hole current	Unipolar: operated with one type of carrier
Current-controlled device: base current controls the amount of collector current	Voltage-controlled device: voltage between two of the terminals (gate and source) controls the current through the device
	Advantage: very high input resistance Applications: low-voltage switching(faster) <u>Two main types of FETs:</u> <ul style="list-style-type: none">• Junction field-effect transistor (JFET)• Metal oxide semiconductor field-effect transistor (MOSFET).





Junction Field Effect Transistor (JFET)

Basic Structure

Symbols

(a) *n* channel

(b) *p* channel

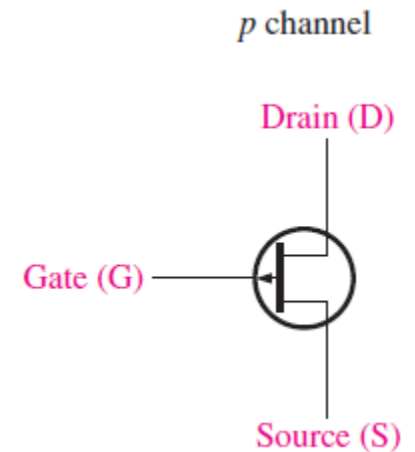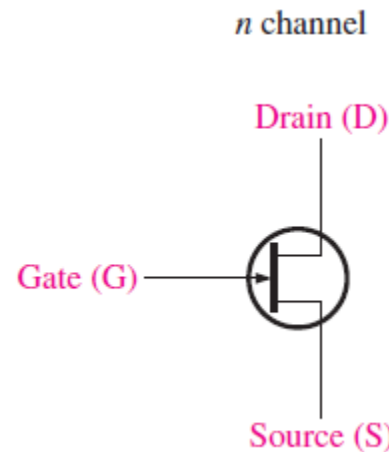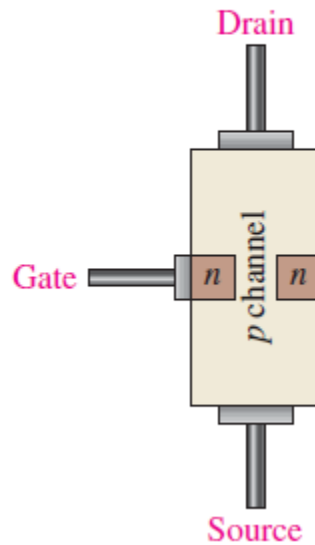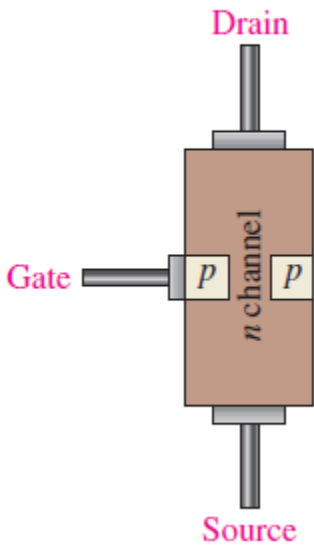


- The JFET is a type of FET that operates with a reverse-biased pn junction to control current in a channel.
- Depending on their structure, JFETs fall into either of two categories, n channel or p channel.


Basic Operation of JFET

- V_{DD} provides a drain-to-source voltage and supplies current from drain to source.
- V_{GG} sets the reverse-bias voltage between the gate and the source, as shown.
- Reverse biasing of the gate-source junction produces a depletion region which increases channel resistance by restricting the channel width \rightarrow **Controlling I_D** .

n-channel JFET Operation

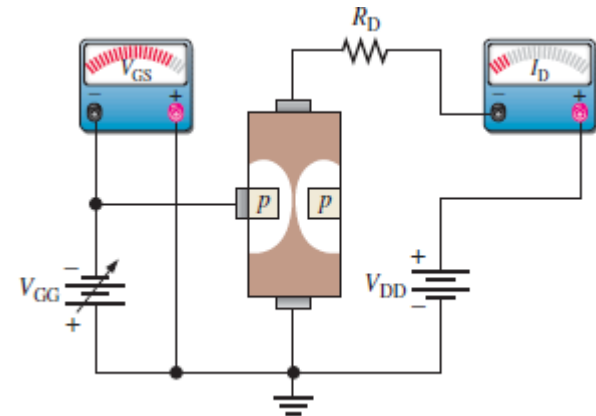

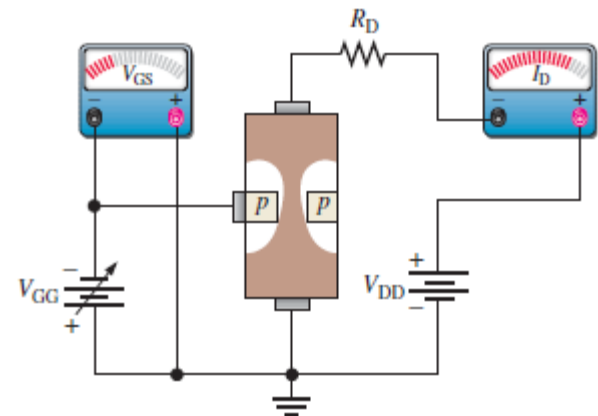Greater V_{GG} narrows the channel (between the white areas) which increases the resistance of the channel and decreases I_D .




Less V_{GG} widens the channel (between the white areas) which decreases the resistance of the channel and increases I_D .

JFET Characteristics and Parameters

When $V_{GS} = 0$

- The JFET operates as a voltage-controlled, **constant-current** device.
- The JFET must be operated between $V_{GS} = 0$ V and $V_{GS(off)}$. For this range of gate-to-source voltages, I_D will vary from a maximum of I_{DSS} to a minimum of almost zero.
- **Pinch-Off Voltage, V_p :** For $V_{GS} = 0$ V, the value of V_{DS} at which I_D becomes essentially constant (point B)
- As V_{DS} increase above the V_p , I_D becomes constant.
- I_{DSS} (Drain to Source current with gate Shorted): is the maximum drain current and it is always specified for the condition, $V_{GS} = 0$ V.


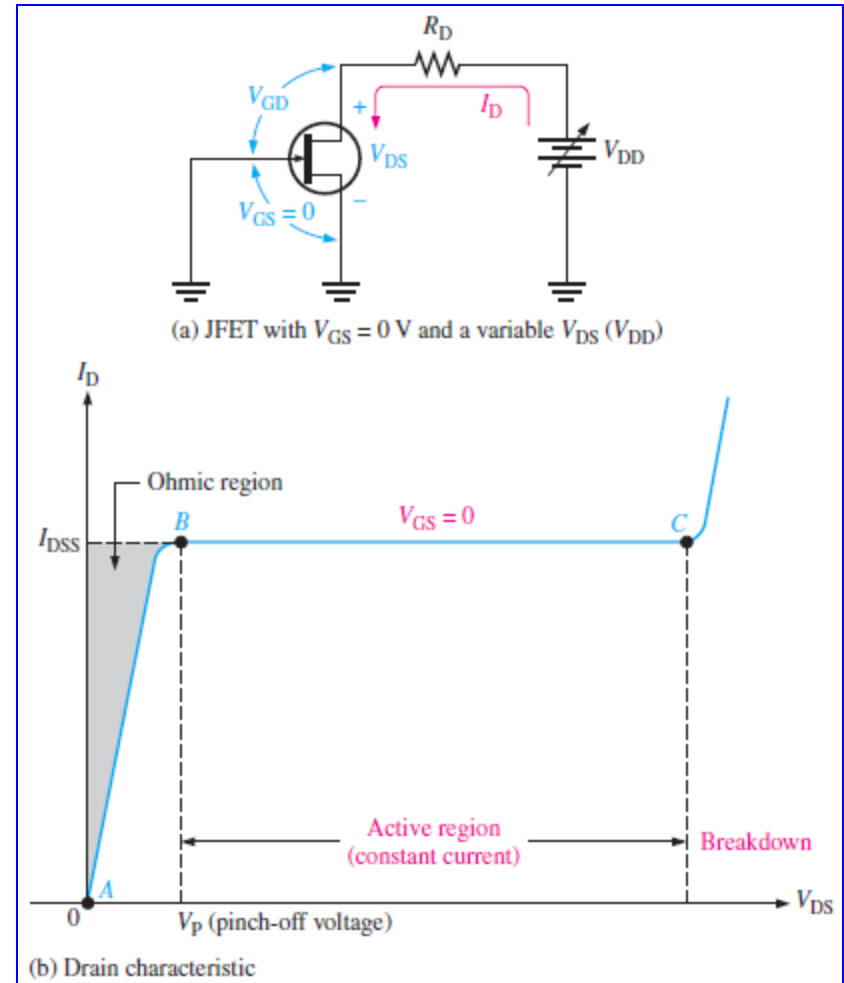
Drain Characteristic Curve for $V_{GS} = 0$



JFET Characteristics and Parameters


When V_{GS} Controls I_D

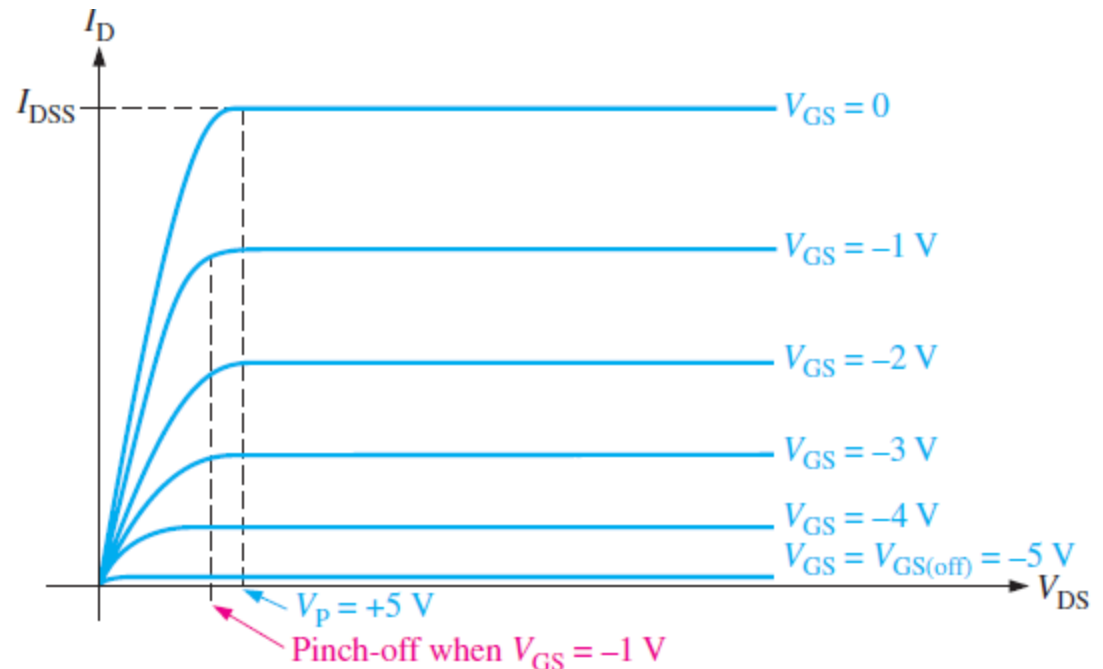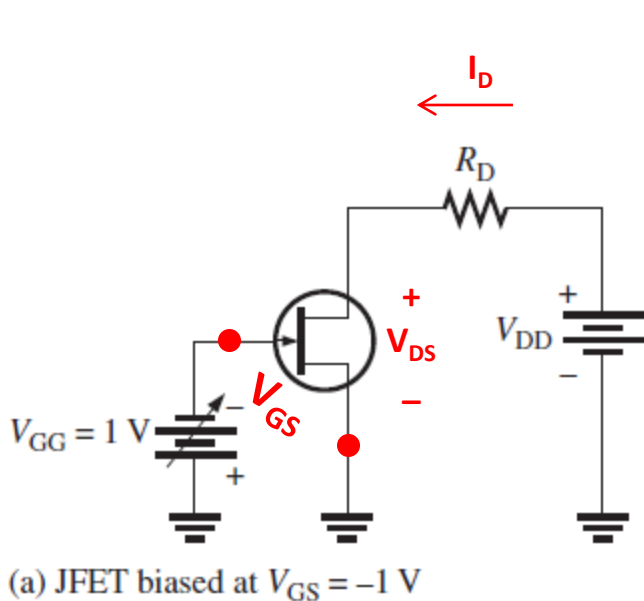- As V_{GS} is set to increasingly more negative values by adjusting V_{GG} , a family of drain characteristic curves is produced.
- Notice that I_D decreases as the magnitude of V_{GS} is increased to larger negative values because of the narrowing of the channel.
- **Cutoff Voltage, $V_{GS(off)}$:** The value of V_{GS} that makes $I_D = \text{zero}$.



P-channel JFET Operation

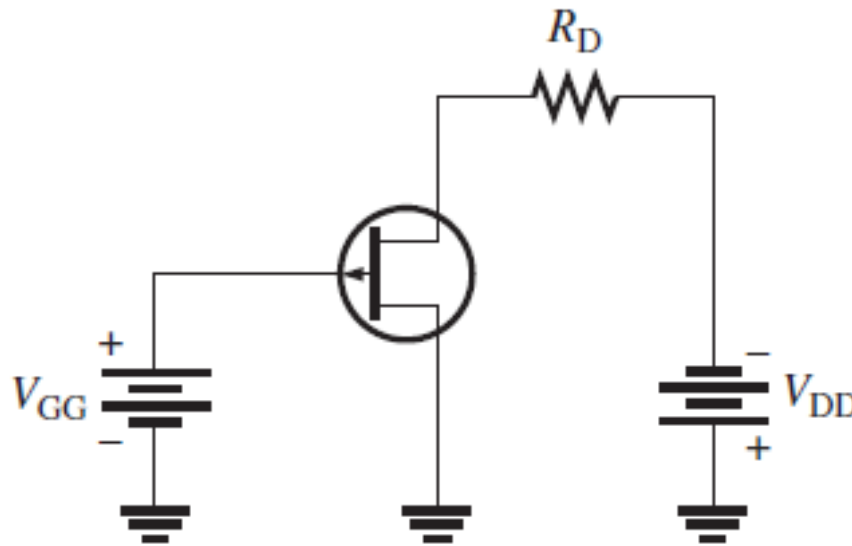The basic operation of a p -channel JFET is the same as for an n -channel device except that a p -channel JFET requires a **negative** V_{DD} and a **positive** V_{GS} , as illustrated below.




A biased p -channel JFET.

EXAMPLE 8-1

For the JFET in Figure 8-11, $V_{GS(off)} = -4\text{ V}$ and $I_{DSS} = 12\text{ mA}$. Determine the *minimum* value of V_{DD} required to put the device in the constant-current region of operation when $V_{GS} = 0\text{ V}$.

► FIGURE 8-11

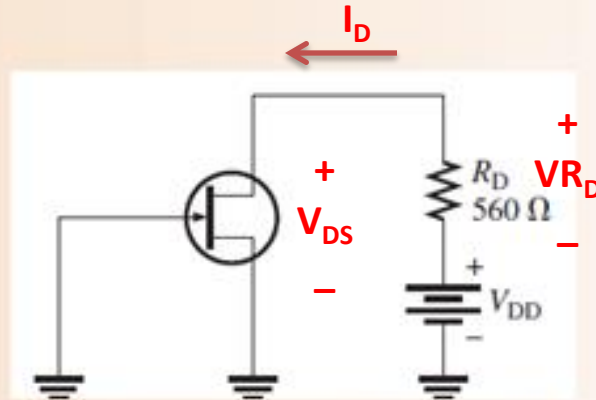

Since $V_{GS(off)} = -4\text{ V}$, $V_P = 4\text{ V}$. The minimum value of V_{DS} for the JFET to be in its constant-current region is

$$V_{DS} = V_P = 4\text{ V}$$

In the constant-current region with $V_{GS} = 0\text{ V}$,

$$I_D = I_{DSS} = 12\text{ mA}$$


The drop across the drain resistor is

$$V_{R_D} = I_D R_D = (12\text{ mA})(560\ \Omega) = 6.72\text{ V}$$

Apply Kirchhoff's law around the drain circuit.


$$V_{DD} = V_{DS} + V_{R_D} = 4\text{ V} + 6.72\text{ V} = 10.7\text{ V}$$

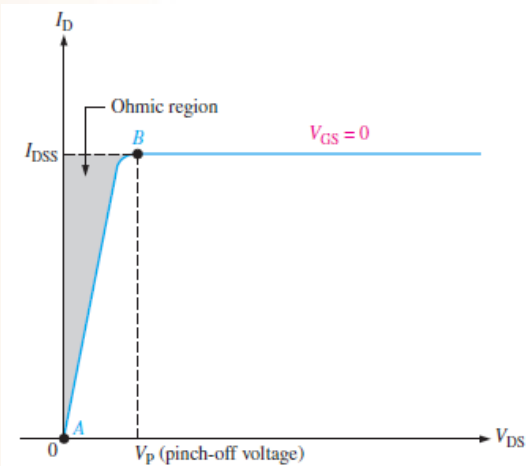This is the value of V_{DD} to make $V_{DS} = V_P$ and put the device in the constant-current region.



JFET Universal Transfer Characteristic

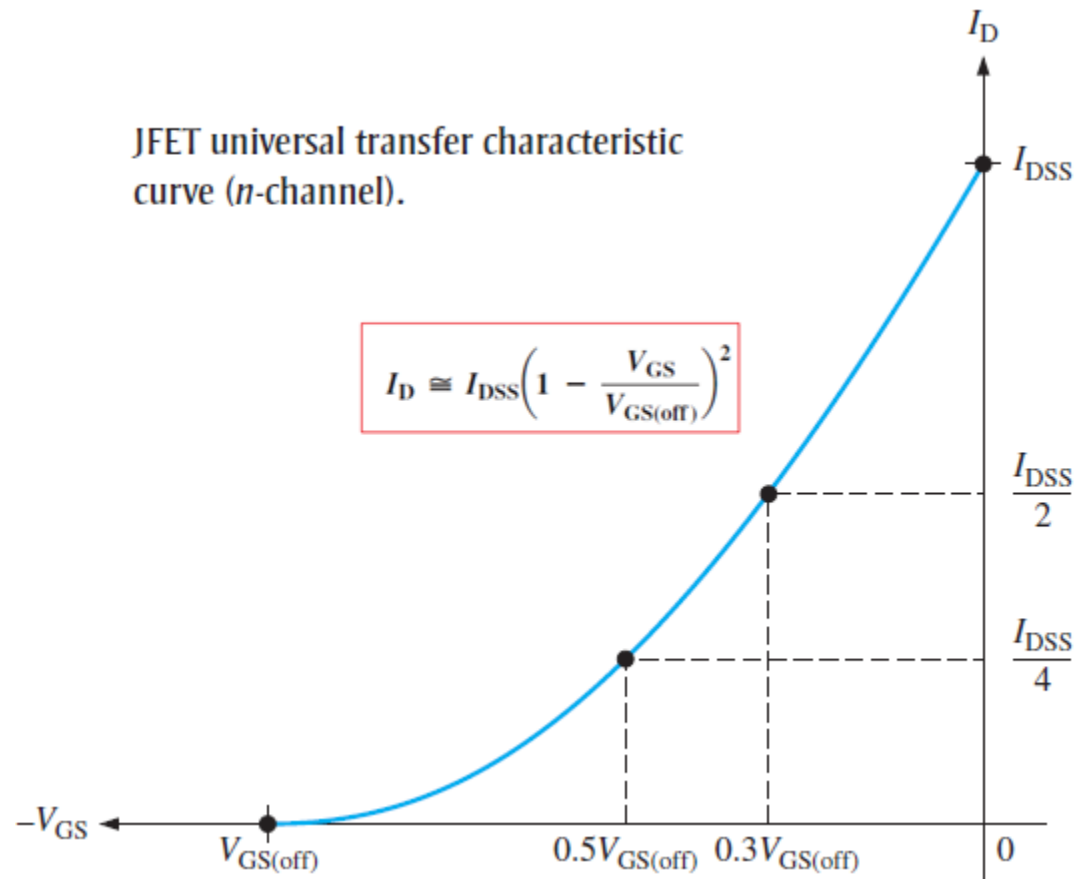- Figure shows a general transfer characteristic curve that illustrates graphically the relationship between V_{GS} and I_D .
- For an n -channel JFET, $V_{GS(off)}$ is negative, and for a p -channel JFET, $V_{GS(off)}$ is positive.



JFET Universal Transfer Characteristic

- The transfer characteristic curve can also be developed from the drain characteristic curves by plotting values of I_D for the values of V_{GS} taken from the family of drain curves at pinch-off. Each point on the transfer characteristic curve corresponds to specific values of V_{GS} and I_D on the drain curves.

The transfer characteristic curve

$$I_D \cong I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

The drain characteristic curves

