

Example of Real DC machines

A dc machine has 12 poles, 28 loops, 12 parallel current path, $R=0.8 \Omega$, $\phi=0.13 \text{ wb}$, $V_B=250 \text{ V}$, $\omega=150 \text{ rad/s}$ and $r=12.5 \text{ cm}$, $l=50\text{cm}$.

- Is this machine motor or generator? Explain.
- Find i and τ_{ind} .
- calculate η .
- if ϕ increased to 0.5 wb, calculate ω_{ss} .

② $K = \frac{ZP}{2\pi a} = \frac{2*28*12}{2\pi*12} = \frac{28}{\pi} = 8.91$

$$E_A = k\phi\omega = 8.91 * 0.13 * 150 = 173.8 \text{ V} < V_B$$
$$\omega_{ss} = \omega_n L = \frac{V_B}{k\phi} = \frac{250}{8.91 * 0.13} = 215.8 > \omega$$

∴ motor

Example of Real DC machines

$$\textcircled{b} \quad i = \frac{\bar{V}_B - E_A}{R} = \frac{250 - 173.8}{0.8} = 95.25 \text{ A}$$
$$T_{in} = k\phi i = 8.91 * 0.13 * 95.25 = 110.36 \text{ N.m}$$

$$\textcircled{c} \quad P_e = V_B \cdot i = 250 * 95.25 = 23.8 \text{ kW}$$

$$P_m = T \cdot \omega = 110.36 * 150 = 16.55 \text{ kW}$$

$$\eta_m = \frac{P_m}{P_e} = \frac{16.55}{23.8} * 100\% = 69.5\%$$

$$\textcircled{d} \quad \omega_{ss} = \frac{\bar{V}_B}{k\phi} = \frac{250}{8.91 * 0.5} = 56.1 \text{ rad/s.}$$