



جامعة فلسطين التقنية - خضوري  
Palestine Technical University - Kadoorie

# Digital Electronics and Logic Design





## Boolean Algebra and Logic Simplification

*Dr. Jafar Saifeddin Jallad*

**Dept. of Electrical Engineering**

**Palestine Technical University**

Tulkaram, Palestine

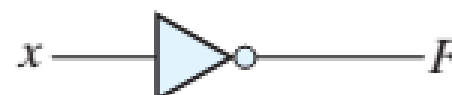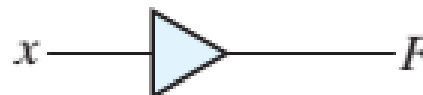Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table border="1"> <thead> <tr> <th><math>x</math></th> <th><math>y</math></th> <th><math>F</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	$x$	$y$	$F$	0	0	0	0	1	0	1	0	0	1	1	1
$x$	$y$	$F$																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table border="1"> <thead> <tr> <th><math>x</math></th> <th><math>y</math></th> <th><math>F</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	$x$	$y$	$F$	0	0	0	0	1	1	1	0	1	1	1	1
$x$	$y$	$F$																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table border="1"> <thead> <tr> <th><math>x</math></th> <th><math>F</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	$x$	$F$	0	1	1	0									
$x$	$F$																	
0	1																	
1	0																	
Buffer		$F = x$	<table border="1"> <thead> <tr> <th><math>x</math></th> <th><math>F</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </tbody> </table>	$x$	$F$	0	0	1	1									
$x$	$F$																	
0	0																	
1	1																	


NAND



$$F = (xy)'$$

$x$	$y$	$F$
0	0	1
0	1	1
1	0	1
1	1	0

NOR

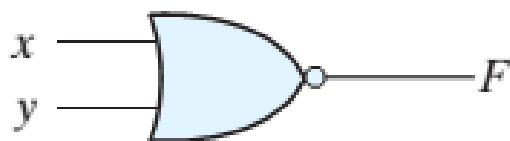

$$F = (x + y)'$$

$x$	$y$	$F$
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR  
(XOR)



$$F = xy' + x'y$$
$$= x \oplus y$$

$x$	$y$	$F$
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive-NOR  
or  
equivalence



$$F = xy + x'y'$$
$$= (x \oplus y)'$$

$x$	$y$	$F$
0	0	1
0	1	0
1	0	0
1	1	1

## Boolean Expressions for the 16 Functions of Two Variables

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	$x$ and $y$
$F_2 = xy'$	$x/y$	Inhibition	$x$ , but not $y$
$F_3 = x$		Transfer	$x$
$F_4 = x'y$	$y/x$	Inhibition	$y$ , but not $x$
$F_5 = y$		Transfer	$y$
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	$x$ or $y$ , but not both
$F_7 = x + y$	$x + y$	OR	$x$ or $y$
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	$x$ equals $y$
$F_{10} = y'$	$y'$	Complement	Not $y$
$F_{11} = x + y'$	$x \subset y$	Implication	If $y$ , then $x$
$F_{12} = x'$	$x'$	Complement	Not $x$
$F_{13} = x' + y$	$x \supset y$	Implication	If $x$ , then $y$
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

## Basic rules of Boolean algebra.

---

**1.**  $A + 0 = A$

**2.**  $A + 1 = 1$

**3.**  $A \cdot 0 = 0$

**4.**  $A \cdot 1 = A$

**5.**  $A + A = A$

**6.**  $A + \bar{A} = 1$

**7.**  $A \cdot A = A$

**8.**  $A \cdot \bar{A} = 0$

**9.**  $\bar{\bar{A}} = A$

**10.**  $A + AB = A$


**11.**  $A + \bar{A}B = A + B$

**12.**  $(A + B)(A + C) = A + BC$


---

$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.

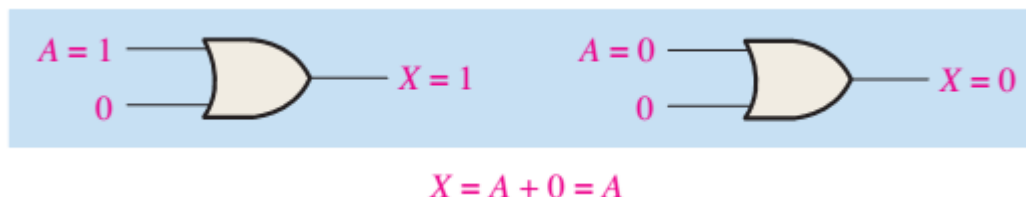
**Rule 1:  $A + 0 = A$**  A variable ORed with 0 is always equal to the variable. If the input variable  $A$  is 1, the output variable  $X$  is 1, which is equal to  $A$ . If  $A$  is 0, the output is 0, which is also equal to  $A$ . This rule is illustrated in Figure 4–8, where the lower input is fixed at 0.



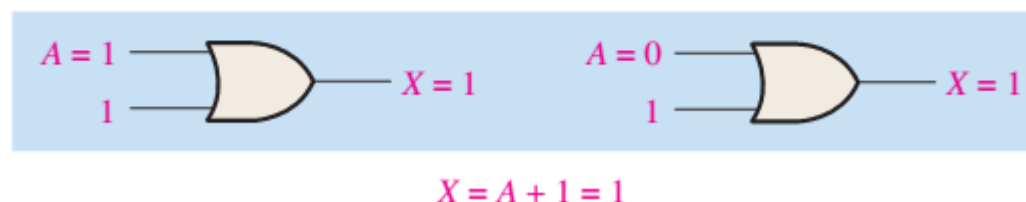
**Rule 2:  $A + 1 = 1$**  A variable ORed with 1 is always equal to 1. A 1 on an input to an OR gate produces a 1 on the output, regardless of the value of the variable on the other input. This rule is illustrated in Figure 4–9, where the lower input is fixed at 1.



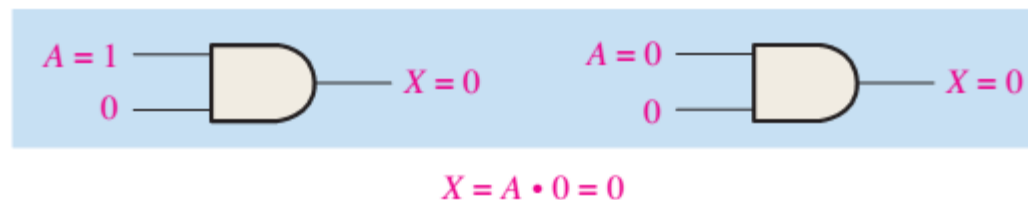
**Rule 3:  $A \cdot 0 = 0$**  A variable ANDed with 0 is always equal to 0. Any time one input to an AND gate is 0, the output is 0, regardless of the value of the variable on the other input. This rule is illustrated in Figure 4–10, where the lower input is fixed at 0.



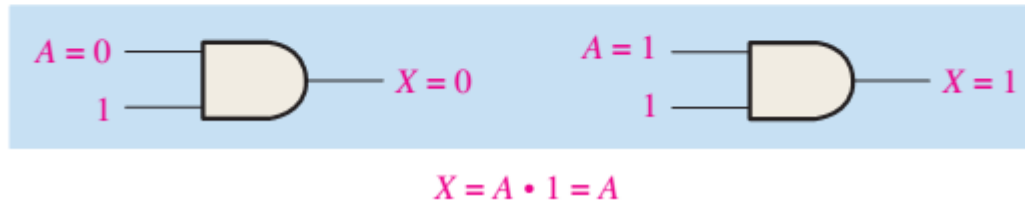
**Rule 4:  $A \cdot 1 = A$**  A variable ANDed with 1 is always equal to the variable. If  $A$  is 0, the output of the AND gate is 0. If  $A$  is 1, the output of the AND gate is 1 because both inputs are now 1s. This rule is shown in Figure 4–11, where the lower input is fixed at 1.



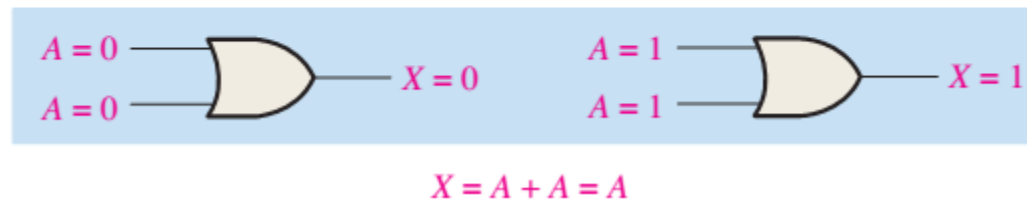
**Rule 5:  $A + A = A$**  A variable ORed with itself is always equal to the variable. If  $A$  is 0, then  $0 + 0 = 0$ ; and if  $A$  is 1, then  $1 + 1 = 1$ . This is shown in Figure 4–12, where both inputs are the same variable.



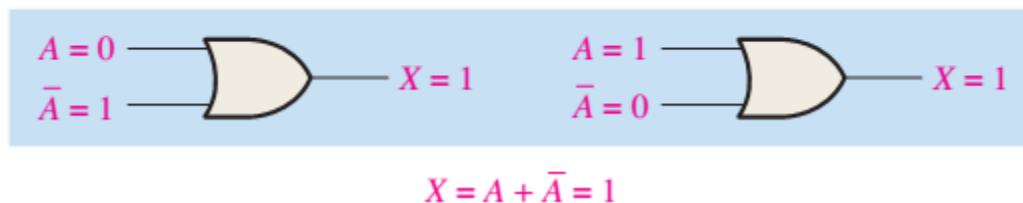
**Rule 6:  $A + \bar{A} = 1$**  A variable ORed with its complement is always equal to 1. If  $A$  is 0, then  $0 + \bar{0} = 0 + 1 = 1$ . If  $A$  is 1, then  $1 + \bar{1} = 1 + 0 = 1$ . See Figure 4–13, where one input is the complement of the other.



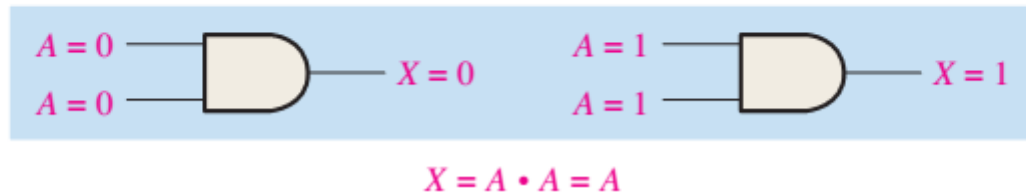
**Rule 7:  $A \cdot A = A$**  A variable ANDed with itself is always equal to the variable. If  $A = 0$ , then  $0 \cdot 0 = 0$ ; and if  $A = 1$ , then  $1 \cdot 1 = 1$ . Figure 4–14 illustrates this rule.



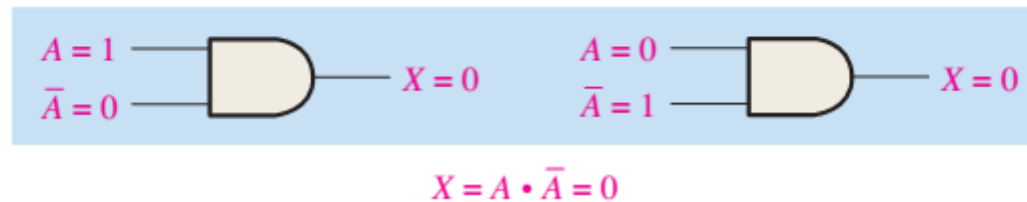**Rule 8:  $A \cdot \bar{A} = 0$**  A variable ANDed with its complement is always equal to 0. Either  $A$  or  $\bar{A}$  will always be 0; and when a 0 is applied to the input of an AND gate, the output will be 0 also. Figure 4–15 illustrates this rule.



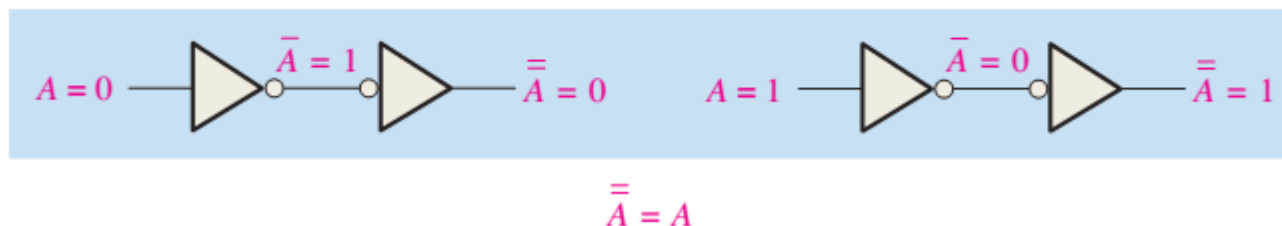**Rule 9:  $\bar{\bar{A}} = A$**  The double complement of a variable is always equal to the variable. If you start with the variable  $A$  and complement (invert) it once, you get  $\bar{A}$ . If you then take  $\bar{A}$  and complement (invert) it, you get  $A$ , which is the original variable. This rule is shown in Figure 4–16 using inverters.






## Commutative Laws

The *commutative law of addition* for two variables is written as


$$A + B = B + A$$

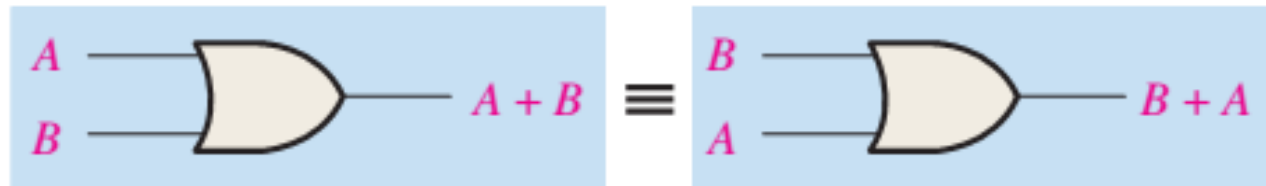

Application of commutative law of addition.

The *commutative law of multiplication* for two variables is

$$AB = BA$$

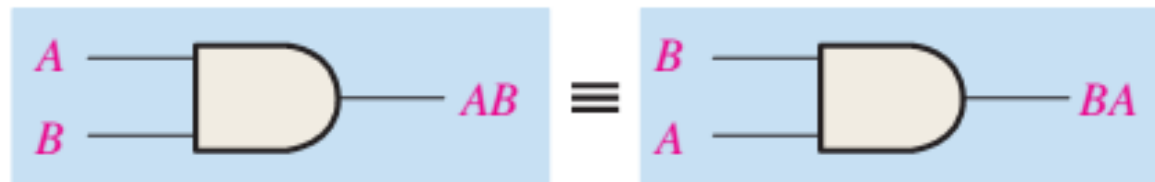


Application of commutative law of multiplication.

## Associative Laws


The *associative law of addition* is written as follows for three variables:

$$A + (B + C) = (A + B) + C$$

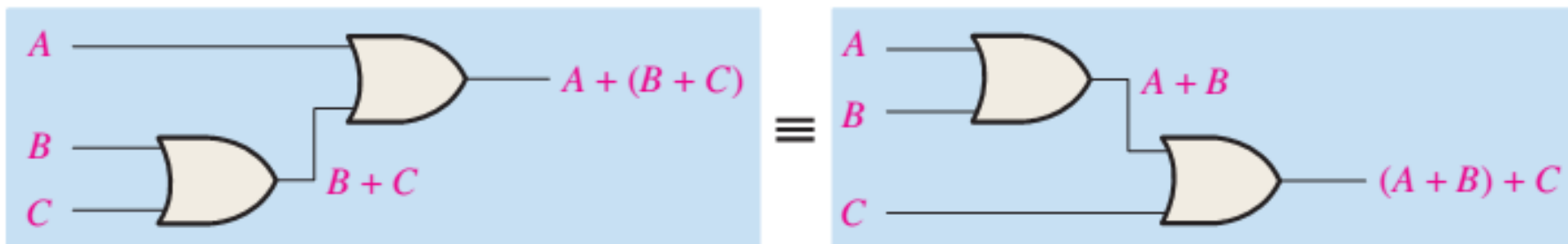

The *associative law of multiplication* is written as follows for three variables:


$$A(BC) = (AB)C$$

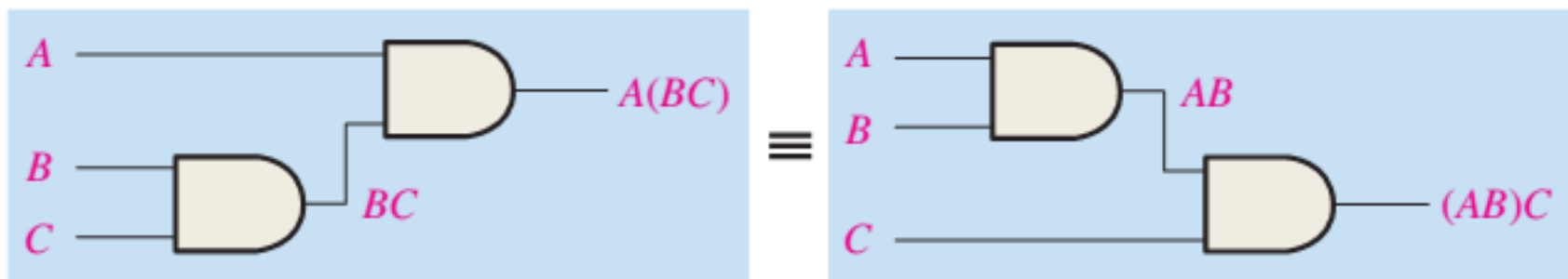

# Distributive Law


The distributive law is written for three variables as follows:

$$A(B + C) = AB + AC$$

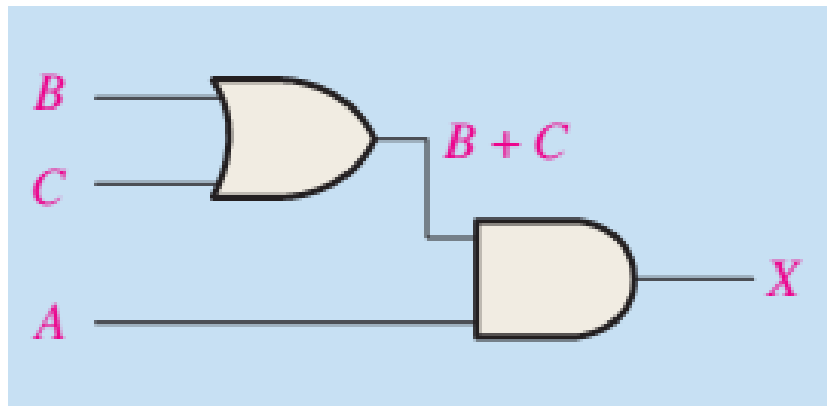

$$X = A(B + C)$$

≡

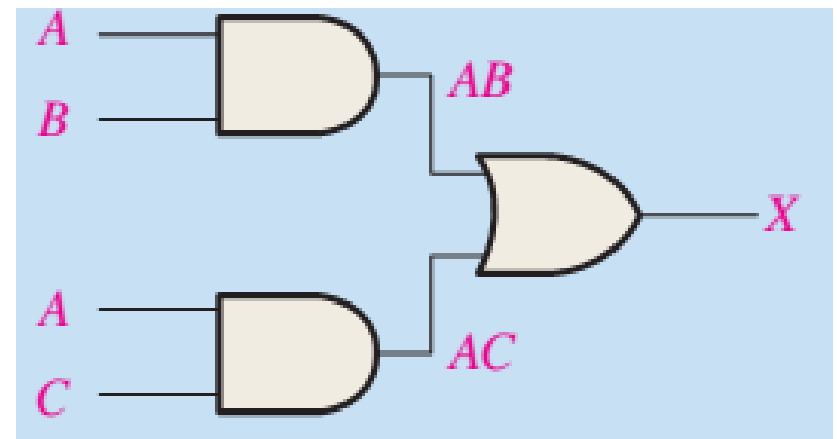

$$X = AB + AC$$


**Rule 10:  $A + AB = A$**  This rule can be proved by applying the distributive law, rule 2, and rule 4 as follows:

$$\begin{aligned}
 A + AB &= A \cdot 1 + AB && \text{Factoring (distributive law)} \\
 &= A \cdot 1 && \text{Rule 2: } (1 + B) = 1 \\
 &= A && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

Rule 10:  $A + AB = A$ . Open file T04-02 to verify.

$A$	$B$	$AB$	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

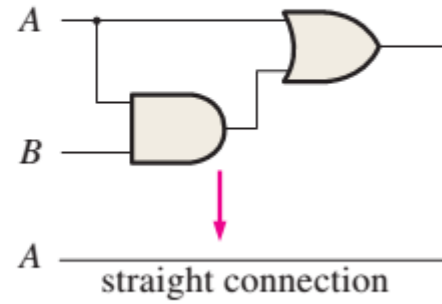

**Rule 11:  $A + \bar{A}B = A + B$**  This rule can be proved as follows:

$$\begin{aligned}
 A + \bar{A}B &= (A + AB) + \bar{A}B && \text{Rule 10: } A = A + AB \\
 &= (AA + AB) + \bar{A}B && \text{Rule 7: } A = AA \\
 &= AA + AB + A\bar{A} + \bar{A}B && \text{Rule 8: adding } A\bar{A} = 0 \\
 &= (A + \bar{A})(A + B) && \text{Factoring} \\
 &= 1 \cdot (A + B) && \text{Rule 6: } A + \bar{A} = 1 \\
 &= A + B && \text{Rule 4: drop the 1}
 \end{aligned}$$

Rule 11:  $A + \bar{A}B = A + B$ . Open file T04-03 to verify.

$A$	$B$	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1


**Rule 12:  $(A + B)(A + C) = A + BC$**  This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= A + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + AB + BC && \text{Rule 2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + BC && \text{Rule 2: } 1 + B = 1 \\
 &= A + BC && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

Rule 12:  $(A + B)(A + C) = A + BC$ . Open file T04-04 to verify.

<i>A</i>	<i>B</i>	<i>C</i>	<i>A + B</i>	<i>A + C</i>	<i>(A + B)(A + C)</i>	<i>BC</i>	<i>A + BC</i>
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

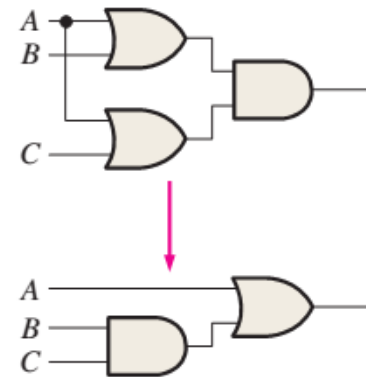

## EXAMPLE

Simplify the following Boolean functions to a minimum number of literals.

1.  $x(x' + y) = xx' + xy = 0 + xy = xy.$

2.  $x + x'y = (x + x')(x + y) = 1(x + y) = x + y.$

3.  $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x.$

4.  $xy + x'z + yz = xy + x'z + yz(x + x')$   
 $= xy + x'z + xyz + x'yz$   
 $= xy(1 + z) + x'z(1 + y)$   
 $= xy + x'z.$

5.  $(x + y)(x' + z)(y + z) = (x + y)(x' + z),$  by duality from function 4.

## DeMorgan's Theorems

**The complement of two or more ANDed variables is equivalent to the OR of the complements of the individual variables.**

The formula for expressing this theorem for two variables is


$$\overline{XY} = \overline{X} + \overline{Y}$$

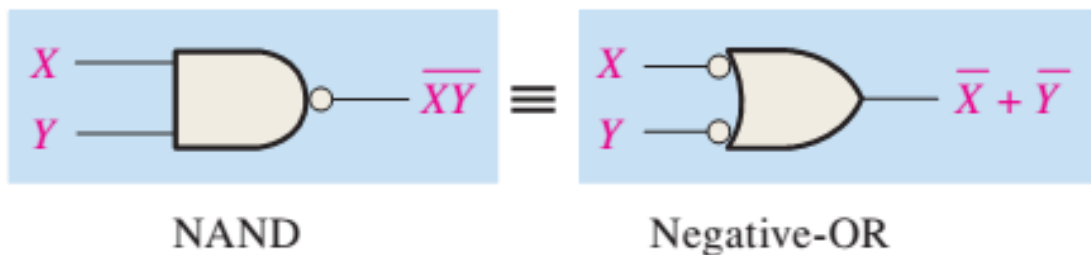**The complement of two or more ORed variables is equivalent to the AND of the complements of the individual variables.**


The formula for expressing this theorem for two variables is

$$\overline{\overline{X} + \overline{Y}} = \overline{\overline{X}} \overline{\overline{Y}}$$





Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X+Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

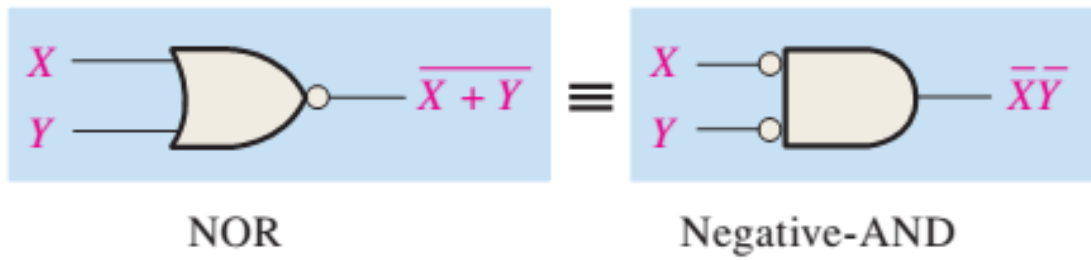

Inputs		Output	
X	Y	$\overline{X+Y}$	$\overline{XY}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Apply DeMorgan's theorems to the expressions  $\overline{XYZ}$  and  $\overline{X + Y + Z}$ .

### Solution

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$
$$\overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$$

Apply DeMorgan's theorems to the expressions  $\overline{WXYZ}$  and  $\overline{W + X + Y + Z}$ .

### Solution

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{Y} + \overline{Z}$$
$$\overline{W + X + Y + Z} = \overline{W} \overline{X} \overline{Y} \overline{Z}$$

## Applying DeMorgan's Theorems

The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + BC} + D(E + \overline{F})}$$

**Step 1:** Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let  $\overline{A + BC} = X$  and  $D(E + \overline{F}) = Y$ .

**Step 2:** Since  $\overline{X + Y} = \overline{X}\overline{Y}$ ,

$$\overline{\overline{A + BC} + D(E + \overline{F})} = \overline{\overline{A + BC}} \overline{D(E + \overline{F})}$$

**Step 3:** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$\overline{\overline{\overline{A + BC}}} \overline{D(E + \overline{F})} = (A + BC) \overline{D(E + \overline{F})}$$

**Step 4:** Apply DeMorgan's theorem to the second term.

$$(A + BC) \overline{D(E + \overline{F})} = (A + BC) (\overline{D} + \overline{E + \overline{F}})$$

**Step 5:** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the  $E + \overline{F}$  part of the term.

$$(A + BC) (\overline{D} + \overline{\overline{E + \overline{F}}}) = (A + BC) (\overline{D} + E + \overline{F})$$

Apply DeMorgan's theorems to each expression:

(a)  $\overline{\overline{A + B} + \overline{C}}$

(b)  $\overline{\overline{A} + B} + CD$

(c)  $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}}$

### Solution

(a)  $\overline{\overline{\overline{A + B} + \overline{C}}} = \overline{\overline{\overline{A + B}}\overline{\overline{C}}} = (A + B)C$

(b)  $\overline{\overline{\overline{A} + B} + CD} = \overline{\overline{\overline{A} + B}}\overline{CD} = (\overline{\overline{A}}\overline{\overline{B}})(\overline{C} + \overline{D}) = A\overline{B}(\overline{C} + \overline{D})$

(c)  $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}} = \overline{((A + B)\overline{C}\overline{D})(E + \overline{F})} = (\overline{A}\overline{B} + C + D)\overline{E}F$

Apply DeMorgan's theorems to each of the following expressions:

(a)  $\overline{(A + B + C)D}$

(b)  $\overline{ABC + DEF}$

(c)  $\overline{\overline{AB} + \overline{CD} + EF}$

### Solution

(a) Let  $A + B + C = X$  and  $D = Y$ . The expression  $\overline{(A + B + C)D}$  is of the form  $\overline{XY} = \overline{X} + \overline{Y}$  and can be rewritten as

$$\overline{(A + B + C)D} = \overline{A + B + C} + \overline{D}$$

Next, apply DeMorgan's theorem to the term  $\overline{A + B + C}$ .

$$\overline{A + B + C} + \overline{D} = \overline{A} \overline{B} \overline{C} + \overline{D}$$

(b) Let  $ABC = X$  and  $DEF = Y$ . The expression  $\overline{ABC + DEF}$  is of the form  $\overline{X + Y} = \overline{X} \overline{Y}$  and can be rewritten as

$$\overline{ABC + DEF} = (\overline{ABC})(\overline{DEF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{ABC}$  and  $\overline{DEF}$ .

$$(\overline{ABC})(\overline{DEF}) = (\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F})$$

- (c) Let  $\overline{AB} = X$ ,  $\overline{CD} = Y$ , and  $EF = Z$ . The expression  $\overline{\overline{AB} + \overline{CD} + EF}$  is of the form  $\overline{X + Y + Z} = \overline{XYZ}$  and can be rewritten as

$$\overline{\overline{AB} + \overline{CD} + EF} = (\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{\overline{AB}}$ ,  $\overline{\overline{CD}}$ , and  $\overline{EF}$ .

$$(\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF}) = (\overline{A} + B)(C + \overline{D})(\overline{E} + \overline{F})$$

Apply DeMorgan's theorems to each expression:

(a)  $\overline{\overline{A + B} + \overline{C}}$

(b)  $\overline{\overline{A + B} + CD}$

(c)  $\overline{(A + B)\overline{CD} + E + \overline{F}}$

## Solution

(a)  $\overline{\overline{A + B} + \overline{C}} = \overline{\overline{\overline{A + B}}\overline{C}} = (A + B)C$

(b)  $\overline{\overline{A + B} + CD} = \overline{\overline{A + B}\overline{CD}} = (\overline{\overline{A}B})(\overline{\overline{C} + \overline{D}}) = A\overline{B}(\overline{C} + \overline{D})$

(c)  $\overline{(A + B)\overline{CD} + E + \overline{F}} = \overline{((A + B)\overline{CD})(E + \overline{F})} = (\overline{A}B + C + D)\overline{EF}$

## EXAMPLE

The Boolean expression for an exclusive-OR gate is  $A\bar{B} + \bar{A}B$ . With this as a starting point, use DeMorgan's theorems and any other rules or laws that are applicable to develop an expression for the exclusive-NOR gate.

## Solution

Start by complementing the exclusive-OR expression and then applying DeMorgan's theorems as follows:


$$\overline{A\bar{B} + \bar{A}B} = \overline{(A\bar{B})(\bar{A}B)} = (\bar{A} + \bar{\bar{B}})(\bar{\bar{A}} + \bar{B}) = (\bar{A} + B)(A + \bar{B})$$

Next, apply the distributive law and rule 8 ( $A \cdot \bar{A} = 0$ ).

$$(\bar{A} + B)(A + \bar{B}) = \bar{A}A + \bar{A}\bar{B} + AB + B\bar{B} = \bar{A}\bar{B} + AB$$

The final expression for the XNOR is  $\bar{A}\bar{B} + AB$ . Note that this expression equals 1 any time both variables are 0s or both variables are 1s.

# Boolean Analysis of Logic Circuits

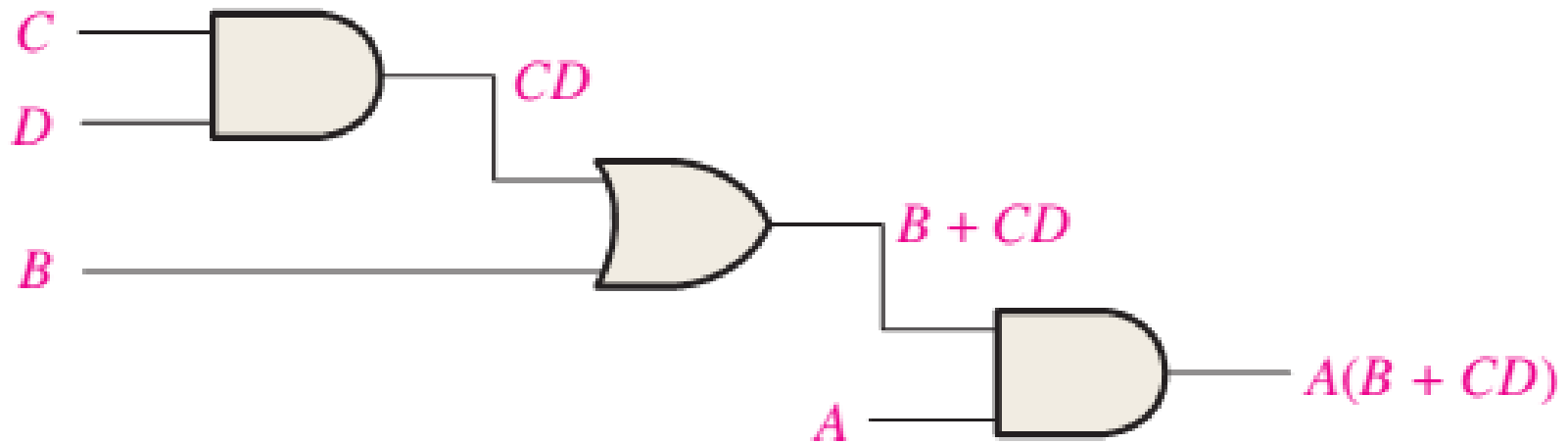



# Constructing a Truth Table for a Logic Circuit

Truth table for the logic circuit in Figure

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

# Logic Simplification Using Boolean Algebra

## EXAMPLE

Using Boolean algebra techniques, simplify this expression:

$$AB + A(B + C) + B(B + C)$$

### Solution

The following is not necessarily the only approach.

**Step 1:** Apply the distributive law to the second and third terms in the expression, as follows:

$$AB + AB + AC + BB + BC$$

**Step 2:** Apply rule 7 ( $BB = B$ ) to the fourth term.

$$AB + AB + AC + B + BC$$

**Step 3:** Apply rule 5 ( $AB + AB = AB$ ) to the first two terms.

$$AB + AC + B + BC$$


**Step 4:** Apply rule 10 ( $B + BC = B$ ) to the last two terms.

$$AB + AC + B$$

**Step 5:** Apply rule 10 ( $AB + B = B$ ) to the first and third terms.

$$B + AC$$

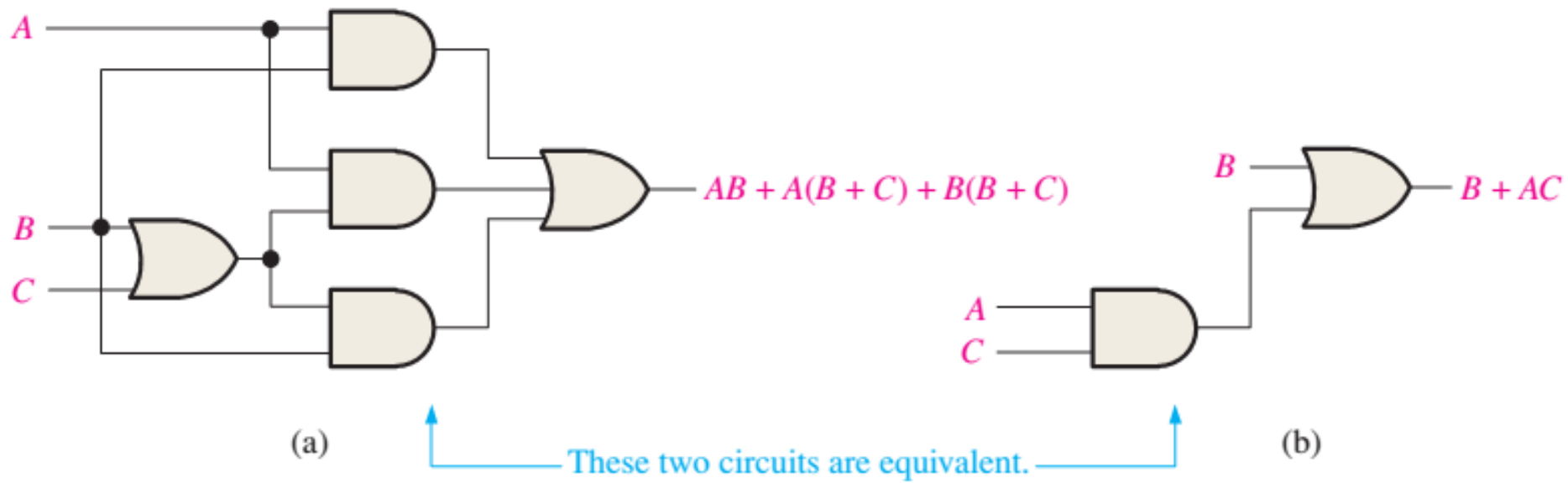At this point the expression is simplified as much as possible. Once you gain experience in applying Boolean algebra, you can often combine many individual steps.



Simplify the following Boolean expression:

$$[\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B}]C$$

Note that brackets and parentheses mean the same thing: the term inside is multiplied (ANDed) with the term outside.

## Solution

**Step 1:** Apply the distributive law to the terms within the brackets.

$$(\overline{A}BC + A\overline{B}BD + \overline{A}\overline{B})C$$

**Step 2:** Apply rule 8 ( $\overline{B}B = 0$ ) to the second term within the parentheses.

$$(\overline{A}BC + A \cdot 0 \cdot D + \overline{A}\overline{B})C$$

**Step 3:** Apply rule 3 ( $A \cdot 0 \cdot D = 0$ ) to the second term within the parentheses.

$$(\overline{A}BC + 0 + \overline{A}\overline{B})C$$

**Step 4:** Apply rule 1 (drop the 0) within the parentheses.

$$(\overline{A}BC + \overline{A}\overline{B})C$$

**Step 5:** Apply the distributive law.

$$\overline{A}BCC + \overline{A}\overline{B}C$$

**Step 6:** Apply rule 7 ( $CC = C$ ) to the first term.

$$\overline{A}BC + \overline{A}\overline{B}C$$

**Step 7:** Factor out  $\overline{B}C$ .

$$\overline{B}C(A + \overline{A})$$

**Step 8:** Apply rule 6 ( $A + \overline{A} = 1$ ).

$$\overline{B}C \cdot 1$$

**Step 9:** Apply rule 4 (drop the 1).

$$\overline{B}C$$

Simplify the following Boolean expression:

$$\overline{A}BC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + A\overline{B}C + ABC$$

### Solution

**Step 1:** Factor  $BC$  out of the first and last terms.

$$BC(\overline{A} + A) + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + A\overline{B}C$$

**Step 2:** Apply rule 6 ( $\overline{A} + A = 1$ ) to the term in parentheses, and factor  $A\overline{B}$  from the second and last terms.

$$BC \cdot 1 + A\overline{B}(\overline{C} + C) + \overline{A}\overline{B}\overline{C}$$

**Step 3:** Apply rule 4 (drop the 1) to the first term and rule 6 ( $\overline{C} + C = 1$ ) to the term in parentheses.

$$BC + A\overline{B} \cdot 1 + \overline{A}\overline{B}\overline{C}$$

**Step 4:** Apply rule 4 (drop the 1) to the second term.

$$BC + A\overline{B} + \overline{A}\overline{B}\overline{C}$$

**Step 5:** Factor  $\overline{B}$  from the second and third terms.

$$BC + \overline{B}(A + \overline{A}\overline{C})$$

**Step 6:** Apply rule 11 ( $A + \overline{A}\overline{C} = A + \overline{C}$ ) to the term in parentheses.

$$BC + \overline{B}(A + \overline{C})$$

**Step 7:** Use the distributive and commutative laws to get the following expression:

$$BC + A\overline{B} + \overline{B}\overline{C}$$

Simplify the following Boolean expression:

$$\overline{AB + AC} + \overline{A}BC$$

### Solution

**Step 1:** Apply DeMorgan's theorem to the first term.

$$(\overline{AB})(\overline{AC}) + \overline{A}BC$$

**Step 2:** Apply DeMorgan's theorem to each term in parentheses.

$$(\overline{A} + \overline{B})(\overline{A} + \overline{C}) + \overline{A}BC$$

**Step 3:** Apply the distributive law to the two terms in parentheses.

$$\overline{A}\overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}BC$$

**Step 4:** Apply rule 7 ( $\overline{A}\overline{A} = \overline{A}$ ) to the first term, and apply rule 10 [ $\overline{A}\overline{B} + \overline{A}BC = \overline{A}\overline{B}(1 + C) = \overline{A}\overline{B}$ ] to the third and last terms.

$$\overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{B}\overline{C}$$

**Step 5:** Apply rule 10 [ $\overline{A} + \overline{A}\overline{C} = \overline{A}(1 + \overline{C}) = \overline{A}$ ] to the first and second terms.

$$\overline{A} + \overline{A}\overline{B} + \overline{B}\overline{C}$$

**Step 6:** Apply rule 10 [ $\overline{A} + \overline{A}\overline{B} = \overline{A}(1 + \overline{B}) = \overline{A}$ ] to the first and second terms.

$$\overline{A} + \overline{B}\overline{C}$$



# Standard Forms of Boolean Expressions


## The Sum-of-Products (SOP) Form

A product term was defined in Section 4–1 as a term consisting of the product (Boolean multiplication) of literals (variables or their complements). When two or more product terms are summed by Boolean addition, the resulting expression is a **sum-of-products (SOP)**. Some examples are

$$AB + ABC$$


$$ABC + CDE + \bar{B}\bar{C}\bar{D}$$

$$\bar{A}B + \bar{A}B\bar{C} + AC$$

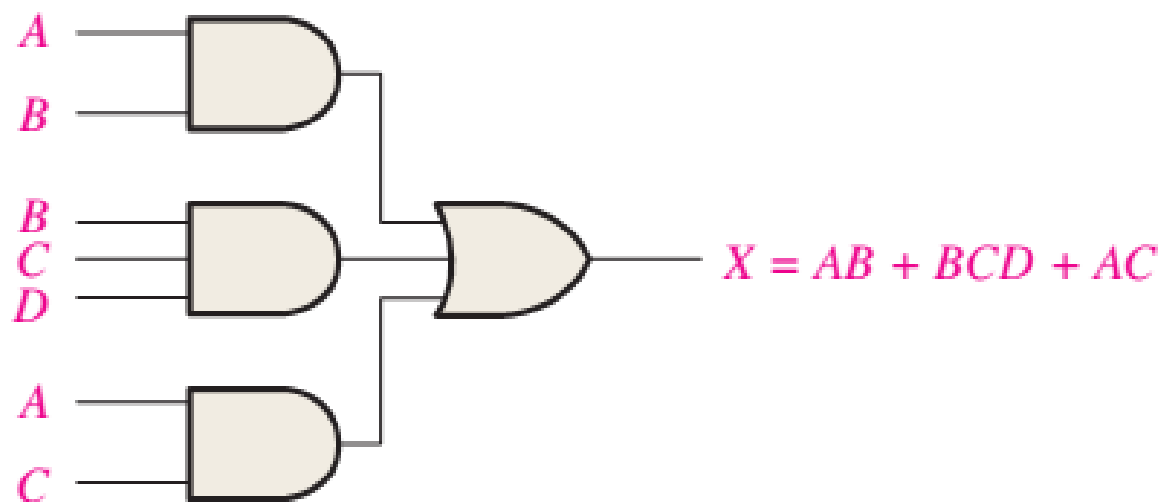

Implementation of the SOP expression  $AB + BCD + AC$ .
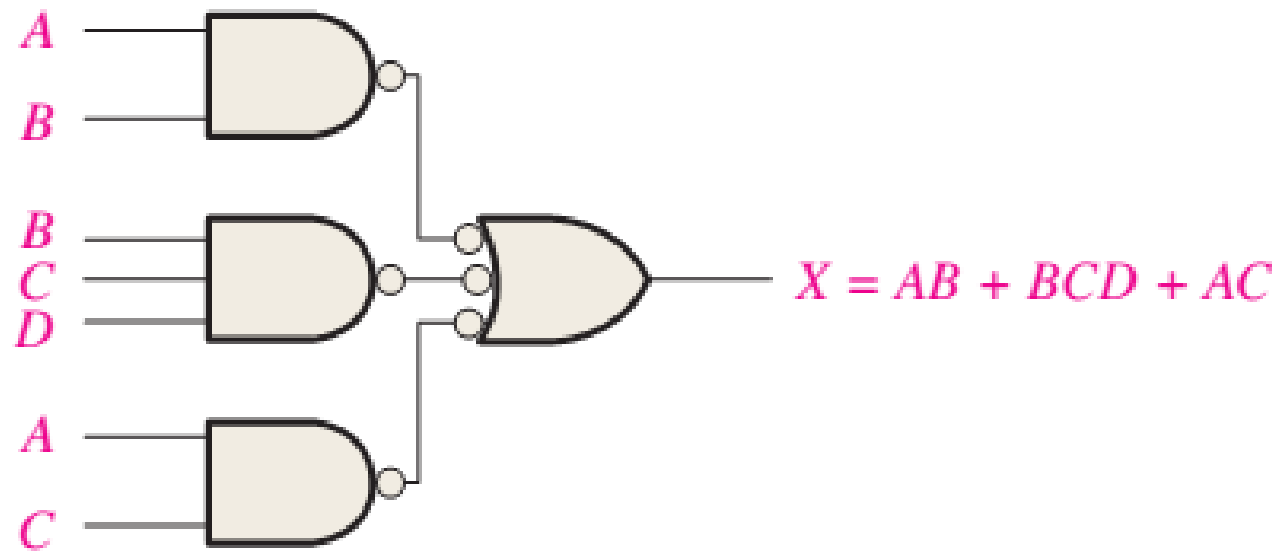
# NAND/NAND Implementation of an SOP Expression



This NAND/NAND implementation is equivalent to the AND/OR

## Conversion of a General Expression to SOP Form

Any logic expression can be changed into SOP form by applying Boolean algebra techniques. For example, the expression  $A(B + CD)$  can be converted to SOP form by applying the distributive law:

$$A(B + CD) = AB + ACD$$

### EXAMPLE

Convert each of the following Boolean expressions to SOP form:

$$(a) AB + B(CD + EF) \quad (b) (A + B)(B + C + D) \quad (c) \overline{\overline{(A + B)} + C}$$

### Solution

$$(a) AB + B(CD + EF) = AB + BCD + BEF$$

$$(b) (A + B)(B + C + D) = AB + AC + AD + BB + BC + BD$$

$$(c) \overline{\overline{(A + B)} + C} = \overline{\overline{(A + B)}}\overline{C} = (A + B)\overline{C} = A\overline{C} + B\overline{C}$$

# The Standard SOP Form

A *standard SOP expression* is one in which *all* the variables in the domain appear in each product term in the expression. For example,  $\overline{A}BCD + \overline{A}\overline{B}CD + \overline{A}BC\overline{D}$  is a standard SOP expression. Standard SOP expressions are important in constructing truth tables.

## Converting Product Terms to Standard SOP

Each product term in an SOP expression that does not contain all the variables in the domain can be expanded to standard form to include all variables in the domain and their complements. As stated in the following steps, a nonstandard SOP expression is converted into standard form using Boolean algebra rule 6 ( $A + \overline{A} = 1$ ) from Table 4–1: A variable added to its complement equals 1.

**Step 1:** Multiply each nonstandard product term by a term made up of the sum of a missing variable and its complement. This results in two product terms. As you know, you can multiply anything by 1 without changing its value.

**Step 2:** Repeat Step 1 until all resulting product terms contain all variables in the domain in either complemented or uncomplemented form. In converting a product term to standard form, the number of product terms is doubled for each missing variable.

# Binary Representation of a Standard Product Term

**An SOP expression is equal to 1 only if one or more of the product terms in the expression is equal to 1.**

A standard product term is equal to 1 for only one combination of variable values. For example, the product term  $A\bar{B}C\bar{D}$  is equal to 1 when  $A = 1, B = 0, C = 1, D = 0$ , as shown below, and is 0 for all other combinations of values for the variables.

$$A\bar{B}C\bar{D} = 1 \cdot \bar{0} \cdot 1 \cdot \bar{0} = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

**EXAMPLE**

Convert the following Boolean expression into standard SOP form:

$$A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D$$

**Solution**

The domain of this SOP expression is  $A, B, C, D$ . Take one term at a time. The first term,  $A\bar{B}C$ , is missing variable  $D$  or  $\bar{D}$ , so multiply the first term by  $D + \bar{D}$  as follows:

$$A\bar{B}C = A\bar{B}C(D + \bar{D}) = A\bar{B}CD + A\bar{B}C\bar{D}$$

In this case, two standard product terms are the result.

The second term,  $\bar{A}\bar{B}$ , is missing variables  $C$  or  $\bar{C}$  and  $D$  or  $\bar{D}$ , so first multiply the second term by  $C + \bar{C}$  as follows:

$$\bar{A}\bar{B} = \bar{A}\bar{B}(C + \bar{C}) = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

The two resulting terms are missing variable  $D$  or  $\bar{D}$ , so multiply both terms by  $D + \bar{D}$  as follows:

$$\begin{aligned} \bar{A}\bar{B} &= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} = \bar{A}\bar{B}C(D + \bar{D}) + \bar{A}\bar{B}\bar{C}(D + \bar{D}) \\ &= \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} \end{aligned}$$

In this case, four standard product terms are the result.

The third term,  $AB\bar{C}D$ , is already in standard form. The complete standard SOP form of the original expression is as follows:

$$A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D = \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + AB\bar{C}D$$

## The Product-of-Sums (POS) Form


A sum term was defined in Section 4–1 as a term consisting of the sum (Boolean addition) of literals (variables or their complements). When two or more sum terms are multiplied, the resulting expression is a **product-of-sums (POS)**. Some examples are

$$(\bar{A} + B)(A + \bar{B} + C)$$

$$(\bar{A} + \bar{B} + \bar{C})(C + \bar{D} + E)(\bar{B} + C + D)$$

$$(A + B)(A + \bar{B} + C)(\bar{A} + C)$$

### Implementation of a POS Expression

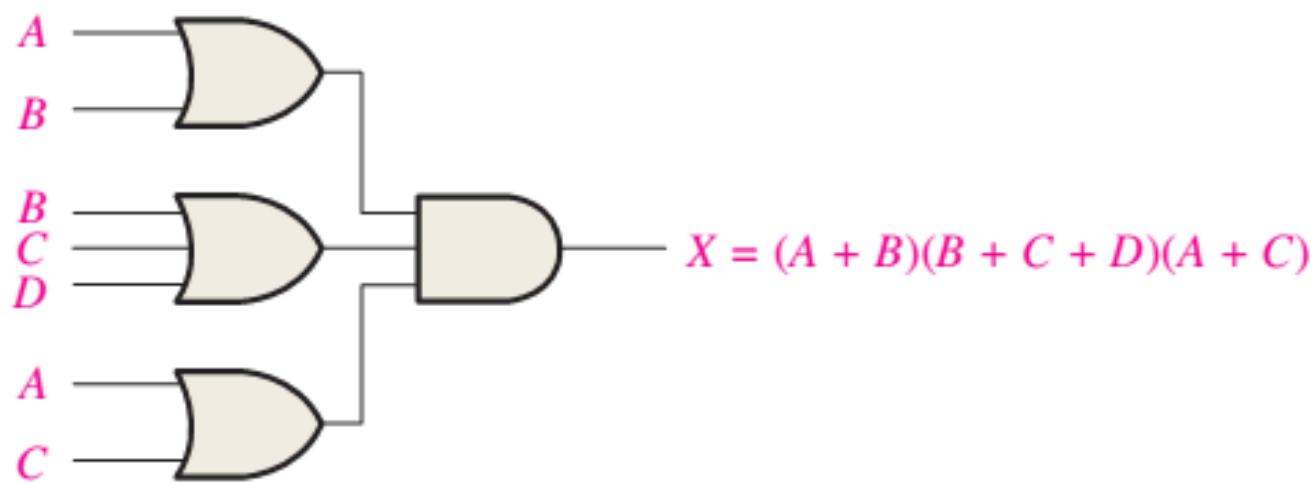

Implementation of the POS expression  $(A + B)(B + C + D)(A + C)$ .



# The Standard POS Form

A *standard POS expression* is one in which *all* the variables in the domain appear in each sum term in the expression. For example,

$$(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + \bar{B} + C + D)(A + B + \bar{C} + D)$$

is a standard POS expression. Any nonstandard POS expression (referred to simply as POS) can be converted to the standard form using Boolean algebra.

## Converting a Sum Term to Standard POS

- Step 1:** Add to each nonstandard product term a term made up of the product of the missing variable and its complement. This results in two sum terms. As you know, you can add 0 to anything without changing its value.
- Step 2:** Apply rule 12 from Table 4–1:  $A + BC = (A + B)(A + C)$
- Step 3:** Repeat Step 1 until all resulting sum terms contain all variables in the domain in either complemented or uncomplemented form.



## Binary Representation of a Standard Sum Term

**A POS expression is equal to 0 only if one or more of the sum terms in the expression is equal to 0.**

A standard sum term is equal to 0 for only one combination of variable values. For example, the sum term  $A + \overline{B} + C + \overline{D}$  is 0 when  $A = 0$ ,  $B = 1$ ,  $C = 0$ , and  $D = 1$ , as shown below, and is 1 for all other combinations of values for the variables.

$$A + \overline{B} + C + \overline{D} = 0 + \overline{1} + 0 + \overline{1} = 0 + 0 + 0 + 0 = 0$$

**EXAMPLE**

Convert the following Boolean expression into standard POS form:

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

**Solution**

The domain of this POS expression is  $A, B, C, D$ . Take one term at a time. The first term,  $A + \bar{B} + C$ , is missing variable  $D$  or  $\bar{D}$ , so add  $D\bar{D}$  and apply rule 12 as follows:

$$A + \bar{B} + C = A + \bar{B} + C + D\bar{D} = (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})$$

The second term,  $\bar{B} + C + \bar{D}$ , is missing variable  $A$  or  $\bar{A}$ , so add  $A\bar{A}$  and apply rule 12 as follows:

$$\bar{B} + C + \bar{D} = \bar{B} + C + \bar{D} + A\bar{A} = (A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})$$

The third term,  $A + \bar{B} + \bar{C} + D$ , is already in standard form. The standard POS form of the original expression is as follows:

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D) = \\ (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

## Converting Standard SOP to Standard POS

The binary values of the product terms in a given standard SOP expression are not present in the equivalent standard POS expression. Also, the binary values that are not represented in the SOP expression are present in the equivalent POS expression. Therefore, to convert from standard SOP to standard POS, the following steps are taken:

- Step 1:** Evaluate each product term in the SOP expression. That is, determine the binary numbers that represent the product terms.
- Step 2:** Determine all of the binary numbers not included in the evaluation in Step 1.
- Step 3:** Write the equivalent sum term for each binary number from Step 2 and express in POS form.

## EXAMPLE

Convert the following SOP expression to an equivalent POS expression:

$$\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$$

## Solution

The evaluation is as follows:

$$000 + 010 + 011 + 101 + 111$$

Since there are three variables in the domain of this expression, there are a total of eight ( $2^3$ ) possible combinations. The SOP expression contains five of these combinations, so the POS must contain the other three which are **001, 100, and 110**. Remember, these are the binary values that make the sum term 0. The equivalent POS expression is

$$(A + B + \overline{C})(\overline{A} + B + C)(\overline{A} + \overline{B} + C)$$

# Boolean Expressions and Truth Tables

## Converting SOP Expressions to Truth Table Format

$$SOP \rightarrow A \Leftrightarrow 1, A' \Leftrightarrow 0$$

### EXAMPLE

Develop a truth table for the standard SOP expression  $\bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC$ .

Inputs			Output	Product Term
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>	
0	0	0	0	
0	0	1	1	$\bar{A}\bar{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$\bar{A}B\bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	$ABC$

# Converting POS Expressions to Truth Table Format

$$POS \rightarrow A \Leftrightarrow 0, A' \Leftrightarrow 1$$

## EXAMP

Determine the truth table for the following standard POS expression:

$$(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

Inputs			Output	Sum Term
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \bar{B} + C)$
0	1	1	0	$(A + \bar{B} + \bar{C})$
1	0	0	1	
1	0	1	0	$(\bar{A} + B + \bar{C})$
1	1	0	0	$(\bar{A} + \bar{B} + C)$
1	1	1	1	

**EXAMPLE**

From the truth table in Table , determine the standard SOP expression and the equivalent standard POS expression.

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

## Solution

There are four 1s in the output column and the corresponding binary values are 011, 100, 110, and 111. Convert these binary values to product terms as follows:

$$011 \longrightarrow \bar{A}BC$$

$$100 \longrightarrow A\bar{B}\bar{C}$$

$$110 \longrightarrow A\bar{B}C$$

$$111 \longrightarrow ABC$$

A	Inputs			Output
	B	C	X	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	1	
1	0	1	0	
1	1	0	1	
1	1	1	1	

The resulting standard SOP expression for the output  $X$  is

$$X = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

For the POS expression, the output is 0 for binary values 000, 001, 010, and 101. Convert these binary values to sum terms as follows:

$$000 \longrightarrow A + B + C$$

$$001 \longrightarrow A + B + \bar{C}$$

$$010 \longrightarrow A + \bar{B} + C$$

$$101 \longrightarrow \bar{A} + B + \bar{C}$$

The resulting standard POS expression for the output  $X$  is

$$X = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + \bar{C})$$



## Minterms and Maxterms for Three Binary Variables

<b>x</b>	<b>y</b>	<b>z</b>	<b>Minterms</b>		<b>Maxterms</b>	
			<b>Term</b>	<b>Designation</b>	<b>Term</b>	<b>Designation</b>
0	0	0	$x'y'z'$	$m_0$	$x + y + z$	$M_0$
0	0	1	$x'y'z$	$m_1$	$x + y + z'$	$M_1$
0	1	0	$x'yz'$	$m_2$	$x + y' + z$	$M_2$
0	1	1	$x'yz$	$m_3$	$x + y' + z'$	$M_3$
1	0	0	$xy'z'$	$m_4$	$x' + y + z$	$M_4$
1	0	1	$xy'z$	$m_5$	$x' + y + z'$	$M_5$
1	1	0	$xyz'$	$m_6$	$x' + y' + z$	$M_6$
1	1	1	$xyz$	$m_7$	$x' + y' + z'$	$M_7$

write the function in standard **minterm**

(SOP) form. To illustrate, we will use the expression

$$X = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + AB\overline{C}\overline{D} + AB\overline{C}D + ABCD$$

<i>ABCD</i>	<i>X</i>	<b>Minterm</b>
0000	0	
0001	1	$m_1$
0010	0	
0011	1	$m_3$
0100	1	$m_4$
0101	1	$m_5$
0110	0	
0111	0	
1000	0	
1001	0	
1010	1	$m_{10}$
1011	0	
1100	1	$m_{12}$
1101	1	$m_{13}$
1110	0	
1111	1	$m_{15}$

$$\begin{aligned} F &= A'B'C + AB'C + AB'C + ABC' + ABC \\ &= m_1 + m_4 + m_5 + m_6 + m_7 \end{aligned}$$



When a Boolean function is in its sum-of-minterms form, it is sometimes convenient to express the function in the following brief notation:

$$F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$$

$$\begin{aligned} F &= (x + y + z)(x + y' + z)(x' + y + z)(x' + y + z') \\ &= M_0 M_2 M_4 M_5 \end{aligned}$$

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

### Truth Table for $F = xy + x'z$


	<b>x</b>	<b>y</b>	<b>z</b>	<b>F</b>
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Minterms


Maxterms

$$F(x, y, z) = \Sigma(1, 3, 6, 7)$$

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

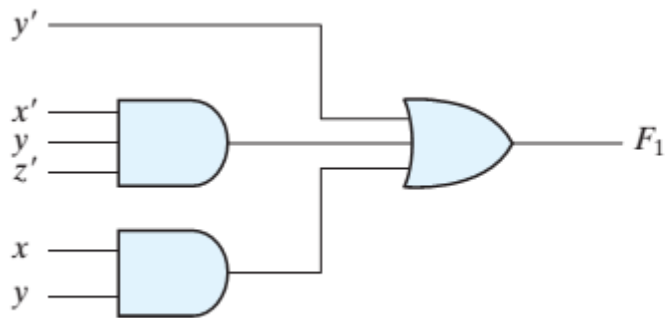


(a) Sum of Products

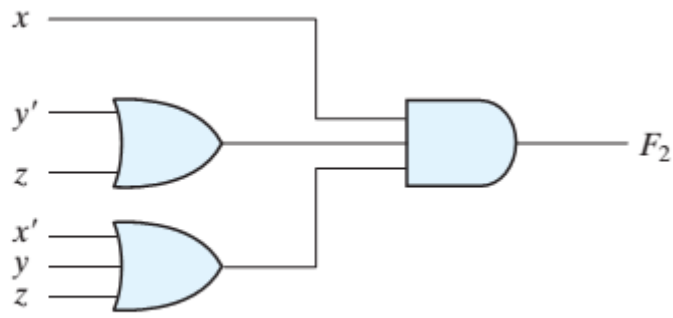


(b) Product of Sums

$$F_1 = y' + xy + x'yz'$$

$$F_2 = x(y' + z)(x' + y + z')$$

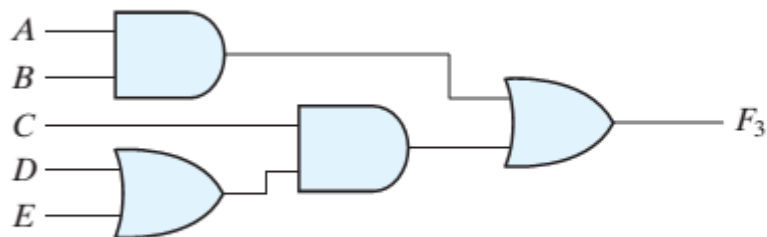

(a)  $AB + C(D + E)$

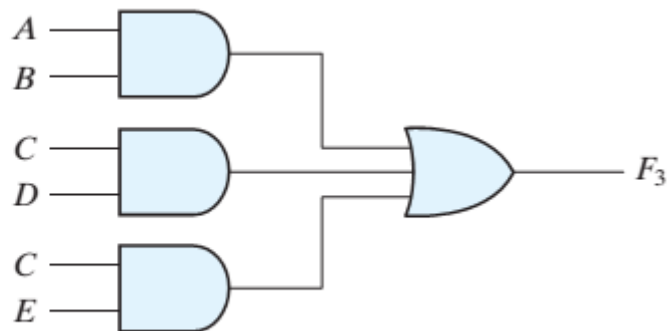

(b)  $AB + CD + CE$

## The Karnaugh Map

A Karnaugh map provides a systematic method for simplifying Boolean expressions and, if properly used, will produce the simplest SOP or POS expression possible, known as the minimum expression. As you have seen, the effectiveness of algebraic simplification depends on your familiarity with all the laws, rules, and theorems of Boolean algebra and on your ability to apply them.

A **Karnaugh map** is similar to a truth table because it presents all of the possible values of input variables and the resulting output for each value. Instead of being organized into columns and rows like a truth table, the Karnaugh map is an array of **cells** in which each cell represents a binary value of the input variables. The cells are arranged in a way so that simplification of a given expression is simply a matter of properly grouping the cells.

Karnaugh maps can be used for expressions with two, three, four, and five variables, but we will discuss only 3-variable and 4-variable situations to illustrate the principles.

The number of cells in a Karnaugh map, as well as the number of rows in a truth table, is equal to the total number of possible input variable combinations. For three variables, the number of cells is  $2^3 = 8$ . For four variables, the number of cells is  $2^4 = 16$ .

# The 3-Variable Karnaugh Map

$AB \backslash C$	0	1
00		
01		
11		
10		

(a)

$AB \backslash C$	0	1
00	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$
01	$\bar{A}B\bar{C}$	$\bar{A}BC$
11	$AB\bar{C}$	$ABC$
10	$A\bar{B}\bar{C}$	$A\bar{B}C$

(b)

A 3-variable Karnaugh map showing Boolean product terms for each cell.

# The 4-Variable Karnaugh Map

<i>AB</i> \ <i>CD</i>	00	01	11	10
00				
01				
11				
10				


(a)

<i>AB</i> \ <i>CD</i>	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$
01	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$
11	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$

(b)


A 4-variable Karnaugh map.



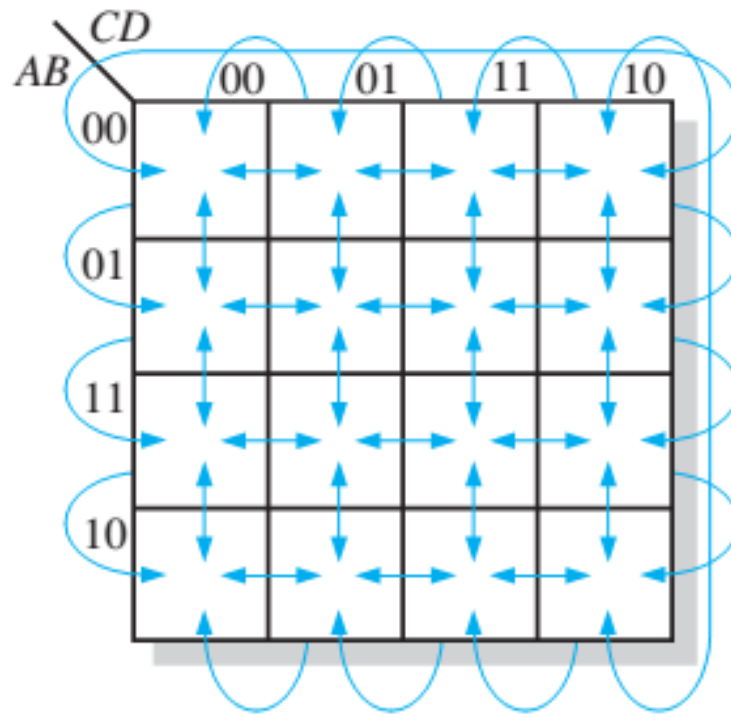

Adjacent cells on a Karnaugh map are those that differ by only one variable. Arrows point between adjacent cells.

# Karnaugh Map SOP Minimization

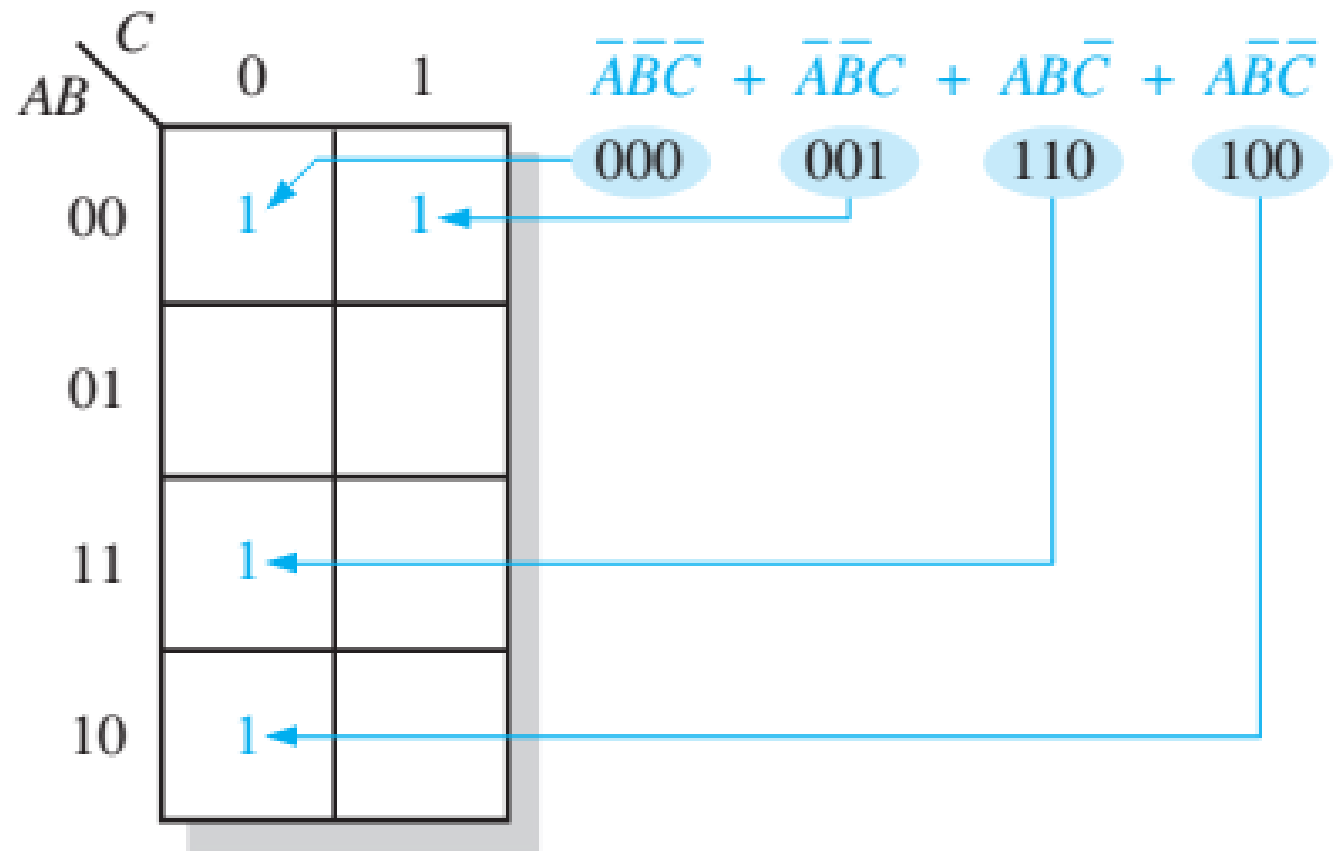

Example of mapping a standard SOP expression.

**EXAMPLE**

Map the following standard SOP expression on a Karnaugh map:


$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

**Solution**

Evaluate the expression as shown below. Place a 1 on the 3-variable Karnaugh map in Figure 4–29 for each standard product term in the expression.

$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

0 0 1    0 1 0    1 1 0    1 1 1

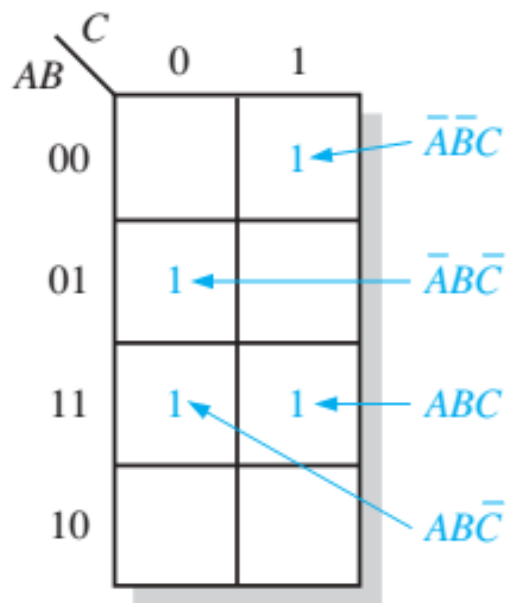

**EXAMPLE**

Map the following standard SOP expression on a Karnaugh map:


$$\bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D + ABCD + A\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D$$

**Solution**

Evaluate the expression as shown below. Place a 1 on the 4-variable Karnaugh map in Figure 4–30 for each standard product term in the expression.

$$\bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D + ABCD + A\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D$$

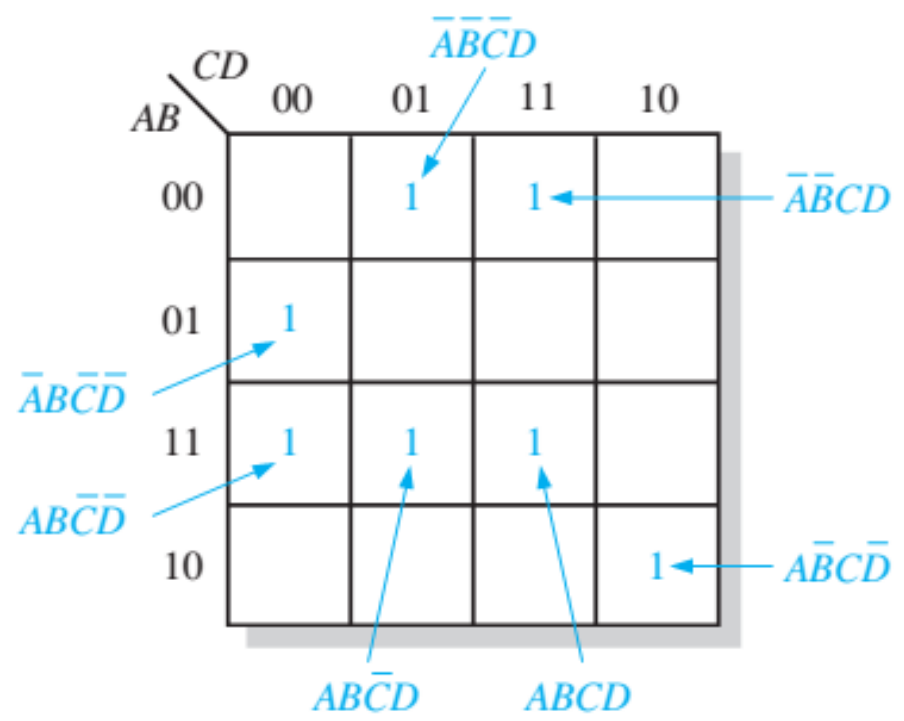0011    0100    1101    1111    1100    0001    1010



**EXAMPLE**

Map the following SOP expression on a Karnaugh map:  $\bar{A} + A\bar{B} + ABC\bar{C}$ .

**Solution**

The SOP expression is obviously not in standard form because each product term does not have three variables. The first term is missing two variables, the second term is missing one variable, and the third term is standard. First expand the terms numerically as follows:

$$\begin{array}{r} \bar{A} + A\bar{B} + ABC\bar{C} \\ 000 \quad 100 \quad 110 \\ 001 \quad 101 \\ 010 \\ 011 \end{array}$$

Map each of the resulting binary values by placing a 1 in the appropriate cell of the 3-variable Karnaugh map in Figure

		<i>C</i>	
		0	1
<i>AB</i>	00	1	1
	01	1	1
	11	1	
	10	1	1

**EXAMPLE**

Map the following SOP expression on a Karnaugh map:

$$\overline{B}\overline{C} + \overline{A}\overline{B} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}CD$$

**Solution**

The SOP expression is obviously not in standard form because each product term does not have four variables. The first and second terms are both missing two variables, the third term is missing one variable, and the rest of the terms are standard. First expand the terms by including all combinations of the missing variables numerically as follows:

$$\begin{array}{rcccccc} \overline{B}\overline{C} & + & \overline{A}\overline{B} & + & A\overline{B}\overline{C} & + & \overline{A}\overline{B}\overline{C}\overline{D} & + & \overline{A}\overline{B}\overline{C}D & + & \overline{A}\overline{B}CD \\ 0000 & & 1000 & & 1100 & & 1010 & & 0001 & & 1011 \\ 0001 & & 1001 & & 1101 & & & & & & \\ 1000 & & 1010 & & & & & & & & \\ 1001 & & 1011 & & & & & & & & \end{array}$$

Map each of the resulting binary values by placing a 1 in the appropriate cell of the 4-variable Karnaugh map in Figure 4–32. Notice that some of the values in the expanded expression are redundant.

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	1	1		
	01				
	11	1	1		
	10	1	1	1	1

# Karnaugh Map Simplification of SOP Expressions

## Grouping the 1s

You can group 1s on the Karnaugh map according to the following rules by enclosing those adjacent cells containing 1s. The goal is to maximize the size of the groups and to minimize the number of groups.

1. A group must contain either 1, 2, 4, 8, or 16 cells, which are all powers of two. In the case of a 3-variable map,  $2^3 = 8$  cells is the maximum group.
2. Each cell in a group must be adjacent to one or more cells in that same group, but all cells in the group do not have to be adjacent to each other.
3. Always include the largest possible number of 1s in a group in accordance with rule 1.
4. Each 1 on the map must be included in at least one group. The 1s already in a group can be included in another group as long as the overlapping groups include noncommon 1s.

## Determining the Minimum SOP Expression from the Map


When all the 1s representing the standard product terms in an expression are properly mapped and grouped, the process of determining the resulting minimum SOP expression begins. The following rules are applied to find the minimum product terms and the minimum SOP expression:

1. Group the cells that have 1s. Each group of cells containing 1s creates one product term composed of all variables that occur in only one form (either uncomplemented or complemented) within the group. Variables that occur both uncomplemented and complemented within the group are eliminated. These are called *contradictory variables*.
2. Determine the minimum product term for each group.
  - (a) For a 3-variable map:
    - (1) A 1-cell group yields a 3-variable product term
    - (2) A 2-cell group yields a 2-variable product term
    - (3) A 4-cell group yields a 1-variable term
    - (4) An 8-cell group yields a value of 1 for the expression
  - (b) For a 4-variable map:
    - (1) A 1-cell group yields a 4-variable product term
    - (2) A 2-cell group yields a 3-variable product term
    - (3) A 4-cell group yields a 2-variable product term
    - (4) An 8-cell group yields a 1-variable term
    - (5) A 16-cell group yields a value of 1 for the expression
3. When all the minimum product terms are derived from the Karnaugh map, they are summed to form the minimum SOP expression.




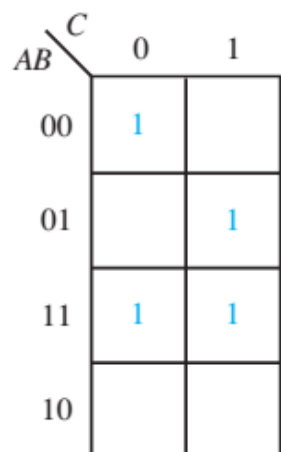**EXAMPLE**


Group the 1s in each of the Karnaugh maps in Figure 4–33.




(a)

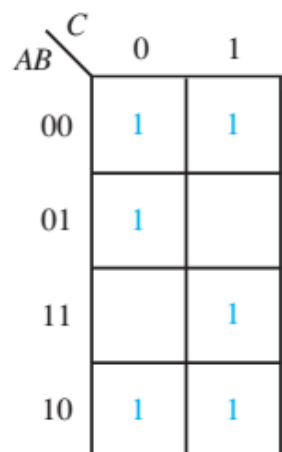


(b)

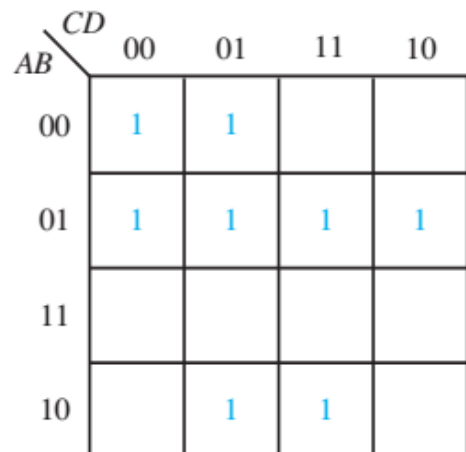


(c)

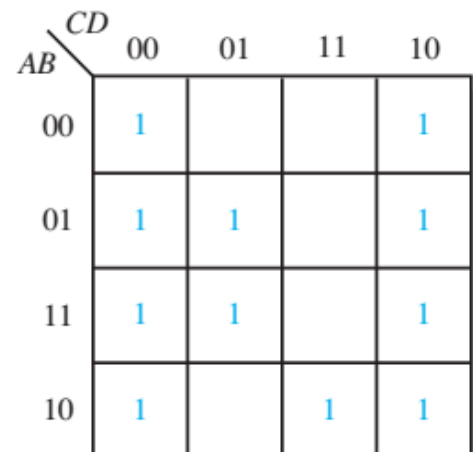


(d)

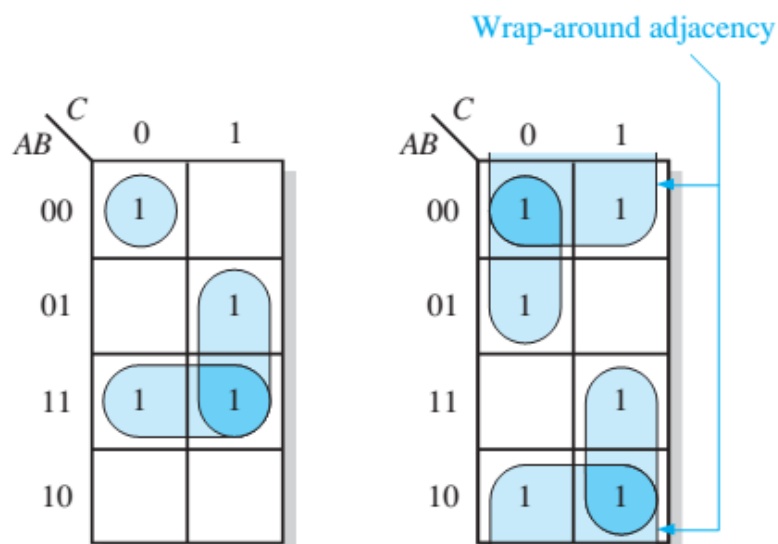


(a)

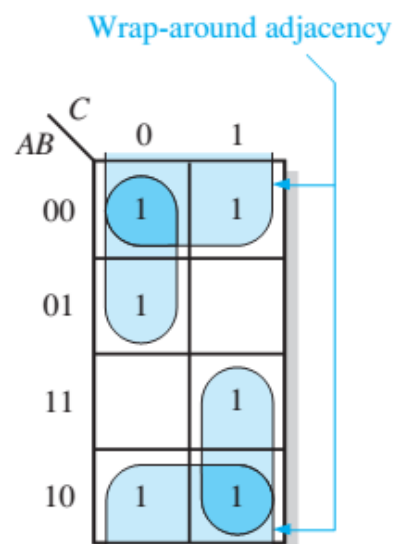

(b)

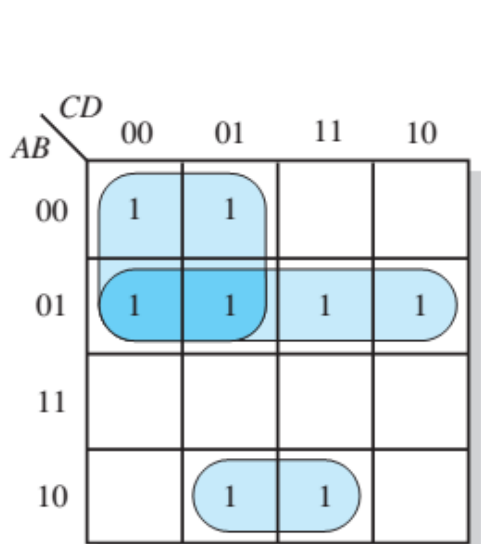


(c)

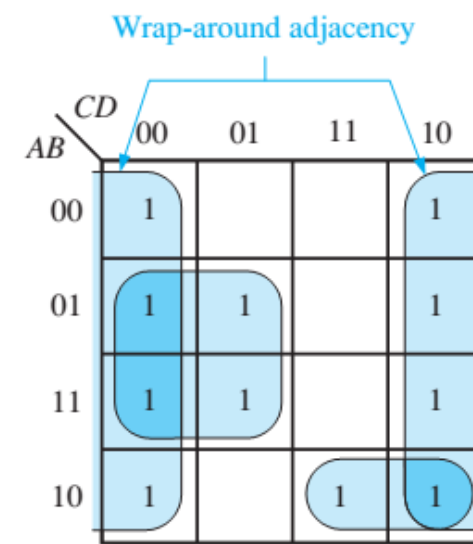

(d)

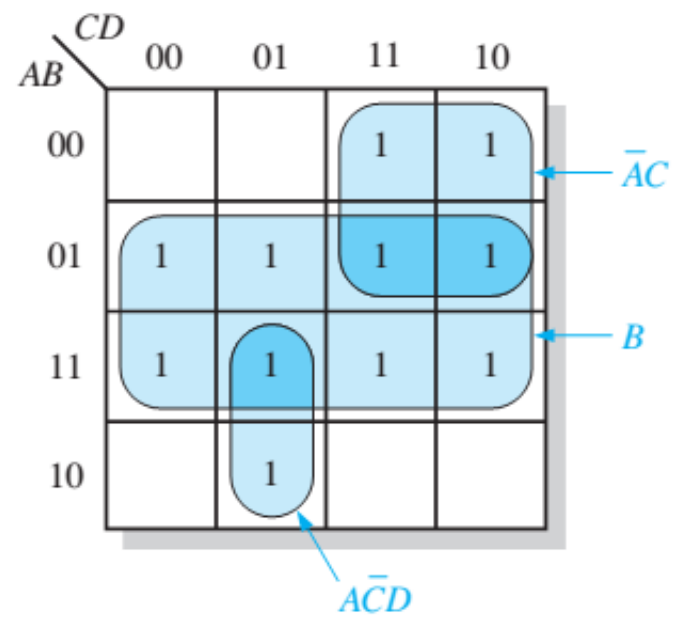**EXAMPLE**

Determine the product terms for the Karnaugh map in Figure 4–35 and write the resulting minimum SOP expression.



A	B	C	D
0	0	1	1
0	0	1	0
0	1	1	1
0	1	1	0

$A'C$

A	B	C	D
1	1	0	1
1	0	0	1

$AC'D$


A	B	C	D
0	1	0	0
0	1	0	1
0	1	1	1
0	1	1	0
1	1	0	0
1	1	0	1
1	1	1	1
1	1	1	0

$B$

$$B + \bar{A}C + \bar{A}\bar{C}D$$

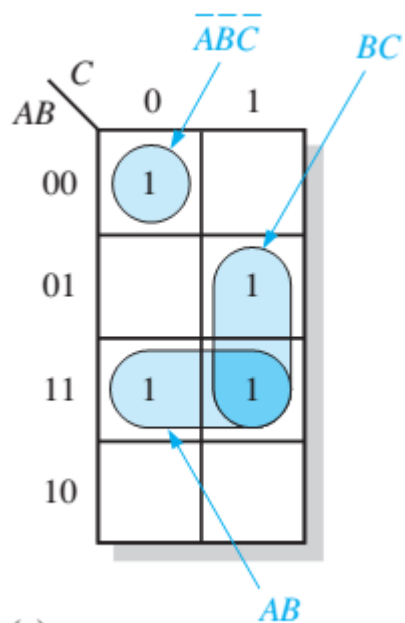
**EXAMPLE**

Determine the product terms for each of the Karnaugh maps in Figure and write the resulting minimum SOP expression.




(a)  $AB + BC + \overline{A}\overline{B}\overline{C}$

(a)

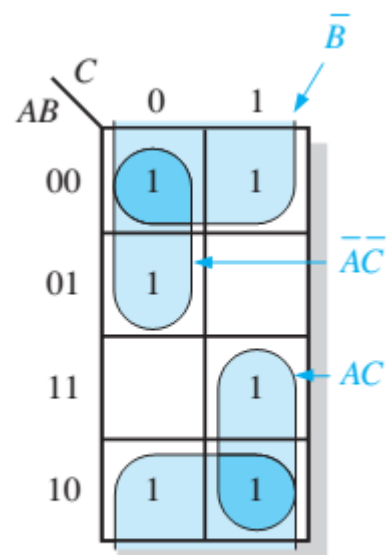


(b)  $\overline{B} + \overline{A}\overline{C} + AC$

(b)

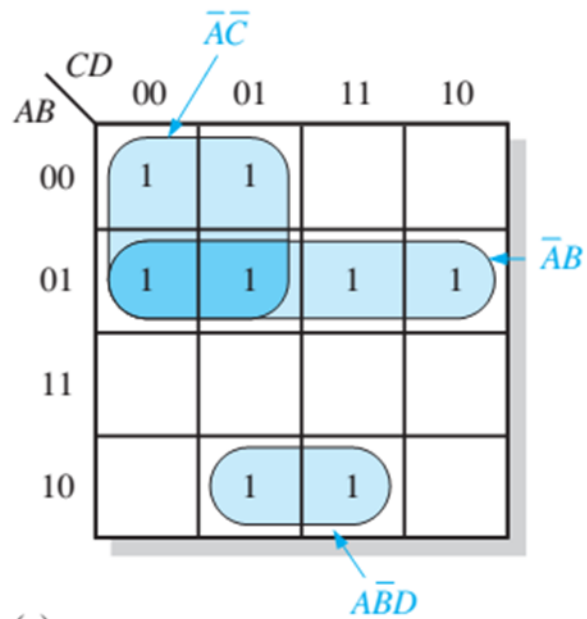

(c)
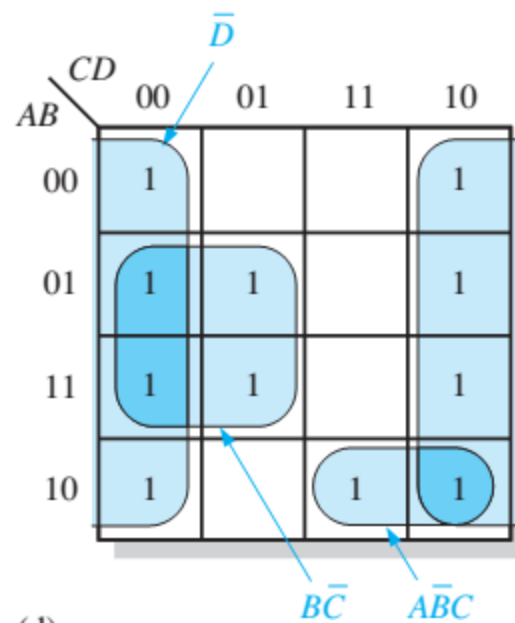
$$(c) \quad \bar{A}B + \bar{A}\bar{C} + \bar{A}BD$$



(d)

$$(d) \quad \bar{D} + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}$$

**EXAMPLE**

Use a Karnaugh map to minimize the following standard SOP expression:


$$\bar{A}\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

**Solution**

The binary values of the expression are

$$101 + 011 + 001 + 000 + 100$$

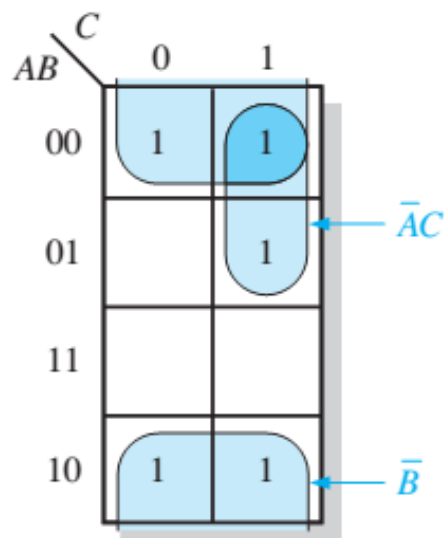Map the standard SOP expression and group the cells as shown in Figure



The resulting minimum SOP expression is

$$\bar{B} + \bar{A}C$$


**EXAMPLE**

Use a Karnaugh map to minimize the following SOP expression:

$$\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}C\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D}$$

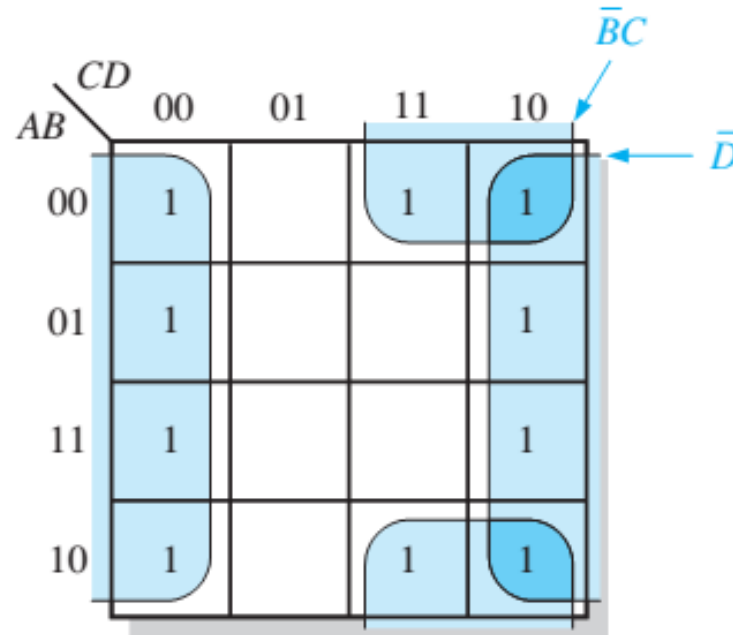**Solution**

The first term  $\overline{B}\overline{C}\overline{D}$  must be expanded into  $A\overline{B}\overline{C}\overline{D}$  and  $\overline{A}\overline{B}\overline{C}\overline{D}$  to get the standard SOP expression, which is then mapped; the cells are grouped as shown in Figure 4–38.




The resulting minimum SOP expression is

$$\overline{D} + \overline{B}C$$
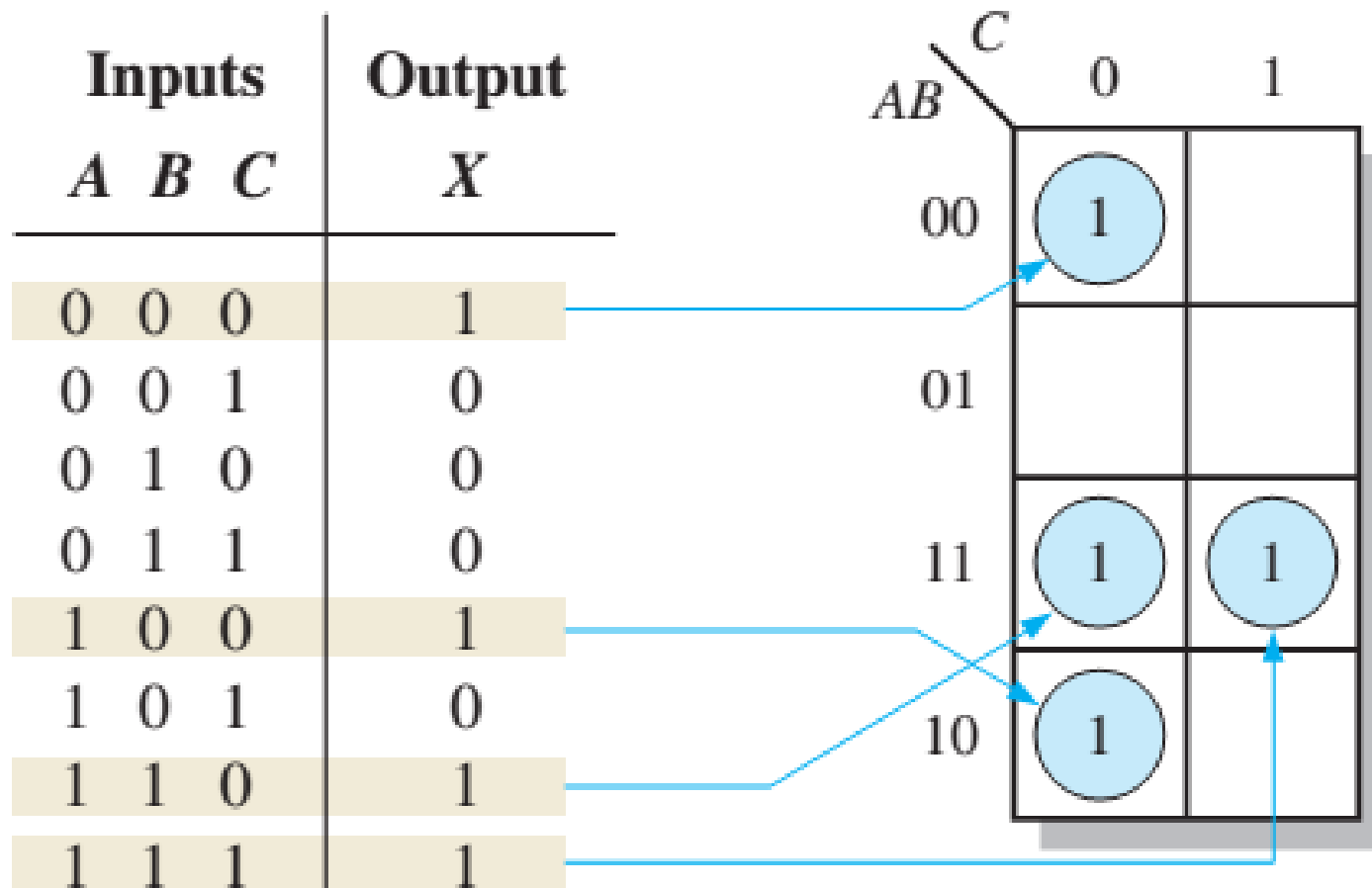
# Mapping Directly from a Truth Table

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$



## “Don’t Care” Conditions


Sometimes a situation arises in which some input variable combinations are not allowed. For example, recall that in the BCD code covered in Chapter 2, there are six invalid combinations: 1010, 1011, 1100, 1101, 1110, and 1111. Since these unallowed states will never occur in an application involving the BCD code, they can be treated as **“don’t care”** terms with respect to their effect on the output. That is, for these “don’t care” terms either a 1 or a 0 may be assigned to the output; it really does not matter since they will never occur.

The “don’t care” terms can be used to advantage on the Karnaugh map. Figure 4–40 shows that for each “don’t care” term, an X is placed in the cell. When grouping the 1s, the Xs can be treated as 1s to make a larger grouping or as 0s if they cannot be used to advantage. The larger a group, the simpler the resulting term will be.



Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

(a) Truth table

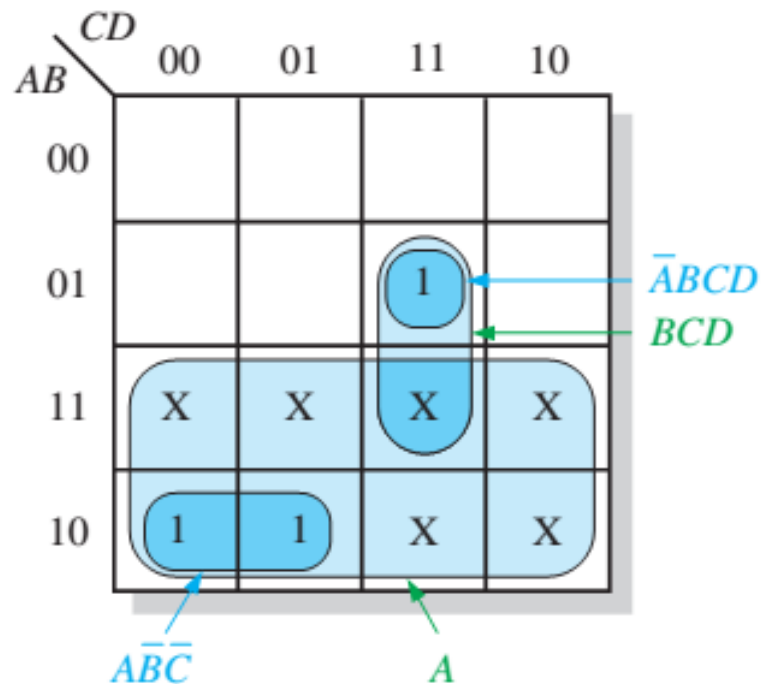


(b) Without “don’t cares”  $Y = \bar{A}BCD + \bar{A}BC\bar{C}$   
 With “don’t cares”  $Y = A + BCD$

Example of the use of “don’t care” conditions to simplify an expression.
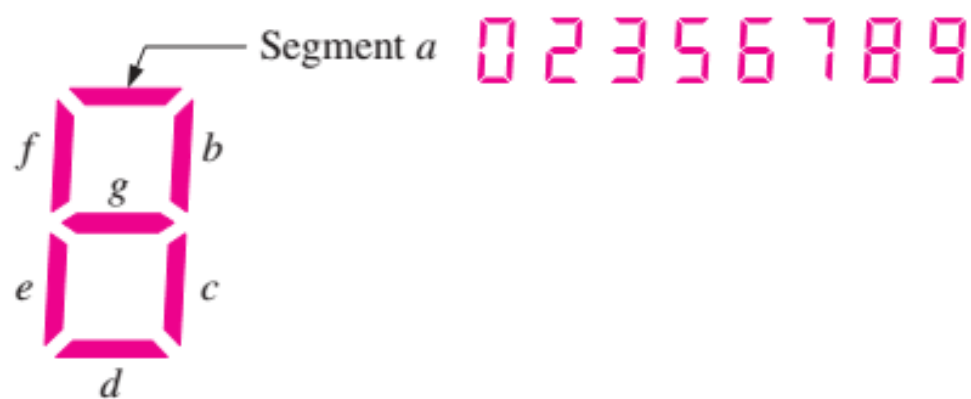
## EXAMPLE

In a 7-segment display, each of the seven segments is activated for various digits. For example, segment  $a$  is activated for the digits 0, 2, 3, 5, 6, 7, 8, and 9, as illustrated in Figure . Since each digit can be represented by a BCD code, derive an SOP expression for segment  $a$  using the variables  $ABCD$  and then minimize the expression using a Karnaugh map.



**FIGURE**


7-segment display.

## Solution

The expression for segment  $a$  is

$$a = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D$$

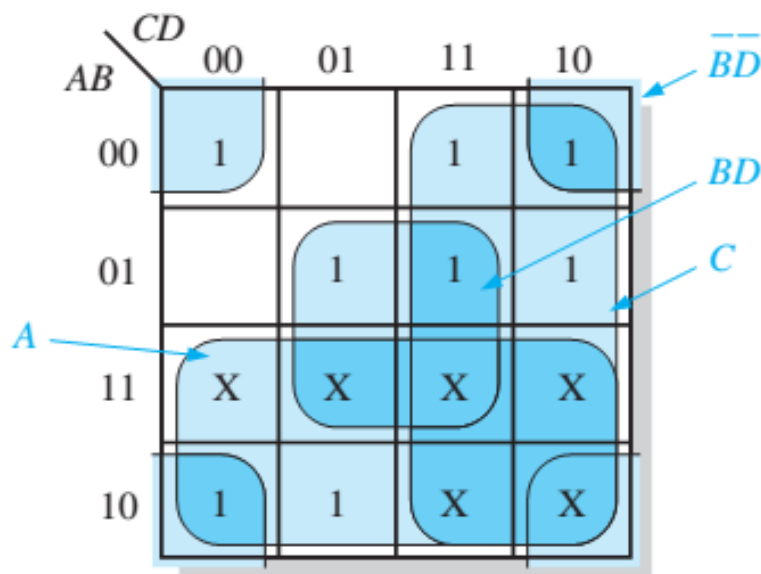Each term in the expression represents one of the digits in which segment  $a$  is used. The Karnaugh map minimization is shown in Figure . X's (don't cares) are entered for those states that do not occur in the BCD code.




**FIGURE**

From the Karnaugh map, the minimized expression for segment  $a$  is

$$a = A + C + BD + \overline{B}\overline{D}$$
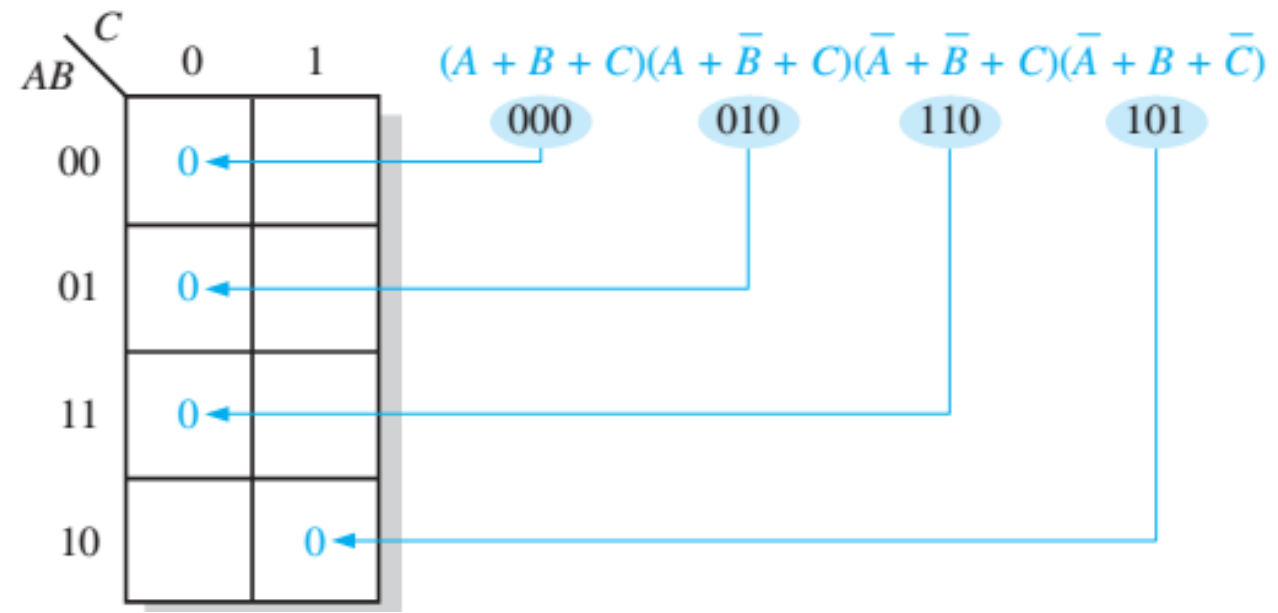
## Mapping a Standard POS Expression

- Step 1:** Determine the binary value of each sum term in the standard POS expression. This is the binary value that makes the term equal to 0.
- Step 2:** As each sum term is evaluated, place a 0 on the Karnaugh map in the corresponding cell.



**EXAMPLE**


Map the following standard POS expression on a Karnaugh map:

$$(\bar{A} + \bar{B} + C + D)(\bar{A} + B + \bar{C} + \bar{D})(A + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + B + \bar{C} + \bar{D})$$

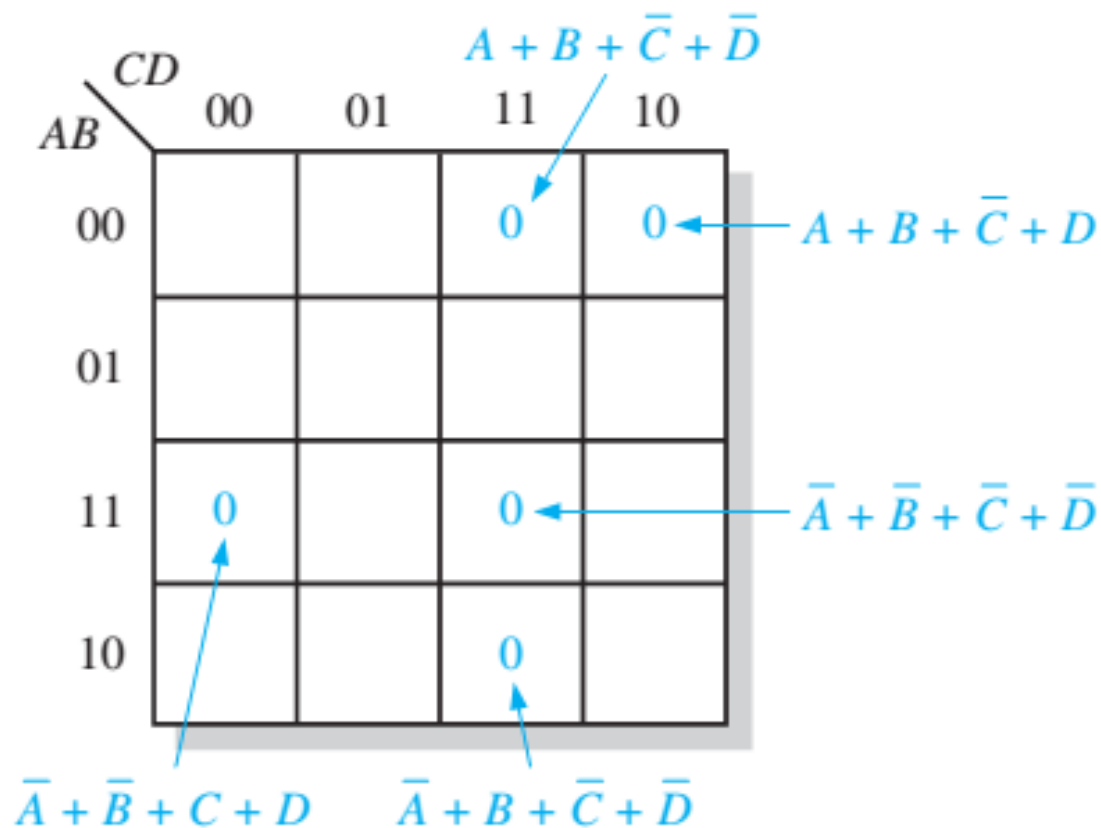**Solution**

Evaluate the expression as shown below and place a 0 on the 4-variable Karnaugh map in Figure 4–44 for each standard sum term in the expression.

$$\begin{array}{cccccc}
 (\bar{A} + \bar{B} + C + D) & (\bar{A} + B + \bar{C} + \bar{D}) & (A + B + \bar{C} + D) & (\bar{A} + \bar{B} + \bar{C} + \bar{D}) & (A + B + \bar{C} + \bar{D}) & \\
 1100 & 1011 & 0010 & 1111 & 0011 & 
 \end{array}$$



# Karnaugh Map Simplification of POS Expressions

## EXAMPLE

Use a Karnaugh map to minimize the following standard POS expression:

$$(A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$$


Also, derive the equivalent SOP expression.

## Solution

The combinations of binary values of the expression are

$$(0 + 0 + 0)(0 + 0 + 1)(0 + 1 + 0)(0 + 1 + 1)(1 + 1 + 0)$$

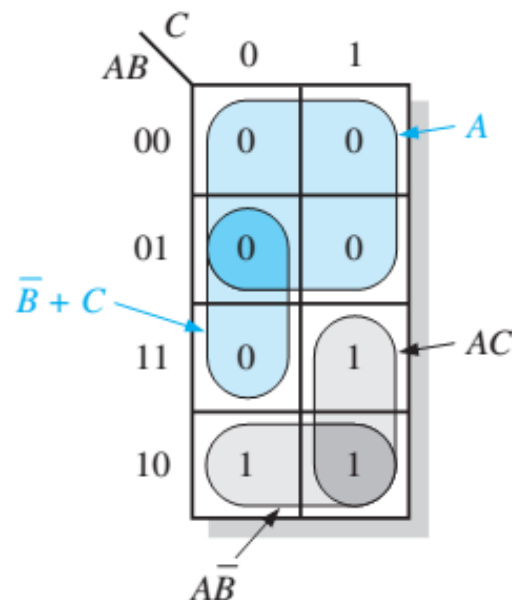Map the standard POS expression and group the cells as shown in Figure



Notice how the 0 in the 110 cell is included into a 2-cell group by utilizing the 0 in the 4-cell group. The sum term for each blue group is shown in the figure and the resulting minimum POS expression is

$$A(\overline{B} + C)$$

Keep in mind that this minimum POS expression is equivalent to the original standard POS expression.

Grouping the 1s as shown by the gray areas yields an SOP expression that is equivalent to grouping the 0s.

$$AC + A\overline{B} = A(\overline{B} + C)$$

**EXAMPLE**

Use a Karnaugh map to minimize the following POS expression:


$$(B + C + D)(A + B + \bar{C} + D)(\bar{A} + B + C + \bar{D})(A + \bar{B} + C + D)(\bar{A} + \bar{B} + C + D)$$

**Solution**

The first term must be expanded into  $\bar{A} + B + C + D$  and  $A + B + C + D$  to get a standard POS expression, which is then mapped; and the cells are grouped as shown in Figure 4-46. The sum term for each group is shown and the resulting minimum POS expression is

$$(C + D)(A + B + D)(\bar{A} + B + C)$$

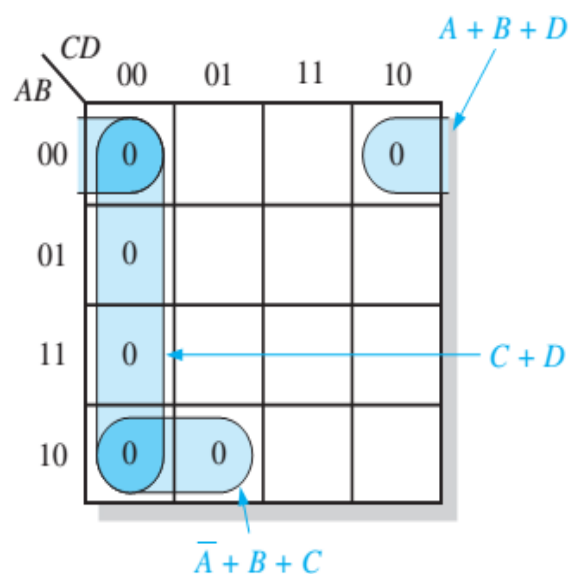Keep in mind that this minimum POS expression is equivalent to the original standard POS expression.





# Converting Between POS and SOP Using the Karnaugh Map


**EXAMPLE**

Using a Karnaugh map, convert the following standard POS expression into a minimum POS expression, a standard SOP expression, and a minimum SOP expression.


$$(\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + B + \bar{C} + D)$$

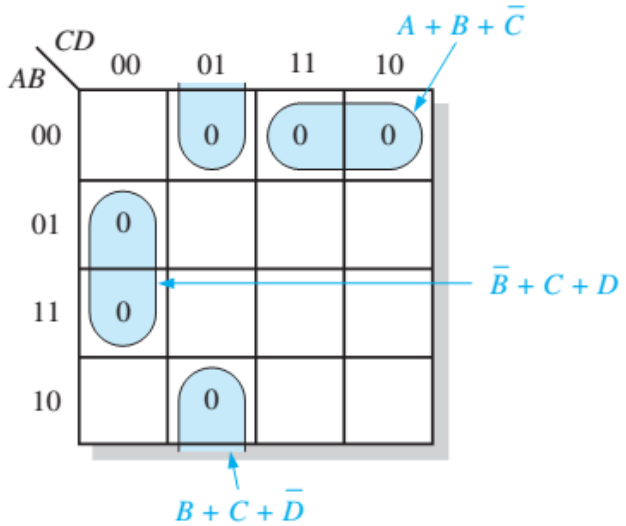**Solution**


The 0s for the standard POS expression are mapped and grouped to obtain the minimum POS expression in Figure (a). In Figure (b), 1s are added to the cells that do not contain 0s. From each cell containing a 1, a standard product term is obtained as indicated. These product terms form the standard SOP expression. In Figure (c), the 1s are grouped and a minimum SOP expression is obtained.



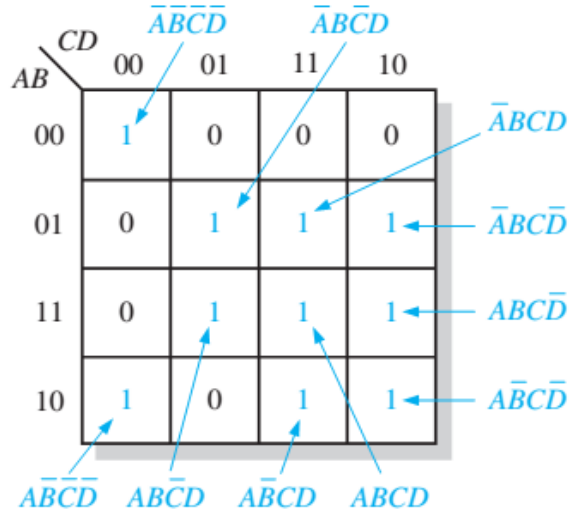(a) Minimum POS:  $(A + B + C)(\bar{B} + \bar{C} + D)(B + C + \bar{D})$



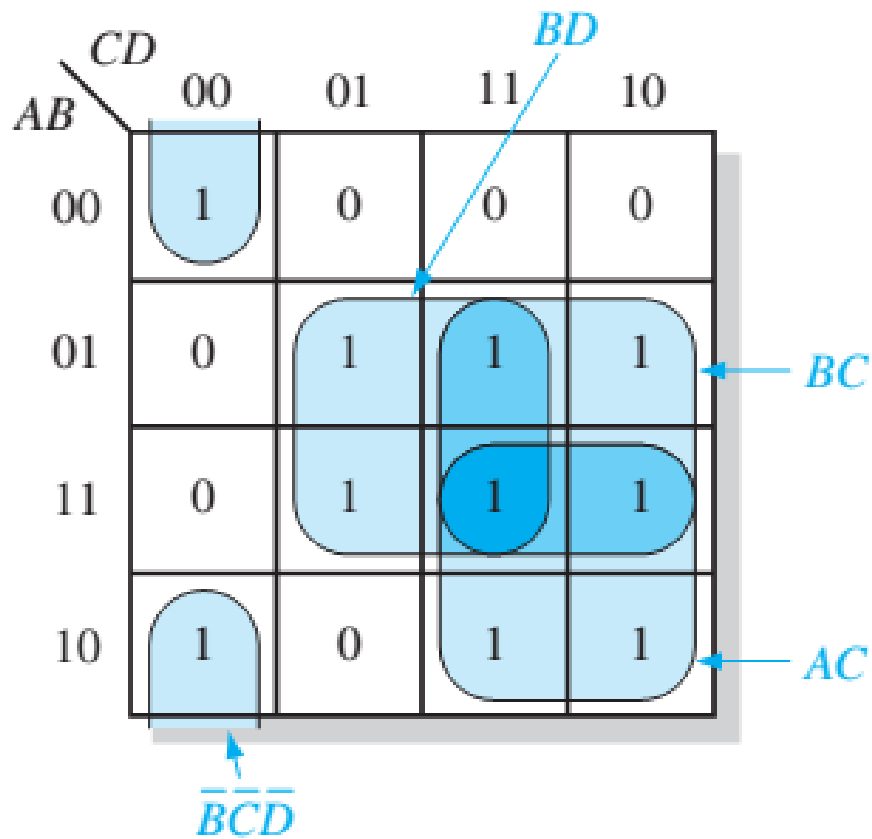(b) Standard SOP:  
 $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$



(c) Minimum SOP:  $AC + BC + BD + \overline{BCD}$

*Thank  
you!*