

Chapter 4


Combinational Logic

4.1 Introduction

- Logic circuits may be *combinational* or *sequential*.
- A *combinational circuit* consists of logic gates whose outputs *at any time* are determined *from only the present combination of inputs*.
 - It performs an operation that can be specified logically by a set of Boolean functions.
- In contrast, *sequential circuits* employ *storage elements* in addition to *logic gates*.
 - Their outputs are a function of the inputs and the state of storage elements.
 - Because the state of the storage elements is a function of previous inputs, the outputs of a sequential circuit *depend not only on present value of inputs*, but *also on past inputs*, and the circuit behavior must be specified by *a time sequence of inputs and internal states*.

 4.2 Combinational Circuits

- A combinational circuit consists of input variables, logic gates, and output variables.
 - n inputs and m outputs
 - Can be specified by truth table
 - Can be described by m Boolean functions




4.3 Analysis Procedure

- The first step in the analysis is to make sure that the given circuit is *combinational* and *not sequential*.
 - The diagram of a combinational circuit has logic gates with no *feedback paths* or *memory elements*.
 - A *feedback path* is a connection from the output of one gate to the input of a second gate that forms part of the input to first gate
- Obtain the output Boolean functions or the truth table

 4.3 Analysis Procedure

- $F_1 = T_2 + T_3$
 - But, $T_3 = F_2' T_1$ and $T_2 = ABC$
- So, $F_1 = ABC + F_2' T_1$
 - $T_1 = A + B + C$ and $F_2 = AB + AC + BC$
- $F_1 = ABC + (A + B + C) (AB + AC + BC)'$
 $= A'BC' + A'B'C + AB'C' + ABC$



4.3 Analysis Procedure

Truth Table

1. Determine the number of input variable in the circuit.
 - For n inputs form the 2^n possible input combinations.
2. Label the outputs of selected gates with arbitrary symbols.
3. Obtain the truth table for the outputs of those gates which are a function of the input variables only.
4. Proceed to obtain the truth table for the outputs of those gates which are a function of previously defined values until the columns for all outputs are determined.

4.3 Analysis Procedure

Truth Table

- Truth table of the previous example

A	B	C	F₂	F'₂	T₁	T₂	T₃	F₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

4.3 Analysis Procedure

4.1 Consider the combinational circuit shown in Fig. P4.1.

 


FIGURE P4.1

- (a)*** Derive the Boolean expressions for T_1 through T_4 . Evaluate the outputs F_1 and F_2 as a function of the four inputs.
- (b)** List the truth table with 16 binary combinations of the four input variables. Then list the binary values for T_1 through T_4 and outputs F_1 and F_2 in the table.
- (c)** Plot the output Boolean functions obtained in part (b) on maps and show that the simplified Boolean expressions are equivalent to the ones obtained in part (a).

4.3 Analysis Procedure

4.2* Obtain the simplified Boolean expressions for output F and G in terms of the input variables in the circuit of Fig. P4.2.

 


FIGURE P4.2

4.4 Design Procedure

- The design of combinational circuits starts from the specification of the design objective and culminates in a logic circuit diagram or a set of Boolean function from which the logic diagram can be obtained.
- The procedure involves the following steps:
 1. Determine the required number of inputs and outputs
 2. Derive the truth table
 3. Obtain the simplified Boolean functions
 4. Draw the logic diagram

4.4 Design Procedure

Code Conversion Example

- Convert binary coded decimal (BCD) to the excess-3 code for the decimal digits?
- *Solution:*
- Four bits to represent a decimal digit:
 - Four input binary variables by the symbols A , B , C , and D
 - Four output variables by W , X , Y , and Z
- Remember, four binary variables may have 16 bit combinations, but only 10 are listed in the truth table.
 - The six bit combinations not listed for the input variables are *don't-care combinations*.

4.4 Design Procedure

Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

4.4 Design Procedure

Code Conversion Example

AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3	m_2 1
	01	m_4 1	m_5	m_7	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9	m_{11} X	m_{10} X

D
 $z = D'$

AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3 1	m_2
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9	m_{11} X	m_{10} X

D
 $y = CD + C'D'$

4.4 Design Procedure

Code Conversion Example

		C			
		00	01	11	10
A	00	m_0	m_1 1	m_3 1	m_2 1
	01	m_4 1	m_5	m_7	m_6
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8	m_9 1	m_{11} X	m_{10} X


$$x = B'C + B'D + BC'D'$$

		C			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9 1	m_{11} X	m_{10} X

$$w = A + BC + BD$$


4.4 Design Procedure

Code Conversion Example

 

4.4 Design Procedure

 - 4.4** Design a combinational circuit with three inputs and one output.
(a) The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.
(b) The output is 1 when the binary value of the inputs is an odd number.
- 4.5** Design a combinational circuit with three inputs, x , y , and z , and three outputs, A , B , and C . When the binary input is 0, 1, 2, or 3, the binary output is two greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is three less than the input.
- 4.9** An ABCD-to-seven-segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in an indicator used to display the decimal digit in a familiar form. The seven outputs of the decoder (a , b , c , d , e , f , g) select the corresponding segments in the display, as shown in Fig. P4.9(a). The numeric display chosen to represent the decimal digit is shown in Fig. P4.9(b). Using a truth table and Karnaugh maps, design the BCD-to-seven-segment decoder, using a minimum number of gates. The six invalid combinations should result in a blank display.



(a) Segment designation



(b) Numerical designation for display

FIGURE P4.9


4.5 Binary Adder-Subtractor

- Digital computers perform a variety of information processing tasks.
 - The most basic arithmetic operation is the *addition of two binary digits*
- A combinational circuit that performs the addition of two bits is called a *half adder*
 - The one that performs the addition of three bits (*two significant bits and a previous carry*) is a *full adder*
 - Two half adders can be employed to implement a full adder
- A *binary adder-subtractor* is a combinational circuit that performs the arithmetic operation of *addition and subtraction* with *binary numbers*.

 4.5 Binary Adder-Subtractor

Half Adder


- $S = x'y + xy'$
- $S = x \oplus y$
- $C = xy$



(a) $S = xy' + x'y$
 $C = xy$

Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

(b) $S = x \oplus y$
 $C = xy$

4.5 Binary Adder-Subtractor

Full Adder

- $S = x'y'z + x'yz' + xy'z' + xyz$

$$S = x \oplus y \oplus z$$

- $C = xy + xz + yz$

Full Adder



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

4.5 Binary Adder-Subtractor

Full Adder

	yz		y	
x	00	01	11	10
0	m_0	1	m_3	m_2
1	m_4	m_5	m_7	m_6
			z	

	yz		y	
x	00	01	11	10
0	m_0	m_1	1	m_2
1	m_4	1	1	1
			z	

  


4.5 Binary Adder-Subtractor

Full Adder

- Implement with 2 *half adder* and 1 *OR*
- From the original function:
 
$$C = xy'z + x'yz + xyz + xyz'$$
$$= z(xy' + x'y) + xy(z + z') = z(x \oplus y) + xy$$



4.5 Binary Adder-Subtractor


Binary Adder

- A digital circuit that produces the arithmetic sum of two binary numbers.
- It can be constructed with *full adders* connected in cascade,
 - The output carry from each full adder connected to the input carry of the next full adder in the chain.

 4.5 Binary Adder-Subtractor

Binary Adder

- A four full-adder circuits to provide a four-bit binary ripple carry adder.
 - The augend's bits of A and the addend bits B are designated by subscript numbers from right to left, with subscript 0 denoting the least significant bit.



4.5 Binary Adder-Subtractor

Binary Adder

- Consider the two binary numbers $A= 1011$ and $B= 0011$.
- Their sum $S= 1110$ is formed with the four-bit adder as follows:

Subscript i :	3 2 1 0	
Input carry	0 1 1 0	C_i
Augend	1 0 1 1	A_i
<u>Addend</u>	<u>0 0 1 1</u>	B_i
Sum	1 1 1 0	S_i
Output carry	0 0 1 1	C_{i+1}

4.5 Binary Adder-Subtractor


Carry Propagation

- The addition of two binary numbers in parallel implies that all the bits of the augend and addend are available for *computation at the same time*.
- *As in any combinational circuit*, the signal must propagate through the gates before the correct *output sum* is available in the output terminals.
- The total *propagation time* is equal to the propagation delay of a typical gate, times the number of gate levels in the circuit.
- The longest propagation delay time in an adder is the time it takes the carry to propagate through the full adder.
- Since each bit of the sum output depends on the value of the input carry, the value of S_i at any given stage in the adder will be in its *steady-state final value only after the input carry to that stage has been propagated*.

 4.5 Binary Adder-Subtractor

Carry Propagation

- The signal from the input carry C_i to the output carry C_{i+1} propagates through an AND gate and an OR gate, which constitute two gate levels.
 - If there are four full adder, the output carry C_4 would have $2 * 4 = 8$ gate level from C_0 to C_4 .
- For an n -bit adder, there are $2n$ gate levels for the carry to propagate from input to output.




4.5 Binary Adder-Subtractor

Carry Propagation

- There are several techniques for reducing the carry propagation time in parallel adder.
- The most widely used technique employs the principle of *carry look-ahead logic*.
- Let $P_i = A_i \oplus B_i$, and $G_i = A_i B_i$
Then $S_i = P_i \oplus C_i$, and $C_{i+1} = G_i + P_i C_i$
 - G_i is called a *carry generate*
 - P_i is called a *carry propagate*
- $C_0 =$ input carry
- $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$
- $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
- Since the Boolean function for each output carry is expressed in sum-of-product form, each function can be implemented with one level of AND gates followed by an OR gate.


4.5 Binary Adder-Subtractor

Carry Propagation – carry look-ahead

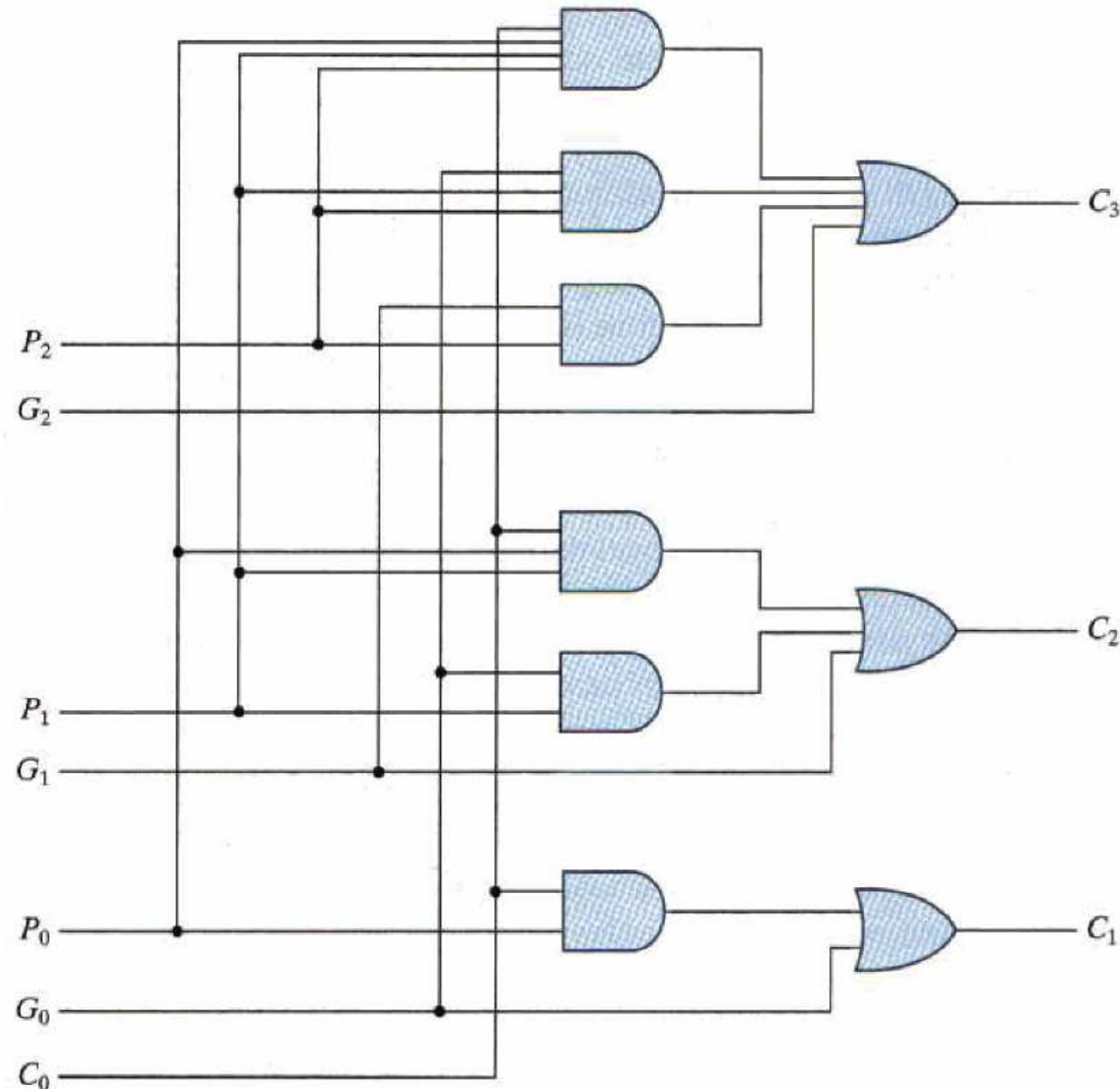

4.5 Binary Adder-Subtractor

Binary Adder with Carry Lookahead

 


4.5 Binary Adder-Subtractor

Binary Subtractor

- The subtraction $A - B$ can be done by taking the 2's complement of B and adding it to A .
 - Take the 1's complement
 - Add 1 to the least significant pair of bits
- 1's complement can be implemented with *XORs*
- A 1 can be added to the sum through the *input carry*
- The *addition* and *subtraction* operations can be combined into one circuit
- The mode input M controls the operation:
 - When $M = 0$, the circuit is an adder ($B \oplus 0 = B, C_0 = 0$)
 - When $M = 1$, the circuit is a subtractor ($B \oplus 1 = B', C_0 = 1$)

4.5 Binary Adder-Subtractor

Binary Subtractor

 

4.5 Binary Adder-Subtractor

Overflow

- When two numbers with n digits each are added and the sum is a number occupying $n+1$ digits, we say that an *overflow* occurred.
 - Overflow is a problem in digital computers
 - $n+1$ bits cannot be accommodated by an n -bit word
- 1. For *unsigned numbers*, an overflow is detected from the *end carry out of the most significant position* (C_{n+1}).
- 2. For *signed numbers*, an overflow cannot occur after an addition if one number is positive and the other is negative (V).

4.5 Binary Adder-Subtractor

Overflow – Signed Numbers

- An overflow may occur if the two numbers added are both positive or both negative, but the result is an opposite sign
- An overflow can be detected by observing *the carry into the sign bit position* and *the carry out of the sign bit position*.
 - See the output variable $V = C_3 \oplus C_4$ in the previous diagram for four-bit adder-subtractor.

carries:	0	1	
+70	0	1000110	
+80	0	1010000	
<u>+150</u>	1	0010110	

carries:	1	0
-70	1	0111010
-80	1	0110000
<u>-150</u>	0	1101010

4.6 Decimal Adder

BCD adder

- Suppose we apply two BCD digits to a four-bit binary adder:
 - The adder will form the sum in binary
 - It will produce a result that ranges from 0 through 19 (9 + 9 + 1 carry).
- The output sum of two decimal digits must be represented in BCD
- Problem: find a rule by which the binary sum is converted to the correct BCD digit representation of the number in the BCD sum?

4.6 Decimal Adder

BCD adder

K	Binary Sum				C	BCD Sum				Decimal
	Z ₈	Z ₄	Z ₂	Z ₁		S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

4.6 Decimal Adder

BCD adder

- When carry occurs, the addition of **0110** (**6**) to the binary sum converts it to the correct BCD representation.

- From truth table, output carry:


$$C = K + Z_8Z_4 + Z_8Z_2$$

- When $C = 1$, binary 0110 is added to the binary sum through the bottom four-bit adder

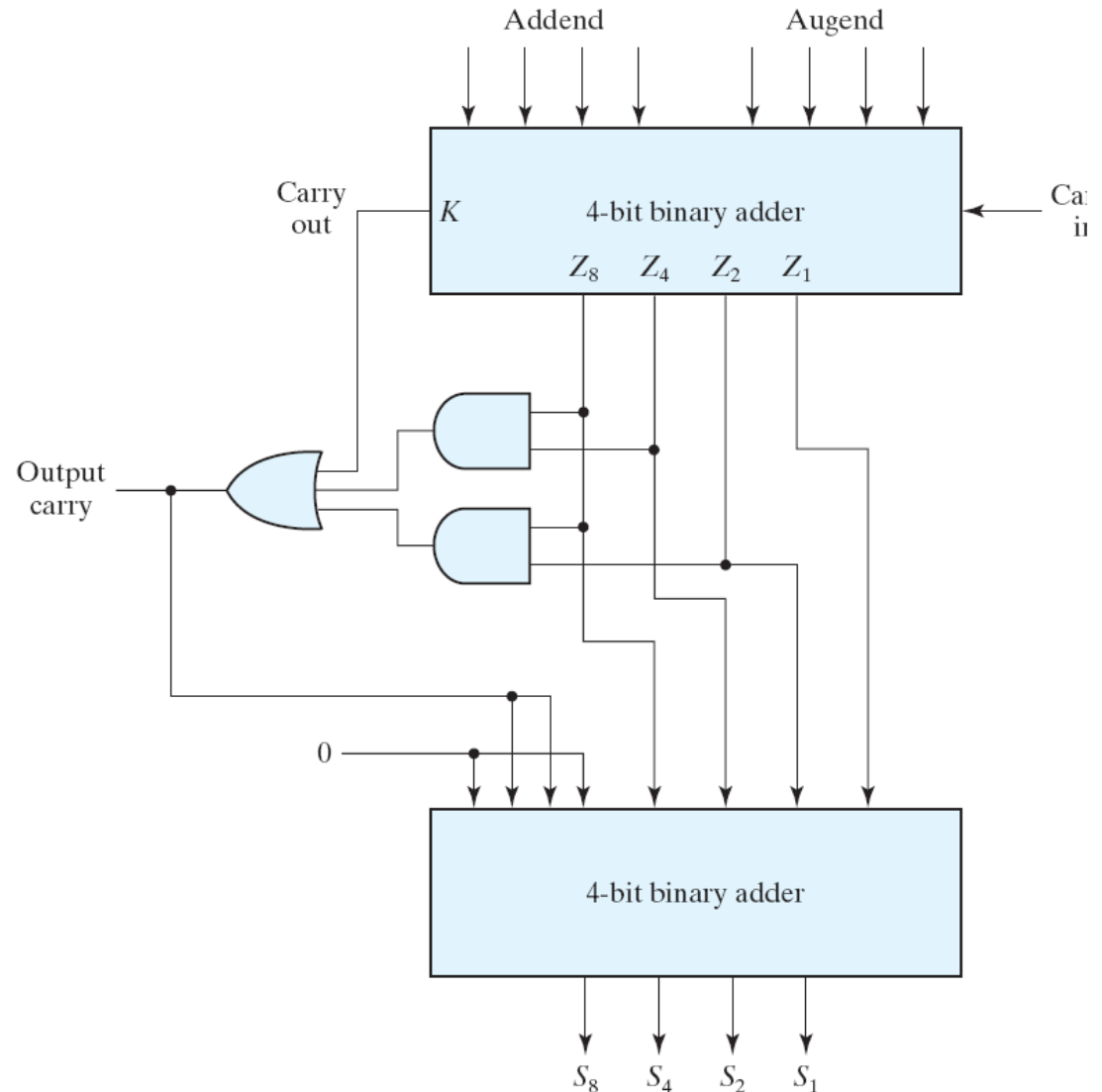4.6 Decimal Adder

BCD adder

- When $C = 1$, binary **0110** is added to the binary sum through the bottom four-bit adder




4.7 Binary Multiplier

- Binary multiplication is performed as decimal multiplication

Multiplicand	B_1	B_0		
Multiplier	A_1	A_0		
	A_0B_1	A_0B_0		
	A_1B_1	A_1B_0		
	C_3	C_2	C_1	C_0

- The product is $C_3C_2C_1C_0$

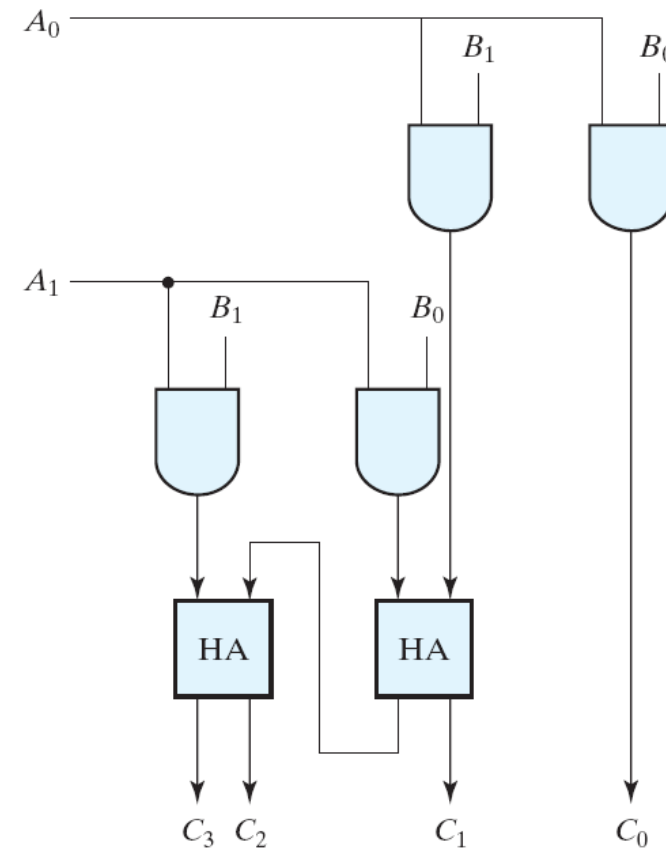


4.7 Binary Multiplier

- Multiplicand: $B_3 B_2 B_1 B_0$
- Multiplier: $\times \underline{A_2 A_1 A_0}$
- Adder 1: $A_0 B_3 A_0 B_2 A_0 B_1 A_0 B_0$
 $A_1 B_3 A_1 B_2 A_1 B_1 A_1 B_0$
- Adder 2: $A_2 B_3 A_2 B_2 A_2 B_1 A_2 B_0$
- The result will be (4×3) bits
 - We need (4×3) AND gates and two four-bit adders to produce a product of seven bits.

4.7 Binary Multiplier

- Four-bit by three-bit binary Multiplier

$$B_3B_2B_1B_0 \times A_2A_1A_0$$

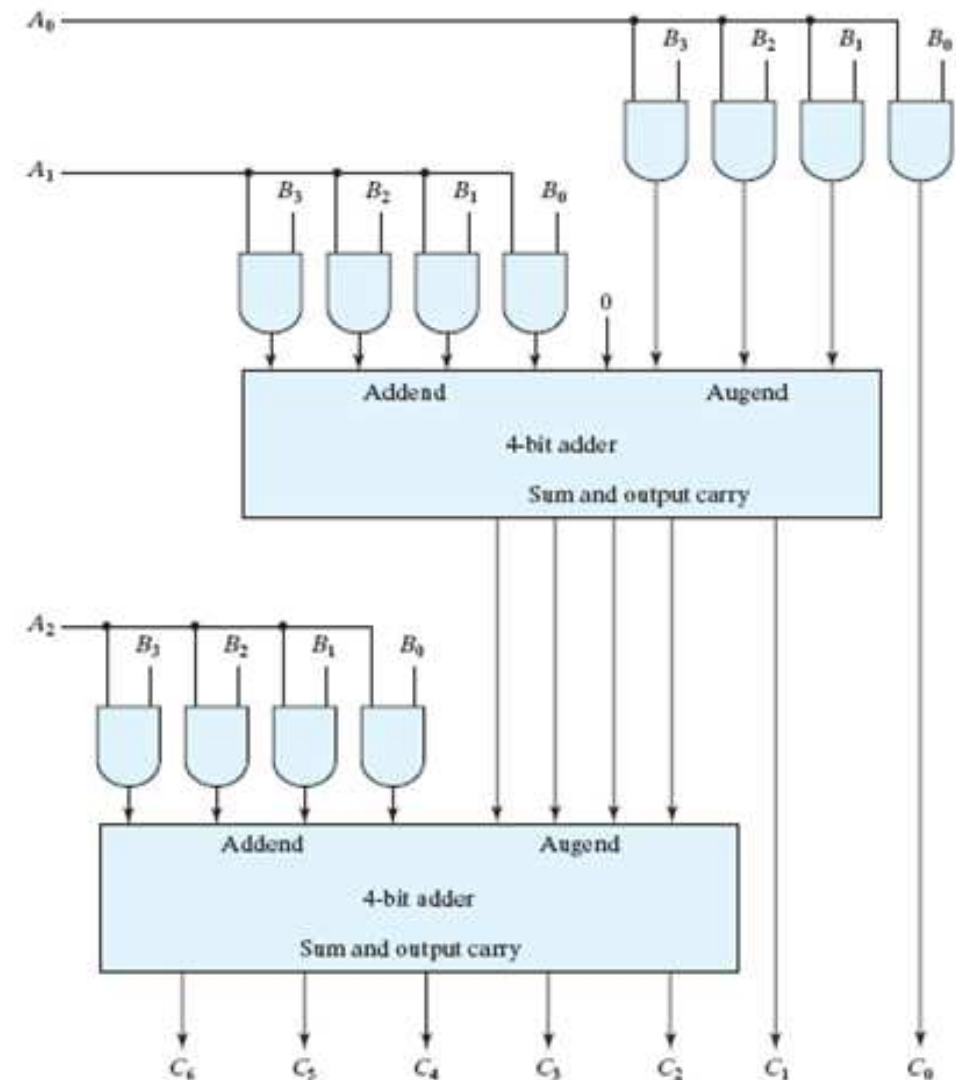

4.8 Magnitude Comparator

- The comparison of two numbers is an operation that determines whether one number is *greater than*, *less than* or *equal* to the other number.
- The circuit for comparing two *n-bit* numbers has 2^{2n} entries in the truth table
- Consider two numbers, *A* and *B*, with four bits each:
$$A = A_3 A_2 A_1 A_0$$
$$B = B_3 B_2 B_1 B_0$$
 - When the numbers are binary, the digits are either 1 or 0


4.8 Magnitude Comparator

- The two numbers are equal if: $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$, and $A_0 = B_0$
 - expressed logically with an exclusive-NOR
- To determine whether A is *greater* or *less* than B , compare the next lower significant pair of digits
- So, let $x_i = (A_i \oplus B_i)' = A_i B_i + A_i' B_i'$, for $i = 0, 1, 2, 3$

Then:

1. $(A = B) = x_3 x_2 x_1 x_0$
2. $(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$
3. $(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$

4.8 Magnitude Comparator

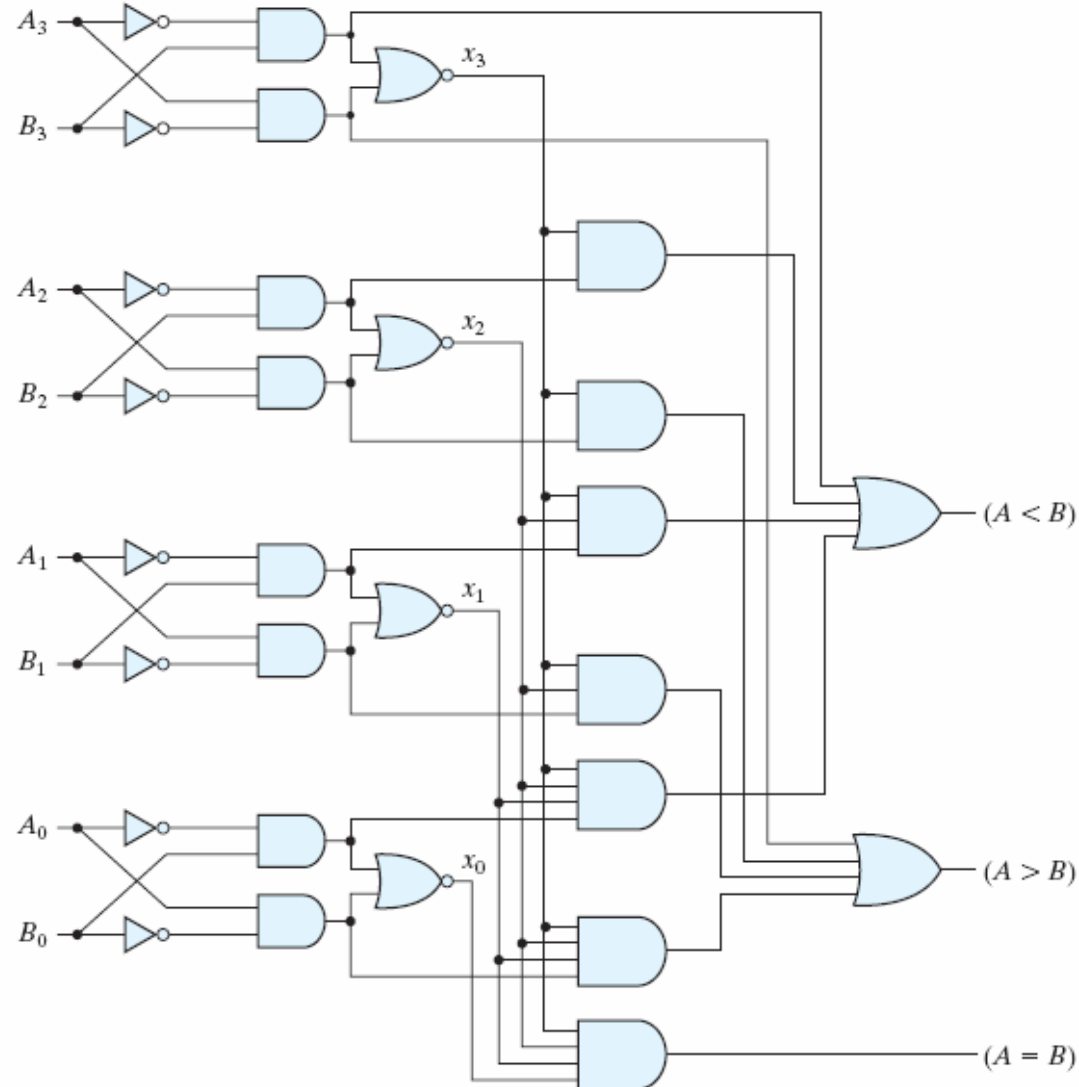

4.9 Decoders


- A combinational circuit that *converts* binary information from n input lines to a maximum of 2^n unique output lines

Truth Table of a Three-to-Eight-Line Decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 4.9 Decoders


- The three inputs are decoded into eight outputs
 - Each representing one of the minterms of the three input variables
- The input variables represents a binary number



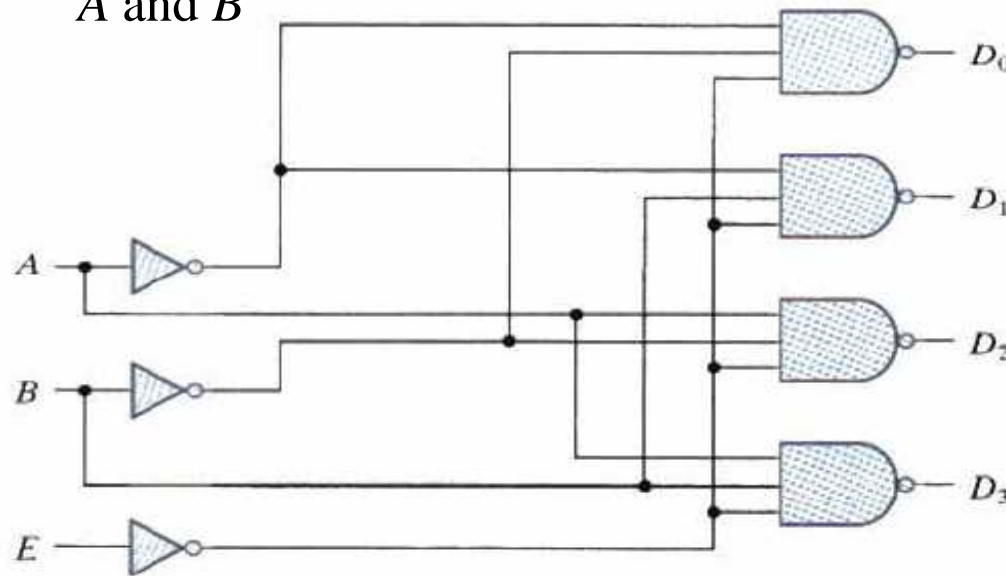4.9 Decoders

Two-to-four-line Decoder with Enable Input

- Some decoders are constructed with NAND gates
- Some also include one *or* more *enable* inputs to control the circuit operation
 - It operates with complemented outputs and a complemented enable
 - The circuit is disabled when E is equal to 1, regardless of the values of the other two inputs
 - The output whose value is equal to 0 represents the minterm selected by inputs A and B




(a) Logic diagram

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

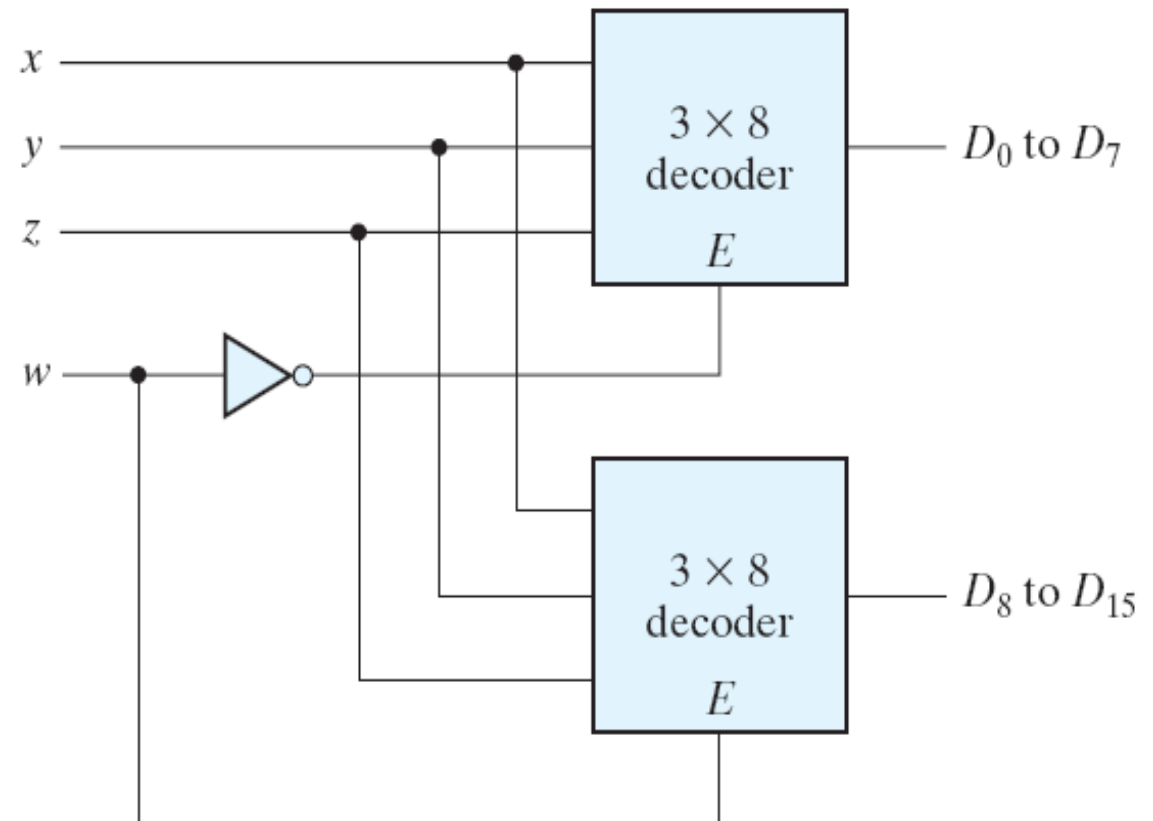4.9 Decoders

- Decoders with enable inputs can be connected together to form a larger decoder circuit
- A 4×16 decoder can be constructed with two 3×8 decoder with enable
 - When $w = 0$, the top decoder is enabled
 - When $w = 1$, the enable conditions are reversed



4.9 Decoders


Combinational Logic Implementation

- A decoder provides the 2^n minterms of n input variables
- Any Boolean function can be expressed in *sum-of-minterms* form
- A decoder together with an external OR gate that forms their logical sum, provides a hardware implementation of the function
 - The inputs to each OR gate are selected from the decoder outputs according to the list of minterms of each function

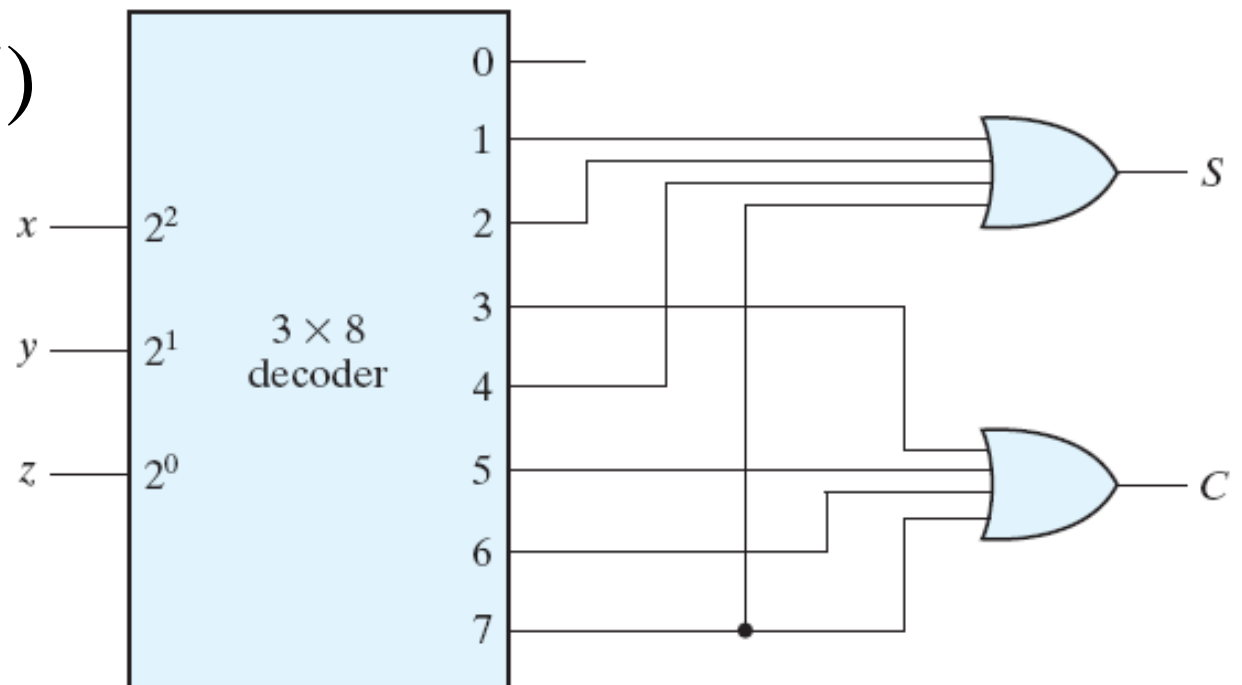4.9 Decoders

Combinational Logic Implementation

- Implementation of a full adder with a 3×8 decoder.
- $S = \Sigma(1, 2, 4, 7)$
- $C = \Sigma(3, 5, 6, 7)$



4.9 Decoders

- 4.25** Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder. Use block diagrams for the components. (HDL—see Problem 4.63.)
- 4.26** Construct a 4-to-16-line decoder with five 2-to-4-line decoders with enable.
- 4.27** A combinational circuit is specified by the following three Boolean functions:

$$F_1(A, B, C) = \Sigma(1, 4, 6)$$

$$F_2(A, B, C) = \Sigma(3, 5)$$

$$F_3(A, B, C) = \Sigma(2, 4, 6, 7)$$

Implement the circuit with a decoder constructed with NAND gates (similar to Fig. 4.19) and NAND or AND gates connected to the decoder outputs. Use a block diagram for the decoder. Minimize the number of inputs in the external gates.

- 4.28** Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions:

(a) $F_1 = x'yz' + xz$

$$F_2 = xy'z' + x'y$$

$$F_3 = x'y'z' + xy$$

(b) $F_1 = (y' + x)z$

$$F_2 = y'z' + x'y + yz'$$

$$F_3 = (x + y)z$$

- Given a three-input Boolean function $F(A, B, C) = \Sigma m(0, 2, 4, 6, 7) + \Sigma d(1)$. Implement the function using a minimal number of **2-to-4 with enable decoders and a NOR gate**

4.10 Encoders

- A digital circuit that performs the *inverse operation of a decoder*
 - An encoder has 2^n (or fewer) input lines and n output lines
- The output lines, generates the binary code corresponding to the input value
- It can be implemented with OR gates
 - Their inputs are determined directly from the truth table

4.10 Encoders

Octal-to-Binary Encoder

- The encoder defined above has the limitation that only one input can be active at any given time.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

4.10 Encoders

- An encoder circuit that includes the priority function
- The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.

4.10 Encoders

Four-input Priority Encoder



- Output variable V indicates whether a *valid input occurs*.
- It can be seen that the input variable D_3 is with the highest priority.

Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

4.10 Encoders


Four-input Priority Encoder

  

 4.10 Encoders


Four-input Priority Encoder

- $V = D_0 + D_1 + D_2 + D_3$
- $x = D_2 + D_3$
- $y = D_3 + D_1 D_2'$




 4.11 Multiplexers

- A combinational circuit that selects binary information from *one of many input lines* and directs it to a *single output line*
- The selection of a particular input line is controlled by a set of *selection lines*
 - 2^n input lines and n selection lines whose bit combinations determine which input is selected



(a) Logic diagram

 


(b) Block diagram

4.11 Multiplexers

Four-to-one-line multiplexer

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

 


(a) Logic diagram

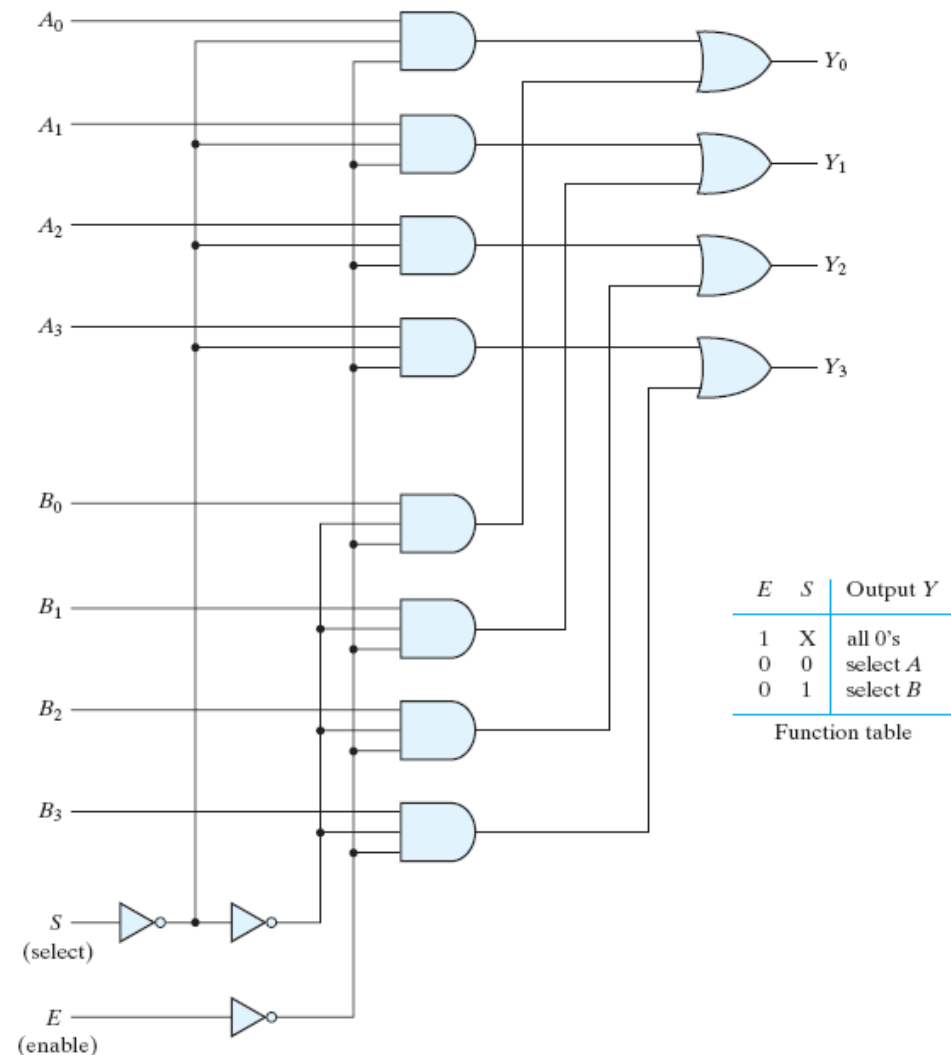4.11 Multiplexers

Quadruple 2-to-1-line multiplexer

- Multiplexer circuits can be combined with common selection inputs to provide multiple-bit selection logic.
- Select 4 bits



4.11 Multiplexers

Boolean Function Implementation

- The minterms of a function are generated in a multiplexer by the circuit associated with the selection inputs
 - The individual minterms can be selected by the data input
- A Boolean function of n variables can be implemented with a multiplexer that has $n-1$ selection input
 - The first $n-1$ variables of the function are connected to the selection inputs of the multiplexer
 - The remaining single variable of the function is used for the data input


4.11 Multiplexers

Boolean Function Implementation

- Consider the Boolean function $F(x, y, z) = \sum(1,2,6,7)$
 - It can be implemented with a four-to-one-line multiplexer using x and y at the select lines

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

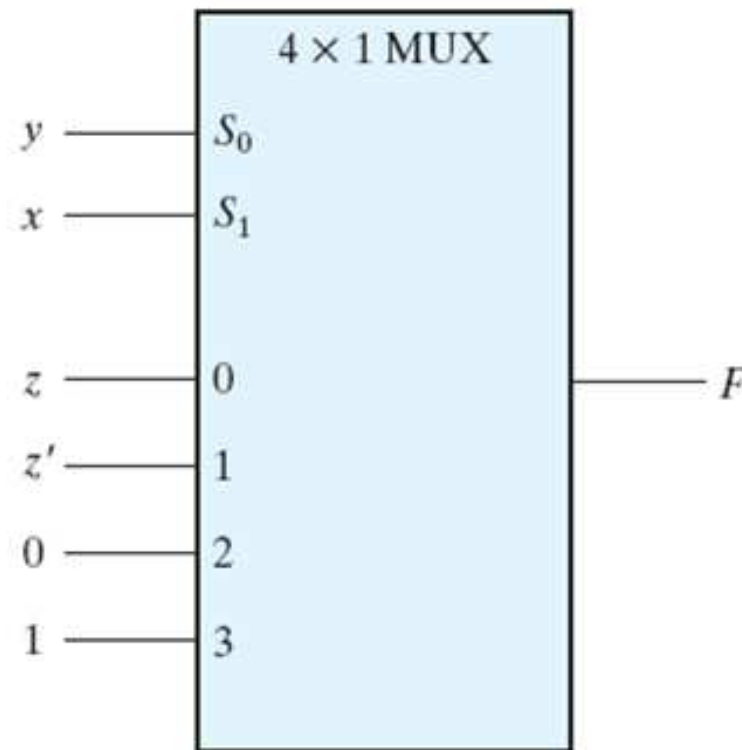


(b) Multiplexer implementation

4.11 Multiplexers

Boolean Function Implementation

- Consider the Boolean function $F(x, y, z) = \sum(1, 2, 6, 7)$
 - Another solution method using x and y at the select lines


	I_0	I_1	I_2	I_3
x'	0	1	2	3
x	4	5	6	7
	0	x'	1	x

 

 4.11 Multiplexers

Boolean Function Implementation

- Consider the Boolean function $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ using inputs A, B and C at the select line



A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

4.11 Multiplexers


Boolean Function Implementation

- Consider the Boolean function
 $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$
using inputs B, C and D at the select lines

	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	0	A'	0	1	1	A	A	A

4.11 Multiplexers

Boolean Function Implementation

 


4.11 Multiplexers

Boolean Function Implementation

- Consider the Boolean function $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ using inputs A and C at the select lines, while inputs B and D at the input lines
 - It can be implemented with a four-to-one-line multiplexer
- $I_0 = B'D + BD'$ $I_1 = B'D$
- $I_2 = B$ $I_3 = B + D$

CD \ AB	00	01	11	10
00		1	1	
01	1			
11	1	1	1	1
10			1	

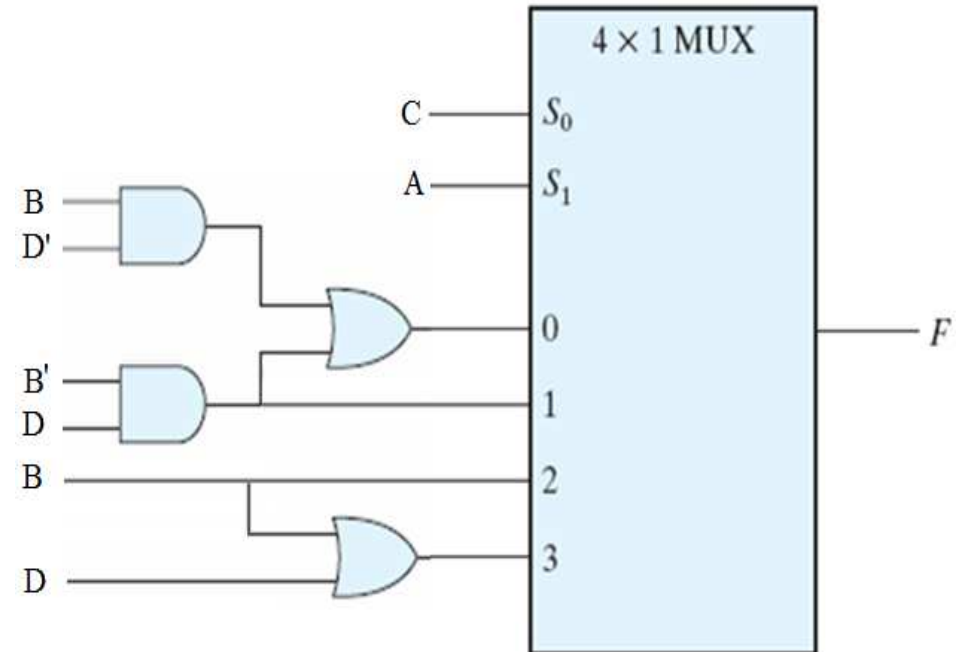

4.11 Multiplexers

Boolean Function Implementation

4.31 Construct a 16×1 multiplexer with two 8×1 and one 2×1 multiplexers. Use block diagrams.

4.32 Implement the following Boolean function with a multiplexer

(a) $F(A, B, C, D) = \Sigma(0, 2, 5, 7, 11, 14)$

(b) $F(A, B, C, D) = \Pi(3, 8, 12)$

4.33 Implement a full adder with two 4×1 multiplexers.

4.34 An 8×1 multiplexer has inputs A , B , and C connected to the selection inputs S_2 , S_1 , and S_0 , respectively. The data inputs I_0 through I_7 are as follows:

(a)* $I_1 = I_2 = I_7 = 0$; $I_3 = I_5 = 1$; $I_0 = I_4 = D$; and $I_6 = D'$.

(b) $I_1 = I_2 = 0$; $I_3 = I_7 = 1$; $I_4 = I_5 = D$; and $I_0 = I_6 = D'$.

Determine the Boolean function that the multiplexer implements.

4.35 Implement the following Boolean function with a 4×1 multiplexer and external gates.

(a)* $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$

(b) $F(A, B, C, D) = \Sigma(1, 2, 4, 7, 8, 9, 10, 11, 13, 15)$

Connect inputs A and B to the selection lines. The input requirements for the four data lines will be a function of variables C and D . These values are obtained by expressing F as a function of C and D for each of the four cases when $AB = 00, 01, 10$, and 11 . The functions may have to be implemented with external gates and with connections to power and ground.

- Design a **full adder** with a minimal number of **2-to-1 multiplexers (Do not use any other gate)**.

4.11 Multiplexers

Three-State Gates

