

Power electronics lab



# Three phase Uncontrolled rectifier

Eng :Eman Abu Hany


# Three phase uncontrolled rectifier

- 1- the uncontrolled Three - pulse  
Mid – point circuit M3U
- 2- the uncontrolled Six - pulse  
Bridge circuit B6U

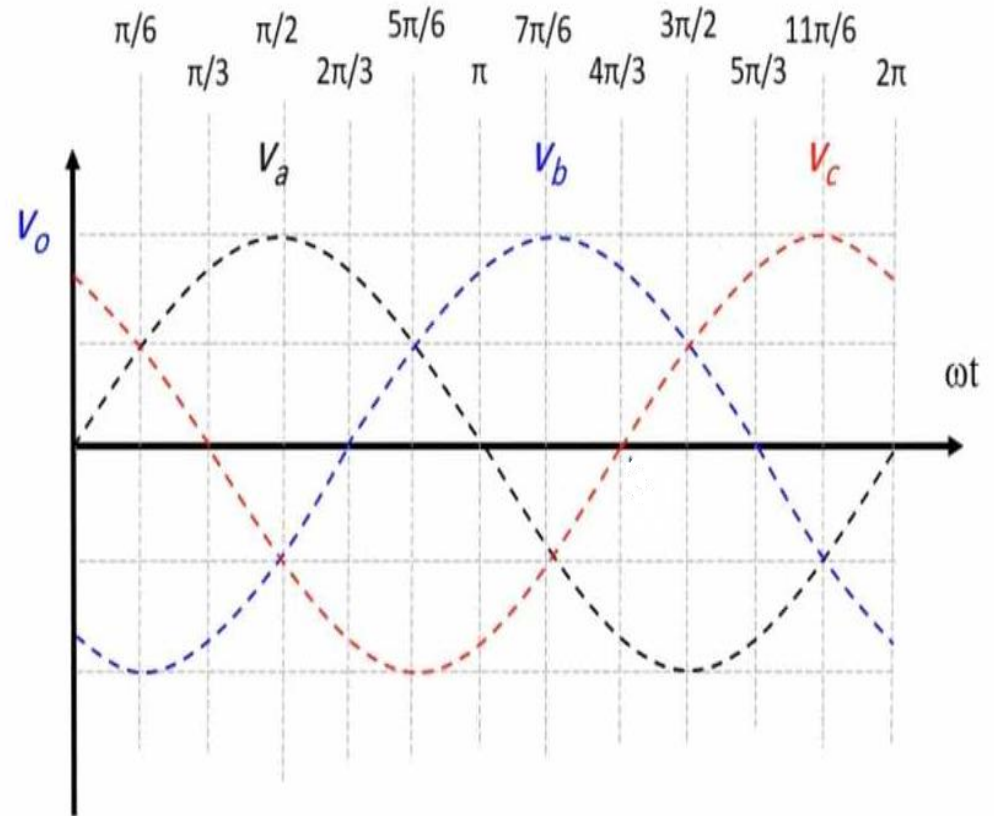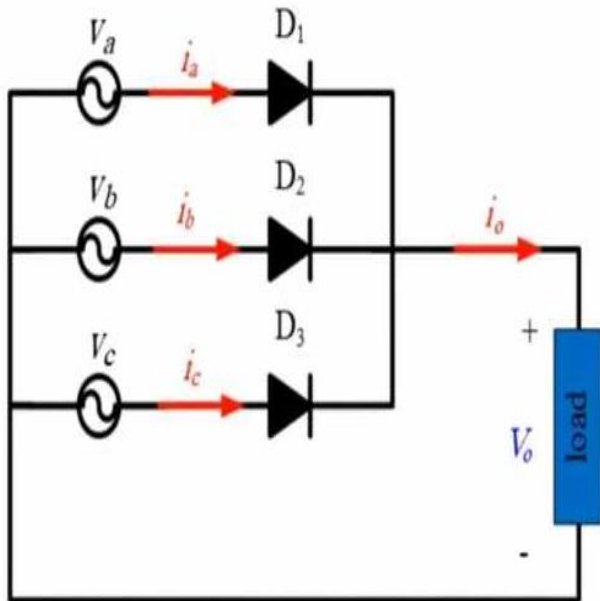
# Three-phase Half-wave Uncontrolled Rectifier



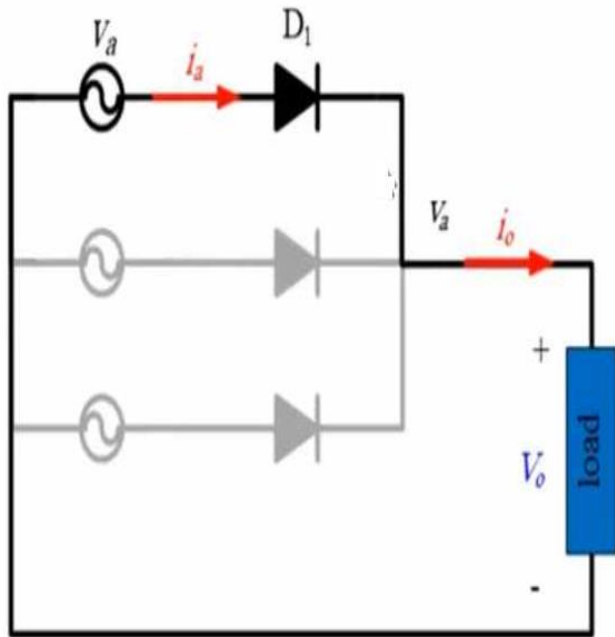
# Three-phase Half-wave Uncontrolled Rectifier




$$\pi/6 \leq \omega t \leq 5\pi/6$$

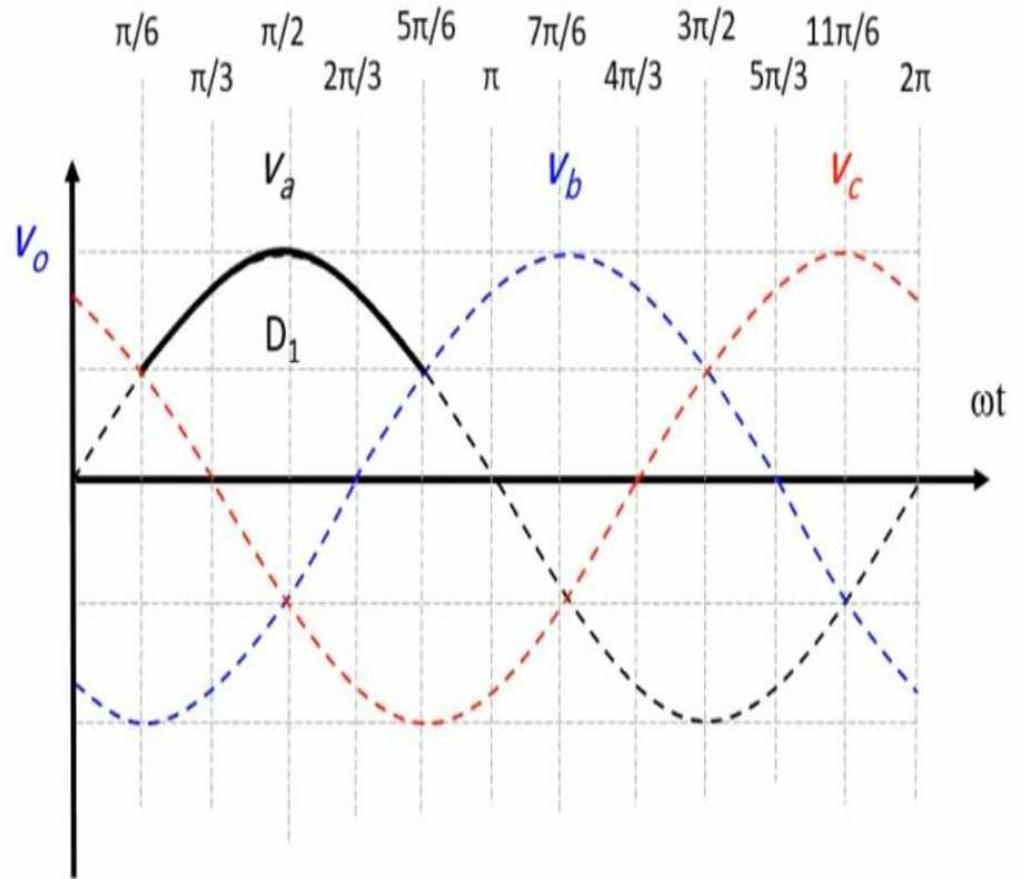

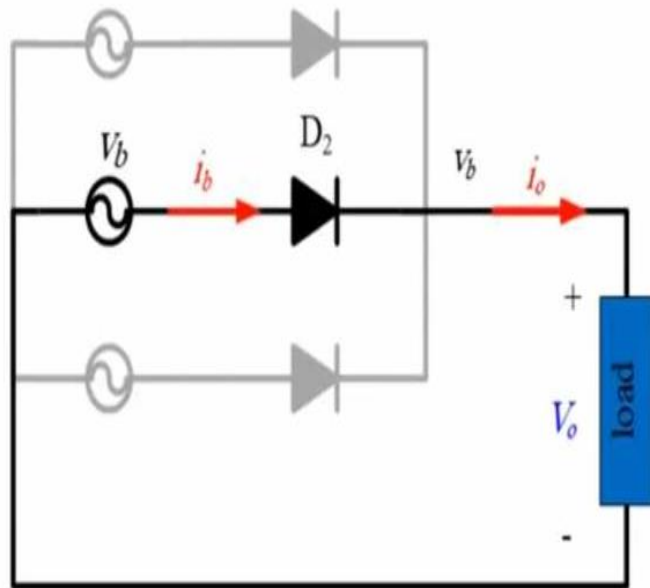
# Three-phase Half-wave Uncontrolled Rectifier




$$5\pi/6 \leq \omega t \leq 3\pi/2$$

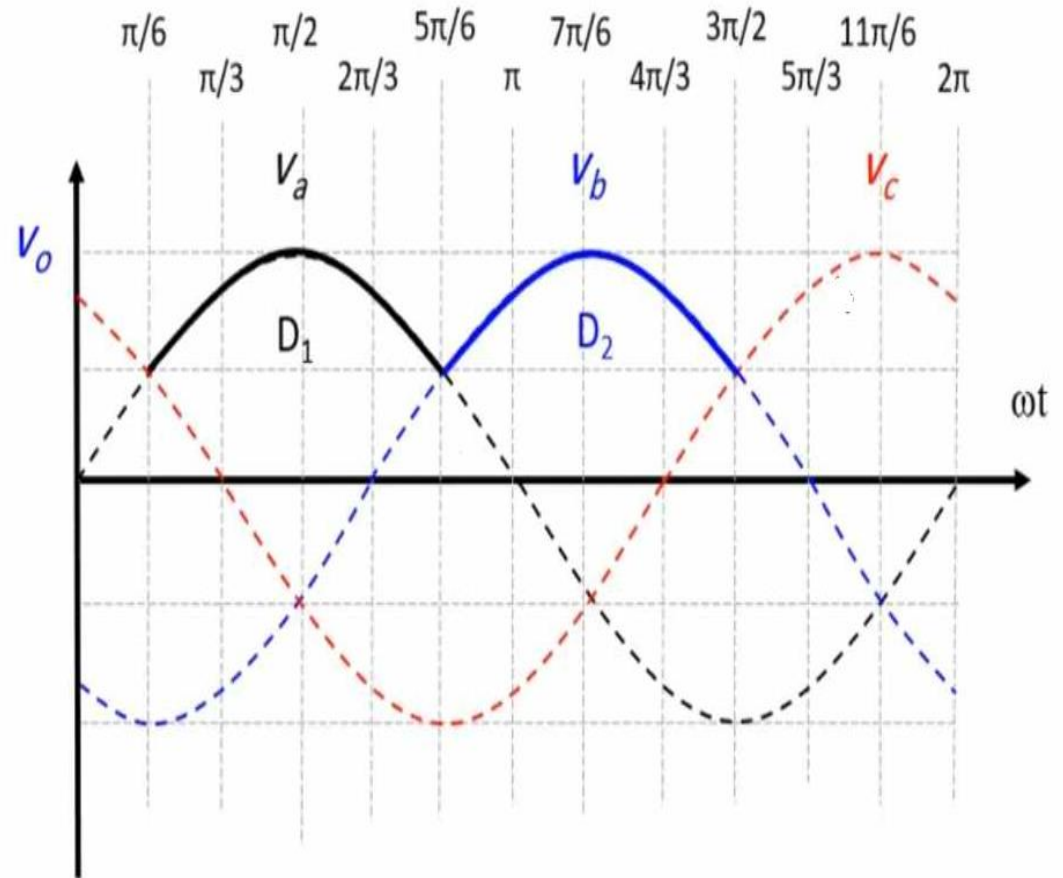


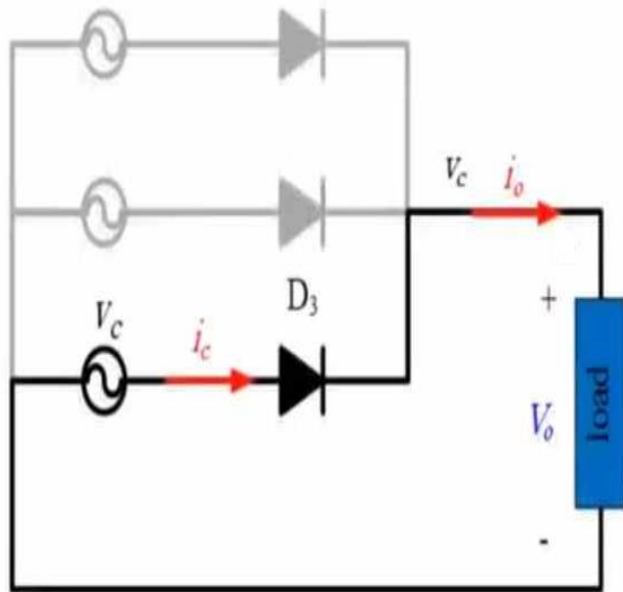
# Three-phase Half-wave Uncontrolled Rectifier




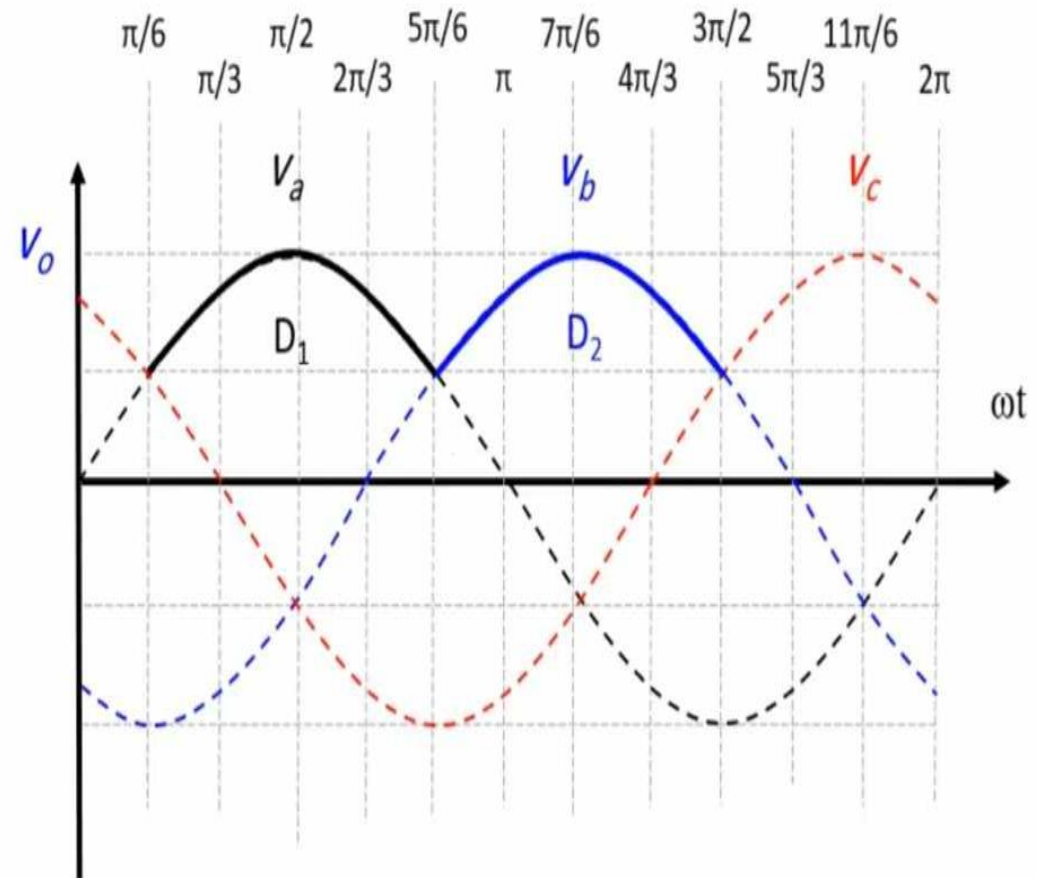
$$3\frac{\pi}{2} \leq \omega t \leq 2\pi + \frac{\pi}{6}$$


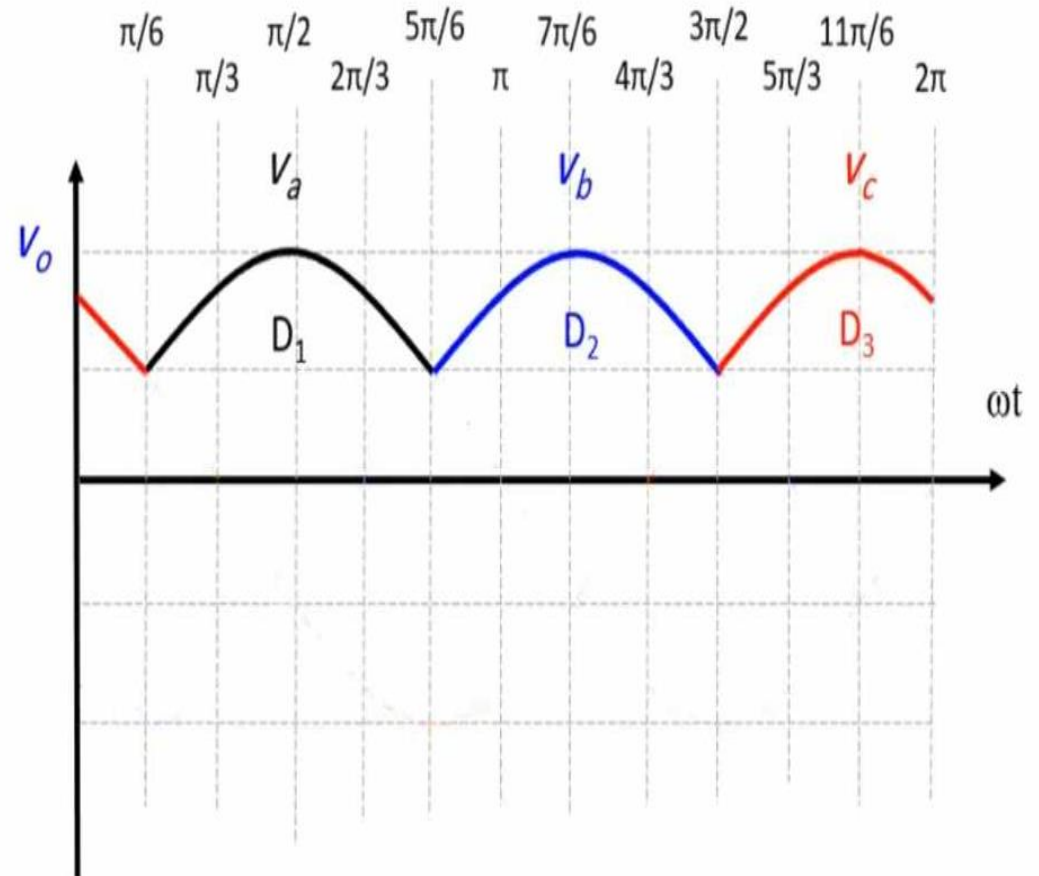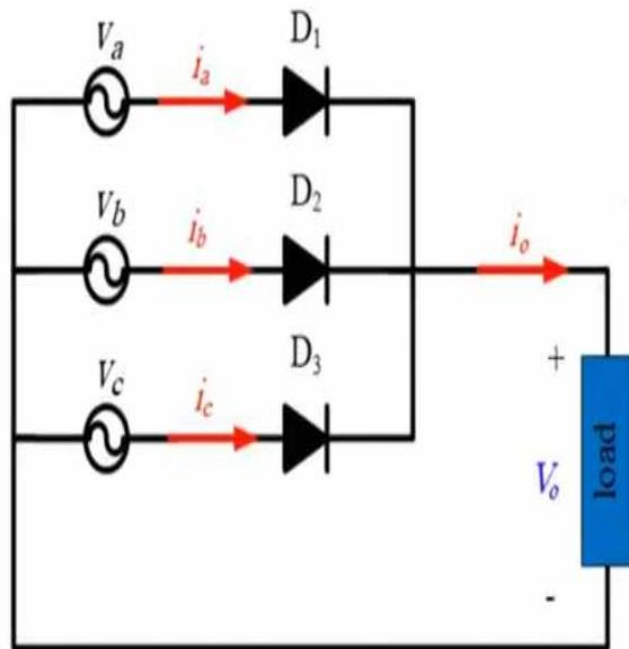
# Three-phase Half-wave Uncontrolled Rectifier





# Diode Voltage

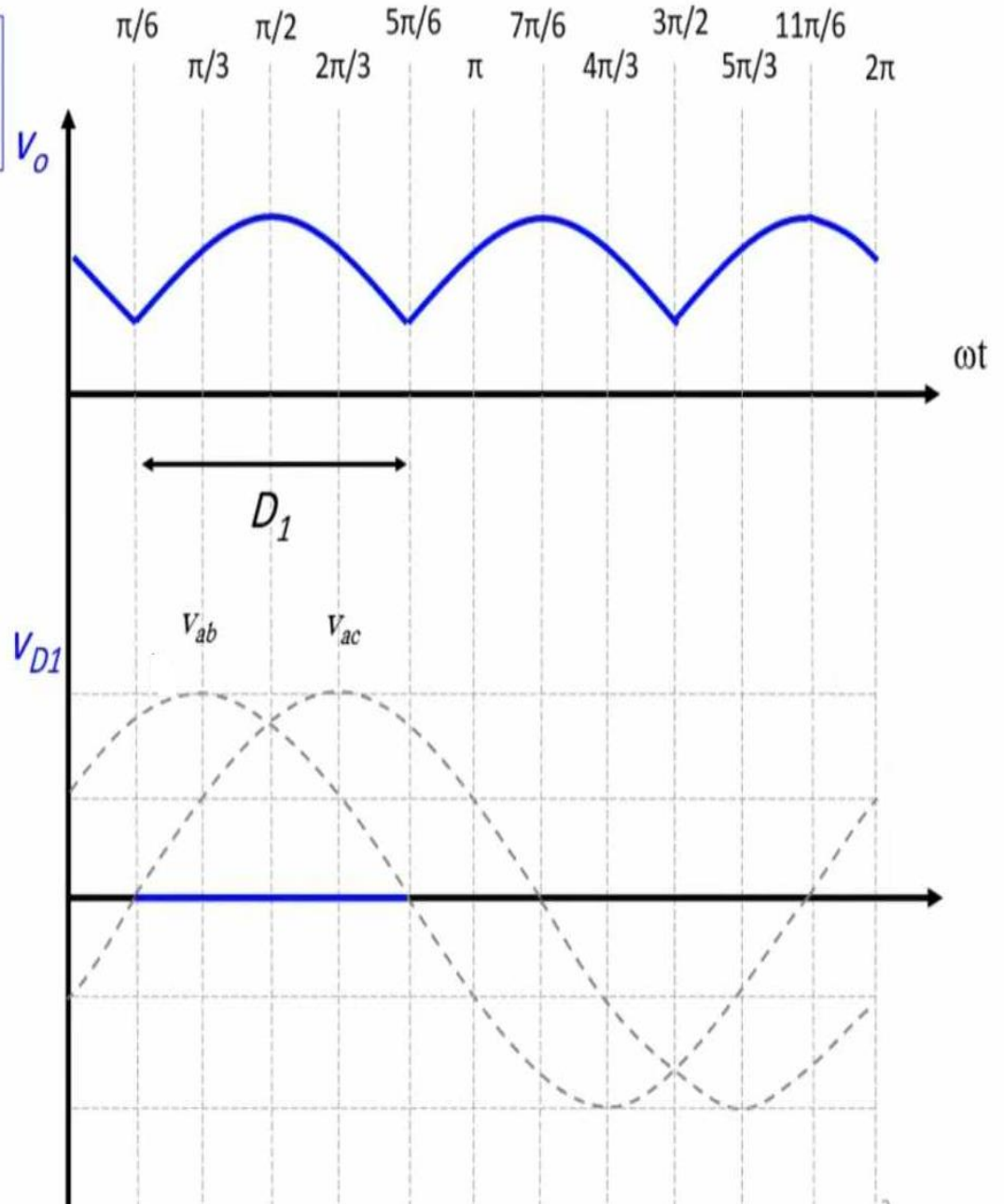
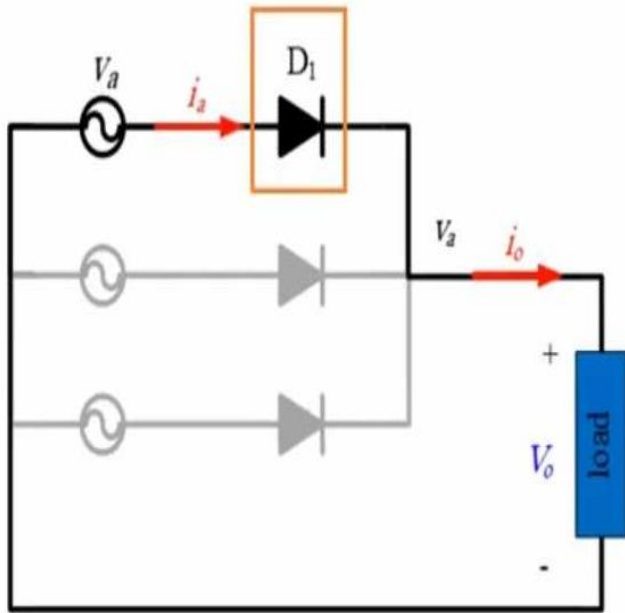






# Diode Voltage

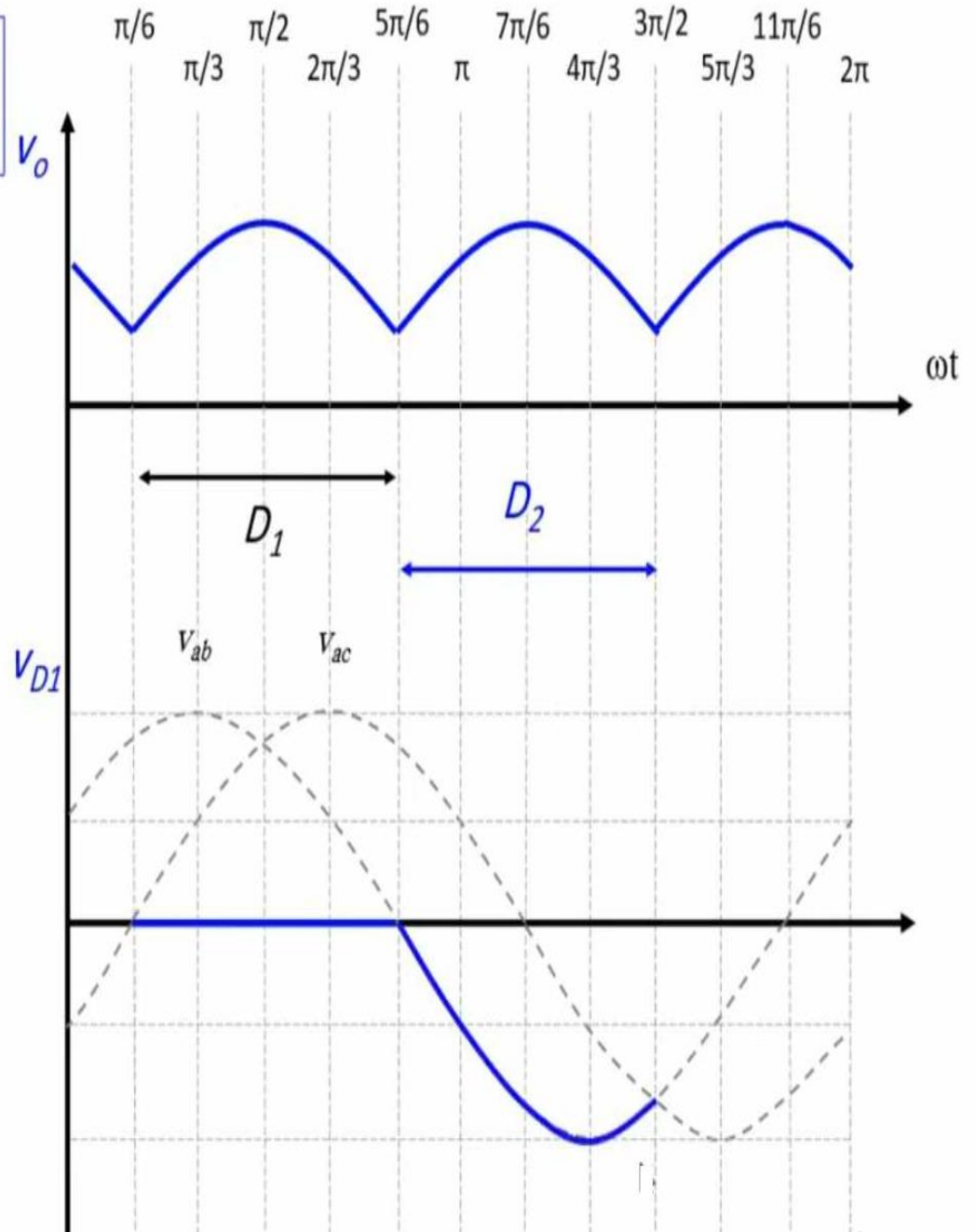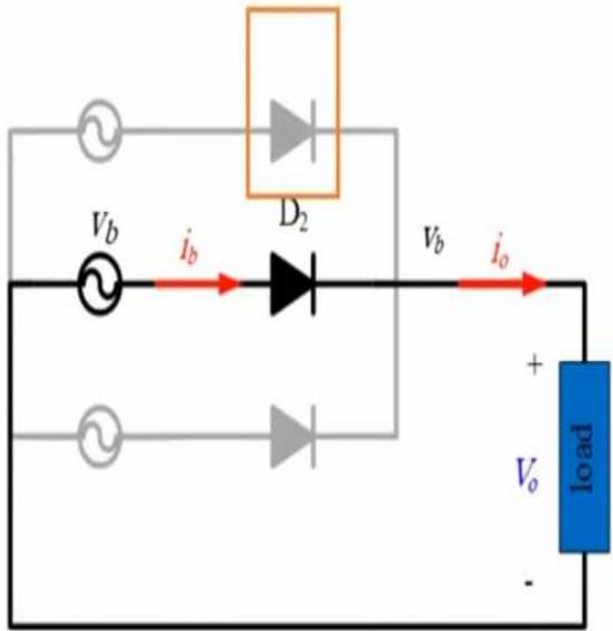

# Diode Voltage

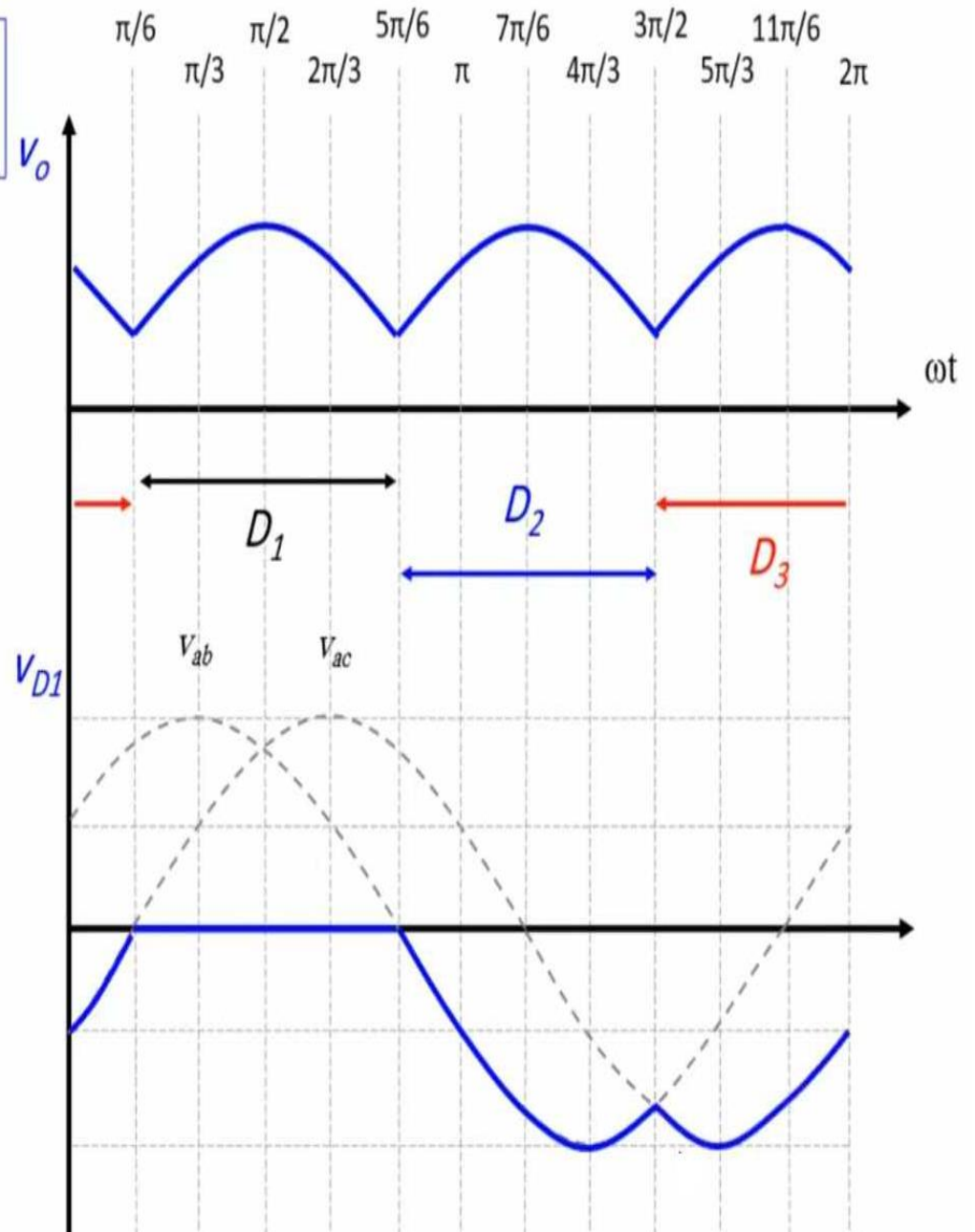
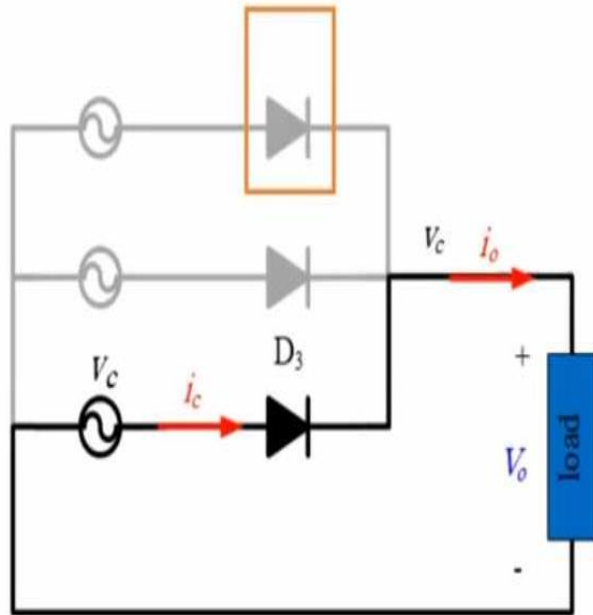


# Diode Voltage

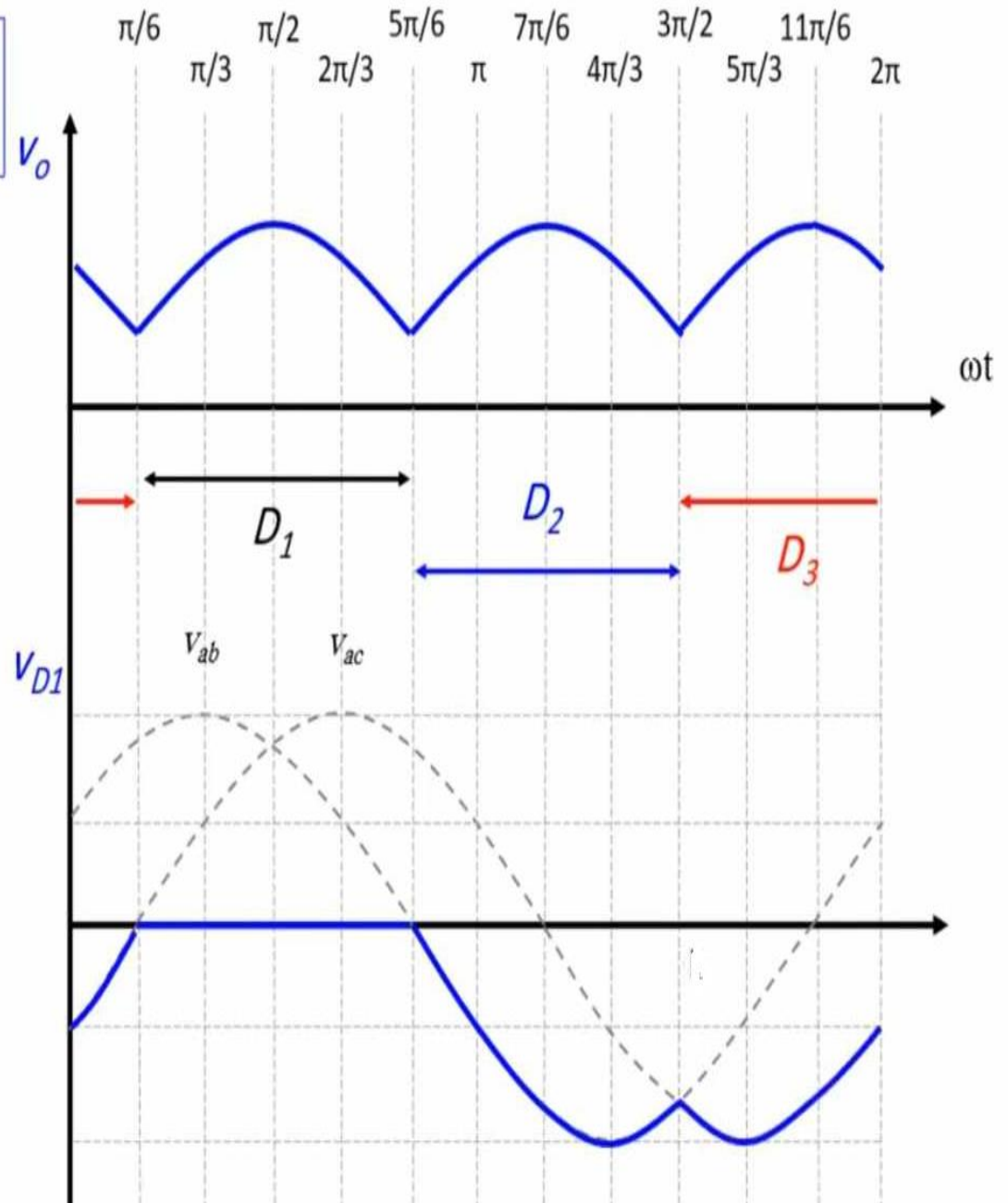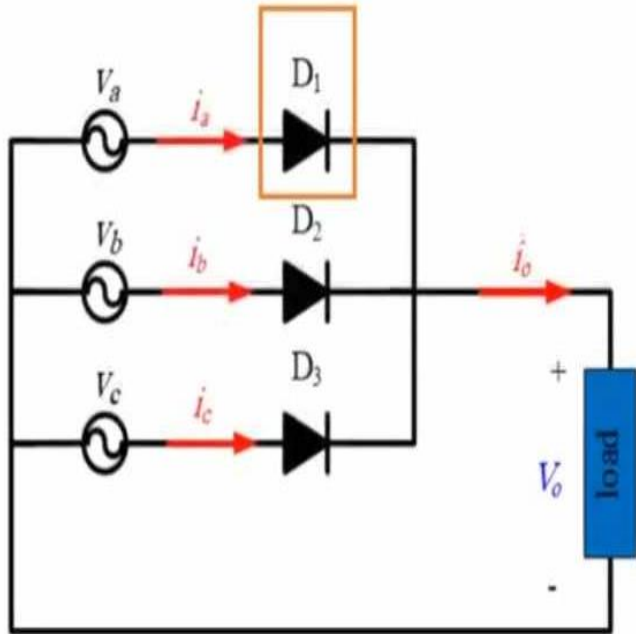



# Three-phase Half-wave Uncontrolled Rectifier

R load

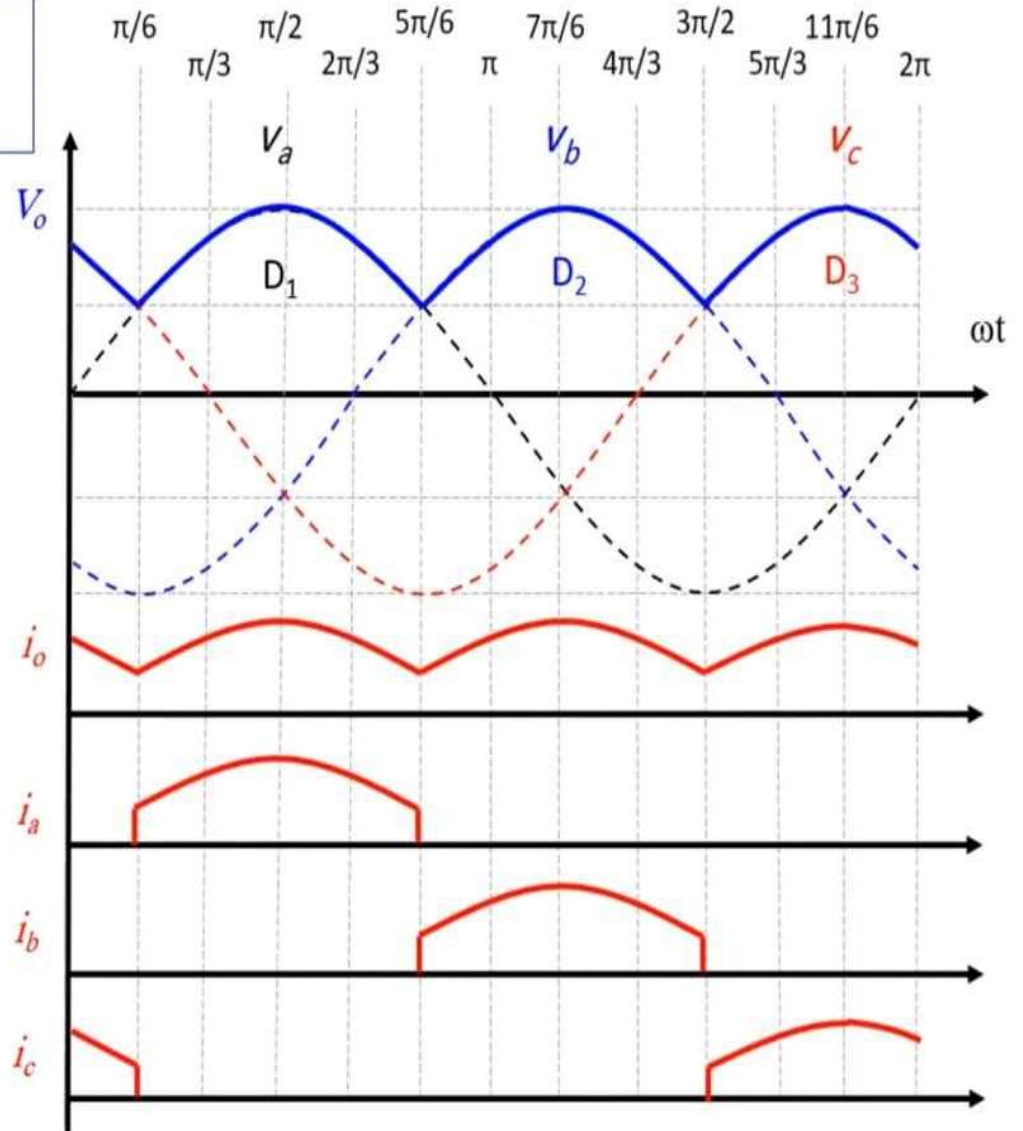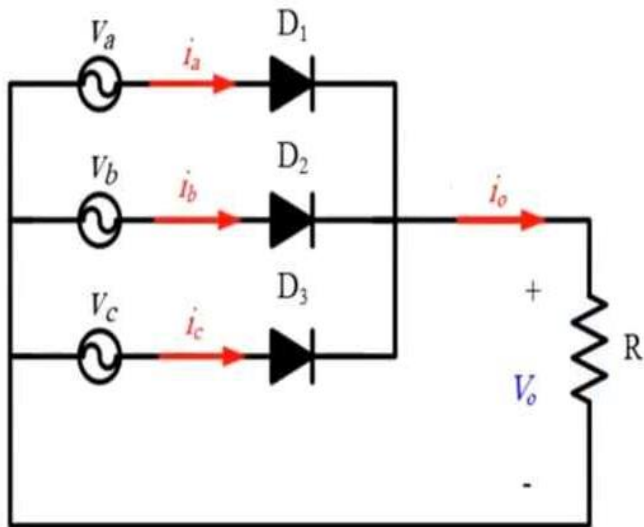

# Three-phase Half-wave Uncontrolled Rectifier

RL load

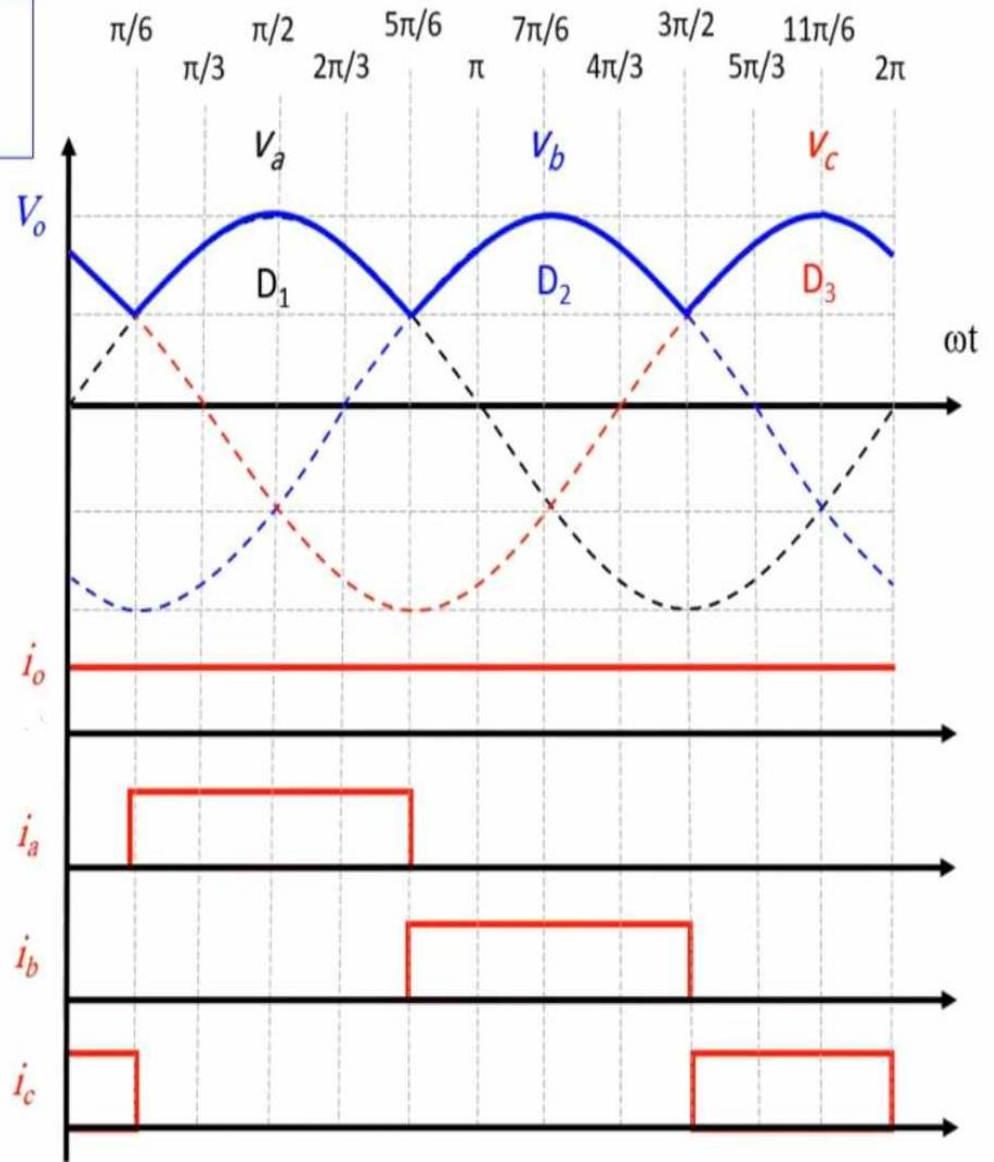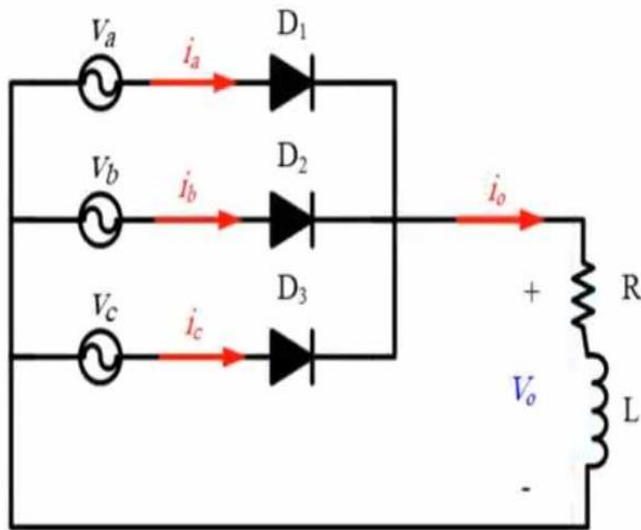

# Output voltage and output current

RL load

The average output voltage


$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi}$$

The average output current

$$I_{o,avg} = \frac{V_{o,avg}}{R} = \frac{3\sqrt{3}V_m}{2\pi R} = I_{o,rms}$$

The rms output voltage
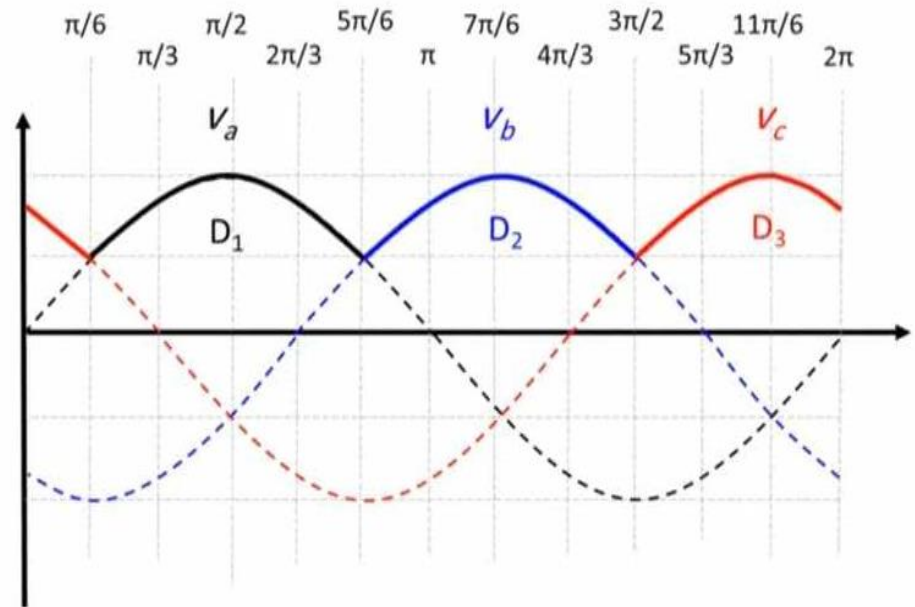
$$v_{o,rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin(\omega t))^2 d\omega t} = \sqrt{3}V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi}}$$



# Supply and Diode Current

RL load

The average supply/Diode current

$$I_{s,avg} = I_{D,avg} = \frac{I_{o,avg}}{3}$$

The rms supply/Diode current

$$I_{s,rms} = I_{D,rms} = \frac{I_{o,rms}}{\sqrt{3}}$$

# Output power and Power factor

The output power

$$P_o = I_{o,rms}^2 R$$

The apparent power

$$S = \mathfrak{V}_{s,rms(phrase)} I_{s,rms}$$

The supply power factor

$$pf = \frac{P_o}{S}$$

# Output voltage and output current

R load

The average output voltage


$$V_{o,avg} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi}$$

The average output current

$$I_{o,avg} = \frac{V_{o,avg}}{R} = \frac{3\sqrt{3}V_m}{2\pi R}$$

The rms output voltage
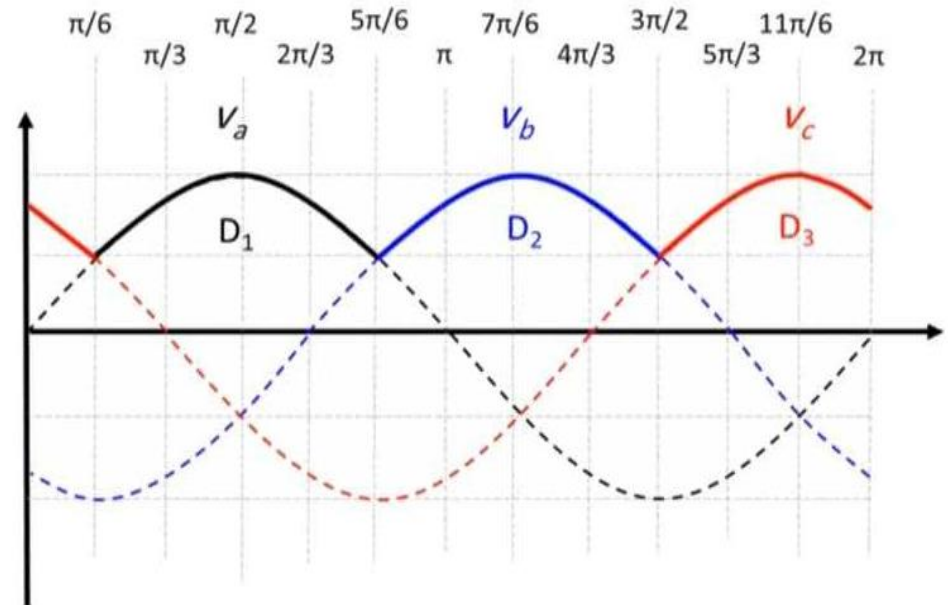
$$V_{o,rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin(\omega t))^2 d\omega t} = \sqrt{3}V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi}}$$



The rms output current

$$I_{o,rms} = \frac{V_{o,rms}}{R}$$



# Supply and Diode Current

R load

The average supply/Diode current

$$I_{s,avg} = I_{D,avg} = \frac{I_{o,avg}}{3}$$

The rms supply/Diode current

$$I_{s,rms} = I_{D,rms} = \frac{I_{o,rms}}{\sqrt{3}}$$

# Output power and Power factor

The output power

$$P_o = I_{o,rms}^2 R$$

The apparent power

$$S = 3V_{s,rms}(\text{phase}) I_{s,rms}$$

The supply power factor

$$pf = \frac{P_o}{S}$$