

Power Electronics Lab

three phase
controlled rectifier

Eng :Eman Abu Hany



Three Phase controlled Rectifier

1- the controlled three - pulse Mid
– point circuit M3C

2- the controlled six - pulse Bridge
Circuit B6C

Three-phase Half-wave Controlled Rectifier


RL load

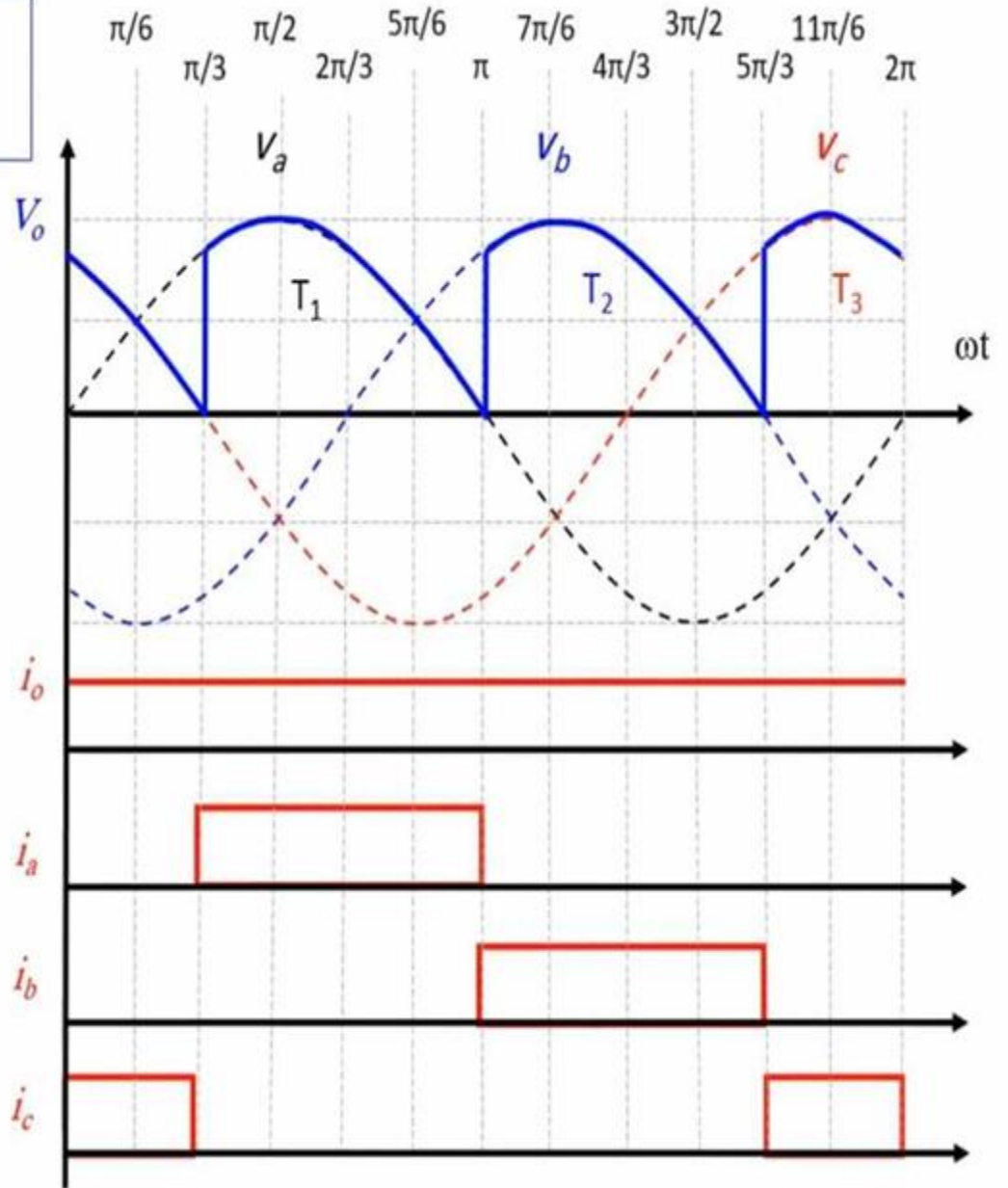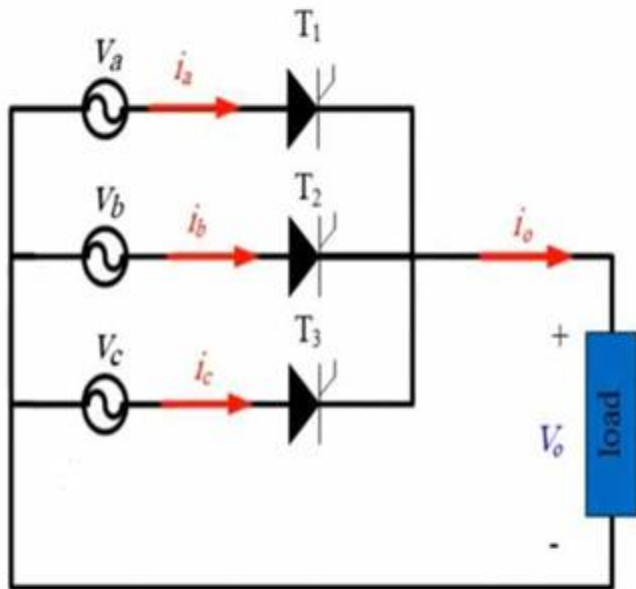

Output Voltage

$$\alpha=0$$


RL load

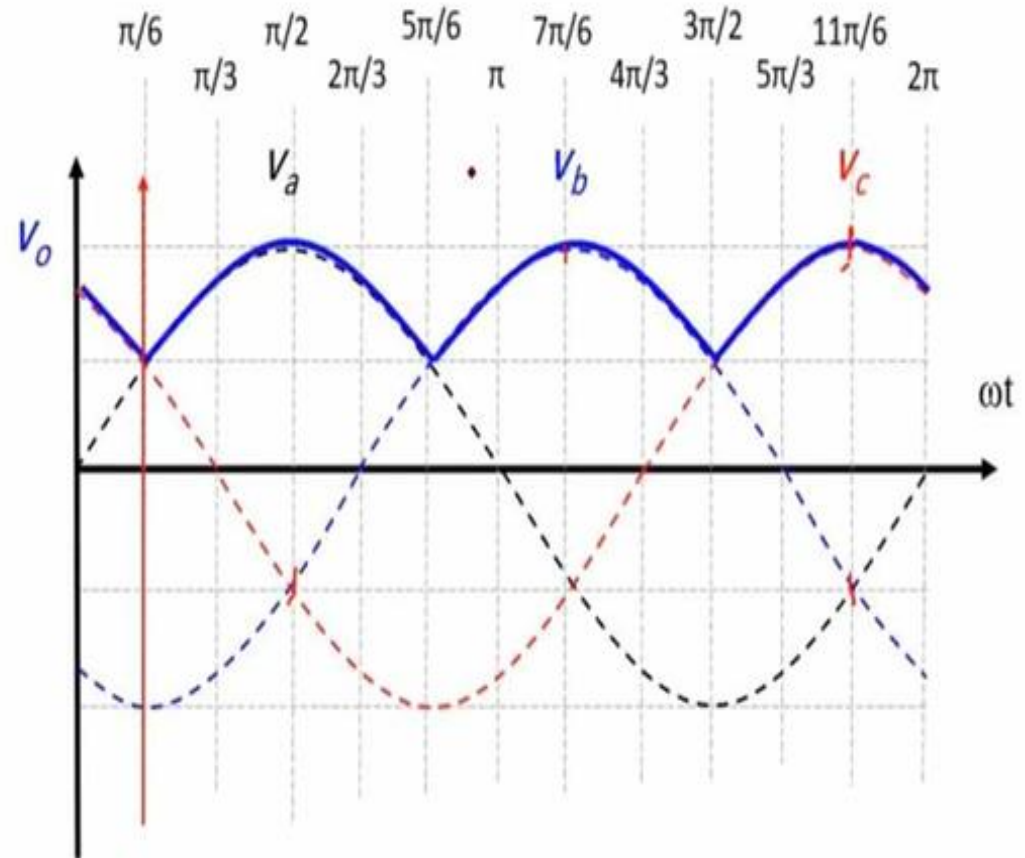

Output Voltage

$$\alpha=30$$

RL load

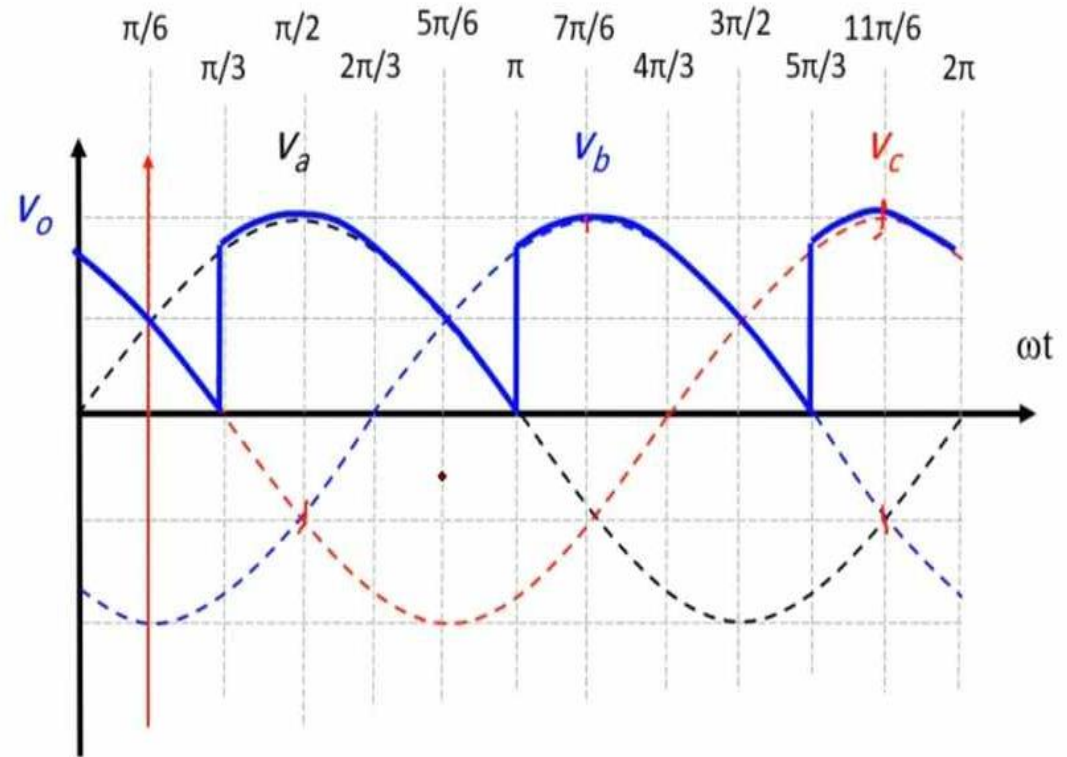


Output Voltage

$$\alpha = 60$$

RL load

$$v_{o,avg} = +ve \quad \alpha < 90$$

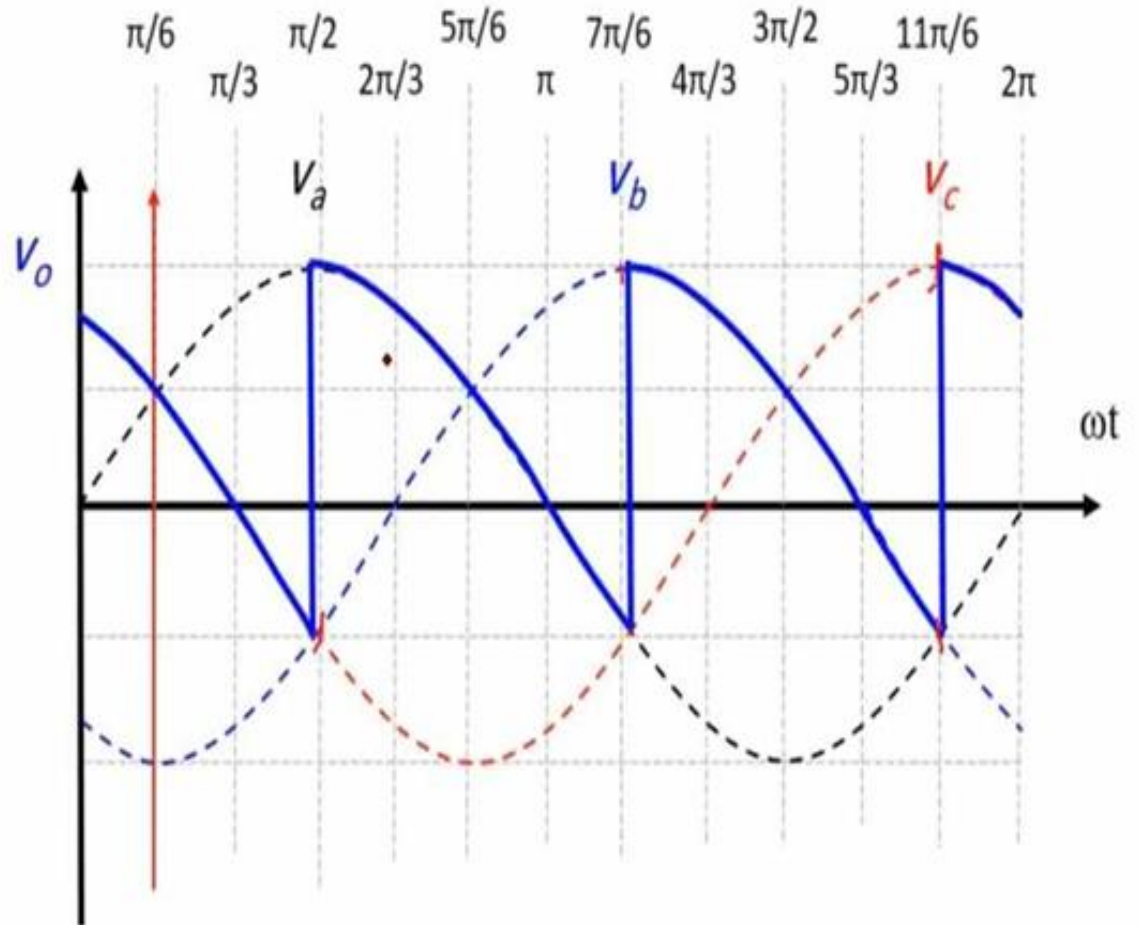


Output Voltage

$$\alpha=90$$

RL load

$$v_{o,avg} = +ve \quad \alpha < 90$$

$$v_{o,avg} = zero \quad \alpha = 90$$

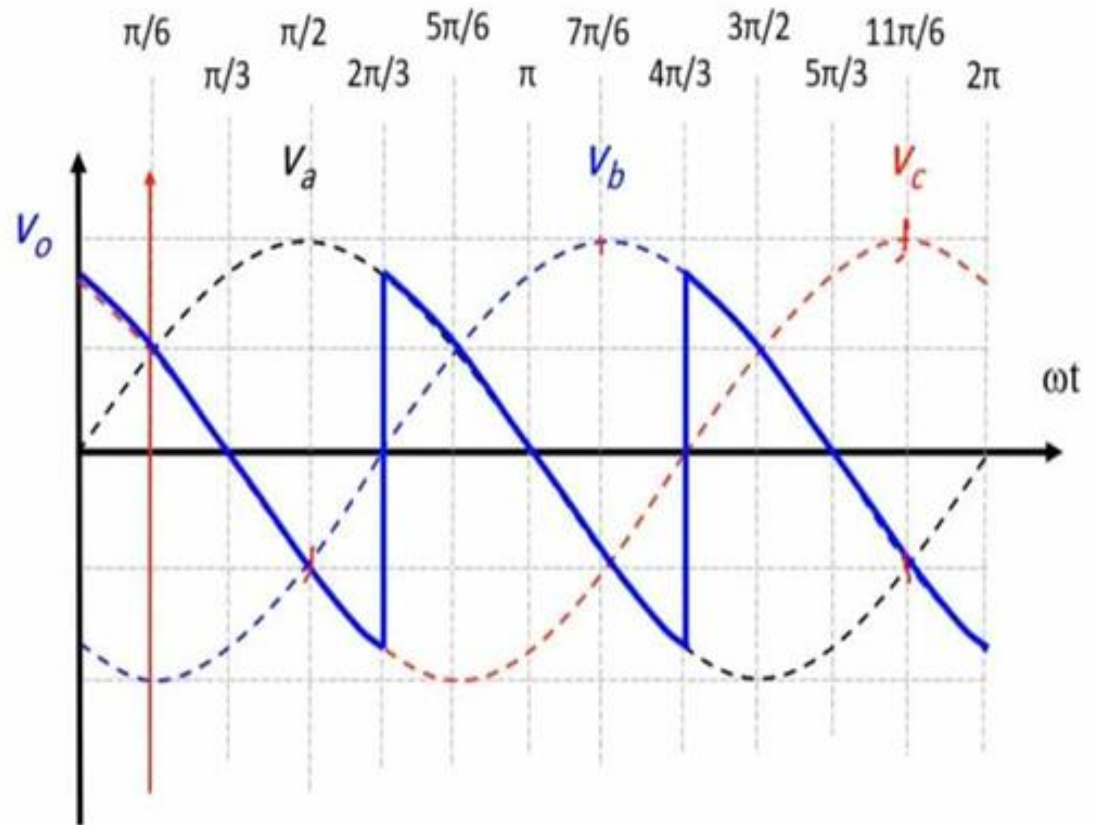


Output Voltage

$$\alpha = 120$$

RL load

$$v_{o,avg} = +ve \quad \alpha < 90$$

$$v_{o,avg} = zero \quad \alpha = 90$$

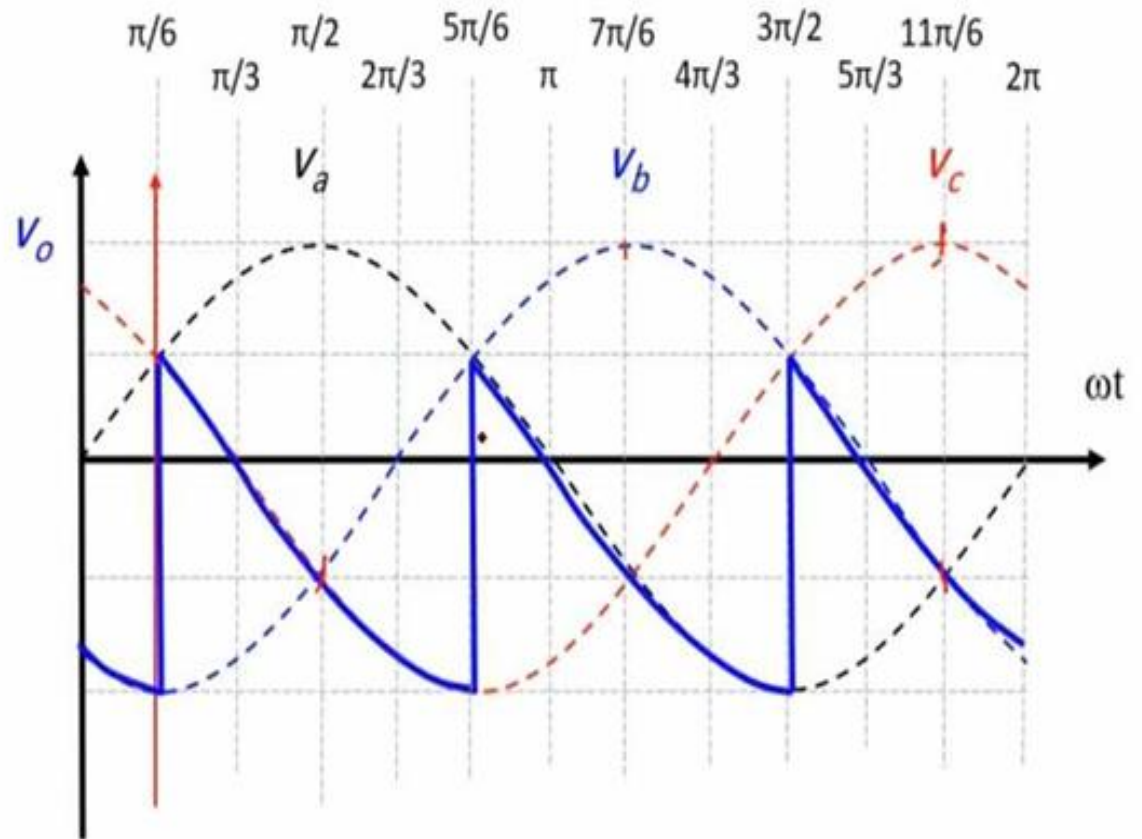

Output Voltage


$$\alpha = 180$$

RL load



$$v_{o,avg} = +ve \quad \alpha < 90$$

$$v_{o,avg} = zero \quad \alpha = 90$$

$$v_{o,avg} = -ve \quad \alpha > 90$$

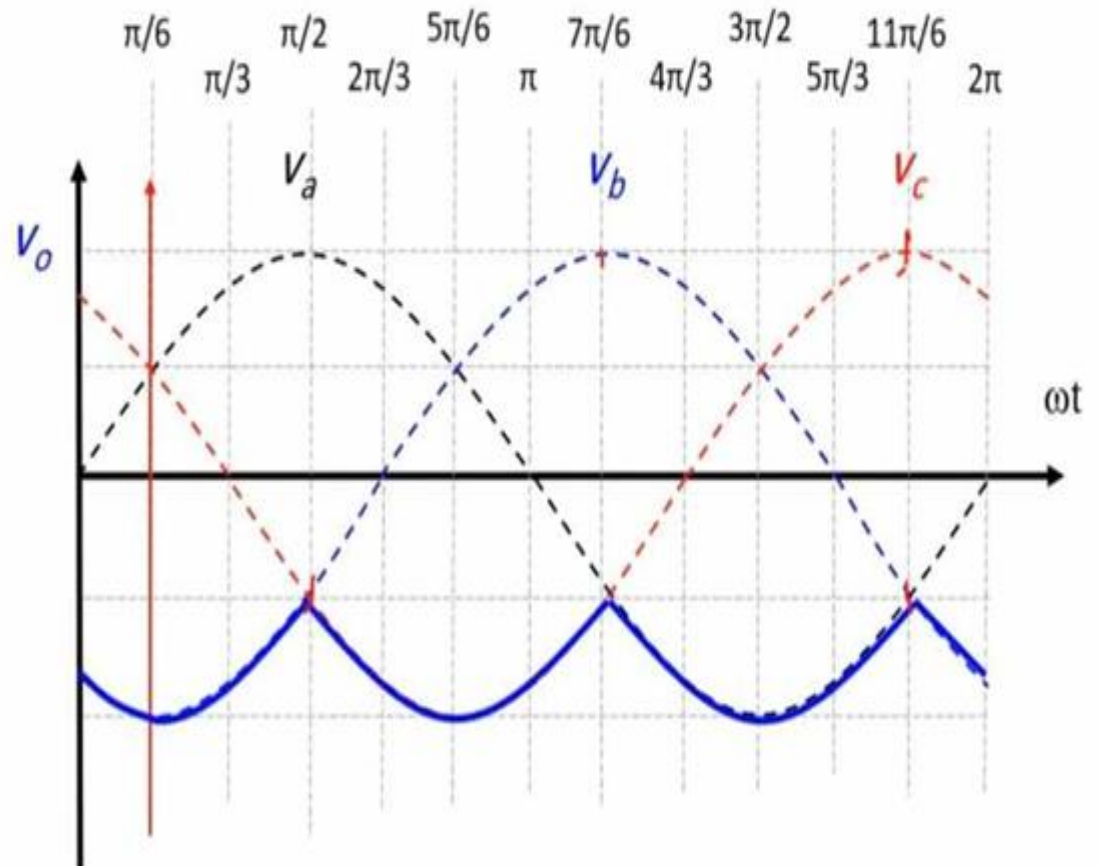

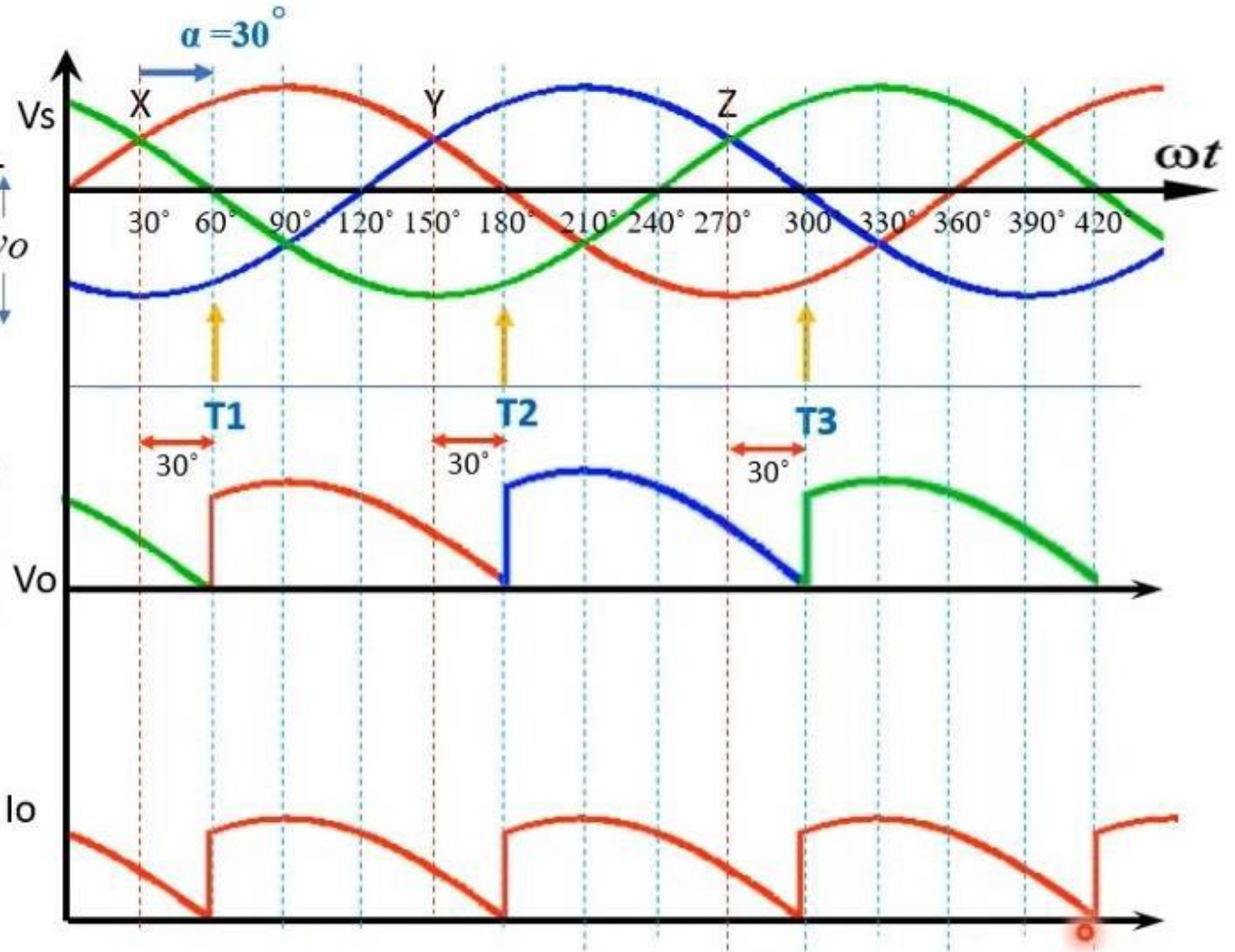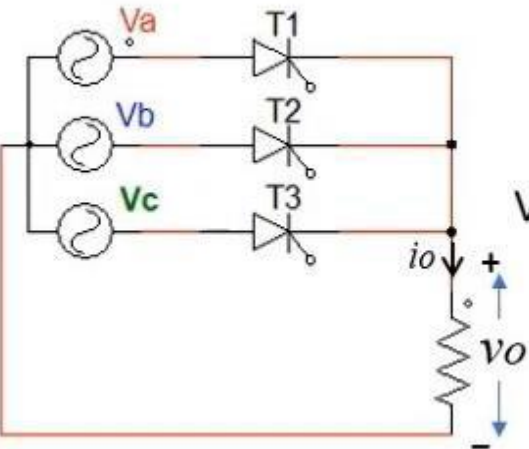1. 3 Φ half wave controlled rectifier, with R load $\alpha=30^\circ$



Triggering angle, $\alpha=30^\circ$



$\omega t = 60^\circ$ to 180° , T1 conduct

$\omega t = 180^\circ$ to 300° , T2 conduct

$\omega t = 300^\circ$ to 420° , T3 conduct

1. 3Φ half wave controlled rectifier

$$0^\circ \leq \alpha \leq 30^\circ$$

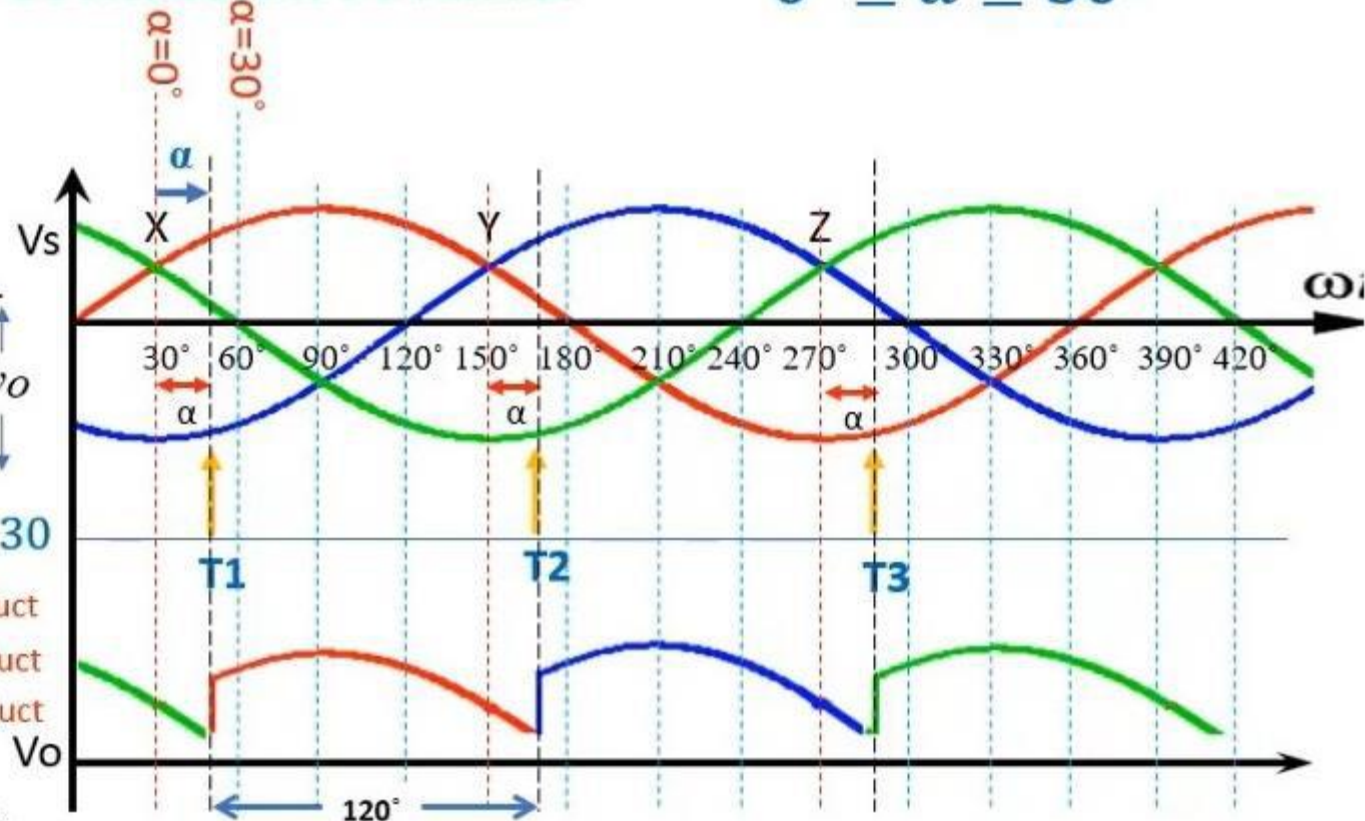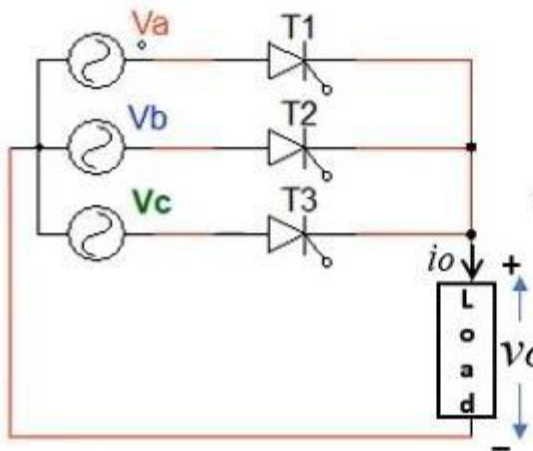

Triggering angle, $0 \leq \alpha \leq 30$

$\omega t = 30^\circ + \alpha$ to $150^\circ + \alpha$, T1 conduct
 $\omega t = 150^\circ + \alpha$ to $270^\circ + \alpha$, T2 conduct
 $\omega t = 270^\circ + \alpha$ to $390^\circ + \alpha$, T3 conduct

Average output voltage,

$$V_0 = \frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \omega t d(\omega t) = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha, \quad \text{where, } V_m \rightarrow \text{maximum phase voltage}$$

$$= \frac{3\sqrt{2}}{2\pi} V \cos \alpha, \quad \text{where, } V \rightarrow \text{rms line voltage}$$

$$\text{RMS o/p voltage, } V_{or} = \left[\frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m^2 \sin^2 \omega t d(\omega t) \right]^{1/2} = V_m \left[\frac{3}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{3} \cos 2\alpha \right) \right]^{1/2}$$

Output voltage and output current

RL load

The average output voltage

$$V_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

The average output current

$$I_{o,avg} = \frac{V_{o,avg}}{R} = \frac{3\sqrt{3}V_m}{2\pi R} \cos(\alpha) = I_{o,rms}$$

The rms output voltage

$$V_{o,rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} (V_m \sin(\omega t))^2 d\omega t} = \sqrt{3}V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos(2\alpha)}$$

Supply and Thyristor Current

RL load

The average supply/Thyristor current

$$I_{s,avg} = I_{T,avg} = \frac{I_{o,avg}}{3}$$

The rms supply/ Thyristor current

$$I_{s,rms} = I_{T,rms} = \frac{I_{o,rms}}{\sqrt{3}}$$

Output power and Power factor

The output power

$$P_o = I_{o,rms}^2 R$$

The apparent power



$$S = \mathcal{V}_{s,rms(\text{phase})} I_{s,rms}$$

The supply power factor

$$pf = \frac{P_o}{S}$$

Three-phase Half-wave Controlled Rectifier

R load

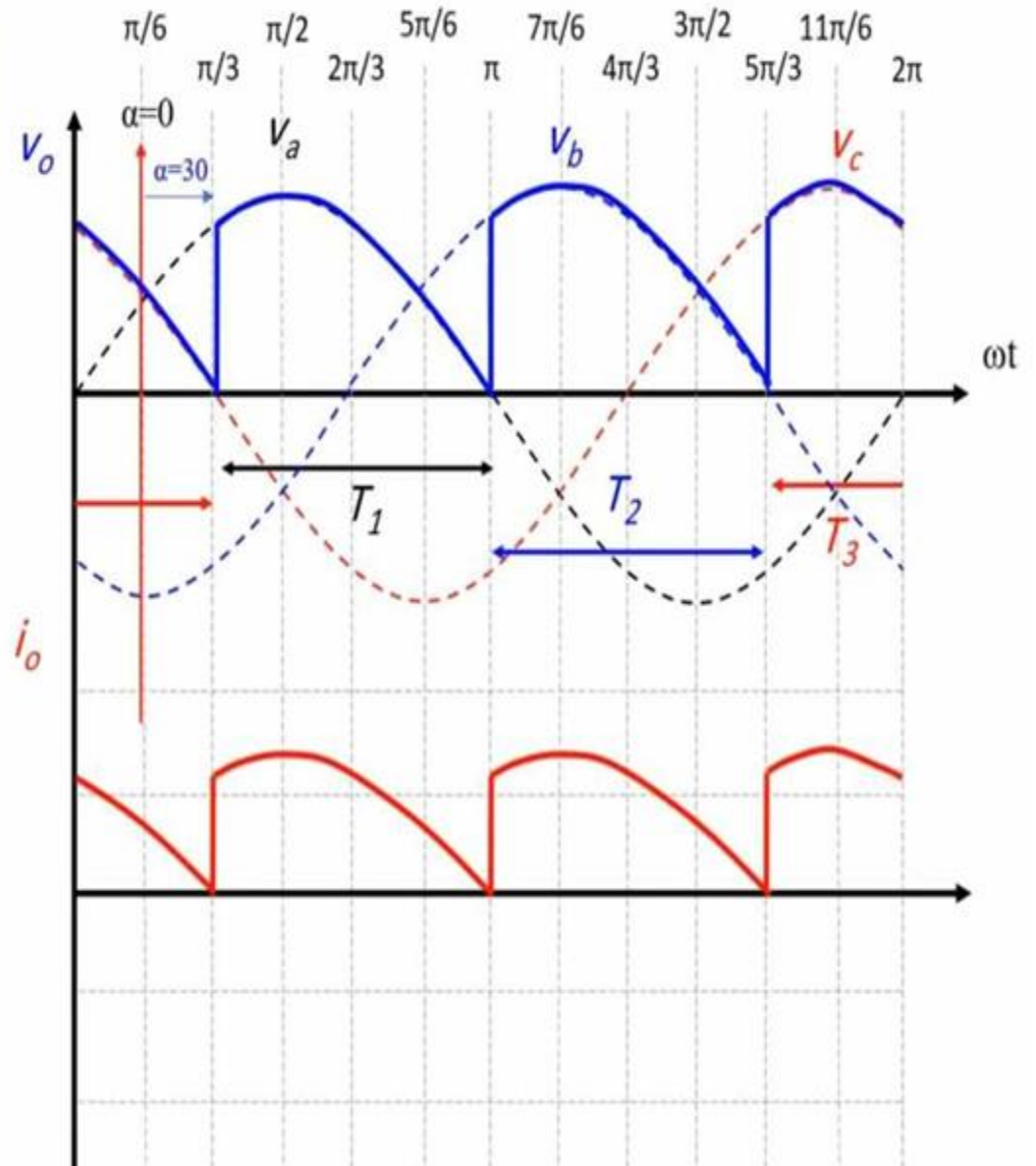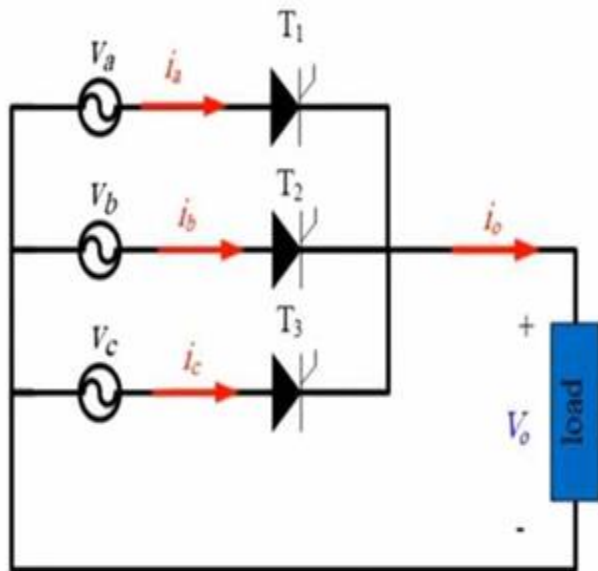


Output Voltage

$\alpha=30$

R load

$\alpha \leq 30$
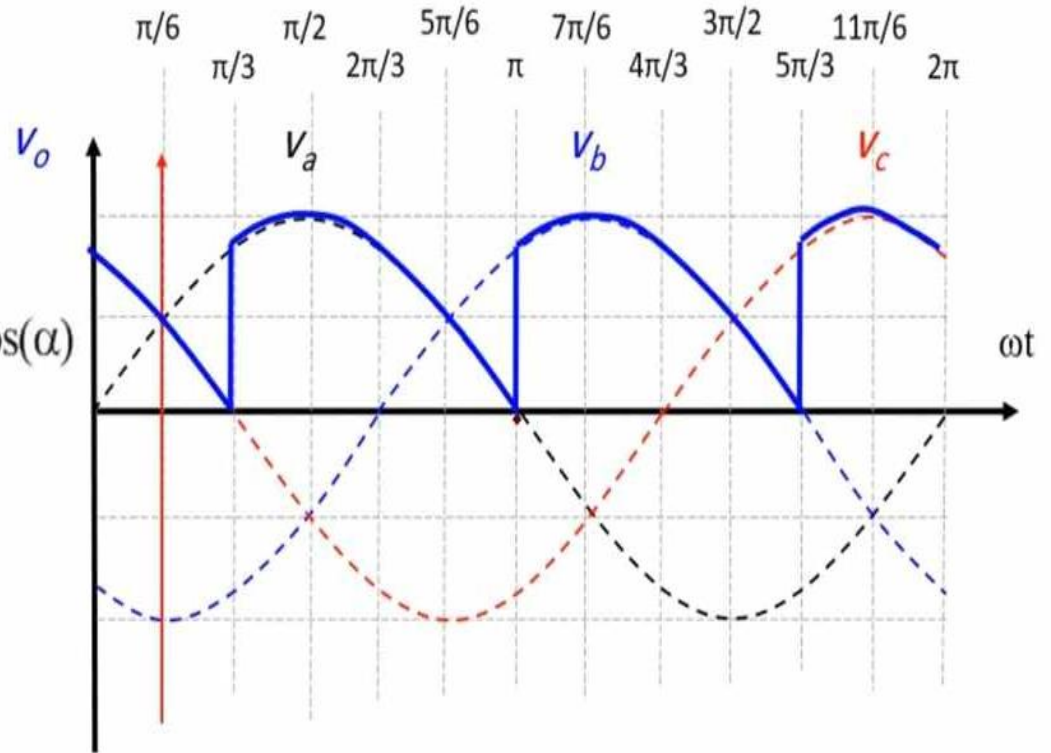
$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$



Output Voltage

$$\alpha = 60$$


R load

$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

$$\alpha \leq 30$$

$$\alpha > 30$$
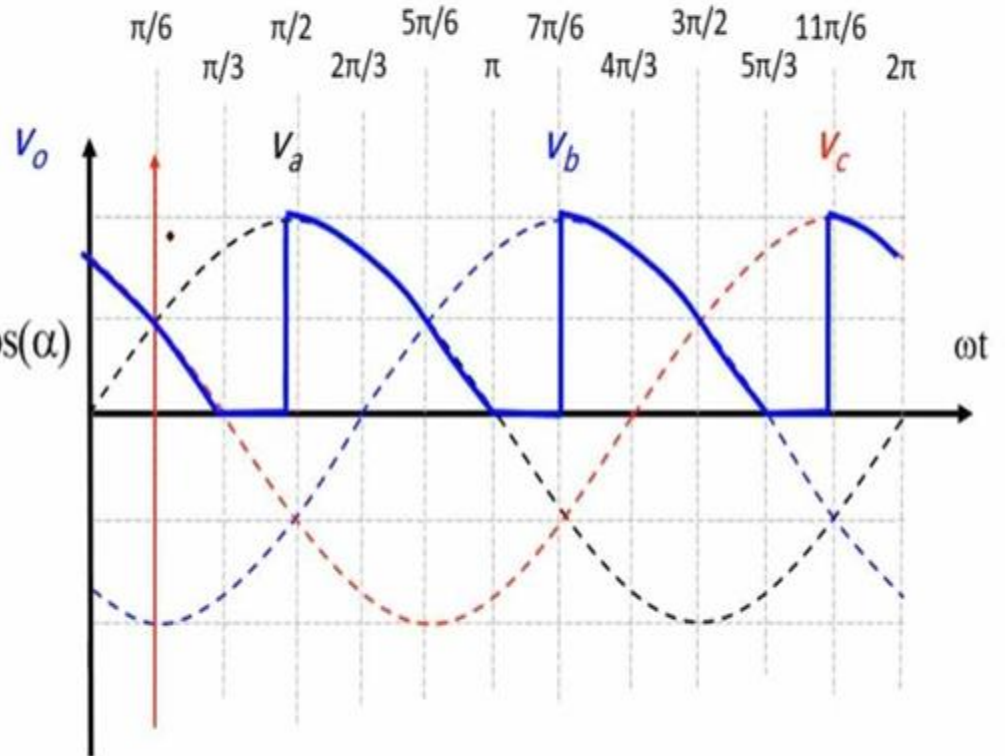
$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{3V_m}{2\pi} [1 + \cos(\alpha + 30)]$$



Output Voltage

$$\alpha = 90$$


R load

$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

$$\alpha \leq 30$$

$$\alpha > 30$$
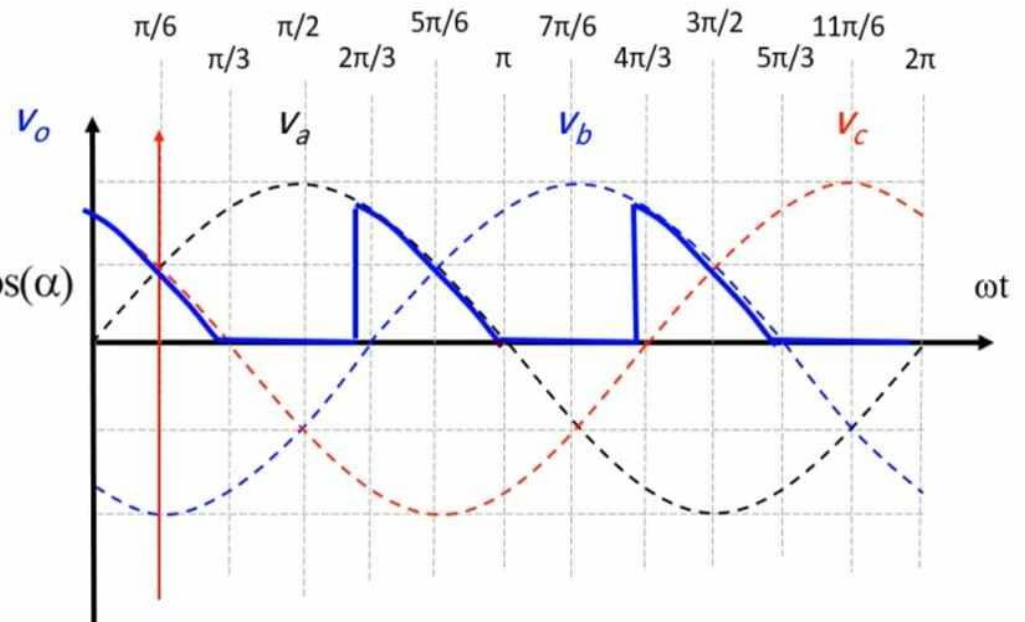
$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{3V_m}{2\pi} [1 + \cos(\alpha + 30)]$$



Output Voltage

$$\alpha = 120$$


R load

$$\alpha \leq 30$$

$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

$$\alpha > 30$$
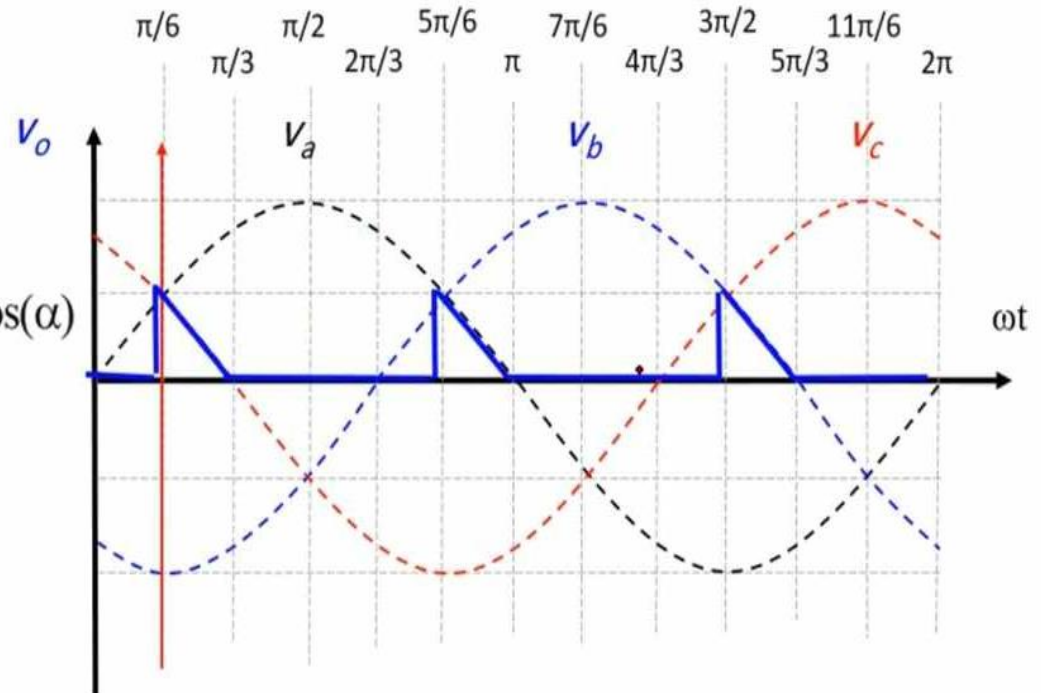
$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{3V_m}{2\pi} [1 + \cos(\alpha + 30)]$$



Output Voltage

$\alpha=150$

R load


$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin(\omega t) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} \cos(\alpha)$$

$\alpha \leq 30$

$\alpha > 30$

$$v_{o,avg} = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{3V_m}{2\pi} [1 + \cos(\alpha + 30)]$$

$0 \leq \alpha \leq 150$

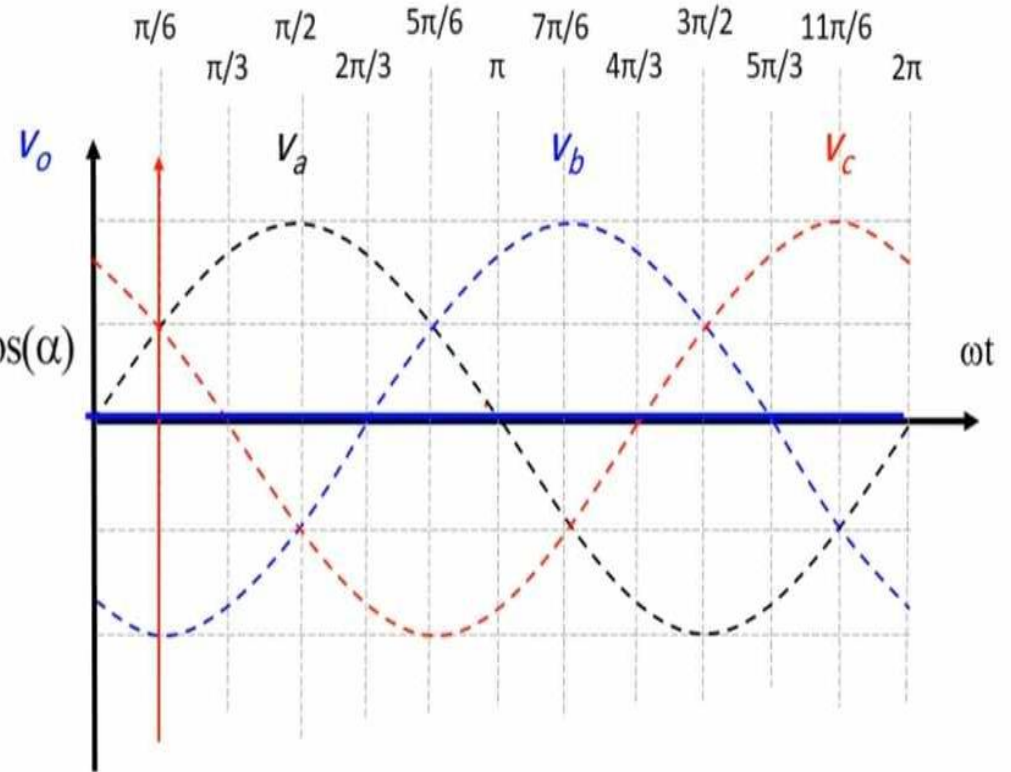

Output voltage and output current

R load

The average output current

$$I_{o,avg} = \frac{V_{o,avg}}{R}$$

The rms output current

$$I_{o,rms} = \frac{V_{o,rms}}{R}$$

The rms output voltage

$$v_{o,rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} (V_m \sin(\omega t))^2 d\omega t} = \sqrt{3} V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos(2\alpha)} \quad \alpha \leq 30$$

$$v_{o,rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} (V_m \sin(\omega t))^2 d\omega t} \quad \alpha > 30$$

Supply and Thyristor Current

R load

The average supply/ Thyristor current

$$I_{s,avg} = I_{T,avg} = \frac{I_{o,avg}}{3}$$

The rms supply/ Thyristor current

$$I_{s,rms} = I_{T,rms} = \frac{I_{o,rms}}{\sqrt{3}}$$

Output power and Power factor

The output power

$$P_o = I_{o,rms}^2 R$$

The apparent power

$$S = \mathfrak{V}_{s,rms(\text{phase})} I_{s,rms}$$

The supply power factor

$$pf = \frac{P_o}{S}$$

