

# Power Electronics Lab

three phase  
controlled rectifier


Eng :Eman Abu Hany

# Three Phase controlled Rectifier

1- the controlled three - pulse Mid  
– point circuit M3C

2- the controlled six - pulse Bridge  
Circuit B6C


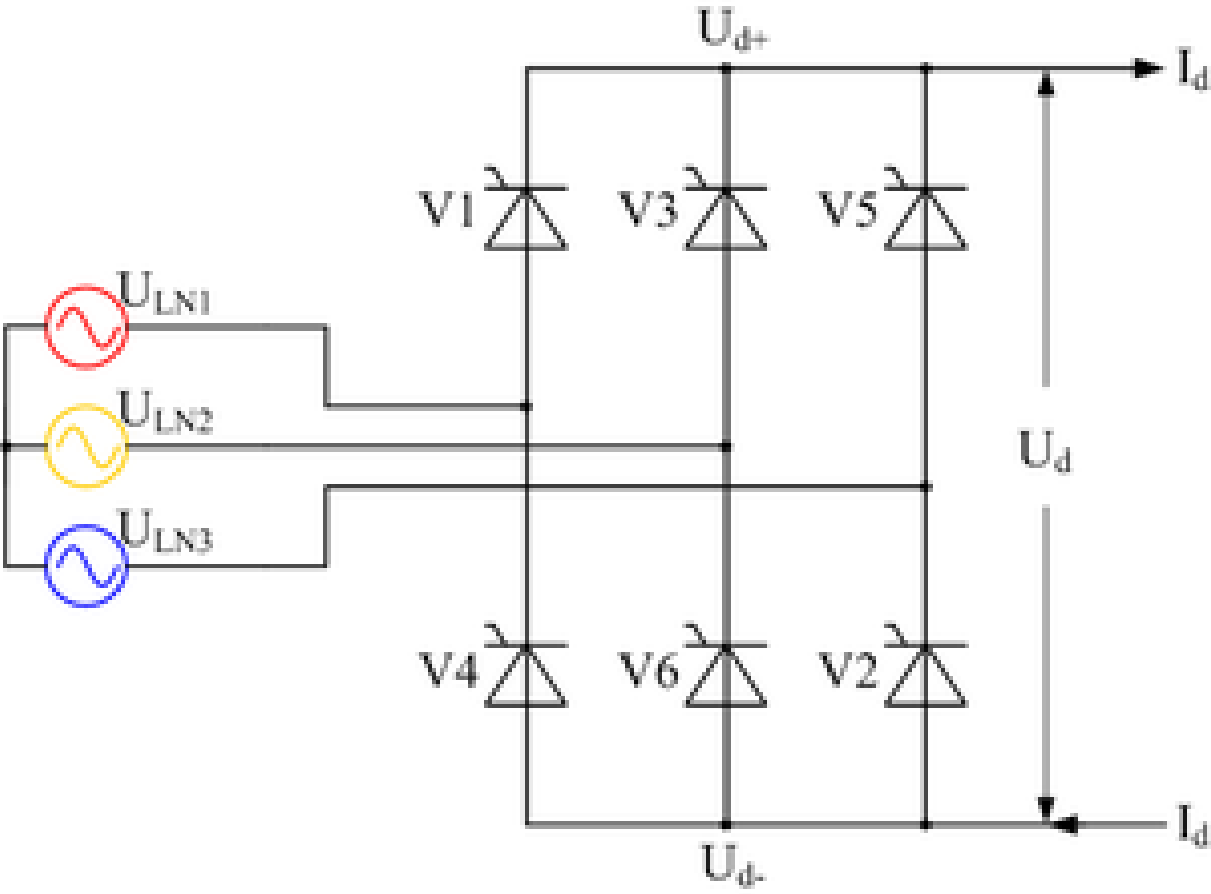
# the controlled six - pulse Bridge Circuit B6C


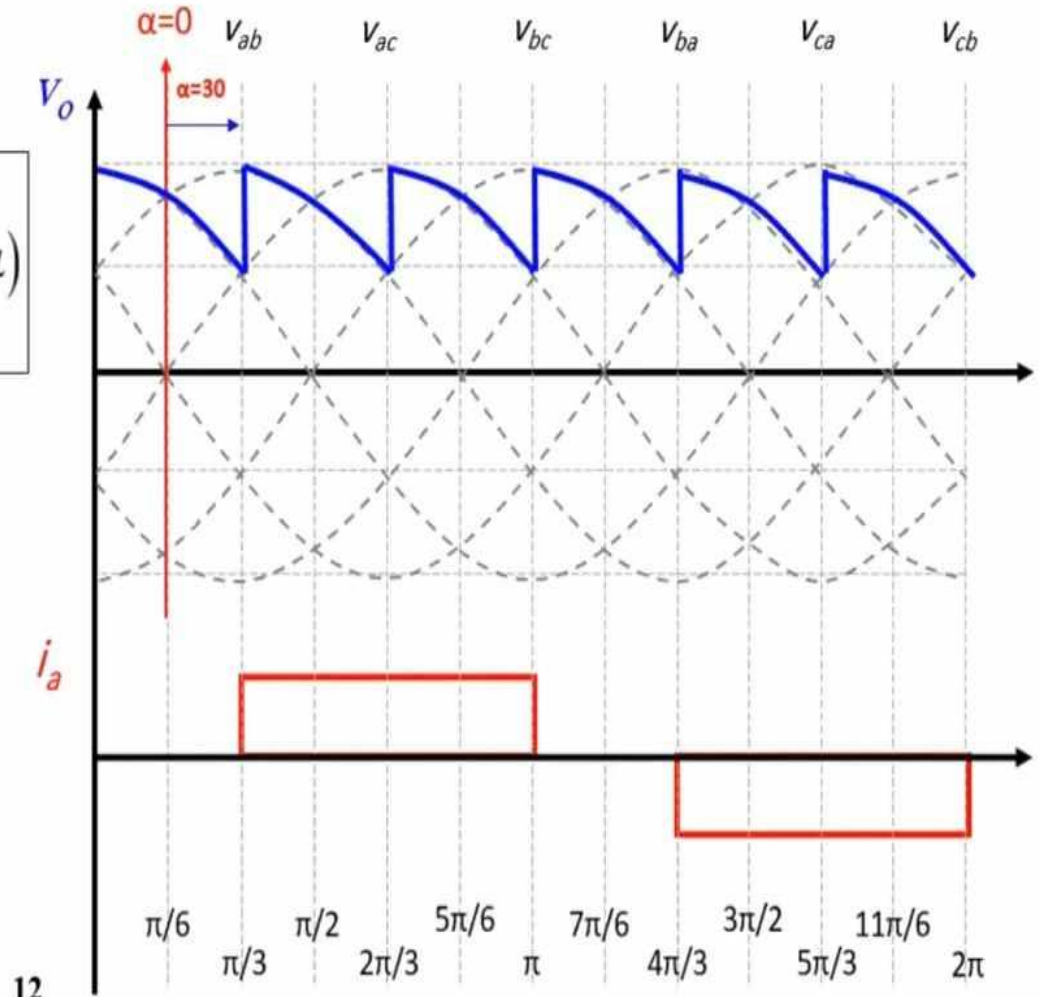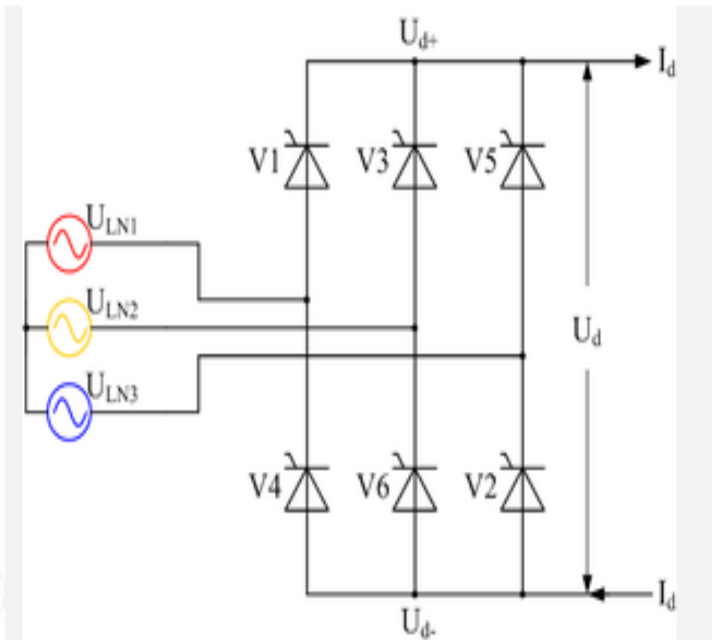
# Output voltage of controlled Rectifier

RL load


$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$


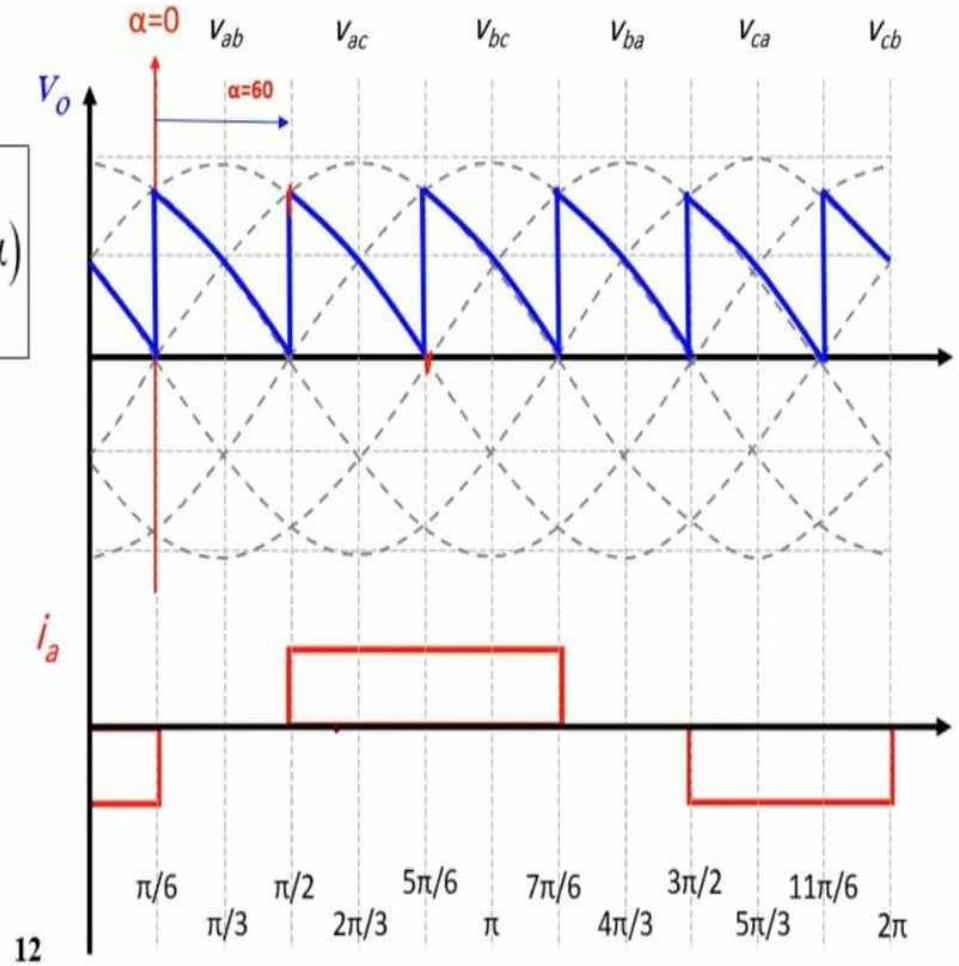
# Output voltage of controlled Rectifier

RL load


$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$


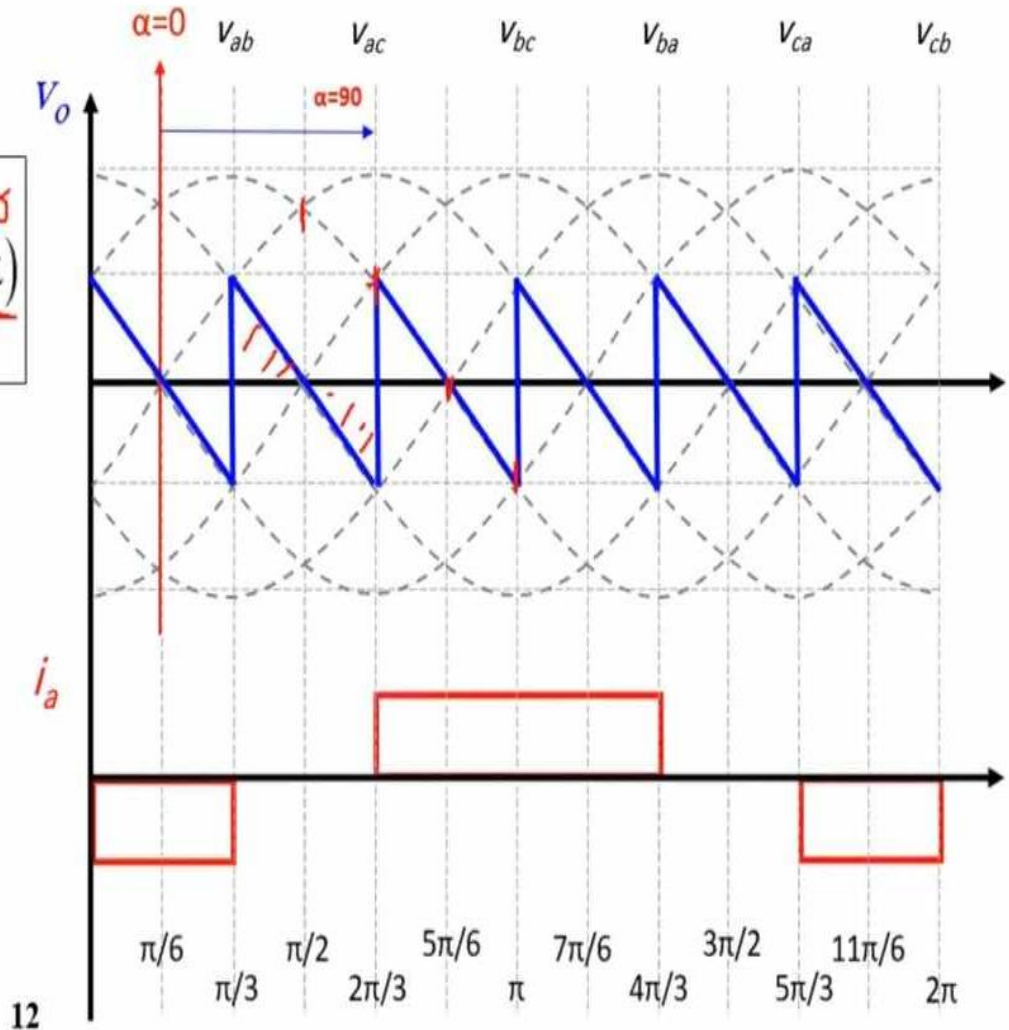
# Output voltage of controlled Rectifier

RL load

$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$



# Output voltage of controlled Rectifier

RL load


$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$

$$0 \leq \alpha \leq 180$$

$$V_{avg} = +ve \quad \alpha < 90$$


$$V_{avg} = zero \quad \alpha = 90$$

$$V_{avg} = -ve \quad \alpha > 90$$

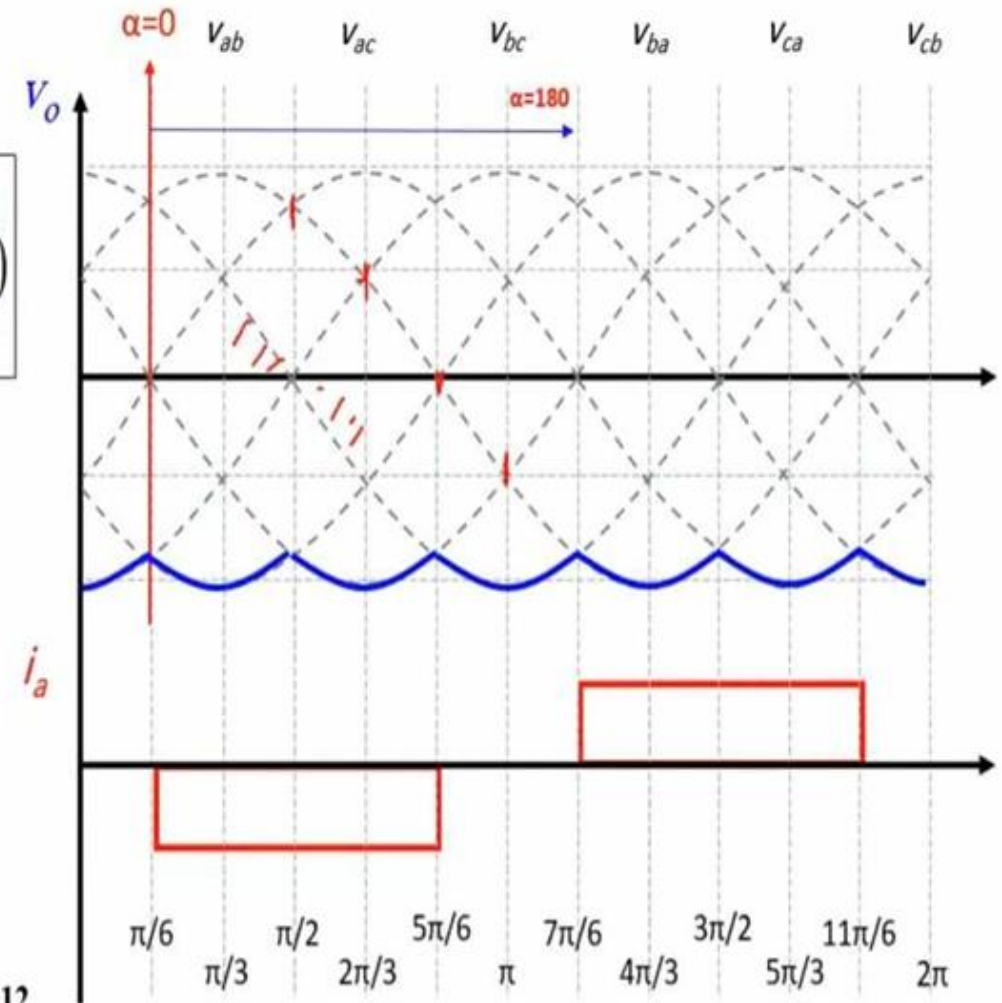

# Output voltage of controlled Rectifier


R load

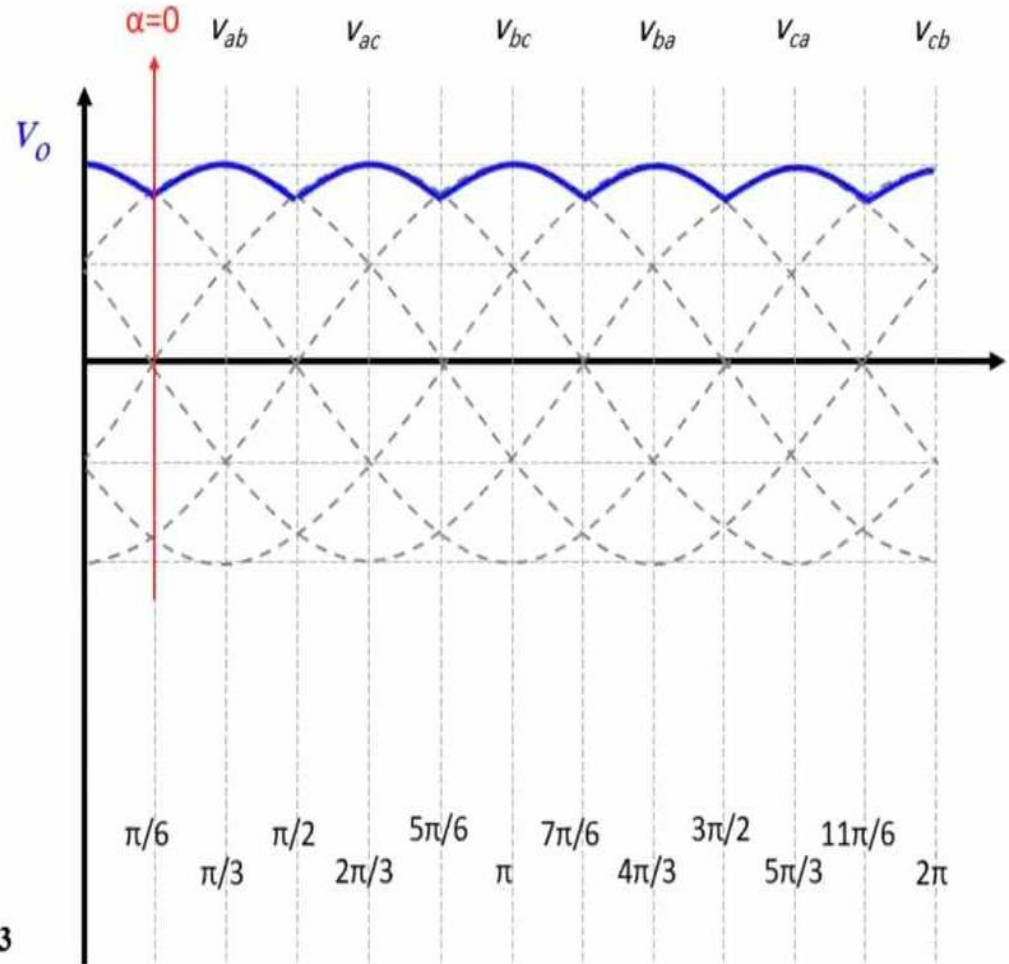




# Output voltage of controlled Rectifier

R load

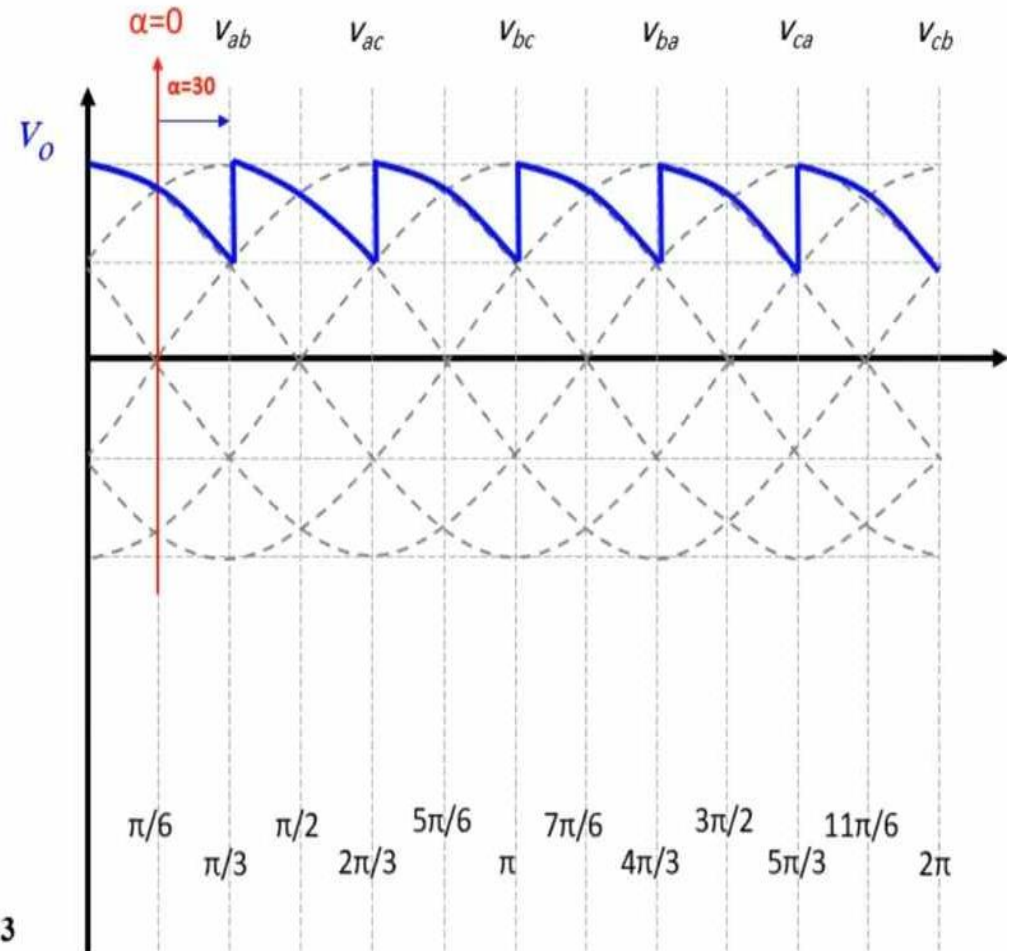

# Output voltage of controlled Rectifier

R load

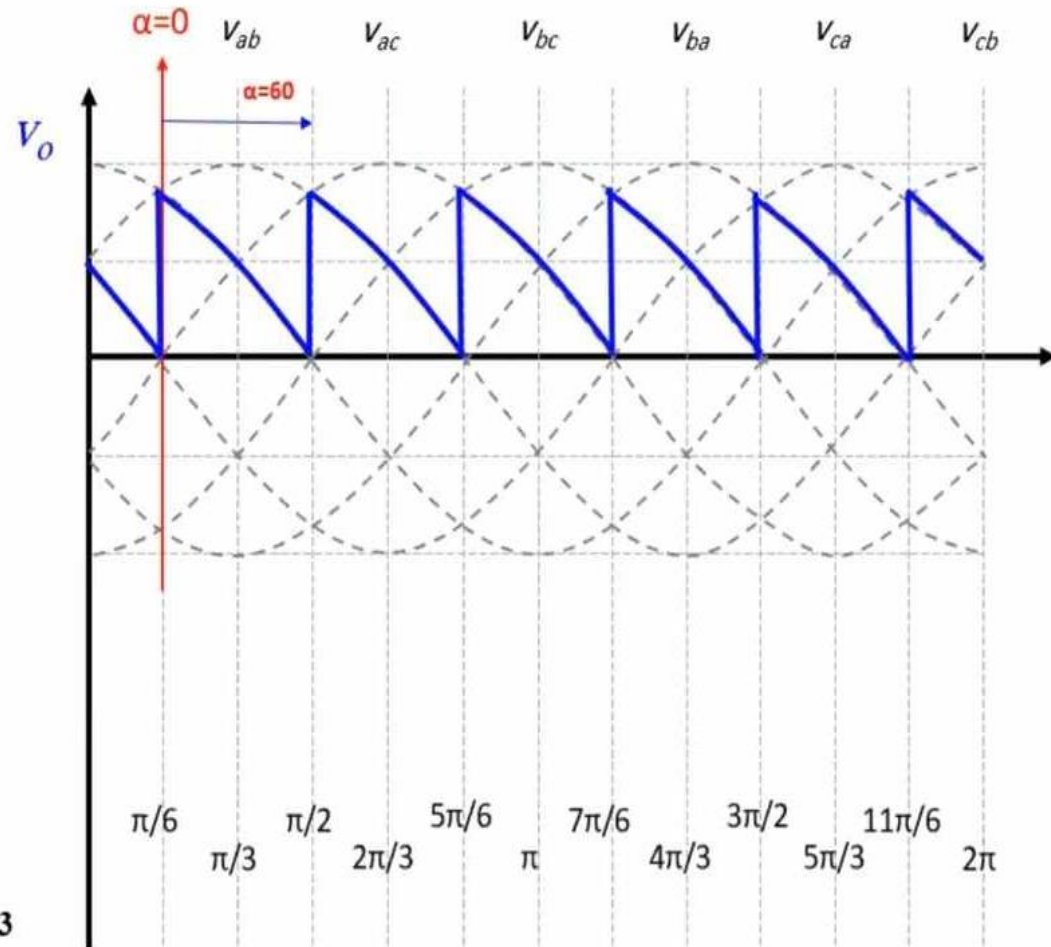


# Output voltage of controlled Rectifier

R load

$$0 \leq \alpha \leq 60^\circ$$
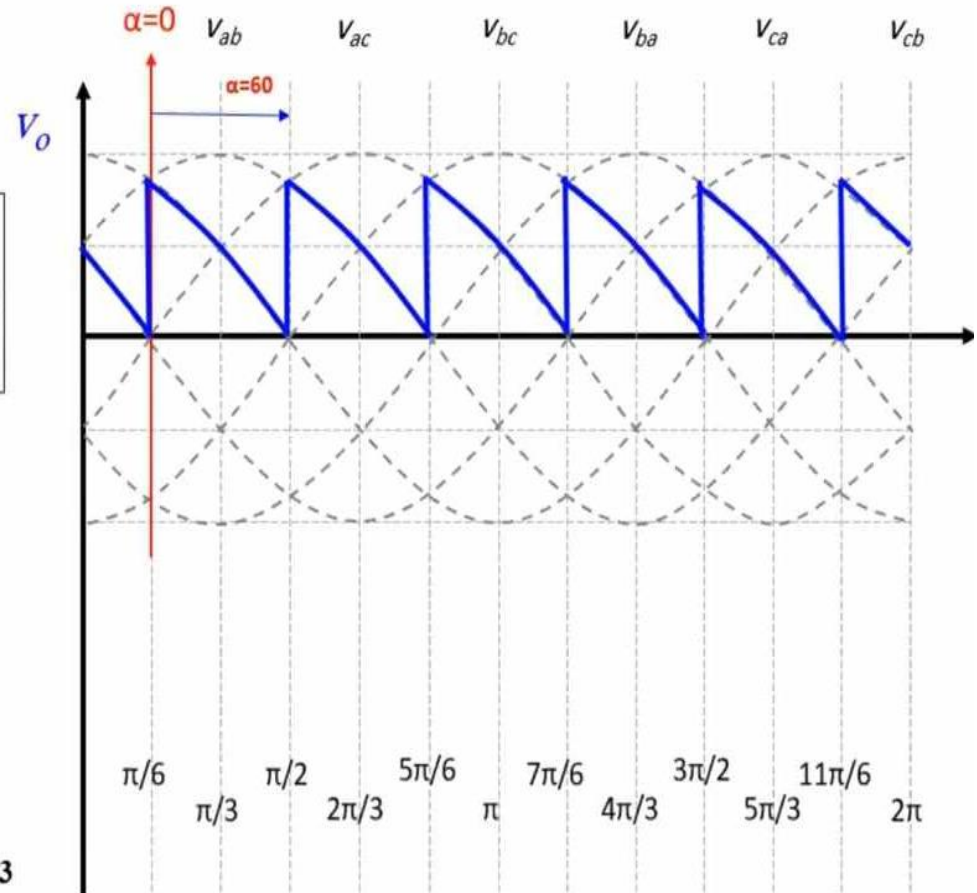
$$v_{avg} = \frac{3}{\pi} \int_{\pi/6+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$



# Output voltage of controlled Rectifier


R load

$$0 \leq \alpha \leq 60$$

$$v_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$

$$60 \leq \alpha < 120$$
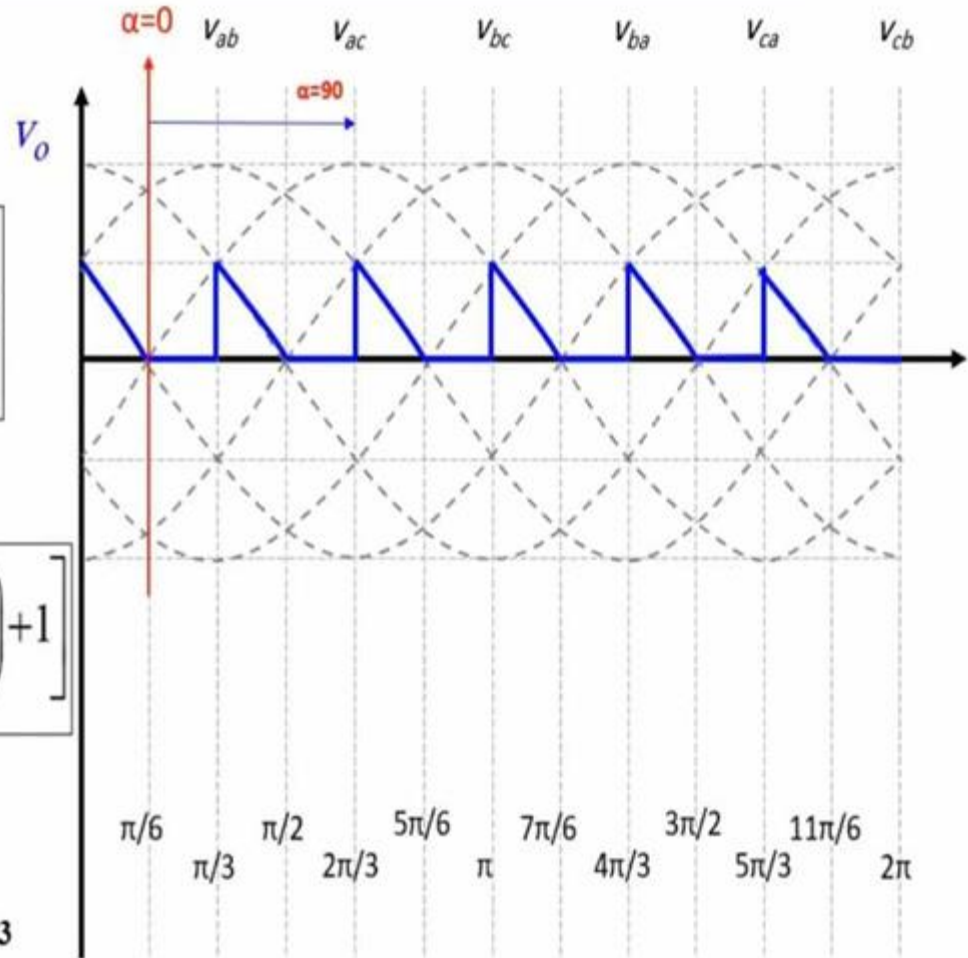
$$v_{avg} = \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \left[ \cos\left(\frac{\pi}{6} + \alpha\right) + 1 \right]$$



# Output voltage of controlled Rectifier

R load

$$0 \leq \alpha \leq 60$$


$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{2\pi/3+\alpha} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \cos(\alpha)$$

$$60 \leq \alpha < 120$$


$$V_{avg} = \frac{3}{\pi} \int_{\pi/3+\alpha}^{\pi} V_{mL} \sin(\omega t) d\omega t = \frac{3V_{mL}}{\pi} \left[ \cos\left(\frac{\pi}{6} + \alpha\right) + 1 \right]$$

$$0 \leq \alpha < 120$$

$$V_{avg} = +ve \quad \alpha < 120$$

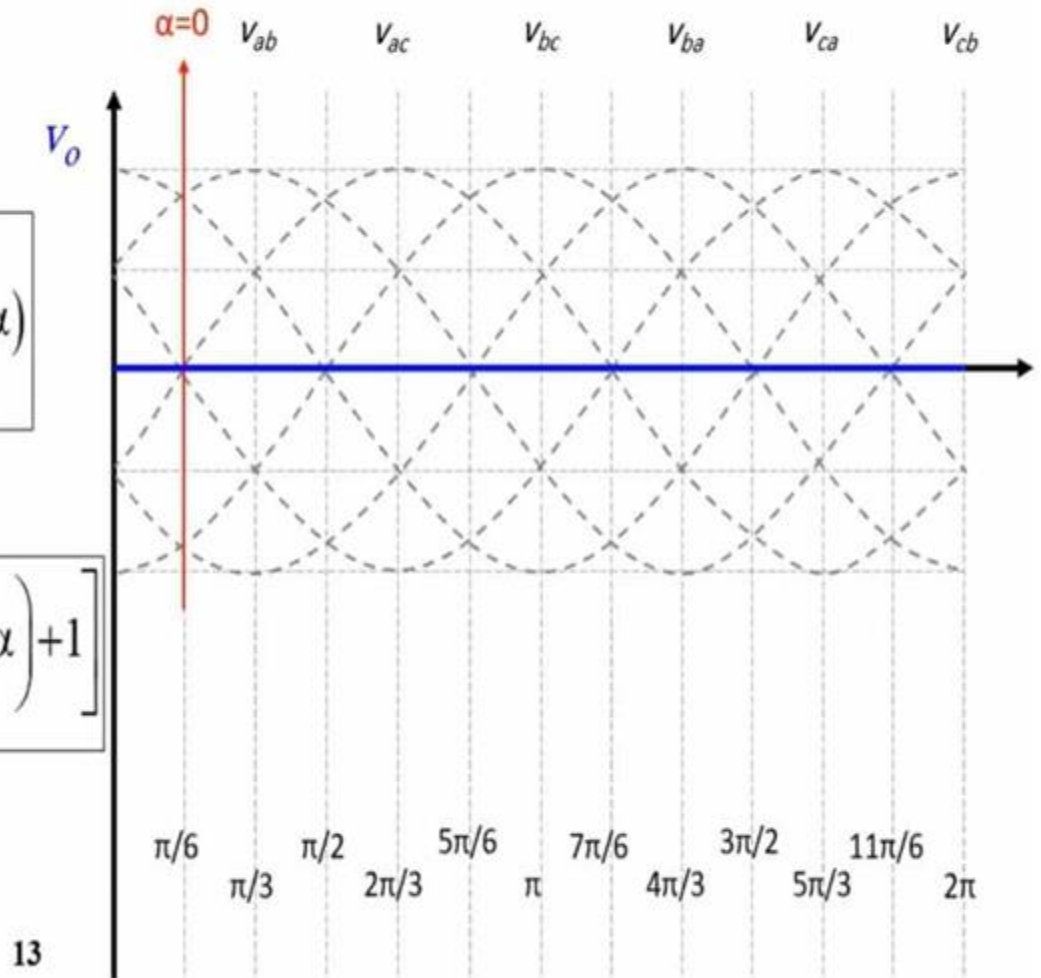

# 3 phase full wave controlled rectifier

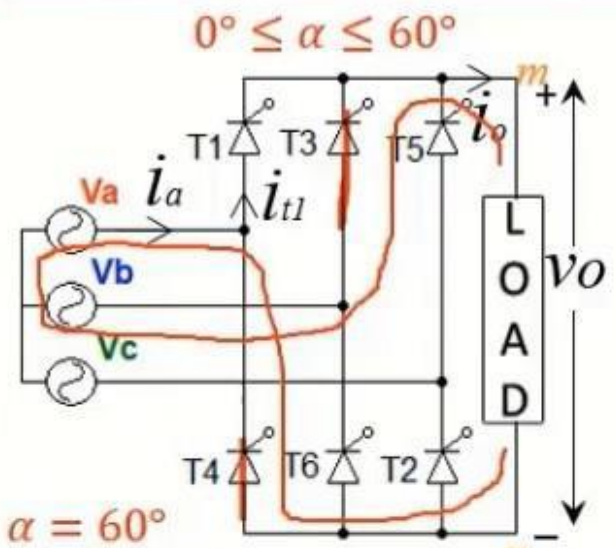

$\alpha = 60^\circ$

$\omega t = 90^\circ \text{ to } 150^\circ$ , T1 and T6 conduct  
 $V_o = V_{ab}$

$\omega t = 150^\circ \text{ to } 210^\circ$ , T1 and T2 conduct  
 $V_o = V_{ac}$

$\omega t = 210^\circ \text{ to } 270^\circ$ , T2 and T3 conduct  
 $V_o = V_{bc}$

$\omega t = 270^\circ \text{ to } 330^\circ$ , T3 and T4 conduct  
 $V_o = V_{ba}$

$\omega t = 330^\circ \text{ to } 390^\circ$ , T4 and T5 conduct  
 $V_o = V_{ca}$

$\omega t = 390^\circ \text{ to } 450^\circ$  T5 and T6 conduct  
 $V_o = V_{cb}$

*A Karmaka*

