



AC TO AC CONVERETERS

SINGLE PHASE AC VOLTAGE REGULATORS

Eng :Eman Abu Hany

AC – AC Converter


AC Voltage Controllers: Phase Control

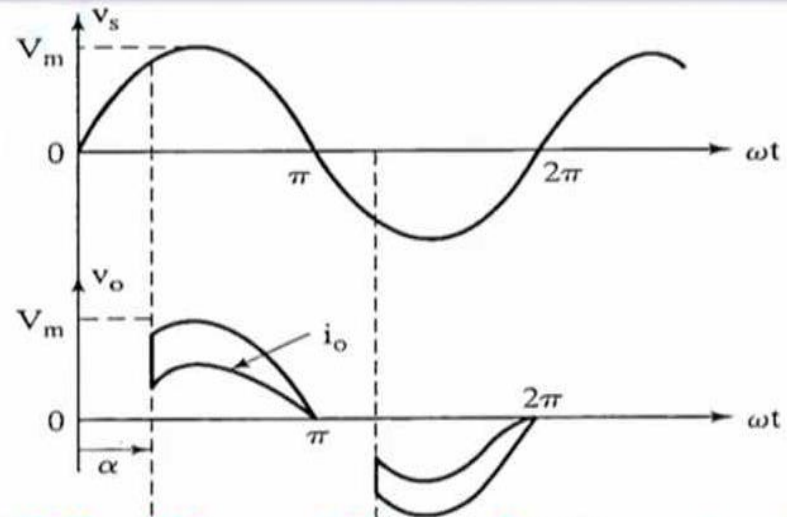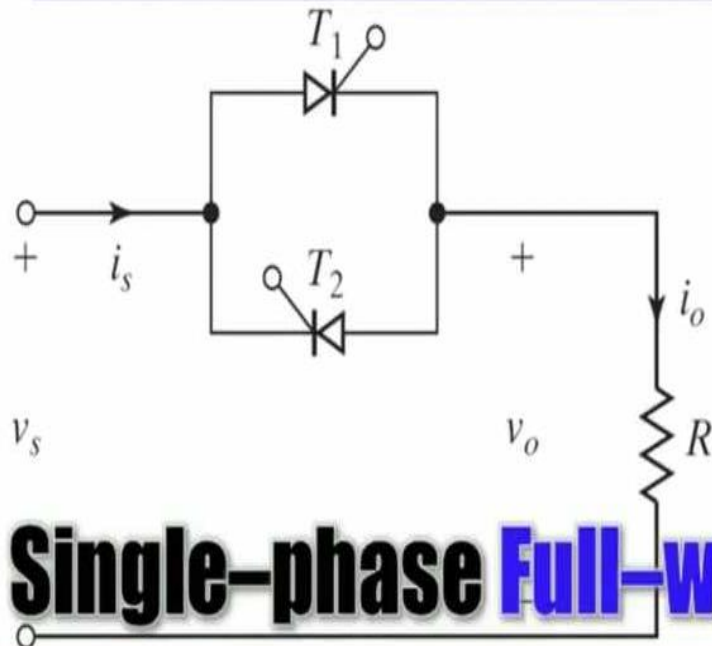


Single-phase Full-wave (Bi-directional) Controller

❑ The principle of **phase** control can be explained with the following single-phase **full-wave (bi-directional) controller**



❑ For Resistive Load:







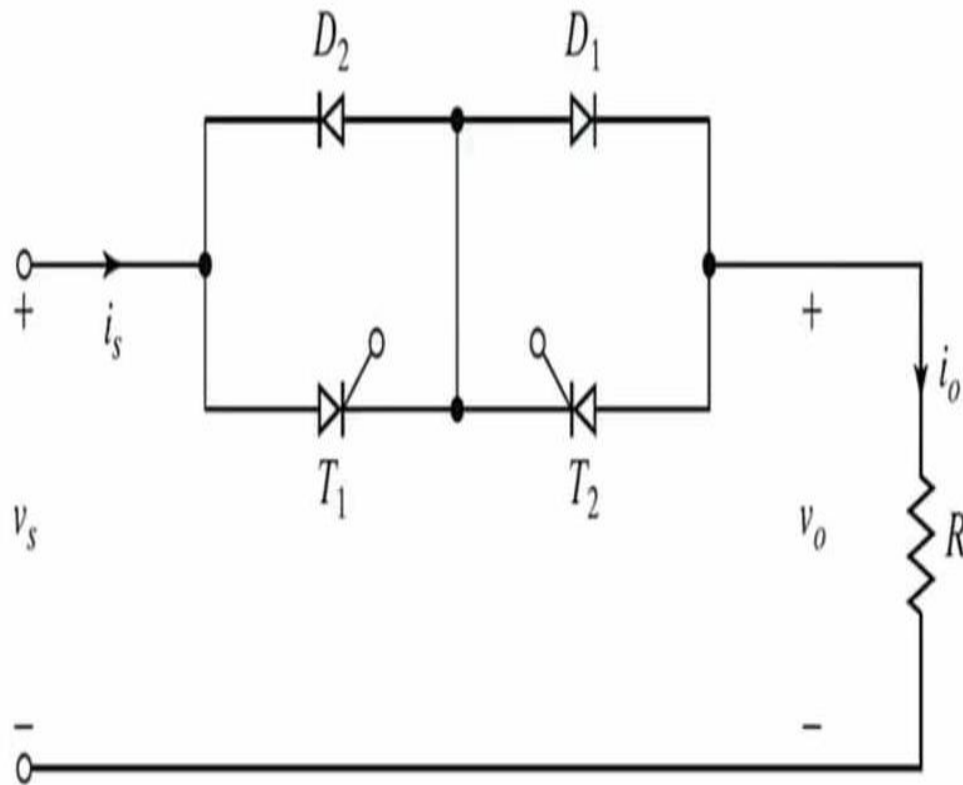





With single common cathode



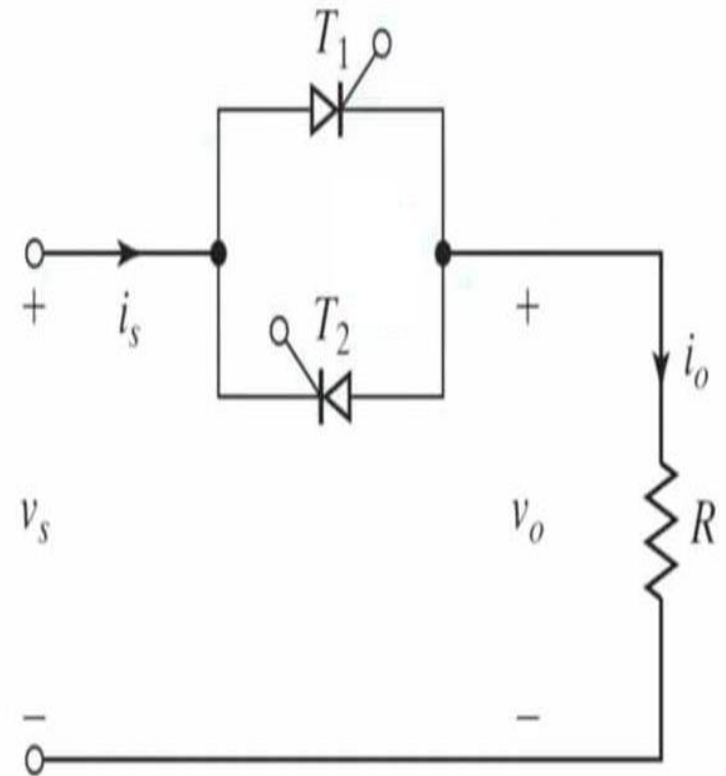


Principle of Phase Control

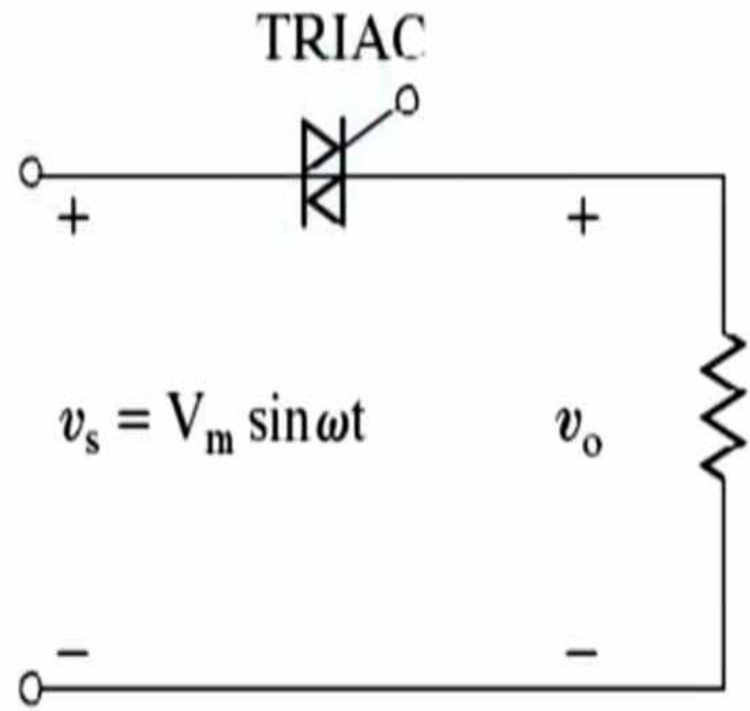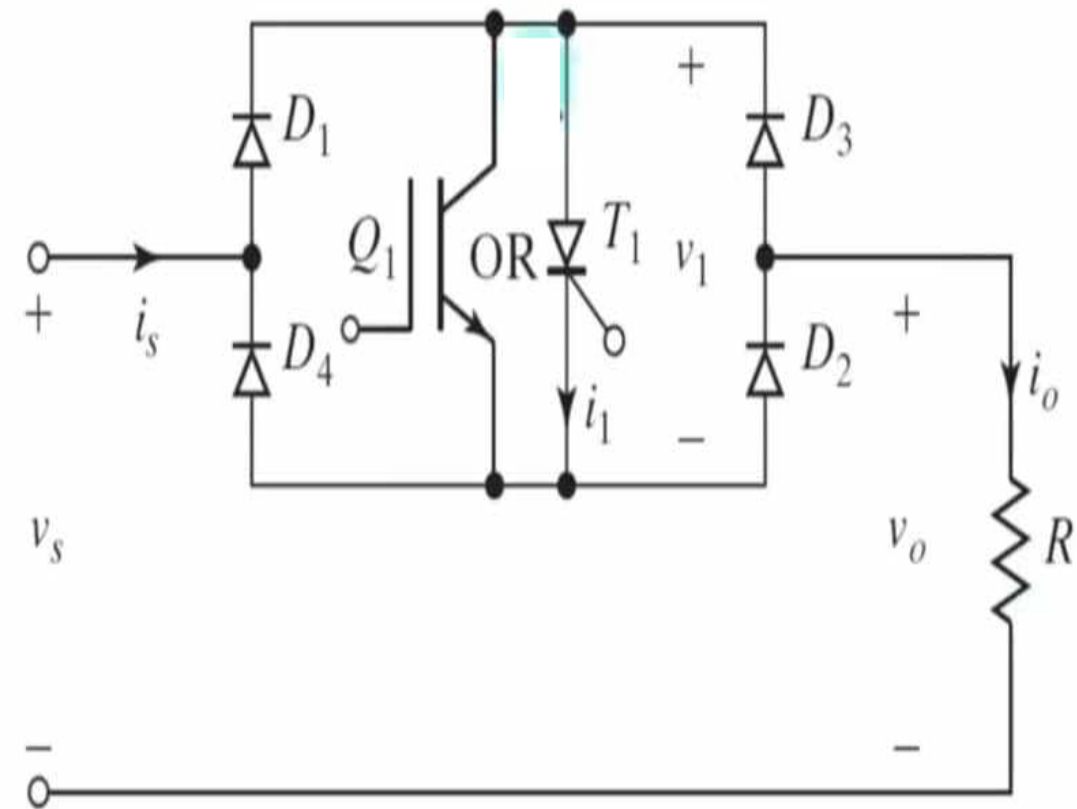

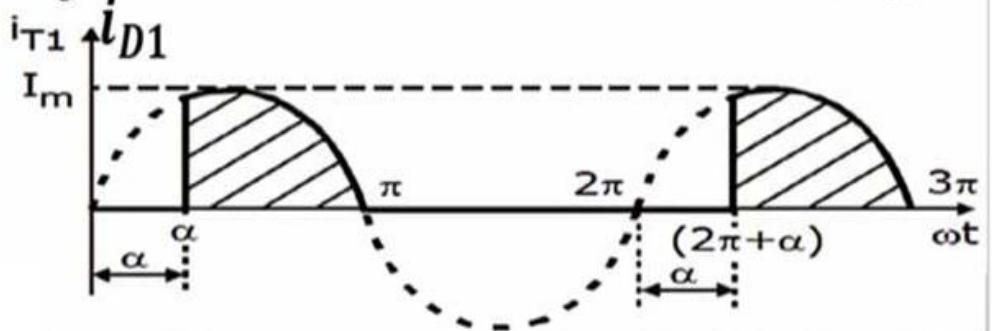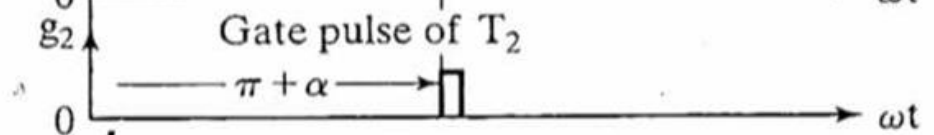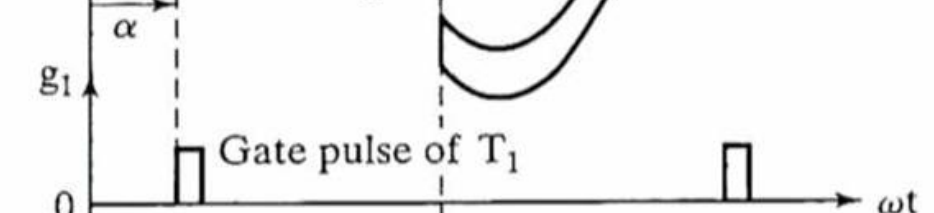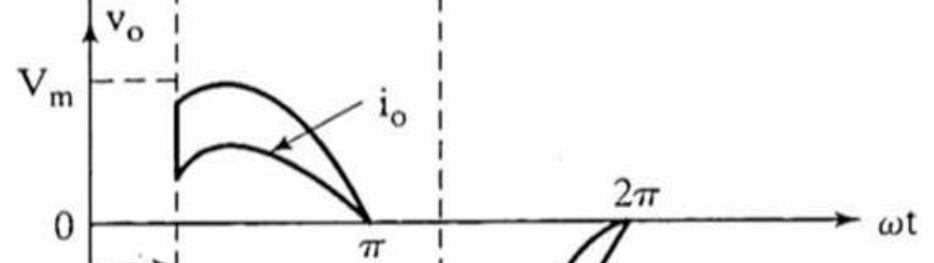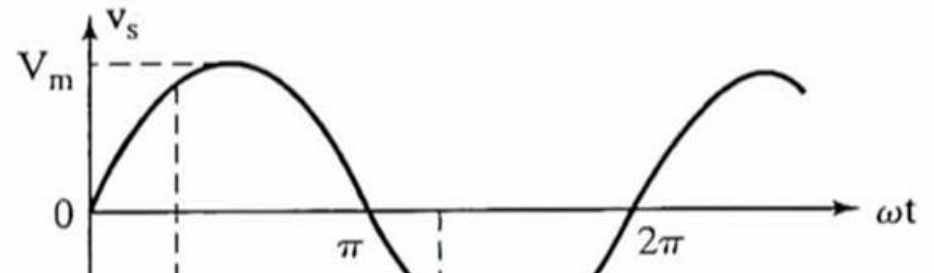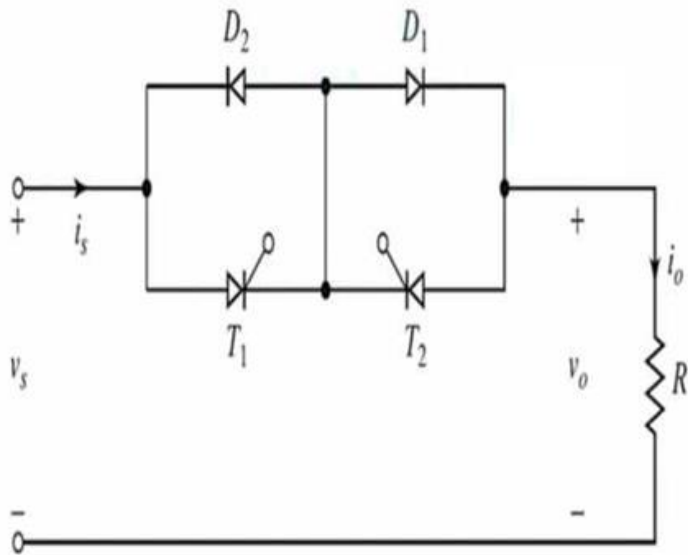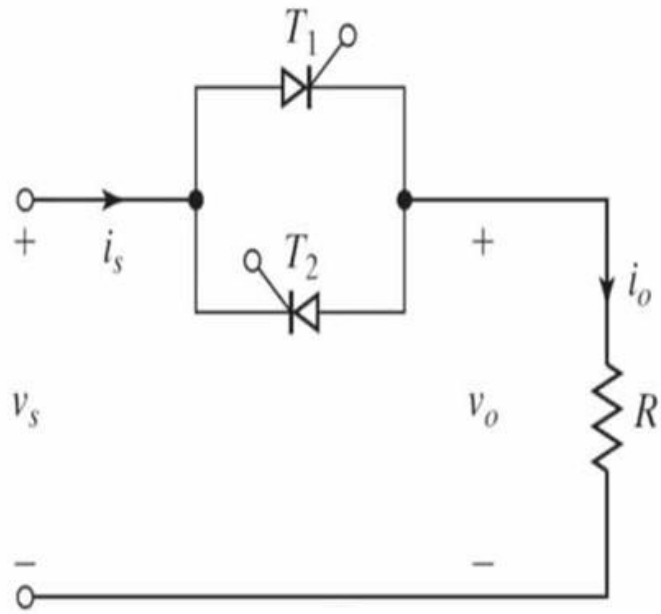

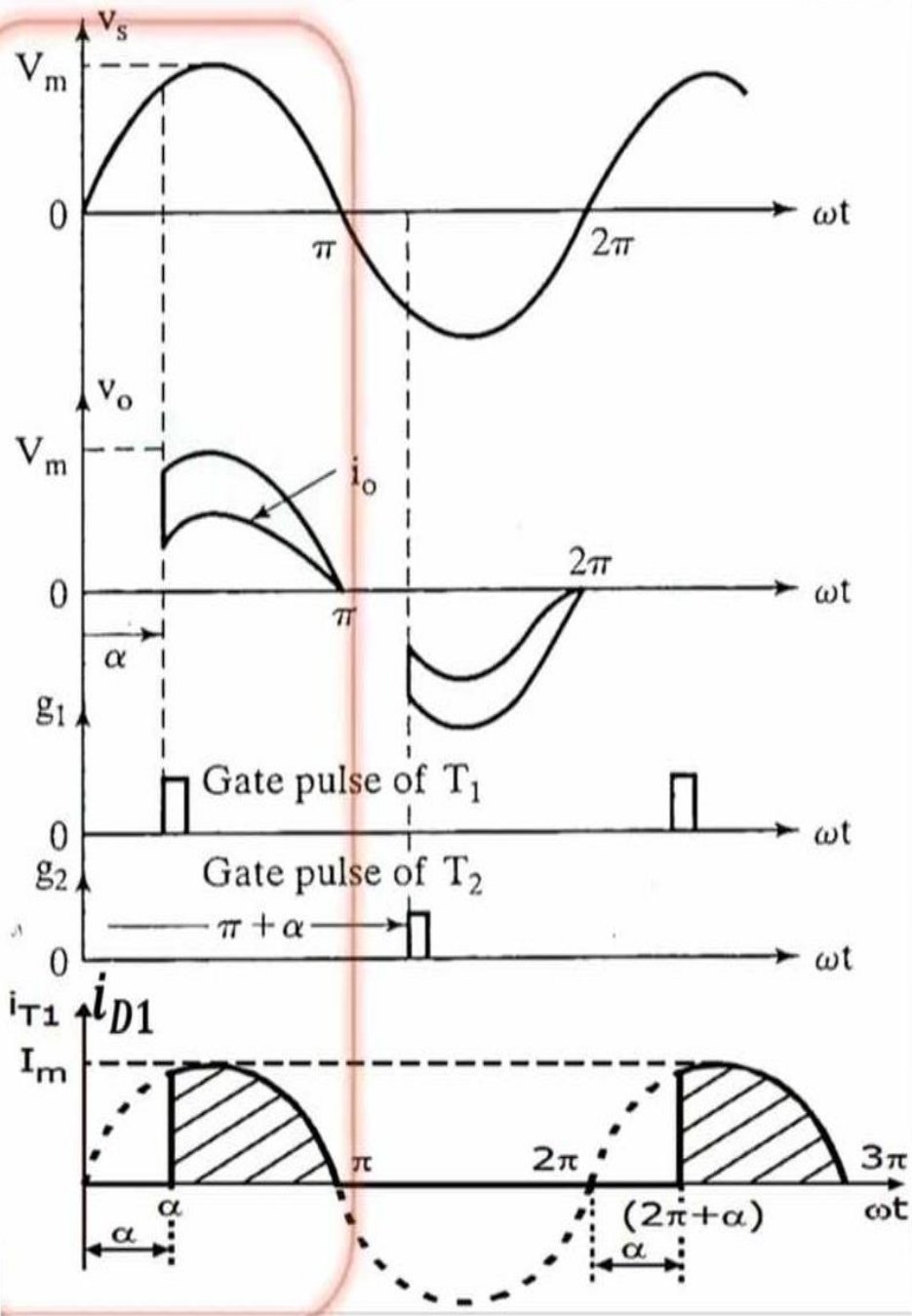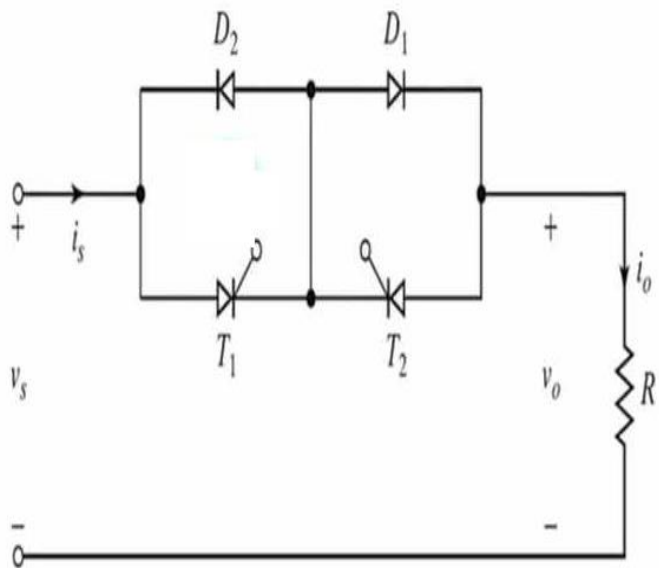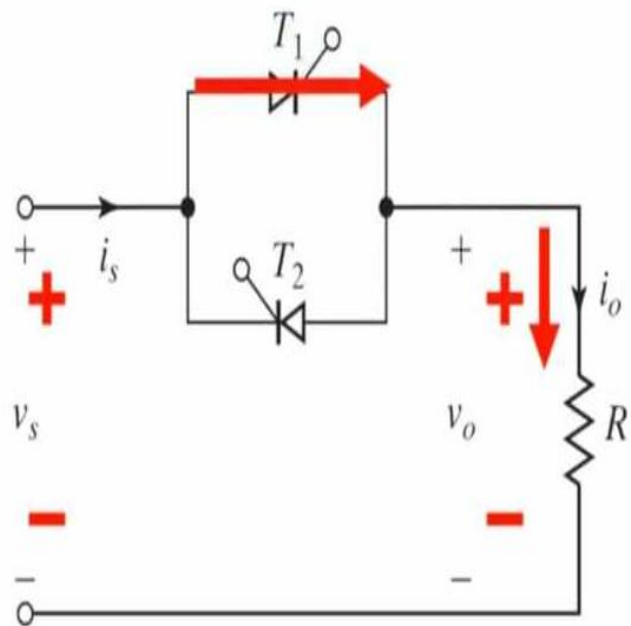

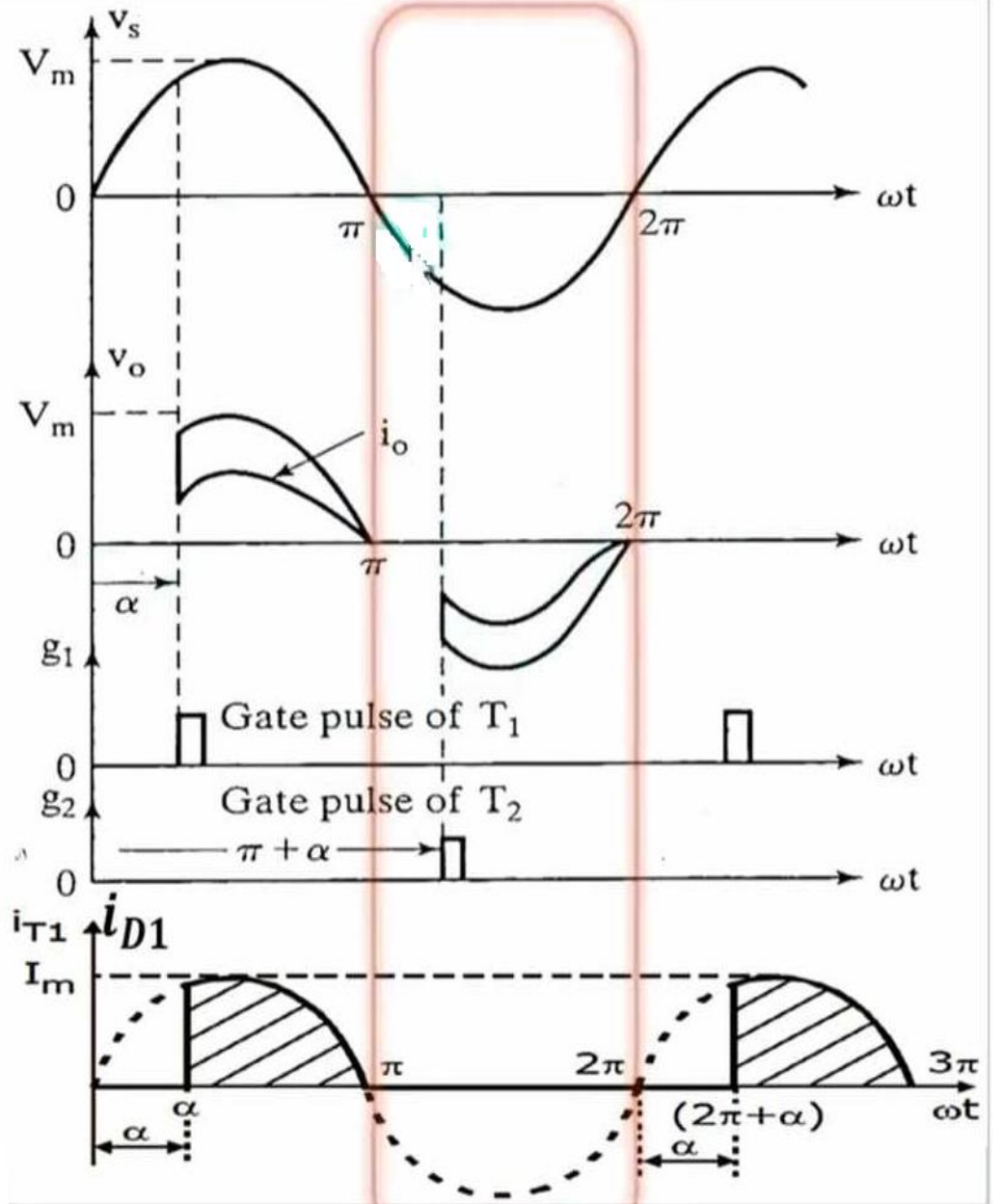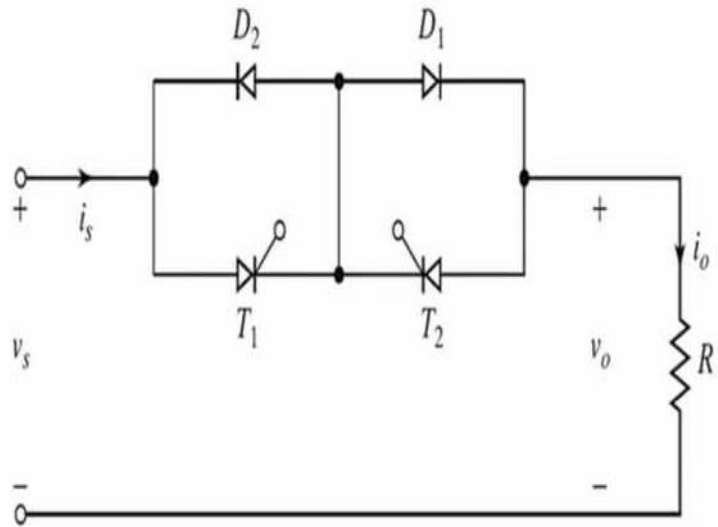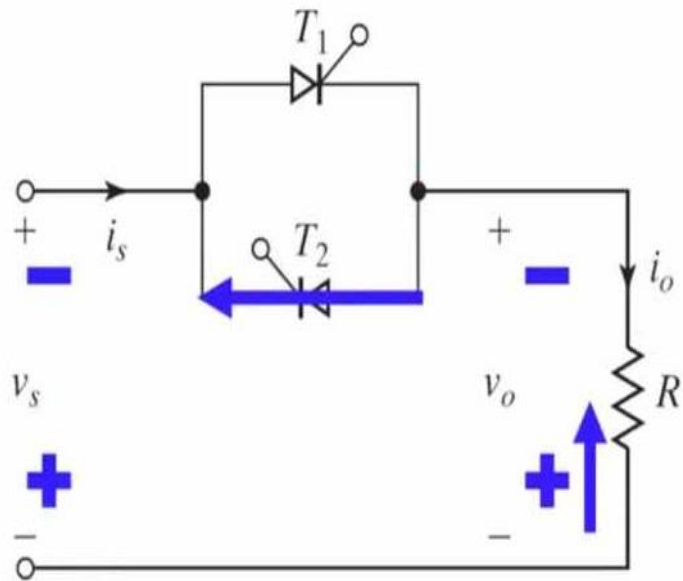


- For sinusoidal wave input supply Voltage:

$$v_s = V_m \sin\omega t = \sqrt{2} V_{s(RMS)} \sin\omega t$$

$$V_{s(RMS)} = V_s = V_m / \sqrt{2}$$

$$V_{s(Avg)} = V_{s(DC)} = 0$$

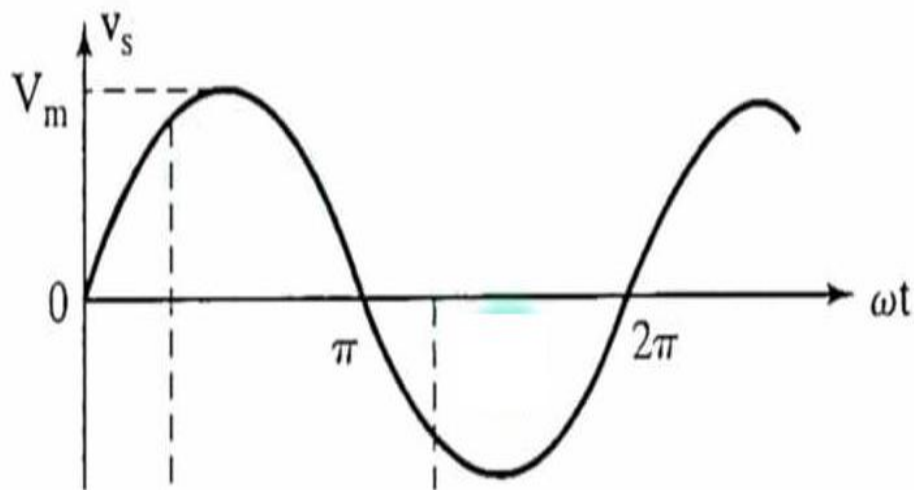

▪ The Average Output Load Voltage:

$$V_{o(Avg)} = \frac{1}{2\pi} \int_0^{2\pi} v_o d\omega t$$

$$= \frac{1}{2\pi} \left(\int_{\alpha}^{\pi} V_m \sin\omega t + \int_{\pi+\alpha}^{2\pi} V_m \sin\omega t \right) d\omega t$$


$$= \frac{-V_m}{2\pi} \left[(\cos\omega t) \Big|_{\alpha}^{\pi} + (\cos\omega t) \Big|_{\pi+\alpha}^{2\pi} \right]$$

$$= \frac{-V_m}{2\pi} \left((\cos(\pi) - \cos(\alpha)) + (\cos(2\pi) - \cos(\pi + \alpha)) \right)$$

$$= \frac{-V_m}{2\pi} \left((-1 - \cos(\alpha)) + (1 + \cos(\alpha)) \right) = 0$$

$$I_{o(Avg)} = \frac{1}{2\pi} \int_0^{2\pi} i_o d\omega t = \frac{1}{2\pi} \left(\int_{\alpha}^{\pi} I_m \sin\omega t + \int_{\pi+\alpha}^{2\pi} I_m \sin\omega t \right) d\omega t = 0$$
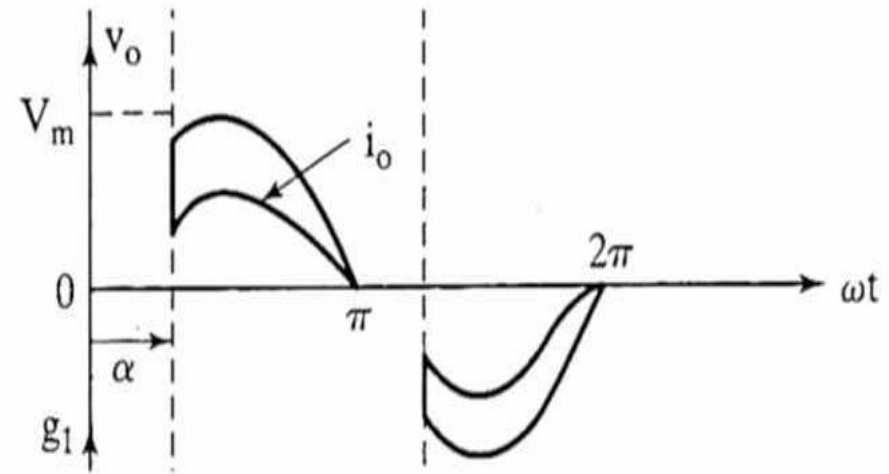
$$I_{o(Avg)} = I_s(Avg) = \frac{V_{o(Avg)}}{R} = 0$$



■ The RMS Output Load Voltage:

$$V_{o(RMS)} = \left(\frac{1}{2\pi} \int_0^{2\pi} v_o^2 d\omega t \right)^{1/2}$$


$$= \left(\frac{1}{2\pi} \left(\int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t + \int_{\pi+\alpha}^{2\pi} V_m^2 \sin^2 \omega t \right) d\omega t \right)^{1/2}$$

$$= \left(\frac{2}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d\omega t \right)^{1/2} = \left(\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} \frac{1}{2} (1 - \cos 2\omega t) d\omega t \right)^{1/2}$$

$$= \left(\frac{V_m^2}{2\pi} \left(\omega t - \frac{1}{2} \sin 2\omega t \right) \Big|_{\alpha}^{\pi} \right)^{1/2} = \left(\frac{V_m^2}{2\pi} \left(\left(\pi - \frac{1}{2} \sin(2\pi) \right) - \left(\alpha - \frac{1}{2} \sin(2\alpha) \right) \right) \right)^{1/2}$$

$$= \frac{V_m}{\sqrt{2}} \left(\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right) \right)^{1/2} = V_s \left(\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right) \right)^{1/2}$$
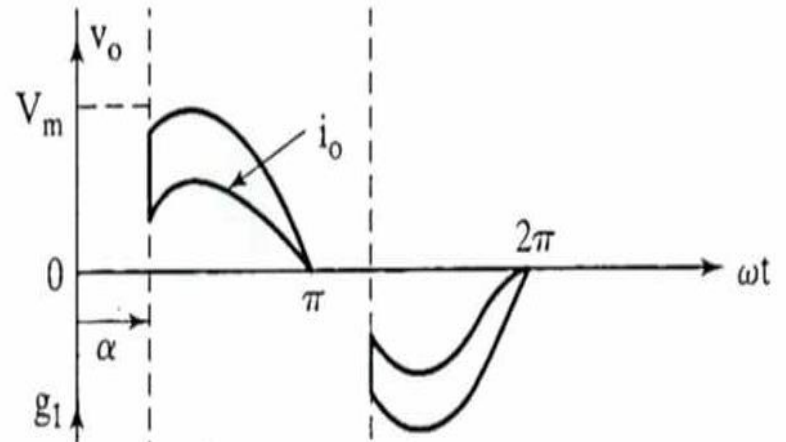
$$I_{o(RMS)} = \frac{V_{o(RMS)}}{R} = \frac{I_m}{\sqrt{2}} \left(\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right) \right)^{1/2}$$




- RMS value of output (**Load**) voltage, $V_o(RMS)$:

$$V_o(RMS) = V_s \sqrt{\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right)}$$

$$\alpha = 0^\circ \Rightarrow V_o(RMS) = 100\% V_s \text{ (Max output)}$$

$$\alpha = 180^\circ \Rightarrow V_o(RMS) = 0\% V_s \text{ (mini output)}$$

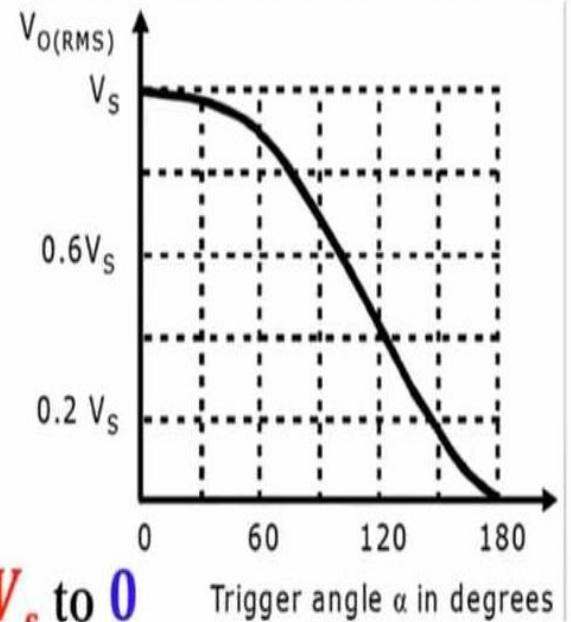- By varying α from **0** to π , V_o can be varied from V_s to **0**




- Power Factor, **PF**:

$$PF = \frac{V_o(RMS)}{V_s(RMS)} = \sqrt{\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right)}$$

- RMS Source & Load Current:
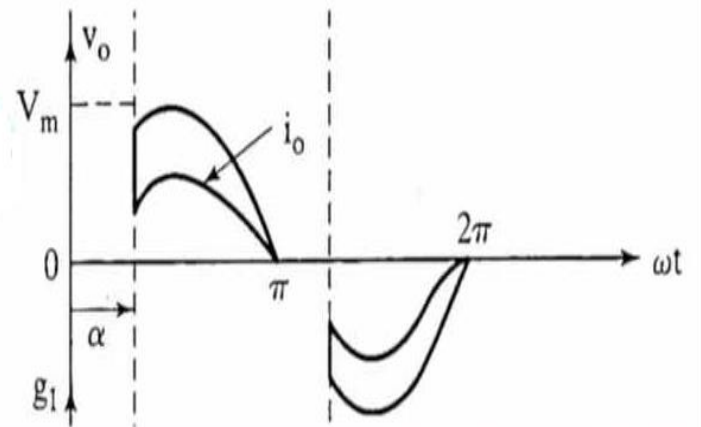
$$I_o(RMS) = I_s(RMS) = \frac{V_o(RMS)}{R}$$



- Average Output (AC) Load Power:

$$P_{o(Avg)} = I_{o(RMS)}^2 R = \frac{V_{o(RMS)}^2}{R} = I_{o(RMS)} V_{o(RMS)}$$

- Average Input Supply **Volt-Amperes**:

$$VA = I_{s(RMS)} V_{s(RMS)}$$


- Power Factor, **PF**, is:

$$PF = \frac{P_{o(Avg)}}{VA} = \frac{I_{o(RMS)} V_{o(RMS)}}{I_{s(RMS)} V_{s(RMS)}}$$

$$= \frac{V_{o(RMS)}}{V_{s(RMS)}} = \sqrt{\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right)}$$

$$\alpha = 0^\circ \Rightarrow PF = 1 \quad \rightarrow \quad P_{o(Avg)} = 100\% P_{s(Avg)} = 100\% VA$$
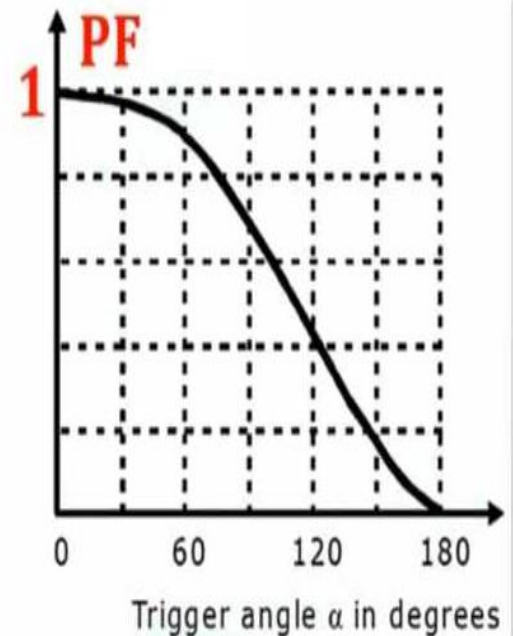
$$\alpha = 180^\circ \Rightarrow PF = 0 \quad \rightarrow \quad P_{o(Avg)} = 0\% P_{s(Avg)} = 0$$




▪ The Average Thyristor Current:

$$I_{T(Avg)} = \frac{1}{2\pi} \int_0^{2\pi} i_T d\omega t$$

$$= \frac{1}{2\pi} \int_{\alpha}^{\pi} I_m \sin\omega t d\omega t$$

$$= \frac{I_m}{2\pi} (-\cos\omega t) \Big|_{\alpha}^{\pi} = \frac{-I_m}{2\pi} (\cos(\pi) - \cos(\alpha)) = \frac{I_m}{2\pi} (1 + \cos(\alpha))$$

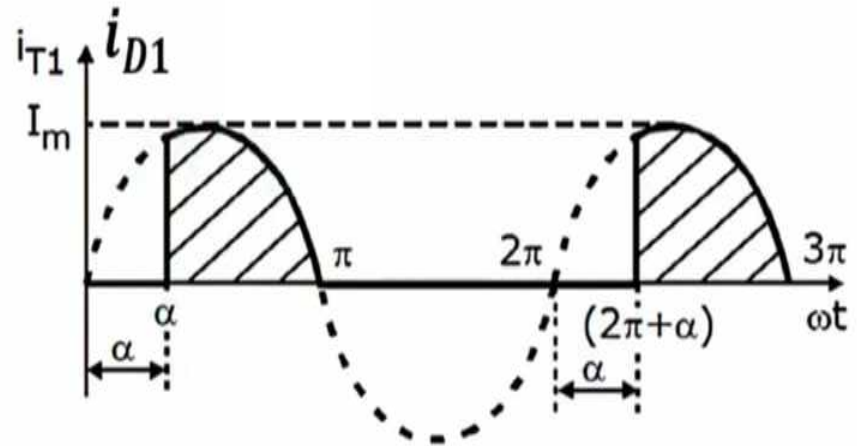

$$I_m = \frac{V_m}{R} = \frac{V_s \sqrt{2}}{R}$$

▪ The RMS Thyristor Current:


$$I_{T(RMS)} = \left(\frac{1}{2\pi} \int_0^{2\pi} i_T^2 d\omega t \right)^{1/2}$$

$$= \left(\frac{1}{2\pi} \int_{\alpha}^{\pi} I_m^2 \sin^2 \omega t d\omega t \right)^{1/2}$$

$$= \left(\frac{I_m^2}{2\pi} \int_{\alpha}^{\pi} \frac{1}{2} (1 - \cos 2\omega t) d\omega t \right)^{1/2} = \left(\frac{I_m^2}{4\pi} \left(\omega t + \frac{1}{2} \sin 2\omega t \right) \Big|_{\alpha}^{\pi} \right)^{1/2}$$



$$= \frac{I_m}{2} \left(\frac{1}{\pi} \left(\left(\pi + \frac{1}{2} \sin(2\pi) \right) - \left(\alpha + \frac{1}{2} \sin(2\alpha) \right) \right) \right)^{1/2}$$
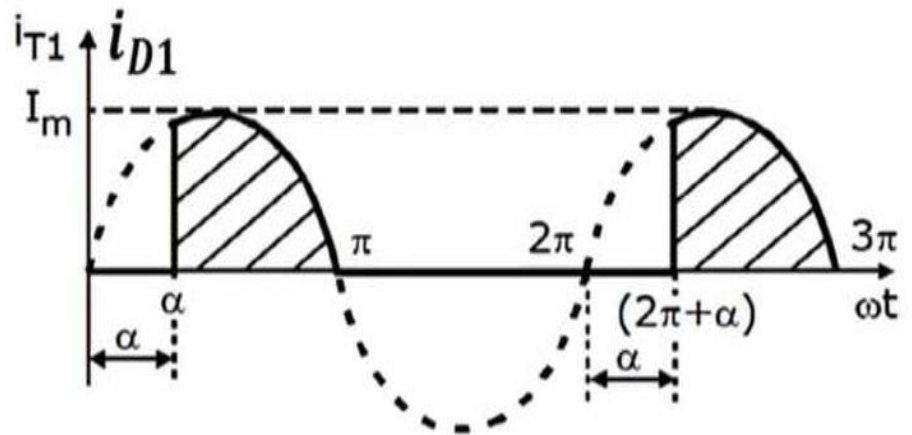
$$= \frac{I_m}{2} \left(\frac{1}{\pi} \left((\pi - \alpha) + \frac{1}{2} \sin(2\alpha) \right) \right)^{1/2}$$



$$I_m = \frac{V_m}{R} = \frac{V_s \sqrt{2}}{R}$$

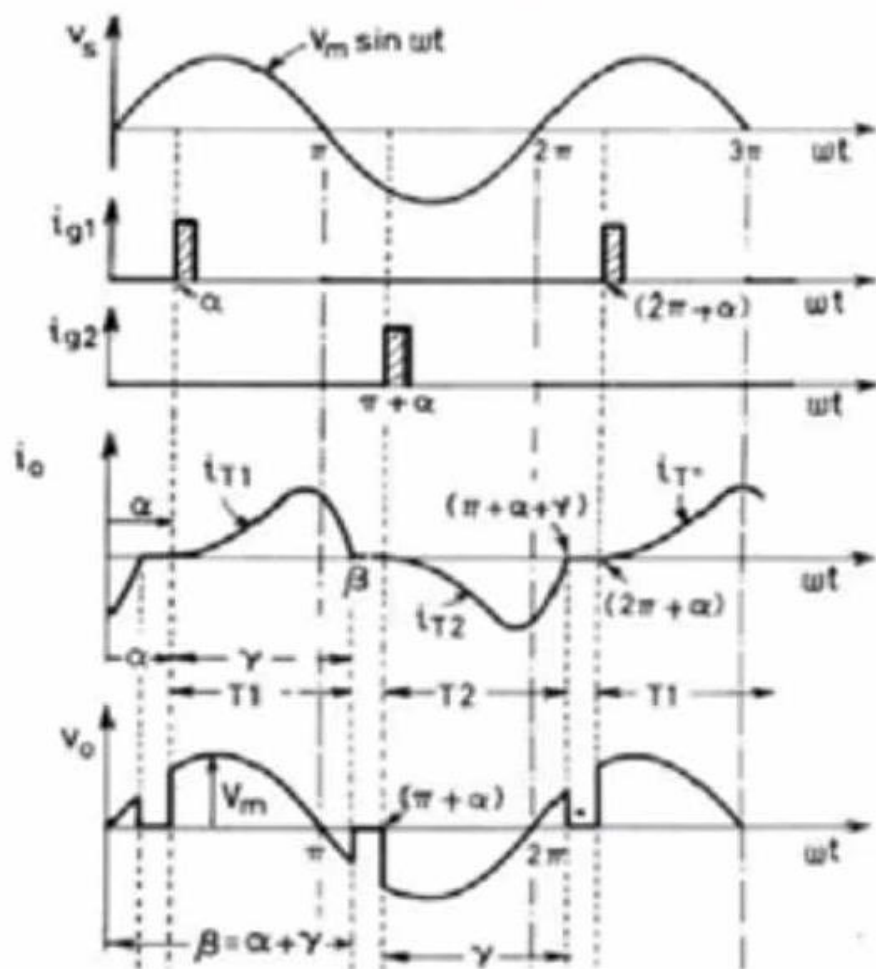
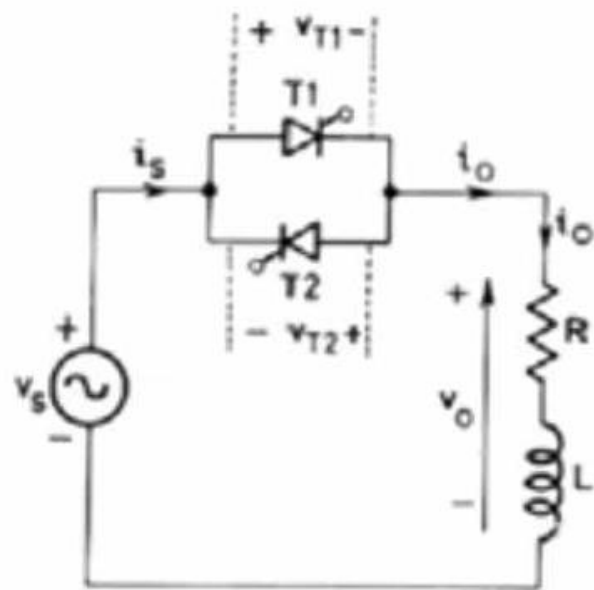
Single-phase AC voltage controller with inductive (RL) load



- The problem of dc input current can be prevented by using bidirectional or full-wave controller.
- the AC current pulses are periodic and symmetrical and there is no DC current component. The load voltage also does not have any DC component.
- The rms output voltage can be varied between 0% to 100%
- Suitable for loads with short time constants.
- The firing pulse (instants) of thyristors of T1 and T2 are 180 degrees apart, each occurring in its respective half cycle.
$$0 \leq \alpha \leq 180$$
- By controlling this instant of firing, the effective voltage occurring across the load can be varied.



AC – AC Converter

AC Voltage Controllers: ON – OFF Control

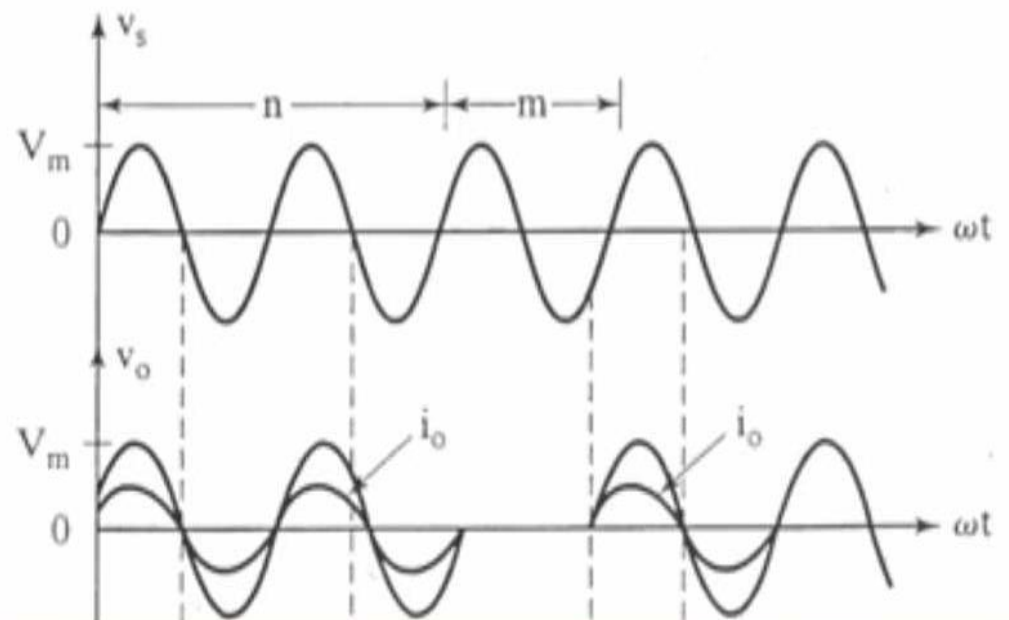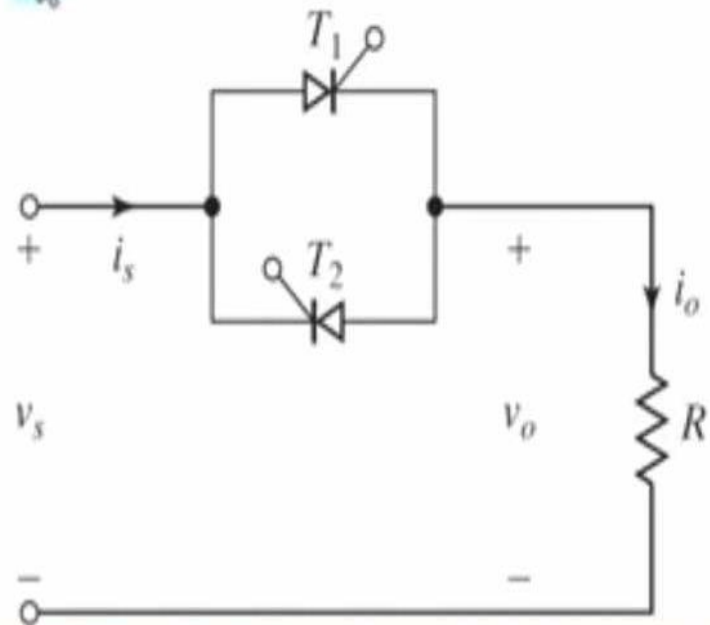



Principle of On – Off Control (Integral Cycle Control)


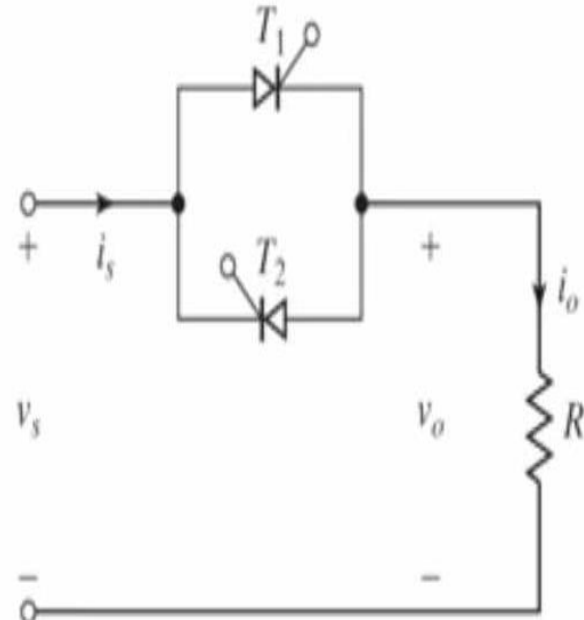
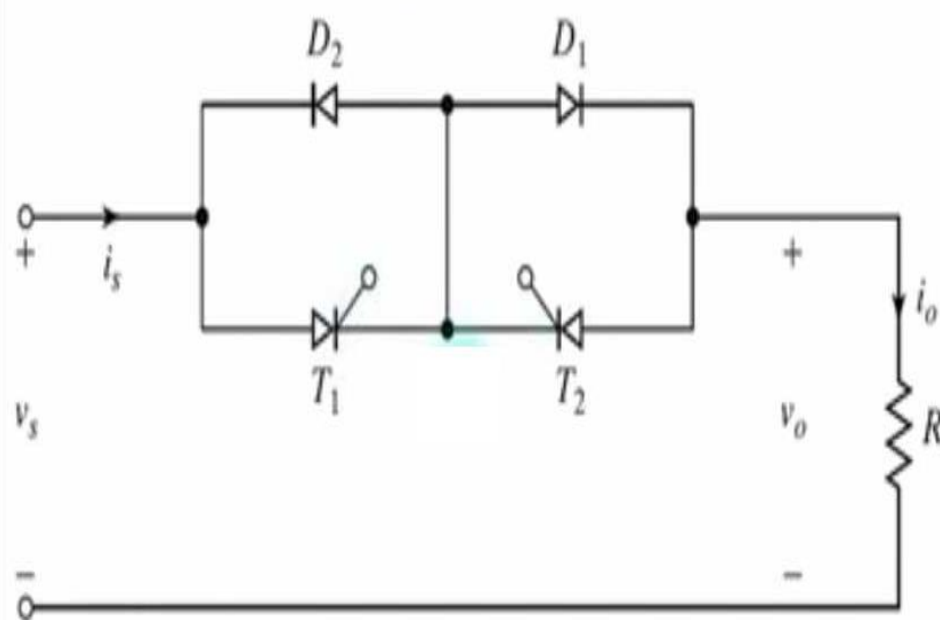
- ❑ The principle of **on-off** control can be explained with the following single-phase **full-wave (bi-directional)** controller
- ❑ For Resistive Load:






With single common cathode

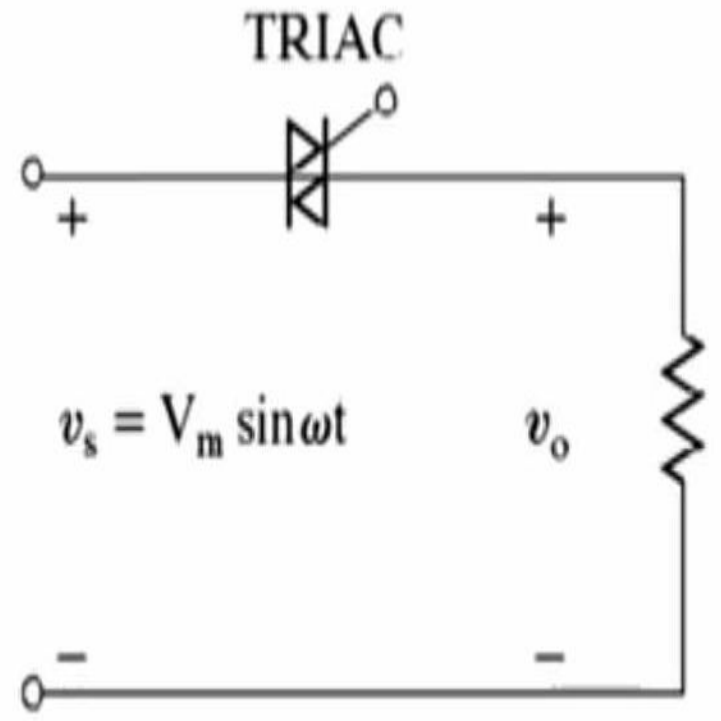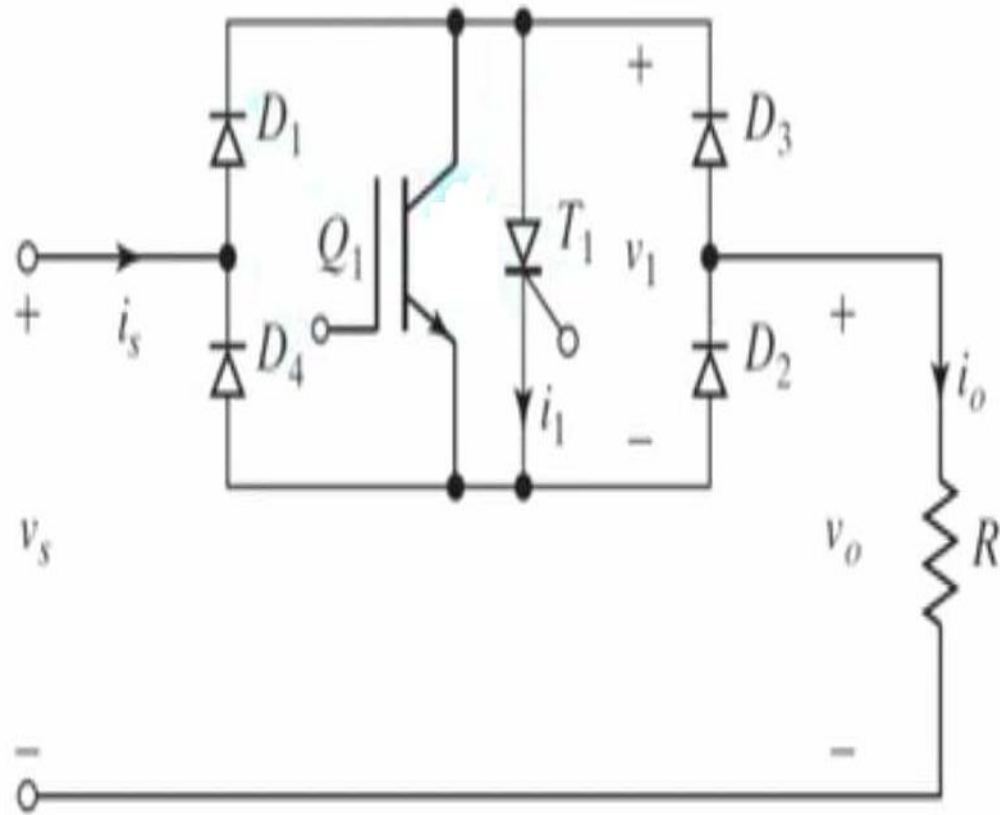Principle of On - Off Control (Integral Cycle Control)







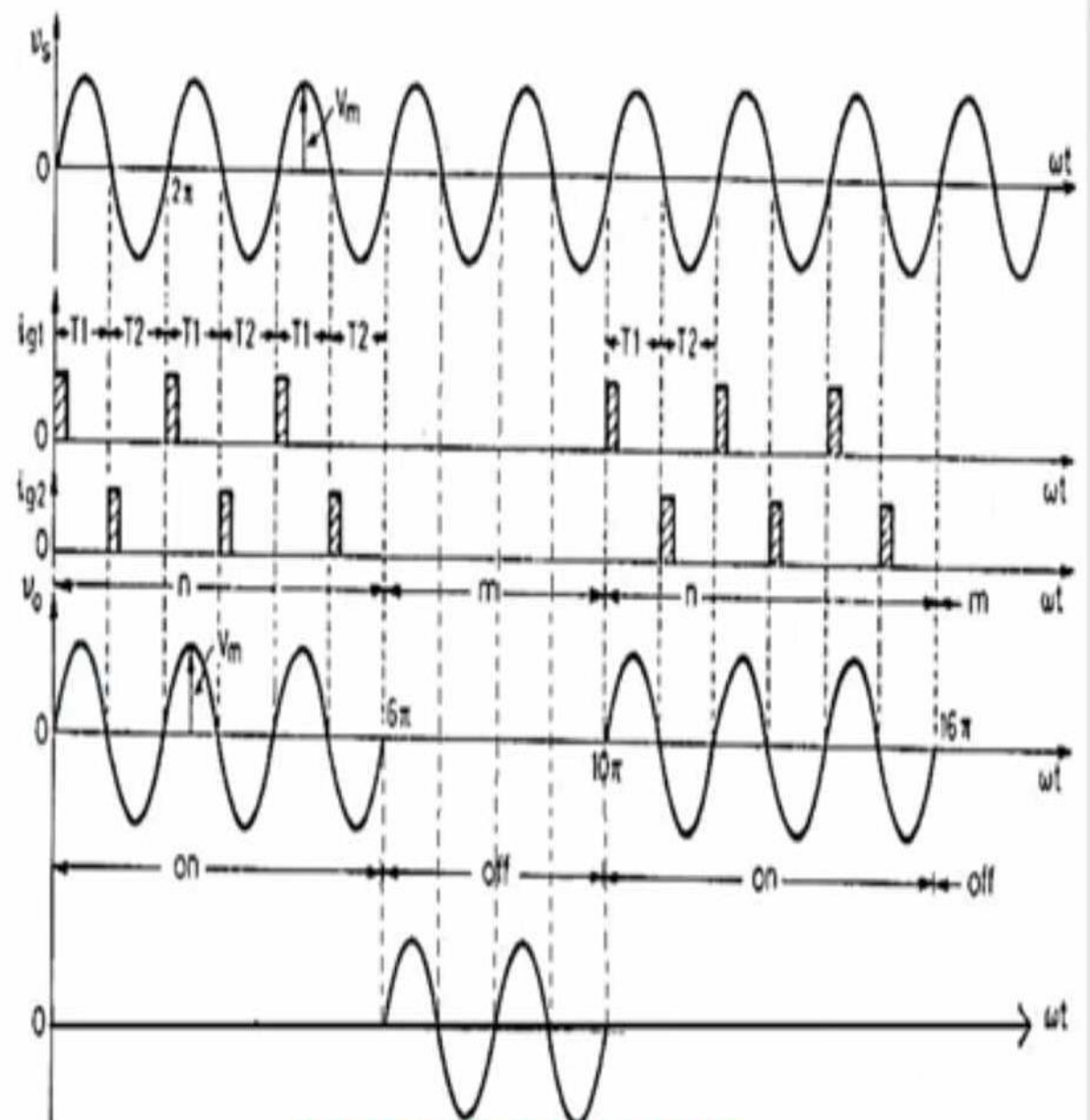
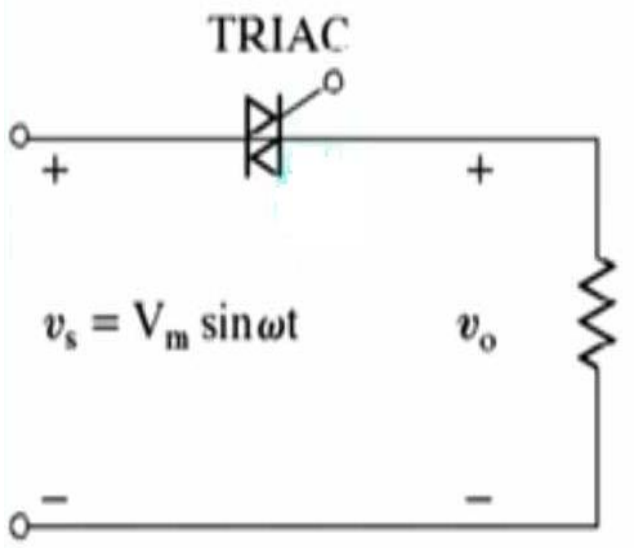
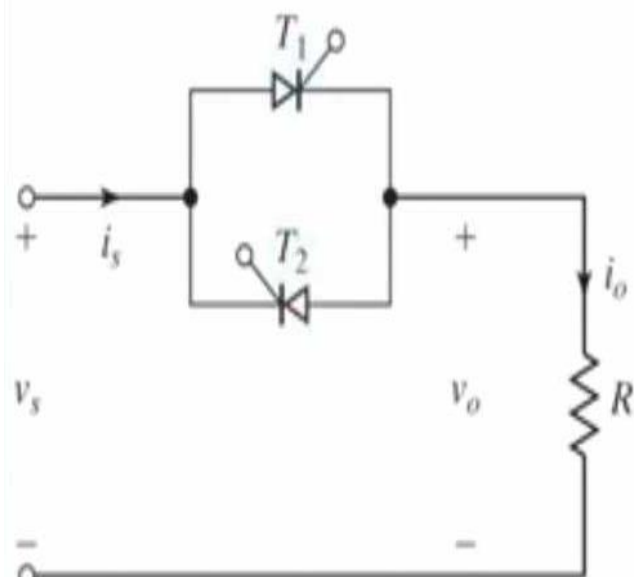


Voltage across thyristors & Triac

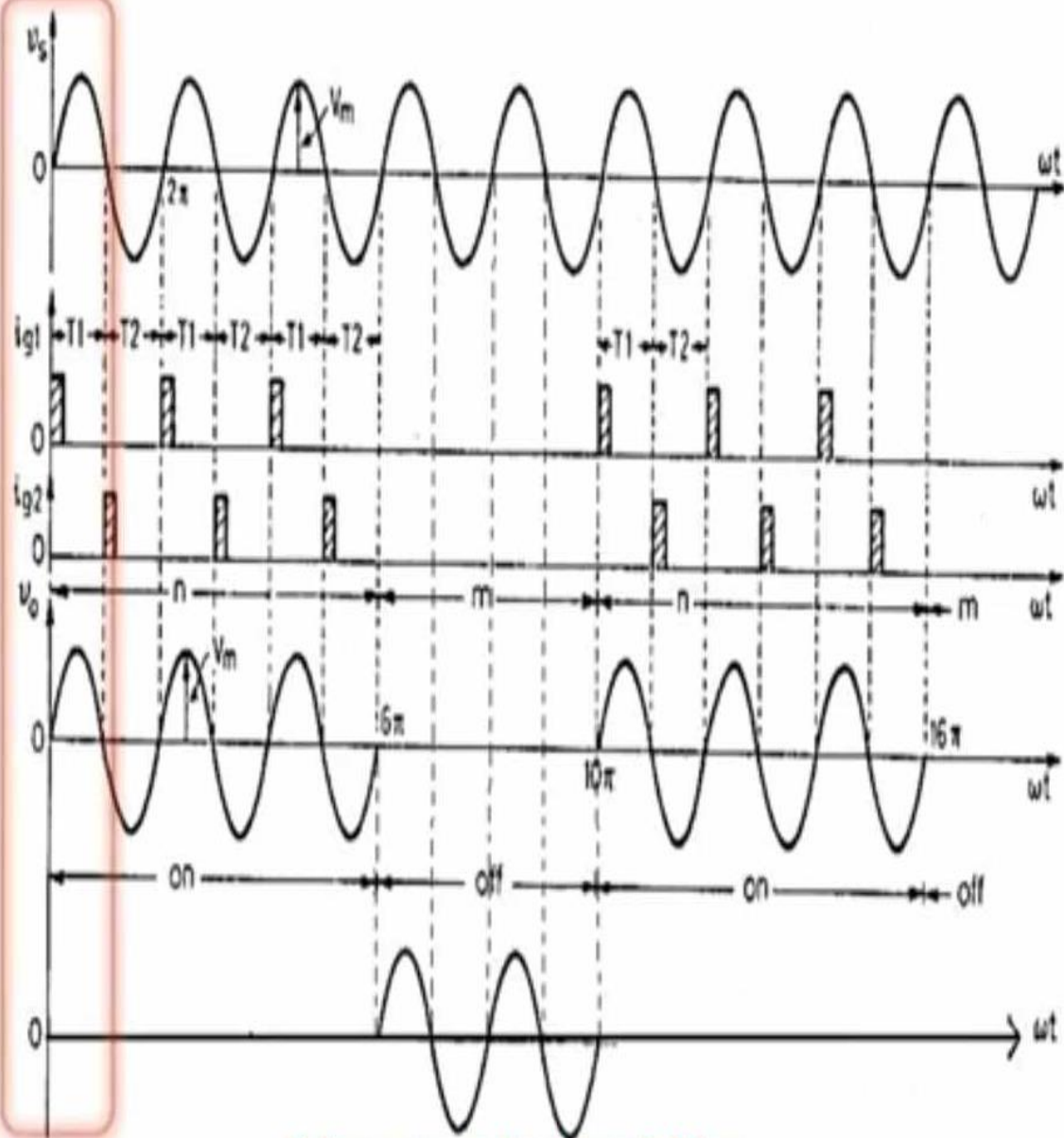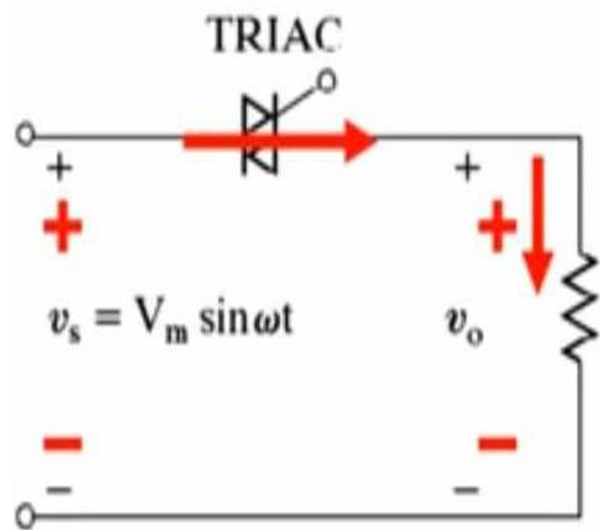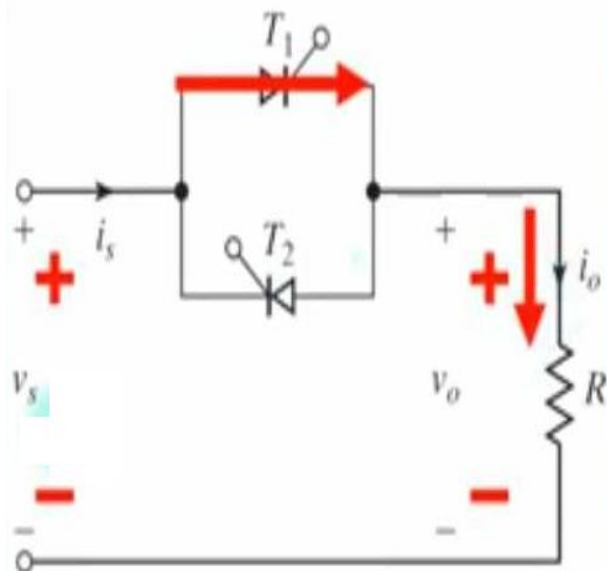





Voltage across thyristors & Triac

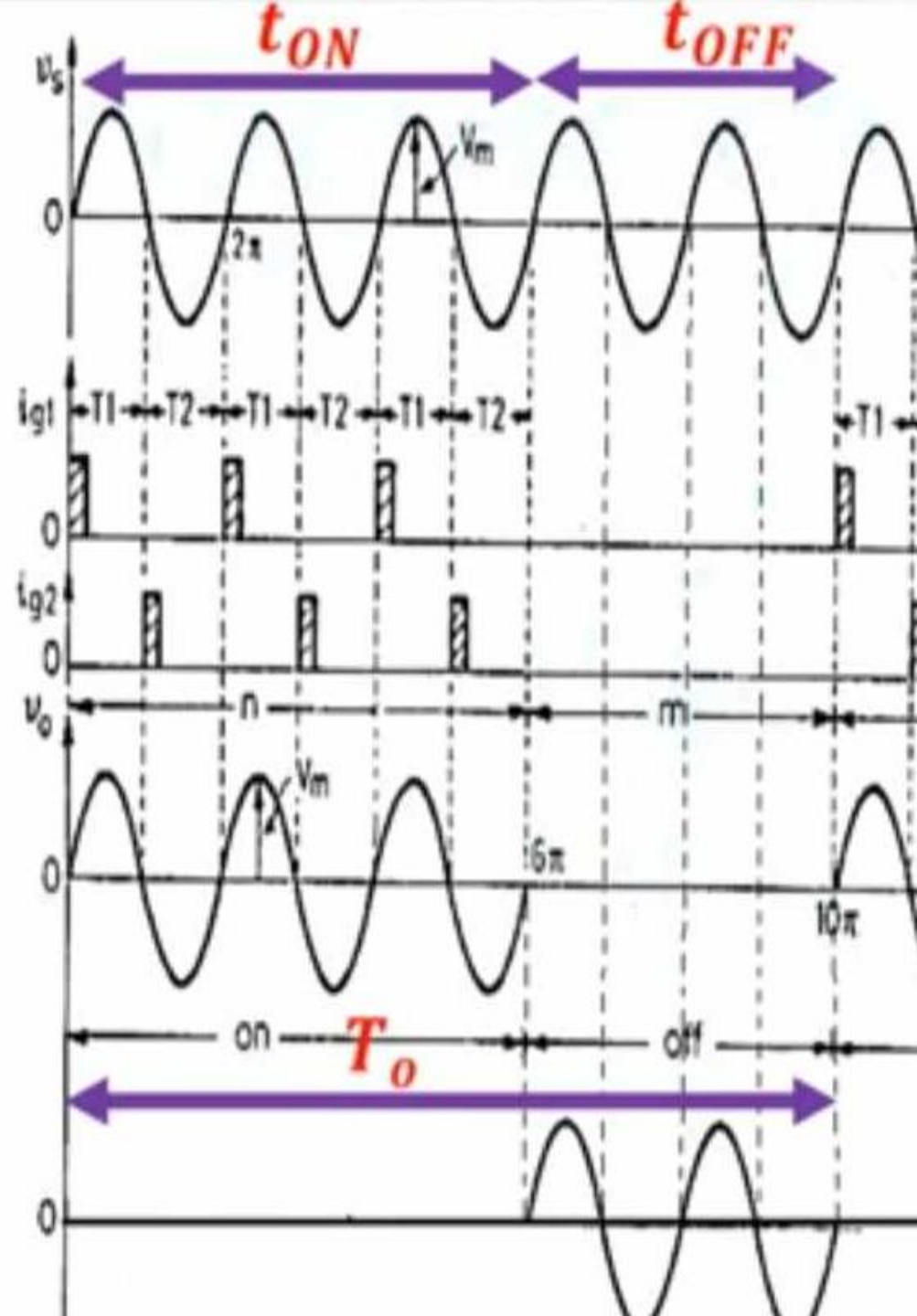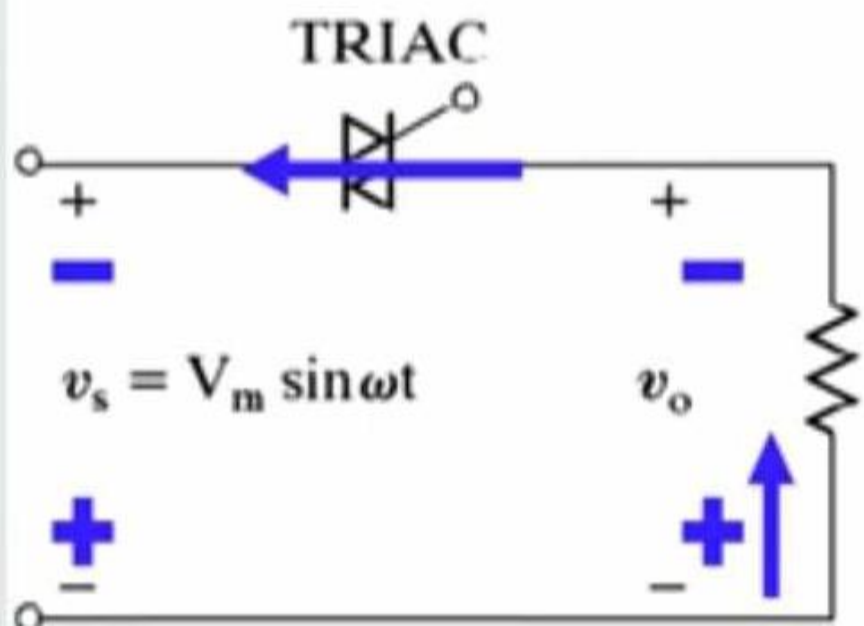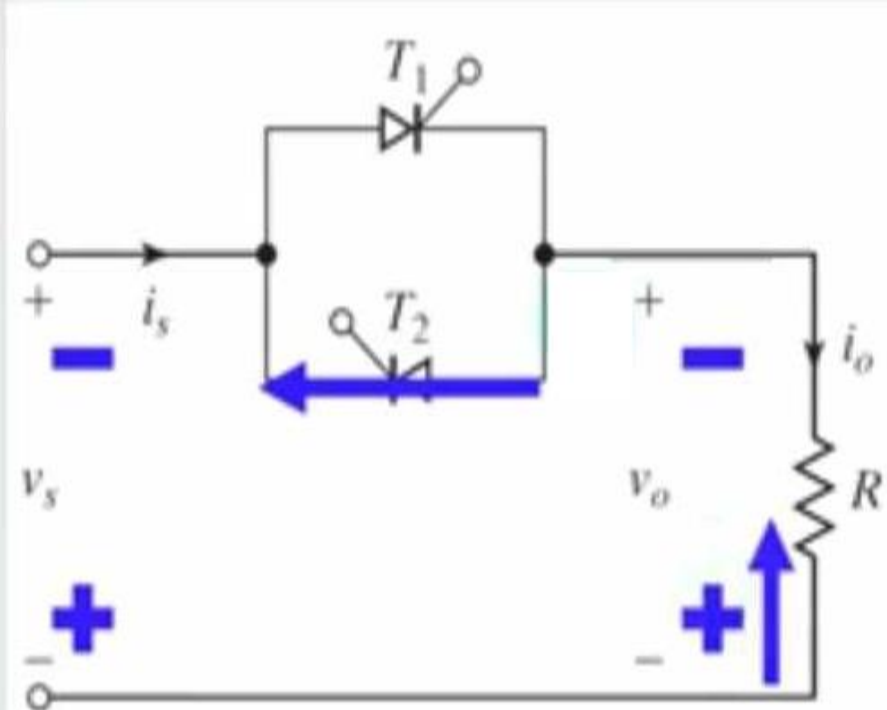

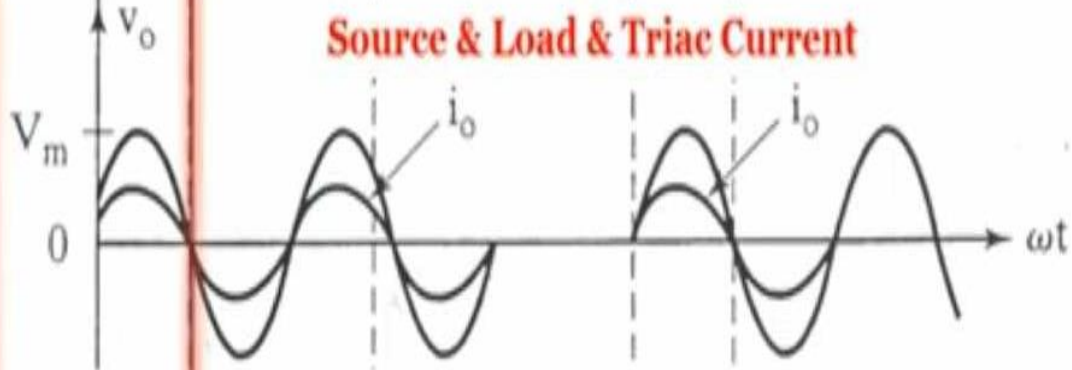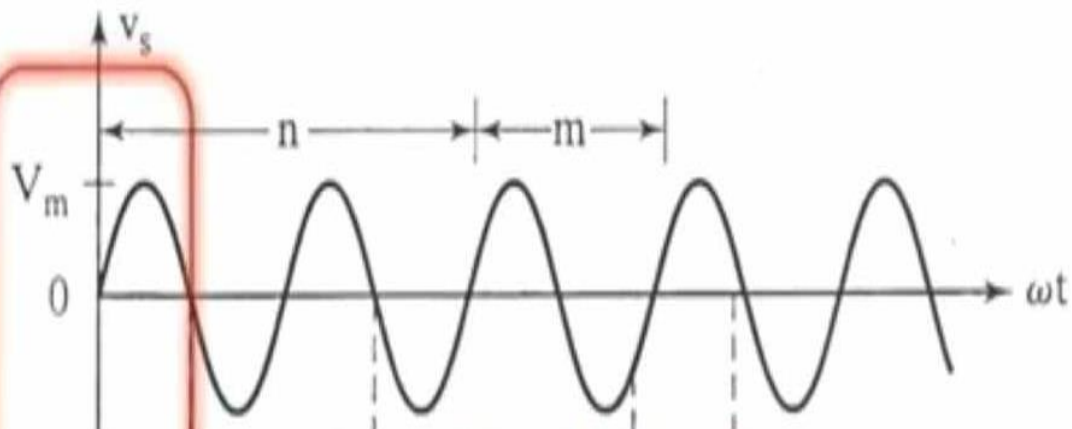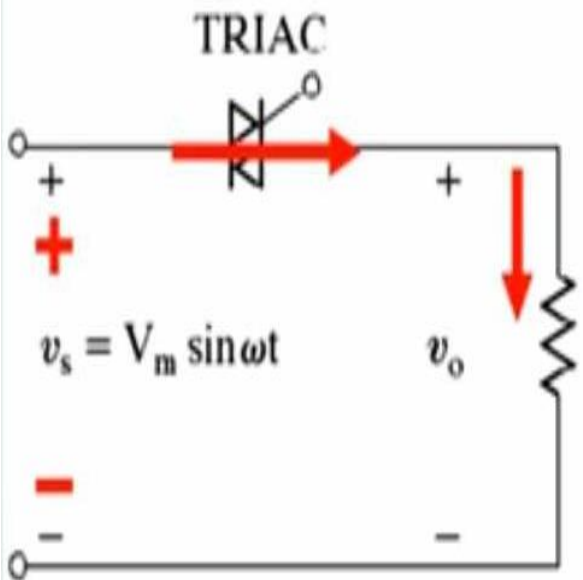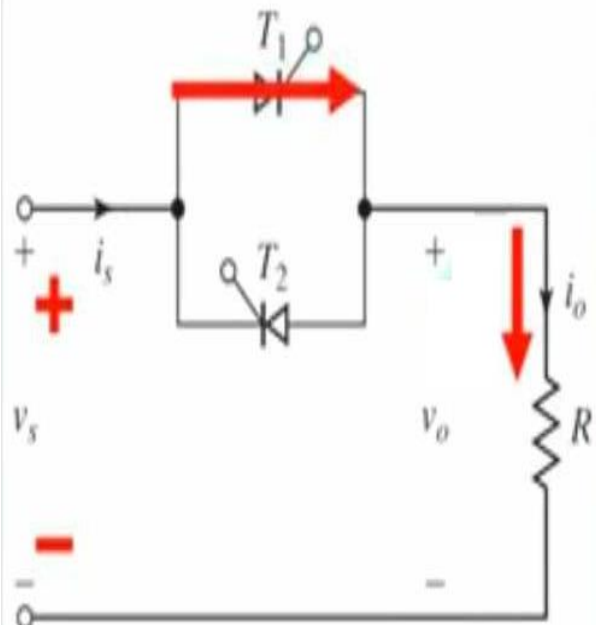


Thyristor T_1 current

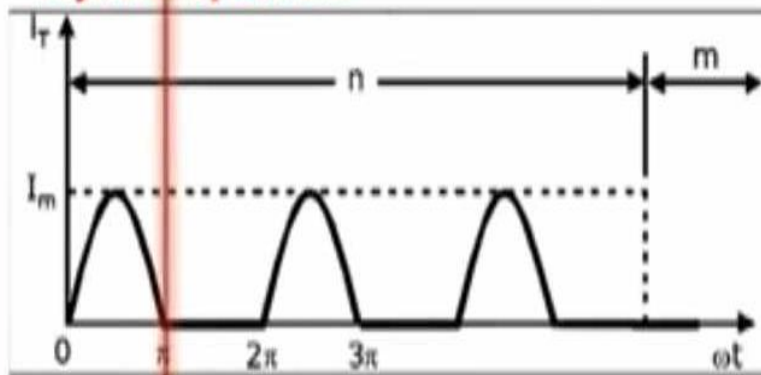

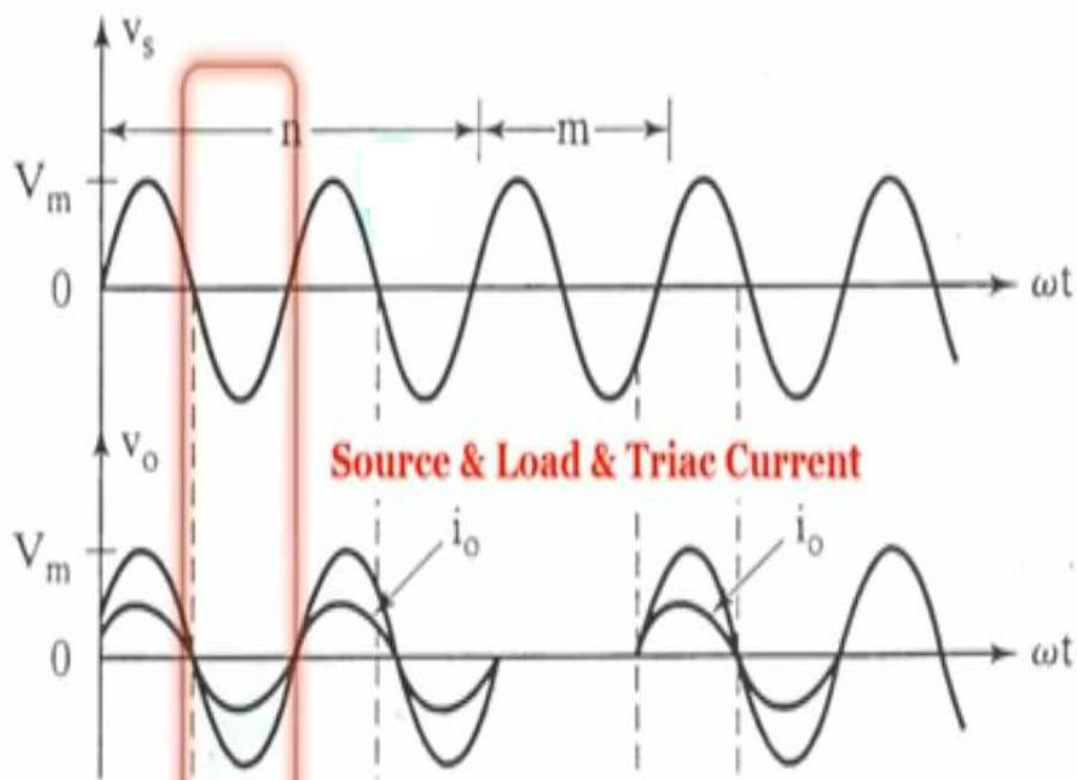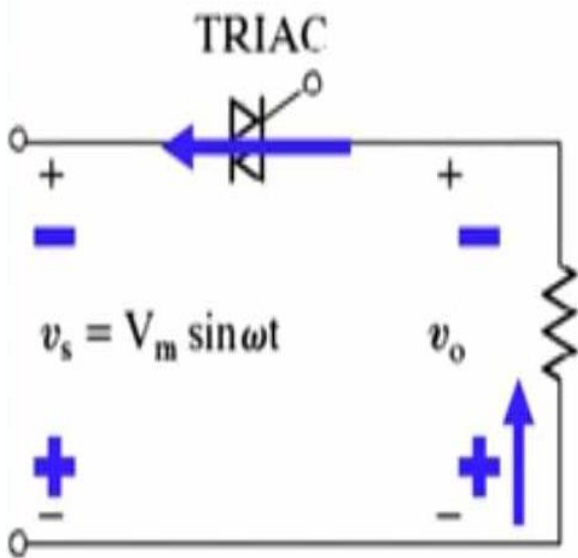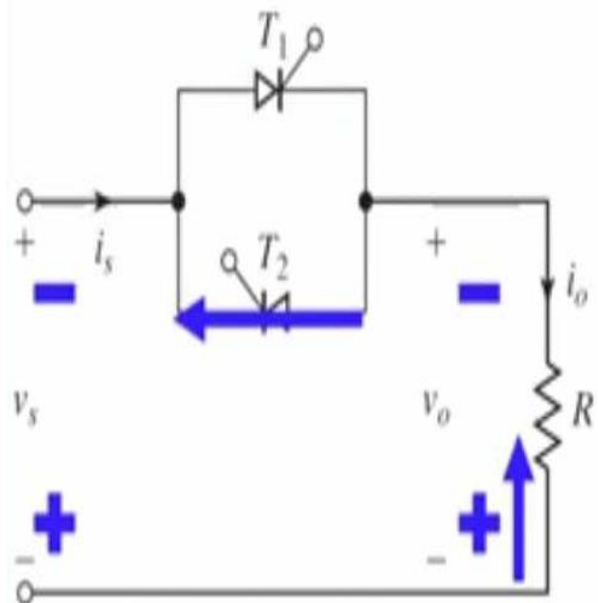

Thyristor T_1 current

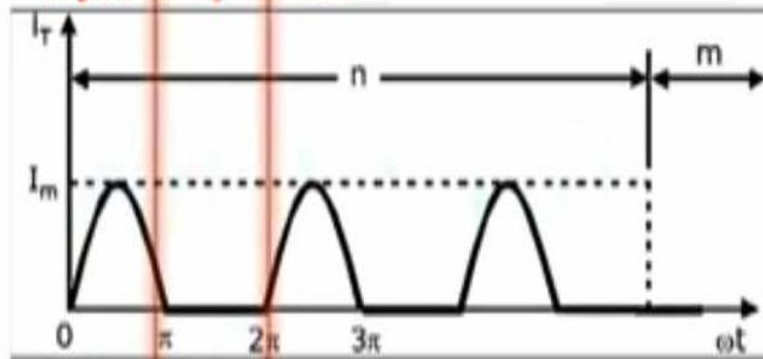


- The input voltage is **connected** to load (thyristors T_1 & T_2 are turned **ON**) for ' n ' number of input cycles during the time interval t_{ON}
- The input voltage is **disconnected** from load (thyristors T_1 & T_2 are turned **OFF**) for ' m ' number of input cycles during the time interval t_{OFF} .
- t_{ON} (AC Controller **ON** time) = nT
- t_{OFF} (AC Controller **OFF** time) = mT
- $T = 1/f =$ Input cycle time (time period), $f =$ Input supply frequency
- $T_o =$ Output time period = $t_{ON} + t_{OFF} = (n + m)T$
- Thyristors T_1 & T_2 are turned **ON** precisely at **zero voltage crossings** of the input supply.
- Due to **zero voltage switching** of thyristors, **the harmonics** generated by switching actions are **reduced**

- For sinusoidal wave input supply Voltage:

$$v_s = V_m \sin\omega t = \sqrt{2} V_{s(RMS)} \sin\omega t$$

$$V_{s(RMS)} = V_s = V_m/\sqrt{2}$$

$$V_{s(Avg)} = V_{s(DC)} = 0$$

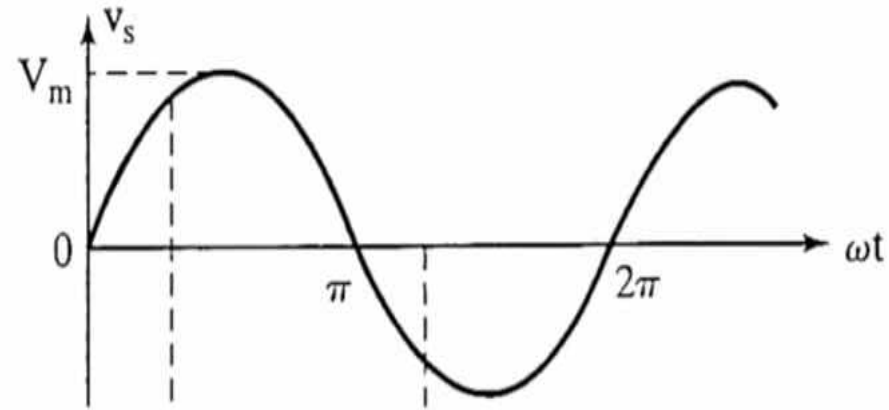


$$\begin{aligned} V_{s(Avg)} &= \frac{1}{T} \int_0^T v_s \, d\omega t = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin\omega t \\ &= \frac{V_m}{2\pi} (-\cos\omega t) \Big|_0^{2\pi} = \frac{-V_m}{2\pi} (\cos(2\pi) - \cos(0)) = 0 \end{aligned}$$

▪ The RMS Voltage for input supply :

$$v_s = V_m \sin\omega t = \sqrt{2} V_s (RMS) \sin\omega t$$


$$V_s (RMS) = V_s = V_m / \sqrt{2}$$

$$V_s (Avg) = V_s (DC) = 0$$

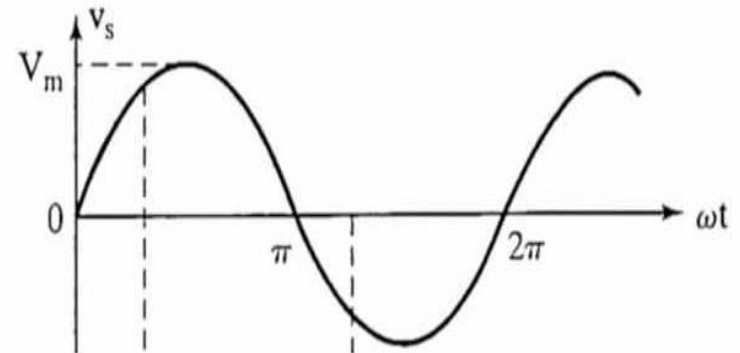

$$\begin{aligned} V_s &= \left(\frac{1}{T} \int_0^T v_s^2 d\omega t \right)^{1/2} = \left(\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t \right)^{1/2} \\ &= \left(\frac{V_m^2}{2\pi} \int_0^{2\pi} \frac{1}{2} (1 - \cos 2\omega t) d\omega t \right)^{1/2} = \left(\frac{V_m^2}{4\pi} \left(\omega t + \frac{1}{2} \sin 2\omega t \right) \Big|_0^{2\pi} \right)^{1/2} \\ &= \left(\frac{V_m^2}{4\pi} \left(2\pi + \frac{1}{2} \sin(2 * 2\pi) - 0 - \frac{1}{2} \sin(0) \right) \right)^{1/2} = \left(\frac{V_m^2}{4\pi} 2\pi \right)^{1/2} = \frac{V_m}{\sqrt{2}} \end{aligned}$$

▪ The Average **Output Load Voltage**:

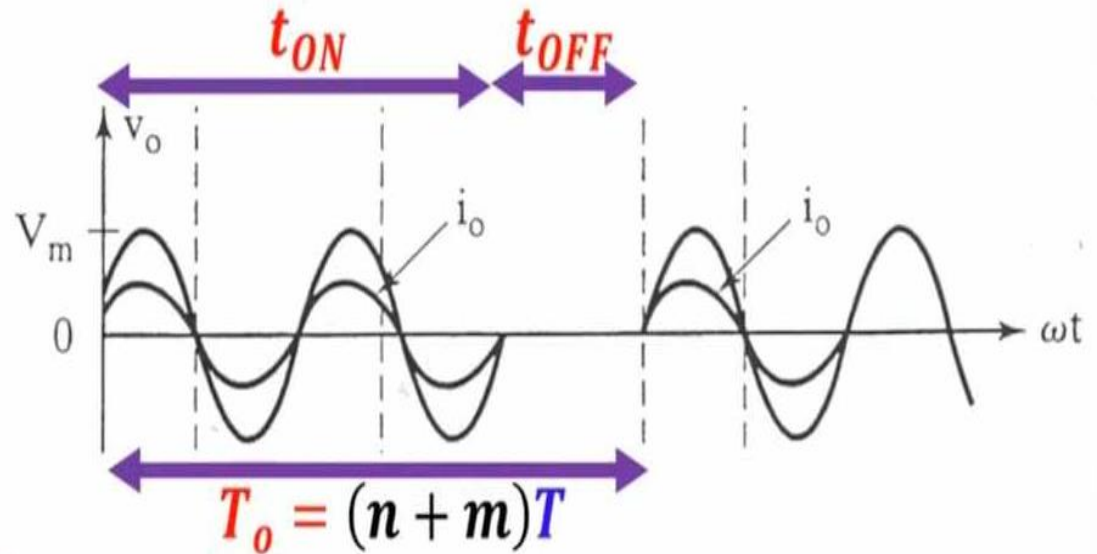

$$V_{o(Avg)} = \frac{1}{T_o} \int_0^{T_o} v_o \, d\omega t$$

$$= \frac{1}{(n+m)T} \cdot n \int_0^{2\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{2\pi} \frac{n}{(n+m)} (-\cos \omega t) \Big|_0^{2\pi}$$

$$= \frac{-V_m}{2\pi} \frac{n}{(n+m)} (\cos(2\pi) - \cos(0)) = 0$$

$$I_{o(Avg)} = I_{Triac(Avg)} = I_s(Avg) = \frac{V_{o(Avg)}}{R} = 0$$

▪ The RMS Output Load Voltage:


$$V_{o(RMS)} = \left(\frac{1}{T_o} \int_0^{T_o} v_o^2 d\omega t \right)^{1/2}$$

$$= \left(\frac{1}{(n+m)T} \cdot n \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t \right)^{1/2}$$

$$= \left(\frac{V_m^2}{2\pi(n+m)} \int_0^{2\pi} \frac{1}{2} (1 - \cos 2\omega t) d\omega t \right)^{1/2} = \left(\frac{V_m^2}{4\pi(n+m)} \left(\omega t + \frac{1}{2} \sin 2\omega t \right) \Big|_0^{2\pi} \right)^{1/2}$$

$$= \left(\frac{V_m^2}{4\pi(n+m)} \left(2\pi + \frac{1}{2} \sin(2 * 2\pi) - 0 - \frac{1}{2} \sin(0) \right) \right)^{1/2}$$
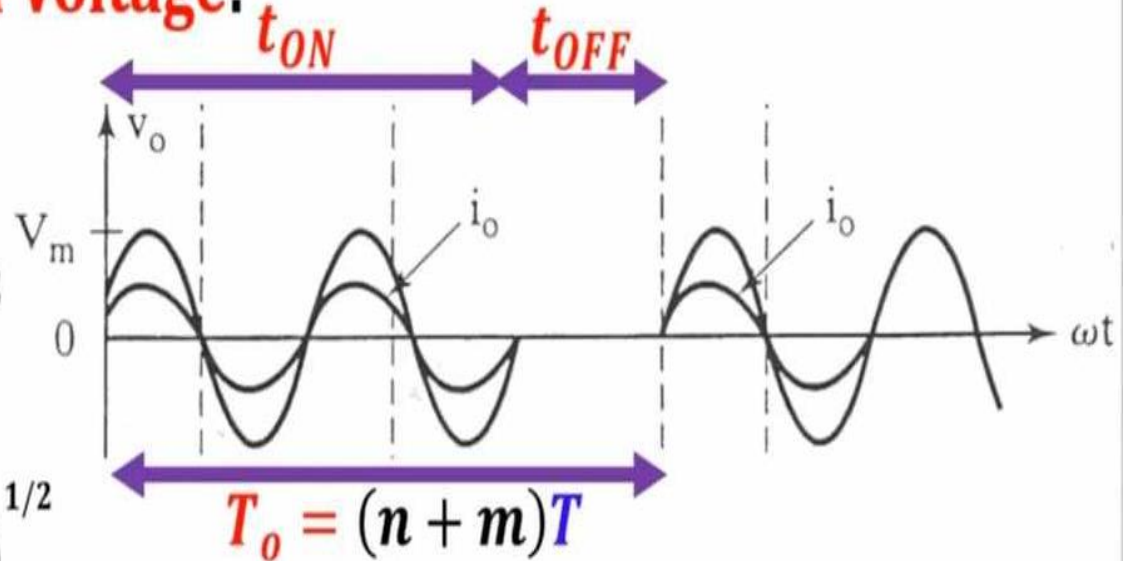
$$= \left(\frac{V_m^2}{4\pi} 2\pi \frac{n}{(n+m)} \right)^{1/2} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{n}{n+m}} = V_s \sqrt{\frac{n}{n+m}} = V_s \sqrt{k}$$



- RMS value of output (**Load**) voltage, $V_o (RMS)$:

$$V_o (RMS) = \frac{V_m}{\sqrt{2}} \sqrt{\frac{n}{n+m}} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{t_{ON}}{T_o}} = V_s (RMS) \sqrt{\frac{n}{n+m}} = V_s (RMS) \sqrt{k}$$

- Power Factor, **PF**, is:


$$PF = \frac{V_o (RMS)}{V_s (RMS)} = \sqrt{k} = \sqrt{\frac{t_{ON}}{T_o}}$$

- Note that the power factor and RMS output voltage vary with the square root of k

- Duty Cycle (k):


$$k = \frac{t_{ON}}{T_o} = \frac{nT}{(n+m)T} = \frac{n}{n+m}$$

Power factor, PF

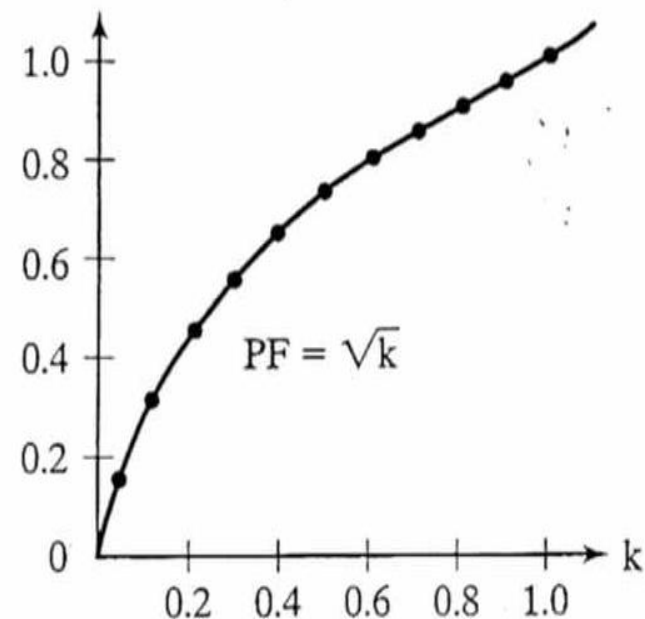

- **RMS Source & Load & Triac Current:**
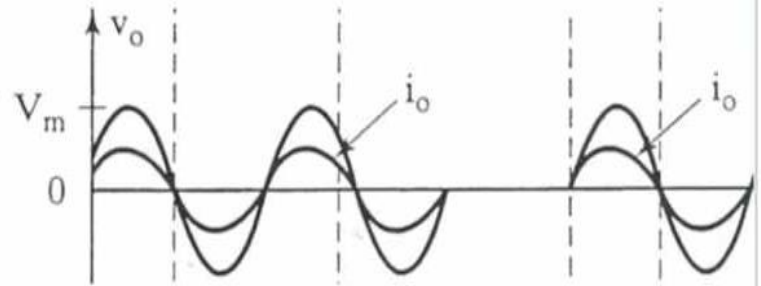
$$I_o(RMS) = I_{Triac}(RMS) = I_s(RMS) = \frac{V_o(RMS)}{R}$$



- **Average Output (AC) Load Power:**

$$P_o(Avg) = I_o^2(RMS)R = \frac{V_o^2(RMS)}{R} = I_o(RMS) V_o(RMS) = \frac{V_s^2(RMS)}{R} k$$


- **Average Input Supply Volt-Amperes:**

$$VA = I_s(RMS) V_s(RMS)$$

- **Power Factor, PF, is:**

$$PF = \frac{P_o(Avg)}{VA} = \frac{I_o(RMS) V_o(RMS)}{I_s(RMS) V_s(RMS)} = \frac{V_o(RMS)}{V_s(RMS)}$$

$$PF = \sqrt{k}$$

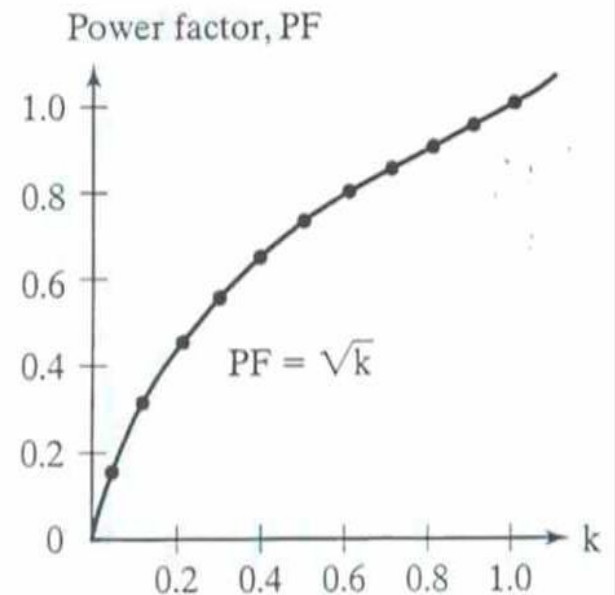

▪ The Average Thyristor Current:


$$I_{Thy(Avg)} = \frac{1}{T_0} \int_0^{T_0} i_{Thy} d\omega t$$

$$= \frac{1}{(n+m)T} n \int_0^{2\pi} I_m \sin\omega t d\omega t$$


$$= \frac{1}{(n+m)T} n \int_0^{\pi} I_m \sin\omega t d\omega t = \frac{I_m}{2\pi} \frac{n}{(n+m)} (-\cos\omega t) \Big|_0^{\pi}$$

$$= \frac{-I_m}{2\pi} \frac{n}{(n+m)} (\cos(\pi) - \cos(0)) = \frac{-I_m}{2\pi} \frac{n}{(n+m)} (-2) = \frac{I_m}{\pi} k$$
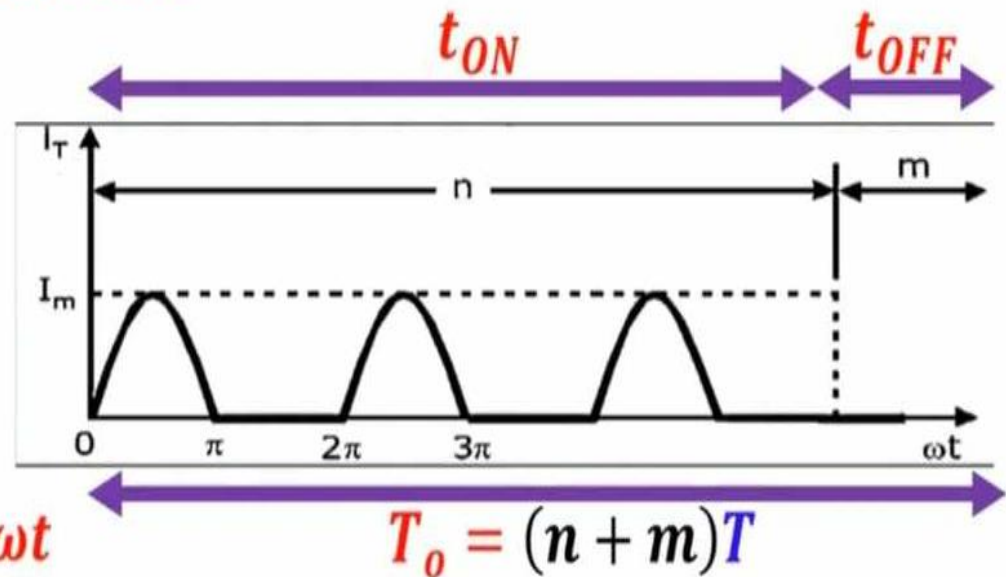
$$I_m = \frac{V_m}{R} = \frac{V_s \sqrt{2}}{R}$$



▪ The RMS Thyristor Current:

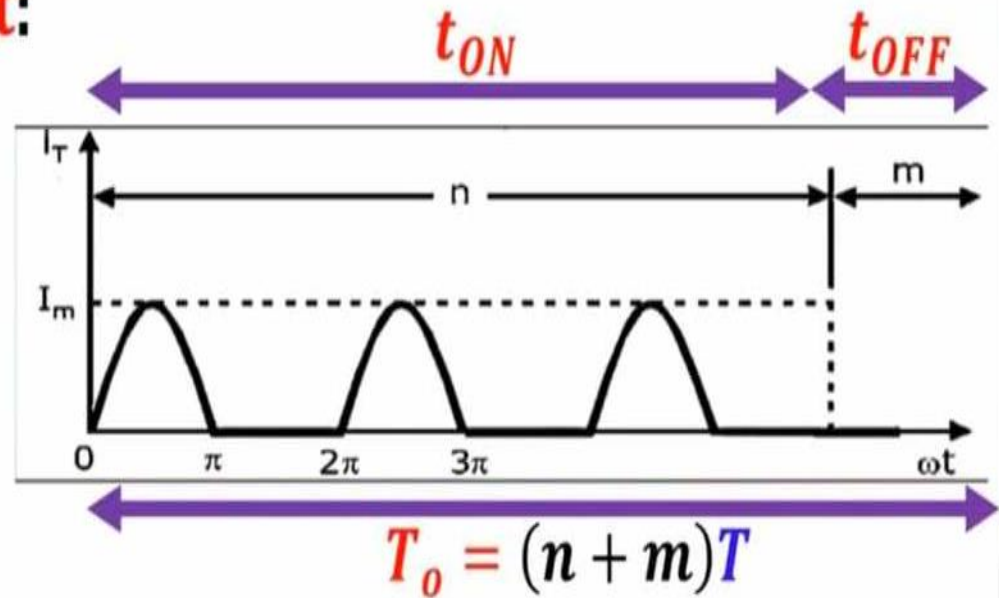

$$I_{Thy (RMS)} = \left(\frac{1}{T_0} \int_0^{T_0} i_{Thy}^2 d\omega t \right)^{1/2}$$

$$= \left(\frac{1}{(n + m)T} \cdot n \int_0^\pi I_m^2 \sin^2 \omega t d\omega t \right)^{1/2}$$

$$= \left(\frac{I_m^2 n}{2\pi (n + m)} \int_0^\pi \frac{1}{2} (1 - \cos 2\omega t) d\omega t \right)^{1/2} = \left(\frac{I_m^2 n}{4\pi (n + m)} \left(\omega t + \frac{1}{2} \sin 2\omega t \right) \Big|_0^\pi \right)^{1/2}$$

$$= \left(\frac{I_m^2 n}{4\pi (n + m)} \left(\pi + \frac{1}{2} \sin(2\pi) - 0 - \frac{1}{2} \sin(0) \right) \right)^{1/2}$$

$$= \left(\frac{I_m^2 n}{4\pi (n + m)} \right)^{1/2} = \frac{I_m}{2} \sqrt{\frac{n}{n + m}} = \frac{I_m}{2} \sqrt{\frac{n}{n + m}} = \frac{I_m}{2} \sqrt{k}$$

$$I_m = \frac{V_m}{R} = \frac{V_s \sqrt{2}}{R}$$

- This type of control is applied in applications which have **high mechanical inertia** and **high thermal time constant**
- Typical examples are **industrial heating** and **speed control of large motors.**
- Duty Cycle ($k =$ Ratio of on time to total output cycle time): **controls average load power** as well as **rms output voltage.**
- Average power delivered to the load can be varied from **0%** through **100%**
- The output voltage and **input** current are asymmetrical (for resistive load)
- There is **no DC component** of input supply current and output voltage i.e., the average value for each is **Zero.**