
 Palestine Technical University - Kadoorie
 جامعة فلسطين التقنية - خضوري


Electrical Engineering Department

Electronics Lab

Exp (2):
Rectifiers (Half wave and Full wave)

Presentation By:
Mr. Tareq Foqha

Summer 2023-2024

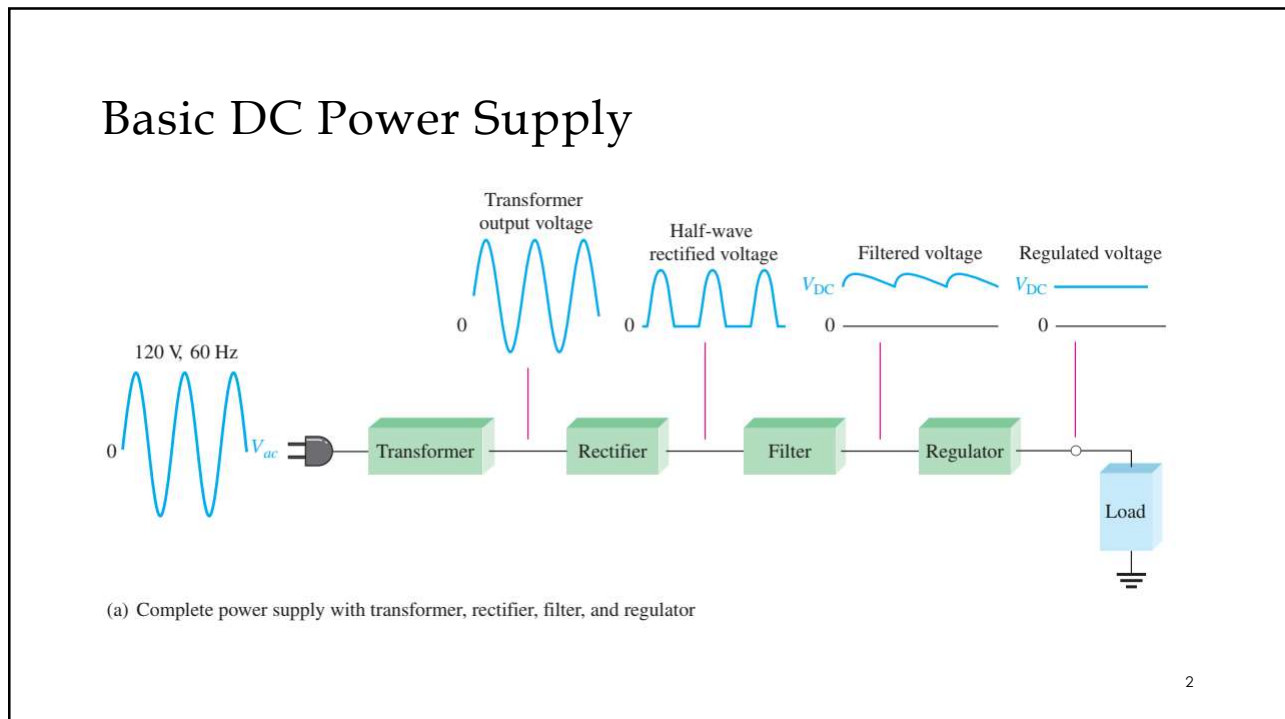

Half Wave Rectifier

120 V, 60 Hz

Half-wave rectified voltage

(b) Half-wave rectifier

$V_{p(out)} = V_{p(in)} - 0.7 \text{ V}$

Area

V_p

V_{AVG}

0

2π

➔

$$V_{AVG} = \frac{V_p}{\pi}$$

$$f_{out} = f_{in}$$

3

Bridge Full Wave Rectifier

0 V

V_{in}

Full-wave rectifier

V_{out}

0 V

pulsating dc output

(a) During the positive half-cycle of the input, D_1 and D_2 are forward-biased and conduct current. D_3 and D_4 are reverse-biased.

(b) During the negative half-cycle of the input, D_3 and D_4 are forward-biased and conduct current. D_1 and D_2 are reverse-biased.

4

Bridge Full Wave Rectifier




$$V_{p(out)} = V_{p(in)} - 1.4 \text{ V}$$

$$V_{AVG} = \frac{2 V_{p(out)}}{\pi}$$

$$f_{out} = 2f_{in}$$

5


Rectifiers with Filters

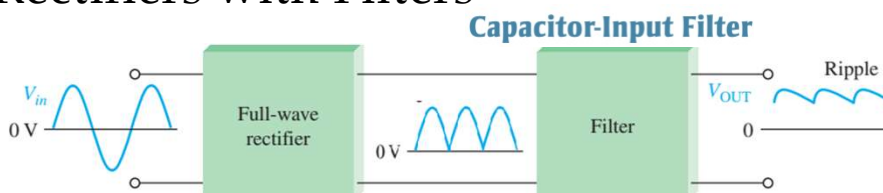

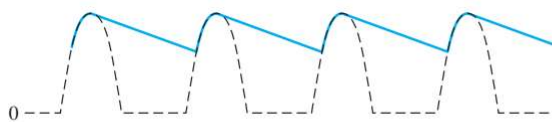
(b) Rectifier with a filter (output ripple is exaggerated)

The small amount of fluctuation in the filter output voltage is called *ripple*.

The variation in the capacitor voltage due to the charging and discharging is called the **ripple voltage**.



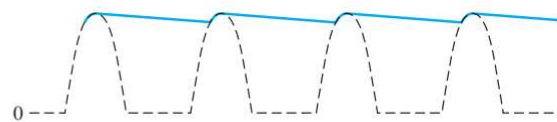(a) Larger ripple (blue) means less effective filtering.




(b) Smaller ripple means more effective filtering. Generally, the larger the capacitor value, the smaller the ripple for the same input and load.

Rectifiers with Filters

Ripple Factor The ripple factor (r) is an indication of the effectiveness of the filter and is defined as

$$r = \frac{V_{r(pp)}}{V_{DC}}$$

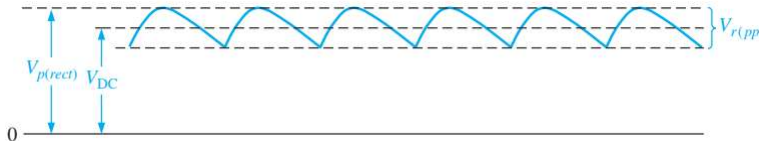

$$V_{r(pp)} \cong \left(\frac{1}{fR_L C} \right) V_{p(rect)}$$

$$V_{DC} \cong \left(1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

The lower the ripple factor, the better the filter. The ripple factor can be lowered by increasing the value of the filter capacitor or increasing the load resistance ($T=RC$).


7

Rectifiers with Filters

Which is better to filter, HW or FW?

► FIGURE 2-45

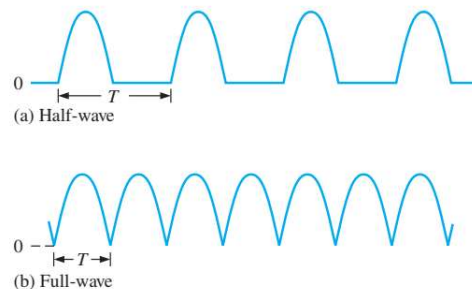The period of a full-wave rectified voltage is half that of a half-wave rectified voltage. The output frequency of a full-wave rectifier is twice that of a half-wave rectifier.




When filtered, the full-wave rectified voltage has a smaller ripple than does a half-wave voltage for the same load resistance and capacitor values. The capacitor discharges less during the shorter interval between full wave pulses

8

Practical Part:

Part 1: Half Wave Rectifiers with and without capacitor

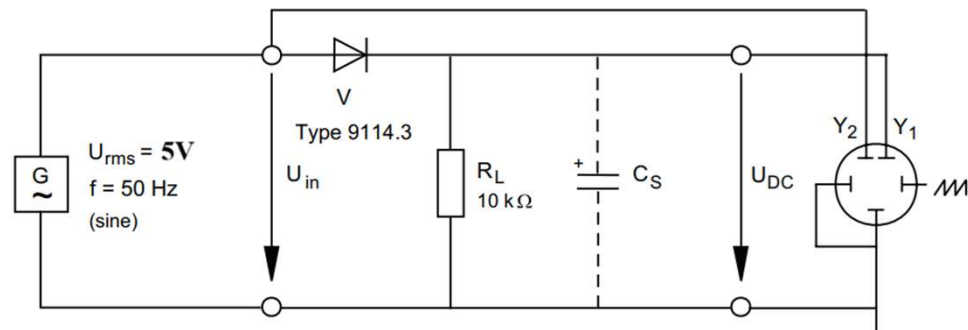1. Set up the circuit according to the Fig. shown below.
2. Measure the input voltage U_{in} and the DC voltage U_{DC}
3. Calculate the ratio U_{DC} to U_{in} .
4. Draw the input and output signals using oscilloscope.
5. Evaluate the peak-to-peak value and the frequency of the ripple voltage U_{rip} from the oscilloscope diagram




Practical Part:

Part 1: Half Wave Rectifiers with and without capacitor

6. connect the smoothing capacitors C_S in parallel to the load resistor R_L as in the following Table and repeat the measurements.

Half-wave rectifier circuit M1				
C_S [μ F]	without	10	100	470
U_{in} [V]				
U_{DC} [V]				
$\frac{U_{DC}}{U_{in}}$				
$U_{rip, pp}$ [V]				
f_{rip} [Hz]				

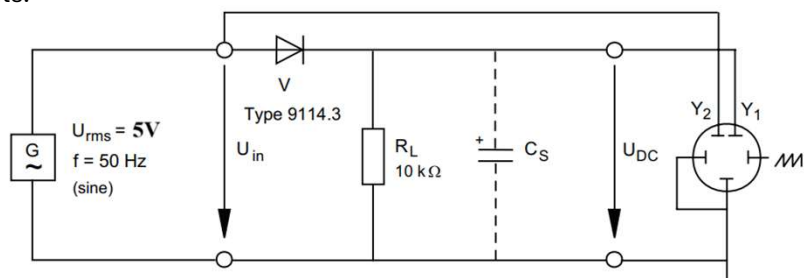


7. Plot the curve of input voltage U_{in} and of DC voltage U_{DC} which results using the smoothing capacitor 10, 100 and 470 micro farad.
8. Calculate the ripple factor (use measured and calculated values).

Practical Part:

Part 1: Half Wave Rectifiers with and without capacitor

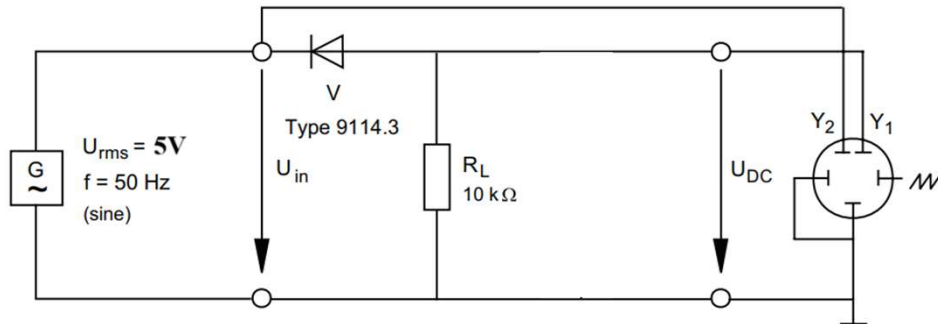
9. disconnect the smoothing capacitors
10. reverse the polarity of the diode in the circuit
11. Draw the input and output signals using oscilloscope.



Practical Part:

Part 2: Full Wave Rectifiers with and without capacitor

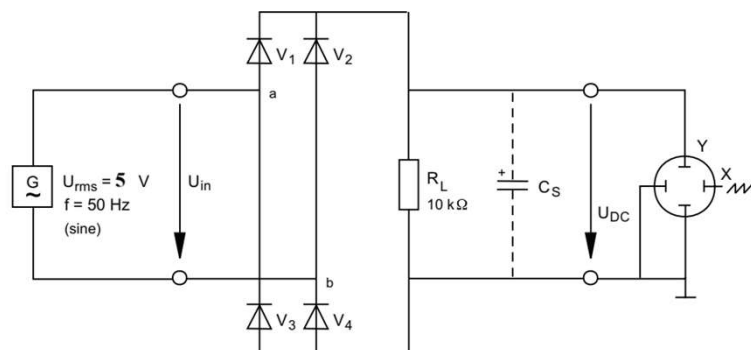1. Set up the circuit according to the Fig. shown below.
2. Measure the input voltage U_{in} and the DC voltage U_{DC}
3. Calculate the ratio U_{DC} to U_{in} .
4. Draw the input and output signals using oscilloscope.
5. Evaluate the peak-to-peak value and the frequency of the ripple voltage U_{rip} from the oscilloscope diagram




Practical Part:

Part 2: Full Wave Rectifiers with and without capacitor

6. connect the smoothing capacitors C_S in parallel to the load resistor R_L as in the following Table and repeat the measurements.

Bridge rectifier circuit B2				
C_S [μ F]	without	10	100	470
U_{in} [V]				
U_{DC} [V]				
$\frac{U_{DC}}{U_{in}} =$				
$u_{rip\ pp}$ [V]				
f_{rip} [Hz]				

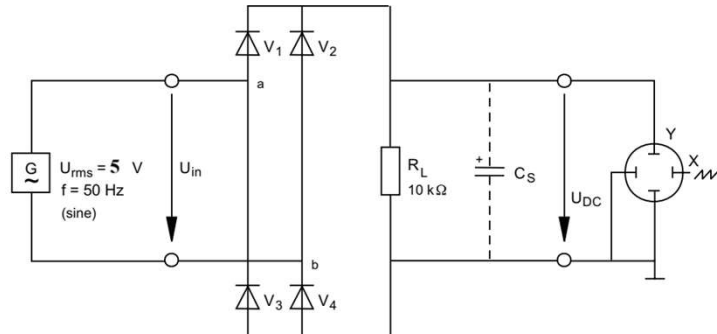

7. Plot the curve of input voltage U_{in} and of DC voltage U_{DC} which results using the smoothing capacitor 10, 100 and 470 micro farad.
8. Calculate the ripple factor (use measured and calculated values).
9. Compare between HW and FW circuits (use the obtained results)