

Physics Lab 2

Experiment no.3 Ohms Law

Objective:

In this experiment you will learn to use the multi-meter to measure voltage, current and resistance

$$V = IR$$


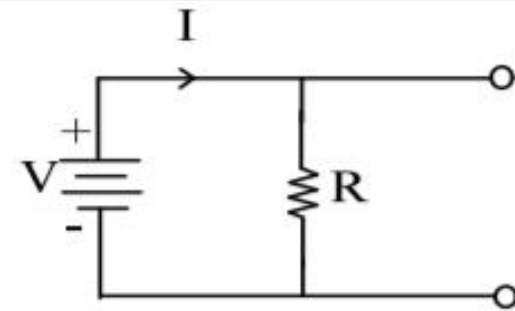


Figure 1: Diagram showing a voltage forcing a current to flow through a resistor.

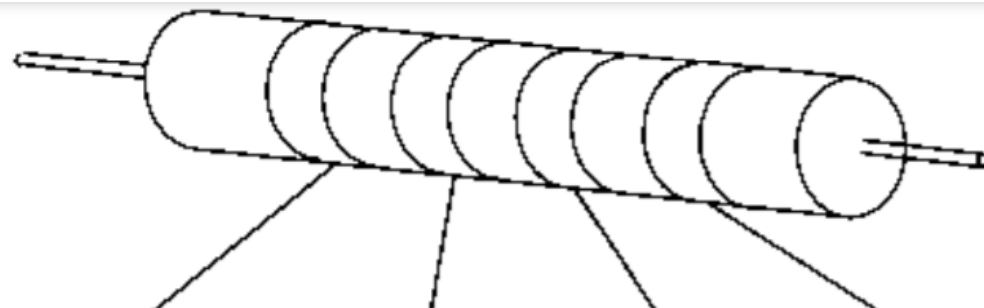

Color	First Color Band Significant Digit	Second Color Band Significant Digit	Third Color Band Significant Digit	Tolerance Band
Black	0	0	1	--
Brown	1	1	10	--
Red	2	2	100	--
Orange	3	3	1,000	--
Yellow	4	4	10,000	--
Green	5	5	100,000	--
Blue	6	6	1,000,000	--
Violet	7	7	--	--
Gray	8	8	--	--
White	9	9	--	--
Gold	--	--	0.10	±5%
Silver	--	--	0.01	±10%
No color	--	--	--	±20%


EXAMPLE

Yellow / Violet / Orange / Silver (resistor colors)

4 / 7 / ×1,000 / ±10%


47,000 Ω ± 10% or (using engineering notation) 47 KΩ ± 10%

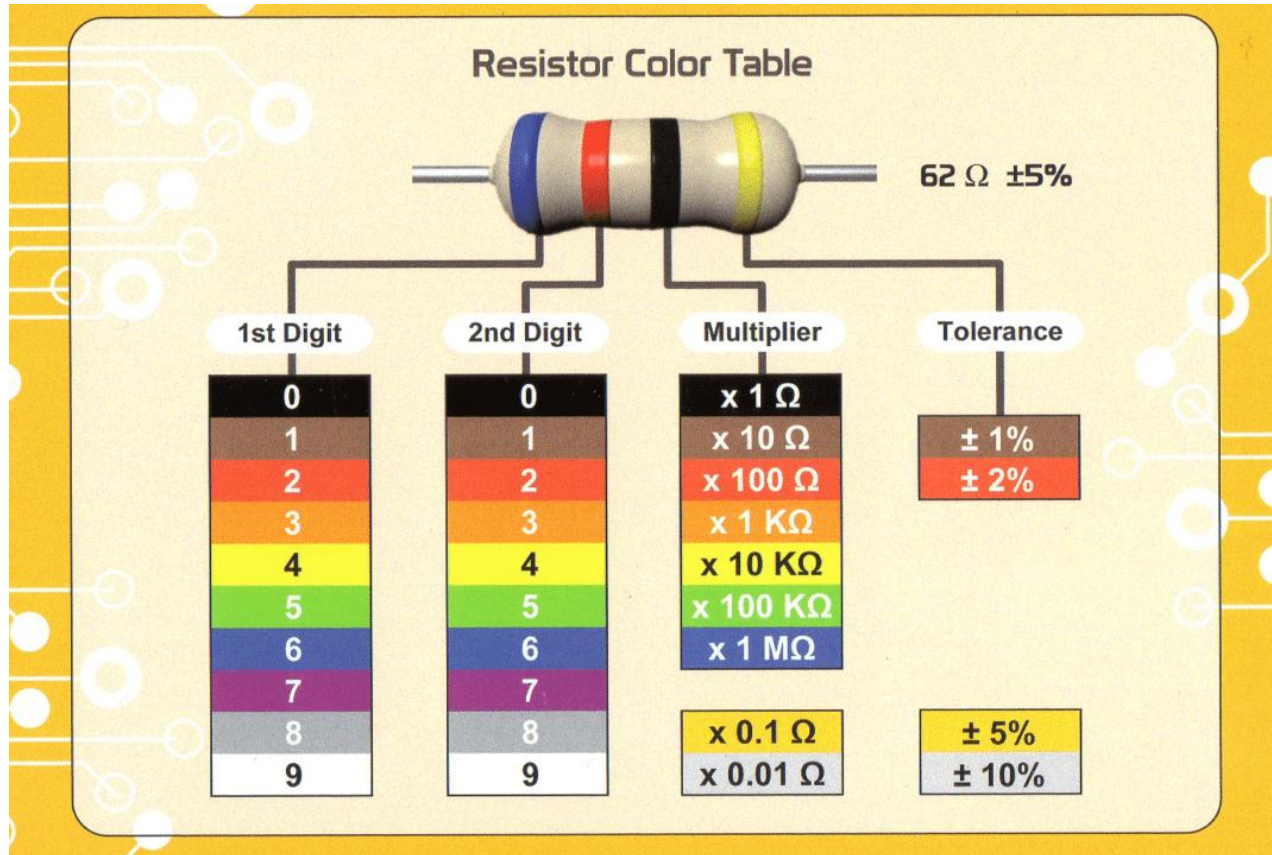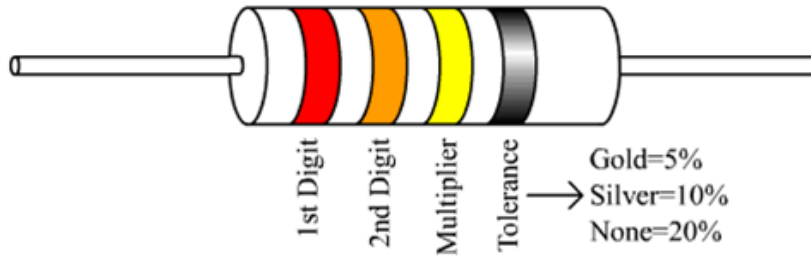
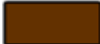








Example:



6 2 x 10⁰ ± 5%


Example 2




	Color	Digit	Multiplier	Tolerance (%)
	Black	0	10^0 (1)	
	Brown	1	10^1	1
	Red	2	10^2	2
	Orange	3	10^3	
	Yellow	4	10^4	
	Green	5	10^5	0.5
	Blue	6	10^6	0.25
	Violet	7	10^7	0.1
	Grey	8	10^8	
	White	9	10^9	
	Gold		10^{-1}	5
	Silver		10^{-2}	10
	(none)			20

Experiment Part :

Part 1: measure resistance in series

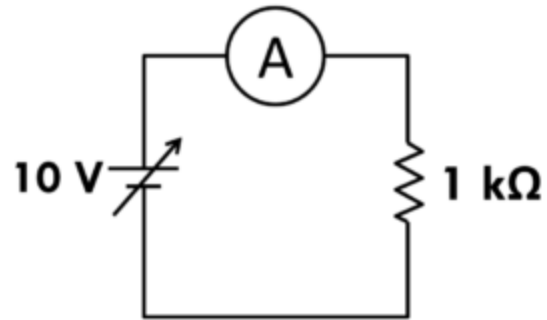


Voltage (V)	Current (mA)
0 V	0 V
1 V	1 mA
2 V	2 mA
3 V	2.99 mA
4 V	4 mA
5 V	5 mA
6 V	6 mA
7 V	6.99 mA
8 V	8 mA
9 V	9 mA
10 V	10 mA

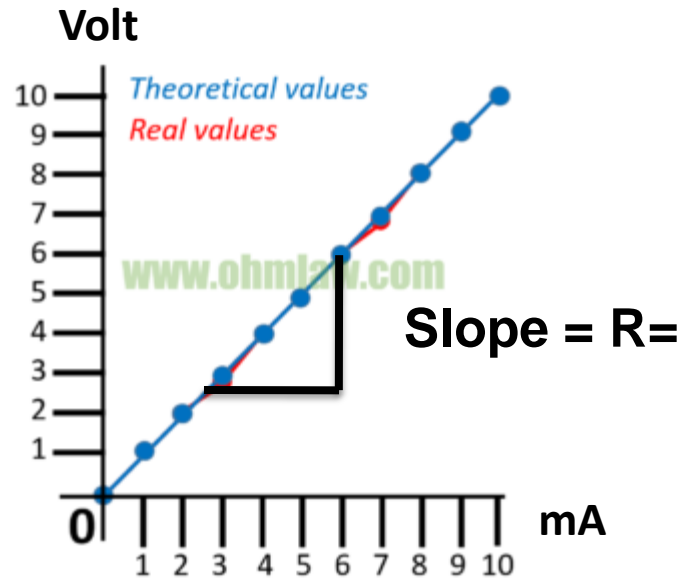


Experiment Part :

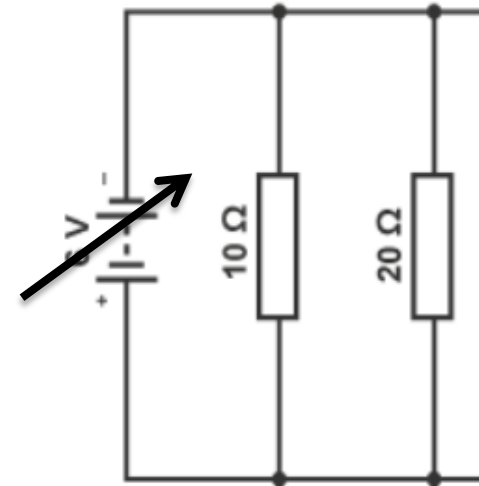Part 1: measure resistance in parallel

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$



Voltage (V)	Current (mA)
0 V	0 mA
1 V	
2 V	
3 V	
4 V	
5 V	
6 V	
7 V	
8 V	
9 V	
10 V	

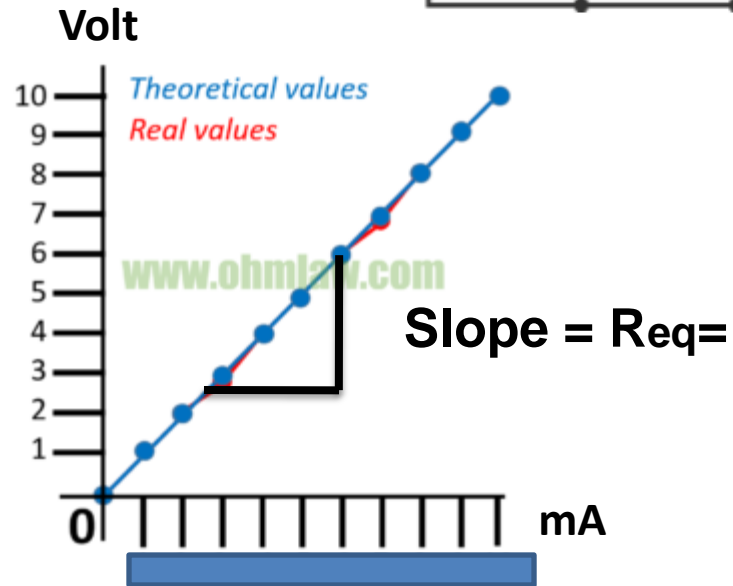

Report :

- 1- Fill the data in the link attached in (LMS) of experiment in the table for both series and parallel
- 2- plot the voltage versus current
- 3- calculate the resistance from the slope
- 4- calculate the percentage errors between R experiment and R theoretical (from colour code)

يتم تسليم التقرير على
LMS