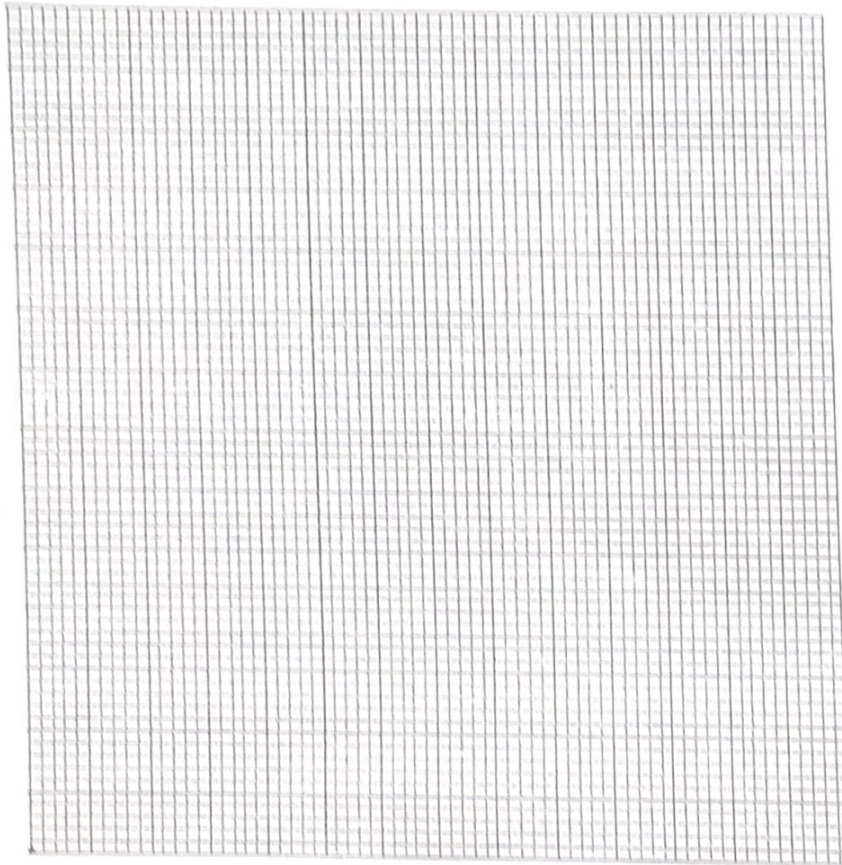


Experiment (7): AC Bridge Meter

Part I

- * C_1 Theoretically is:
- * Plot C_g versus $\frac{L_{AC}}{L_{BC}}$ and fit it to the best straight line.

C_g	L_{BC}	L_{AC}	$\frac{L_{AC}}{L_{BC}}$
68			
100			
470			
1000			
2200			




- *The slope is
- * C_1 Experimentally is:
- *The Percentage Error in C_1 is.....

Part 2

* C_2 Theoretically is:

* Plot C_s versus $\frac{L_{AC}}{L_{BC}}$ and fit it to the best straight line.

C_s	L_{BC}	L_{AC}	$\frac{L_{AC}}{L_{BC}}$
68			
100			
470			
1000			
2200			

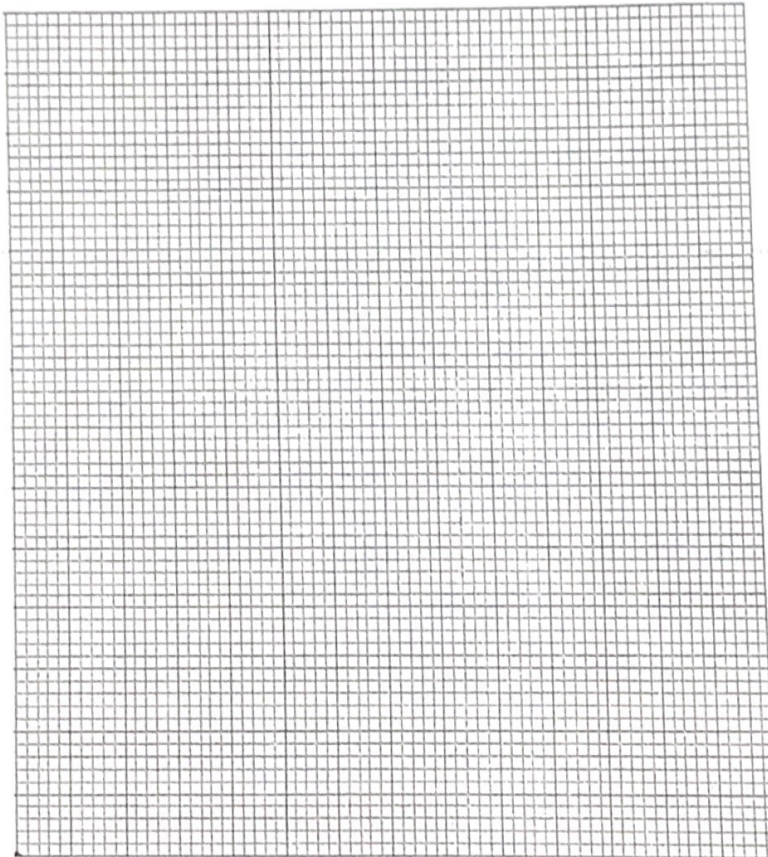

*The slope is

* C_2 Experimentally is:


*The Percentage Error in C_2 is.....

Part 3

* C_{series} Theoretically is:

* Plot C_{series} versus $\frac{L_{AC}}{L_{BC}}$ and fit it to the best straight line.

C_s	L_{BC}	L_{AC}	$\frac{L_{AC}}{L_{BC}}$
68			
100			
470			
1000			
2200			

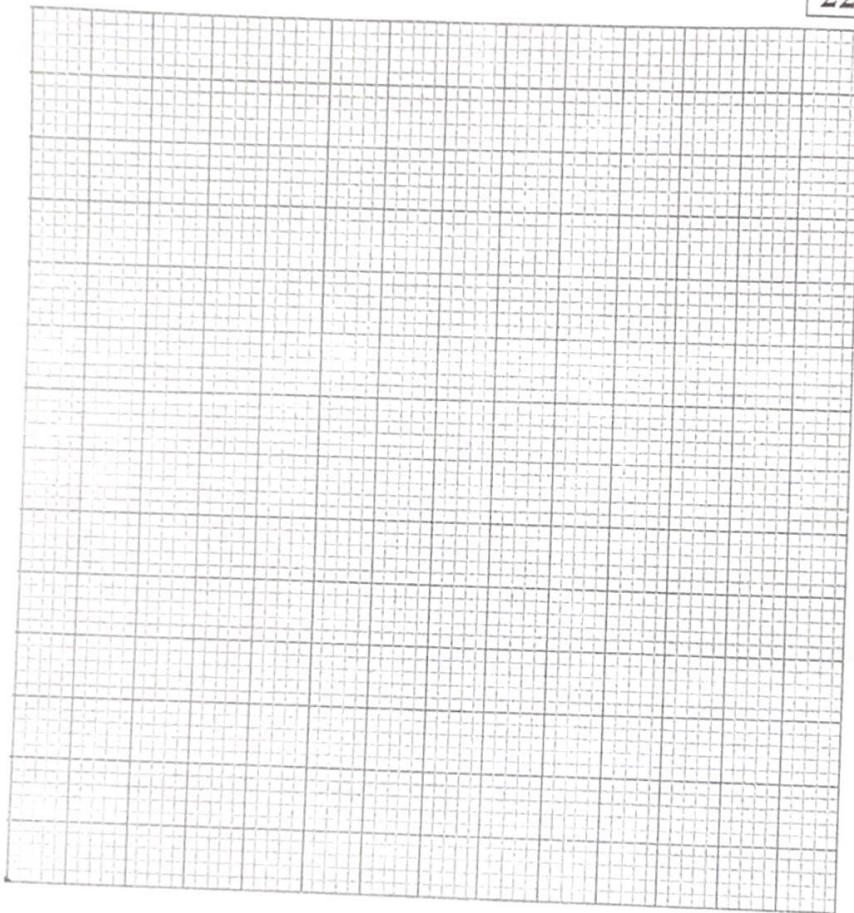

*The slope is

* C_{series} Experimentally is:


*The Percentage Error in C_{series} is.....

Part 4

* $C_{parallel}$ Theoretically is:

* Plot $C_{parallel}$ versus $\frac{L_{AC}}{L_{BC}}$ and fit it to the best straight line.

C_s	L_{BC}	L_{AC}	$\frac{L_{AC}}{L_{BC}}$
68			
100			
470			
1000			
2200			

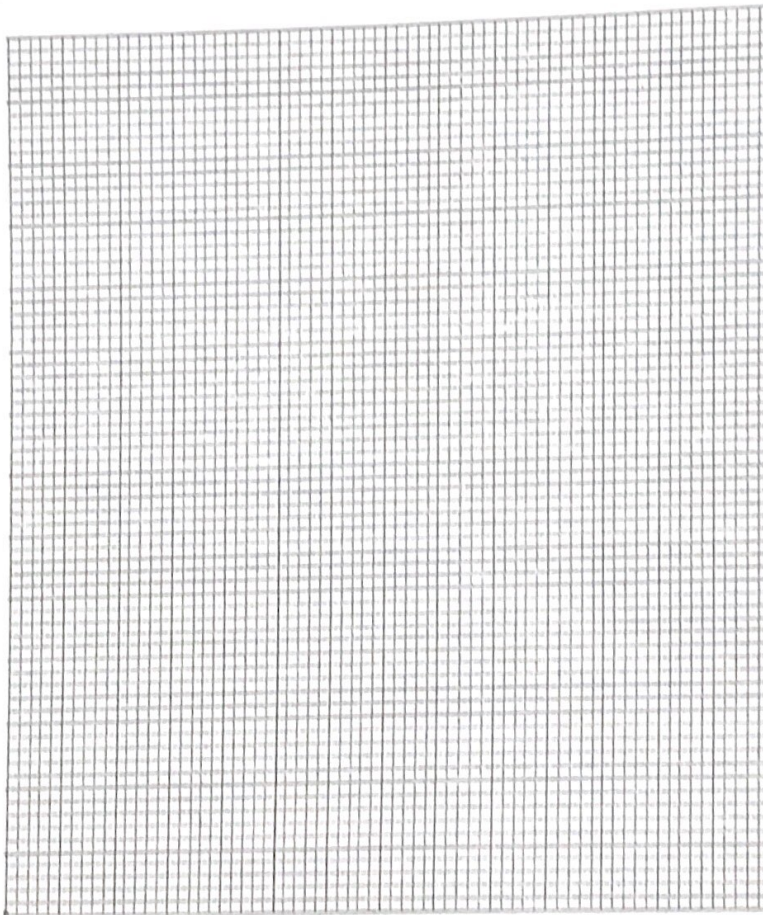

*The slope is

* $C_{parallel}$ Experimentally is:

*The Percentage Error in $C_{parallel}$ is.....