


Chapter 3

Voltage and current laws

VOLTAGE AND CURRENT DIVISION

Voltage divider rule (VDR) for resistors in series

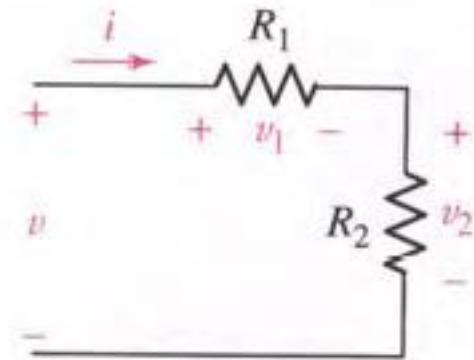
$$v_k = \frac{R_k}{R_1 + R_2 + \dots + R_N} v$$



Current divider rule (CDR) : only for two parallel resistors

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

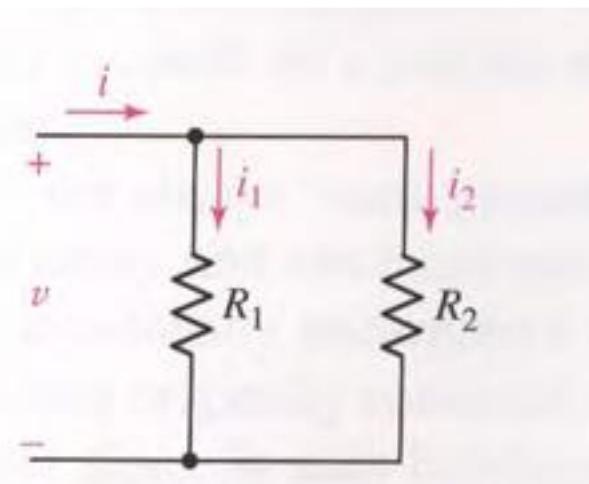

Question

Using VDR find V_x

$$R_{T1} = 5\Omega$$

$$V_x = \frac{10(2)}{2+3+5} = \frac{20}{10} = 2v$$

Question : find i_1, i_2, v_3

$$R_{t1} = \frac{240(40+20)}{240+(40+20)} = \frac{240(60)}{240+60} = \frac{14400}{300} = 48\Omega$$

$$R_{t2} = 2 + R_{t1} = 2 + 48 = 50\Omega$$

$$R_{t3} = \frac{50(50)}{50+50} = 25\Omega$$



CDR

$$i_1 = \frac{120m(125)}{125+25} = \frac{15}{150} = 0.1A = 100mA$$

$$i_2 = \frac{i_1(50)}{50+50} = \frac{100mA(50)}{100} = 50mA$$

$$i_3 = \frac{i_2(240)}{240+60} = \frac{50mA(240)}{300} = 40mA$$
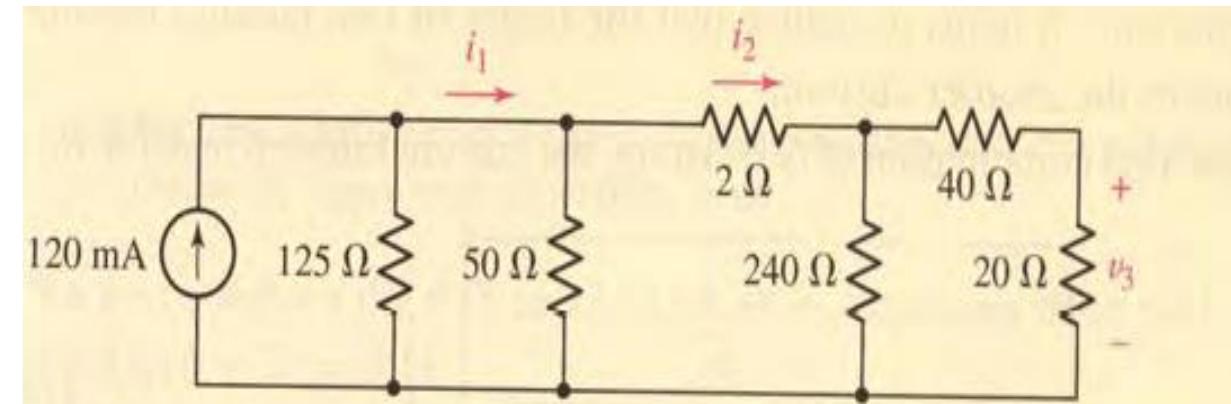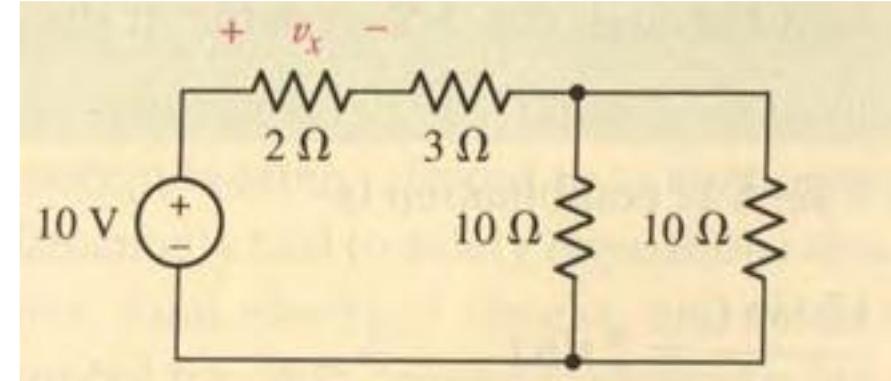
$$v_3 = 20(i_3) = 20(40mA) = 800mv = 0.8v$$




EXAMPLE

Using the voltage divider rule, determine the voltages V_1 and V_2 of Fig.

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(4\ \Omega)(24\text{ V})}{4\ \Omega + 2\ \Omega} = 16\text{ V}$$

$$V_2 = \frac{R_2 E}{R_1 + R_2} = \frac{(2\ \Omega)(24\text{ V})}{4\ \Omega + 2\ \Omega} = 8\text{ V}$$

$$E = +24\text{ V}$$

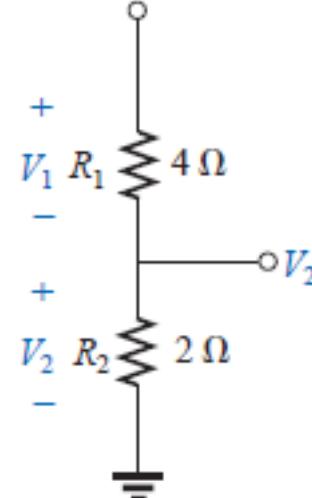

EXAMPLE

For the network of Fig.

- Calculate V_{ab} .
- Determine V_b .

Solutions:

- Voltage divider rule:


$$V_{ab} = \frac{R_1 E}{R_T} = \frac{(2\ \Omega)(10\text{ V})}{2\ \Omega + 3\ \Omega + 5\ \Omega} = +2\text{ V}$$

- Voltage divider rule:

$$V_b = V_{R_2} + V_{R_3} = \frac{(R_2 + R_3)E}{R_T} = \frac{(3\ \Omega + 5\ \Omega)(10\text{ V})}{10\ \Omega} = 8\text{ V}$$

or $V_b = V_a - V_{ab} = E - V_{ab} = 10\text{ V} - 2\text{ V} = 8\text{ V}$

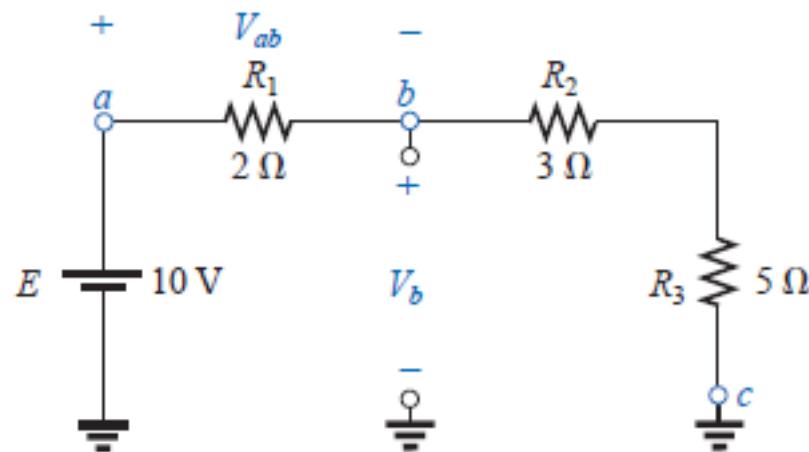- $V_c = \text{ground potential} = 0\text{ V}$



EXAMPLE Design the voltage divider of Fig. such that $V_{R_1} = 4V_{R_2}$.

Solution: The total resistance is defined by

$$R_T = \frac{E}{I} = \frac{20 \text{ V}}{4 \text{ mA}} = 5 \text{ k}\Omega$$

Since $V_{R_1} = 4V_{R_2}$,

$$R_1 = 4R_2$$

Thus $R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$


and

$$5R_2 = 5 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

and

$$R_1 = 4R_2 = 4 \text{ k}\Omega$$

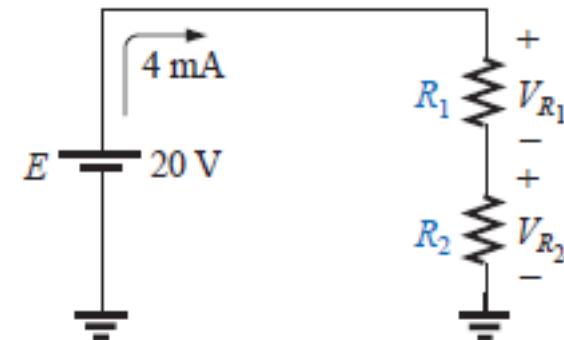

EXAMPLE

- Determine V_2 using Kirchhoff's voltage law.
- Determine I .
- Find R_1 and R_3 .

Solutions:

- Kirchhoff's voltage law (clockwise direction):

$$-E + V_3 + V_2 + V_1 = 0$$

or


$$E = V_1 + V_2 + V_3$$

and $V_2 = E - V_1 - V_3 = 54 \text{ V} - 18 \text{ V} - 15 \text{ V} = 21 \text{ V}$

b. $I = \frac{V_2}{R_2} = \frac{21 \text{ V}}{7 \Omega} = 3 \text{ A}$

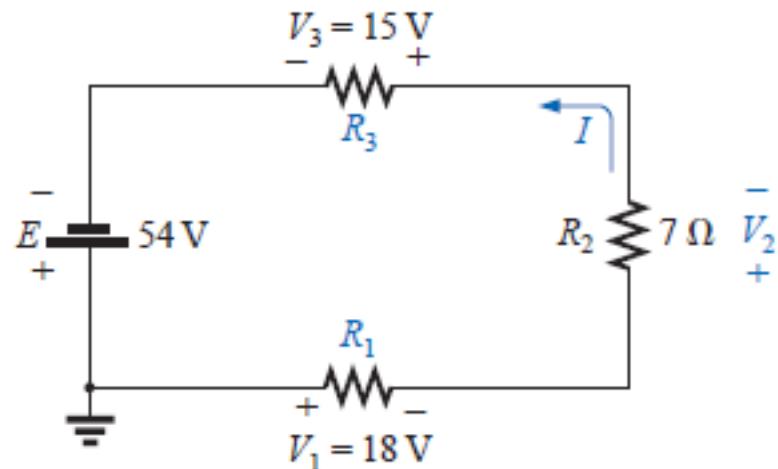c. $R_1 = \frac{V_1}{I} = \frac{18 \text{ V}}{3 \text{ A}} = 6 \Omega$

$R_3 = \frac{V_3}{I} = \frac{15 \text{ V}}{3 \text{ A}} = 5 \Omega$



EXAMPLE



Determine I and the voltage across the $7\text{-}\Omega$ resistor

Solution: The network is redrawn in Fig. 5.22.

$$R_T = (2)(4\ \Omega) + 7\ \Omega = 15\ \Omega$$

$$I = \frac{E}{R_T} = \frac{37.5\text{ V}}{15\ \Omega} = 2.5\text{ A}$$
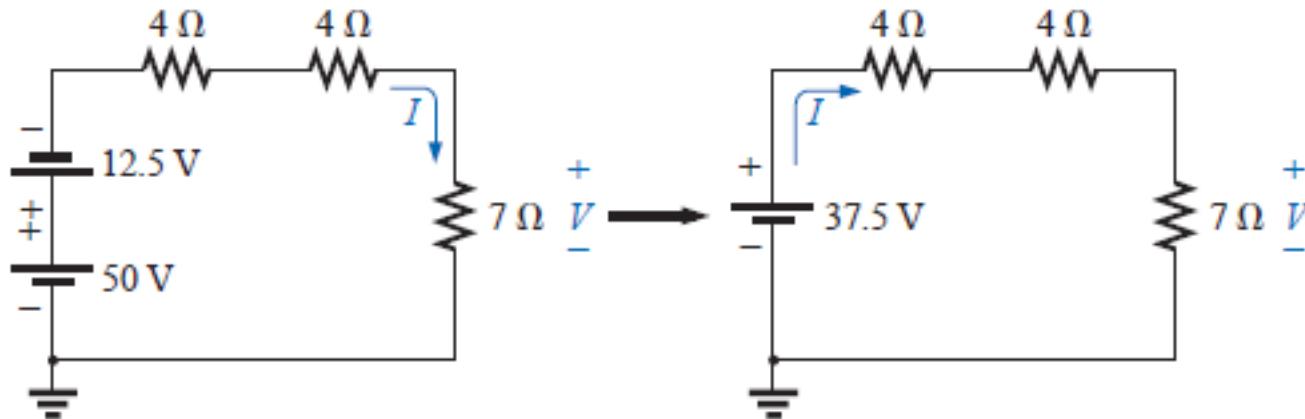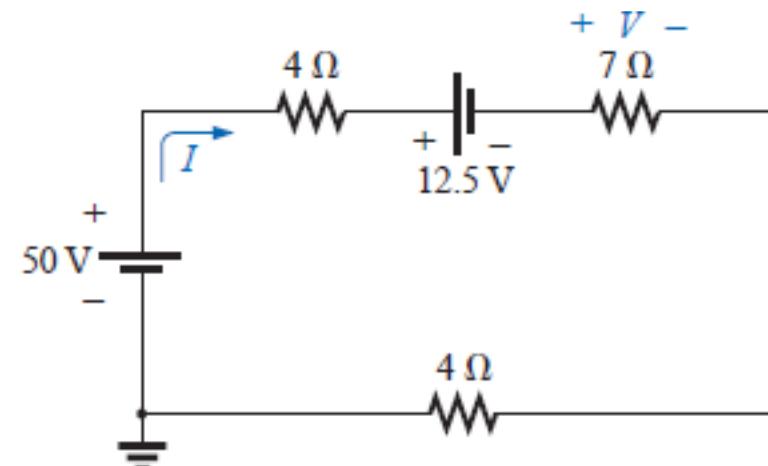
$$V_{7\Omega} = IR = (2.5\text{ A})(7\ \Omega) = 17.5\text{ V}$$



EXAMPLE Find V_1 and V_2 for the network

Solution: For path 1, starting at point a in a clockwise direction:

$$+25\text{ V} - V_1 + 15\text{ V} = 0$$

and


$$V_1 = 40\text{ V}$$

For path 2, starting at point a in a clockwise direction:

$$-V_2 - 20\text{ V} = 0$$

and

$$V_2 = -20\text{ V}$$

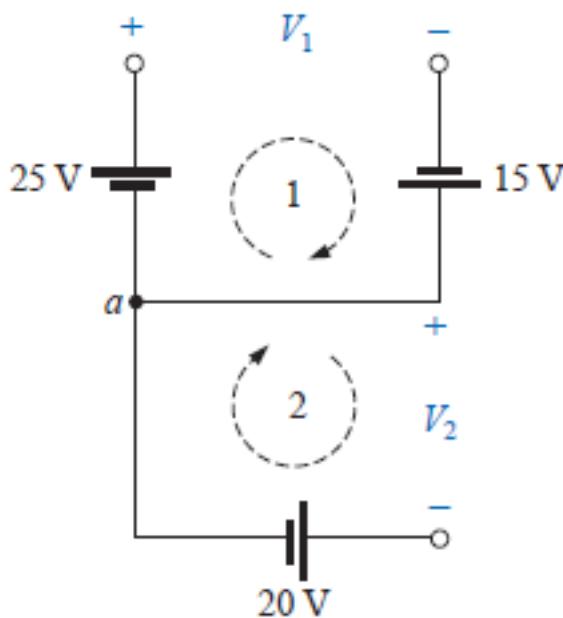

EXAMPLE

- Find the total resistance
- Calculate the source current I_s .
- Determine the voltages V_1 , V_2 , and V_3 .
- Calculate the power dissipated by R_1 , R_2 , and R_3 .
- Determine the power delivered by the source, and compare it to the sum of the power levels of part (d).

Solutions:

a. $R_T = R_1 + R_2 + R_3 = 2 \Omega + 1 \Omega + 5 \Omega = 8 \Omega$

b. $I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{8 \Omega} = 2.5 \text{ A}$

c. $V_1 = IR_1 = (2.5 \text{ A})(2 \Omega) = 5 \text{ V}$

$V_2 = IR_2 = (2.5 \text{ A})(1 \Omega) = 2.5 \text{ V}$

$V_3 = IR_3 = (2.5 \text{ A})(5 \Omega) = 12.5 \text{ V}$

d. $P_1 = V_1 I_1 = (5 \text{ V})(2.5 \text{ A}) = 12.5 \text{ W}$

$P_2 = I_2^2 R_2 = (2.5 \text{ A})^2(1 \Omega) = 6.25 \text{ W}$

$P_3 = V_3^2/R_3 = (12.5 \text{ V})^2/5 \Omega = 31.25 \text{ W}$

e. $P_{\text{del}} = EI = (20 \text{ V})(2.5 \text{ A}) = 50 \text{ W}$

$P_{\text{del}} = P_1 + P_2 + P_3$

$50 \text{ W} = 12.5 \text{ W} + 6.25 \text{ W} + 31.25 \text{ W}$

$50 \text{ W} = 50 \text{ W}$ (checks)

