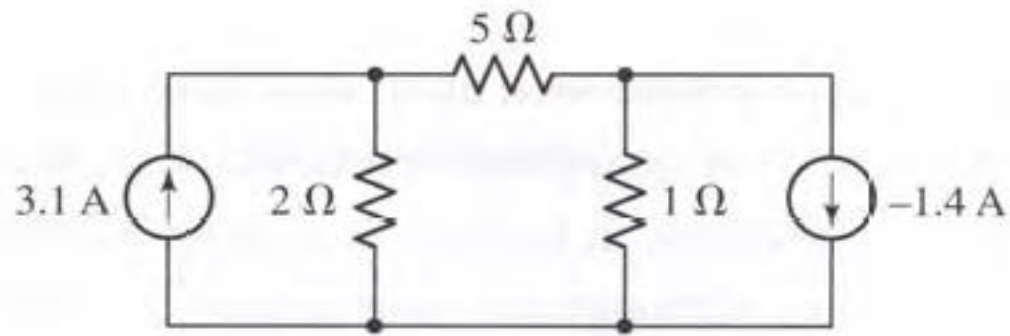


# Chapter 4


## Basic Nodal and Mesh Analysis

## Summary of Basic Nodal Analysis Procedure


1. **Count the number of nodes ( $N$ ).**
2. **Designate a reference node.** The number of terms in your nodal equations can be minimized by selecting the node with the greatest number of branches connected to it.
3. **Label the nodal voltages** (there are  $N - 1$  of them).
4. **Write a KCL equation for each of the nonreference nodes.** Sum the currents flowing *into* a node from sources on one side of the equation. On the other side, sum the currents flowing *out of* the node through resistors. Pay close attention to “-” signs.
5. **Express any additional unknowns such as currents or voltages other than nodal voltages in terms of appropriate nodal voltages.** This situation can occur if voltage sources or dependent sources appear in our circuit.
6. **Organize the equations.** Group terms according to nodal voltages.
7. **Solve the system of equations for the nodal voltages** (there will be  $N - 1$  of them).



(a)

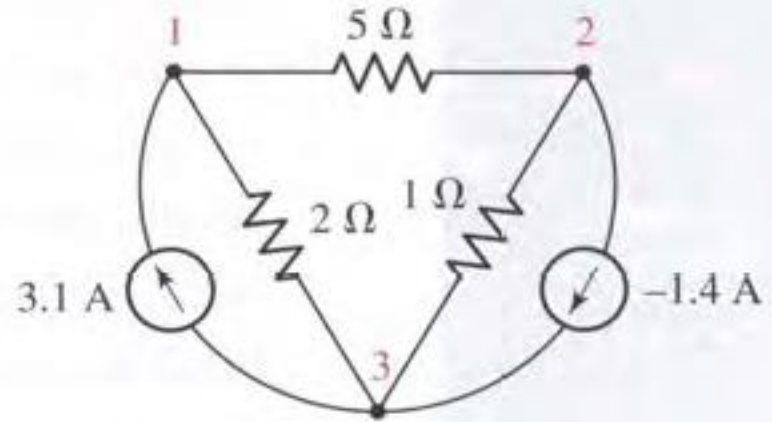


(b)

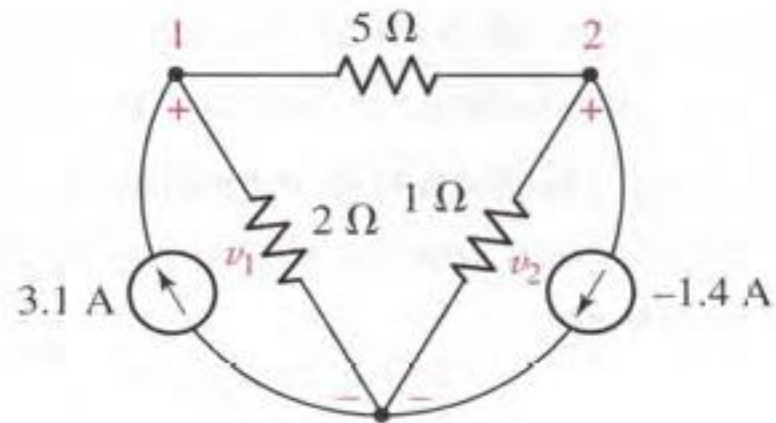

Reference node

(c)

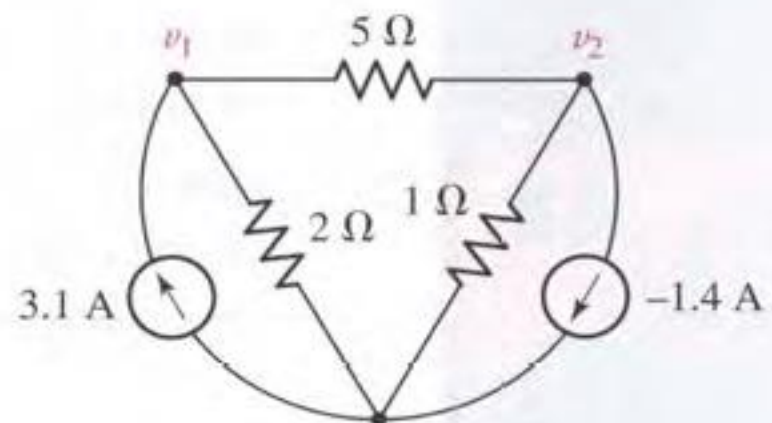

Ref.

(d)

KCL at node 1

$$\frac{v_1}{2} + \frac{v_1 - v_2}{5} = 3.1$$

$$0.7v_1 - 0.2v_2 = 3.1$$

KCL at node 2


$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} = -(-1.4)$$

$$-0.2v_1 + 1.2v_2 = 1.4$$

The results are  $v_1 = 5$  V and  $v_2 = 2$  V.

$$v_{5\Omega} = v_1 - v_2 = 3$$
 V.

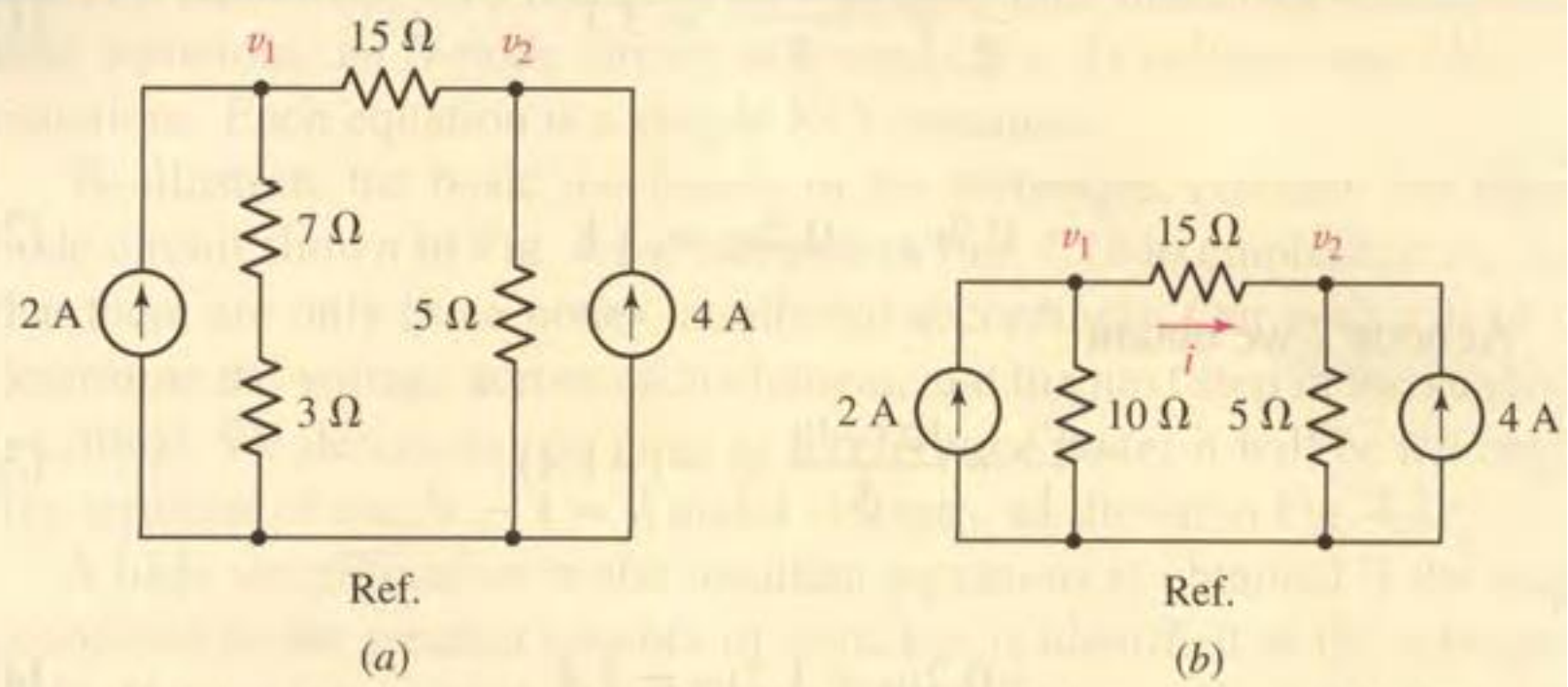Determine the current flowing left to right through the 15  $\Omega$  resistor of Fig. 4.2a.



Writing an appropriate KCL equation for node 1,

$$2 = \frac{v_1}{10} + \frac{v_1 - v_2}{15}$$

KCL for node 2

$$4 = \frac{v_2}{5} + \frac{v_2 - v_1}{15}$$

Rearranging, we obtain

$$5v_1 - 2v_2 = 60$$

and


$$-v_1 + 4v_2 = 60$$

$v_1 = 20$  V and  $v_2 = 20$  so that  $v_1 - v_2 = 0$ .

*zero current* is flowing through the  $15 \Omega$  resistor



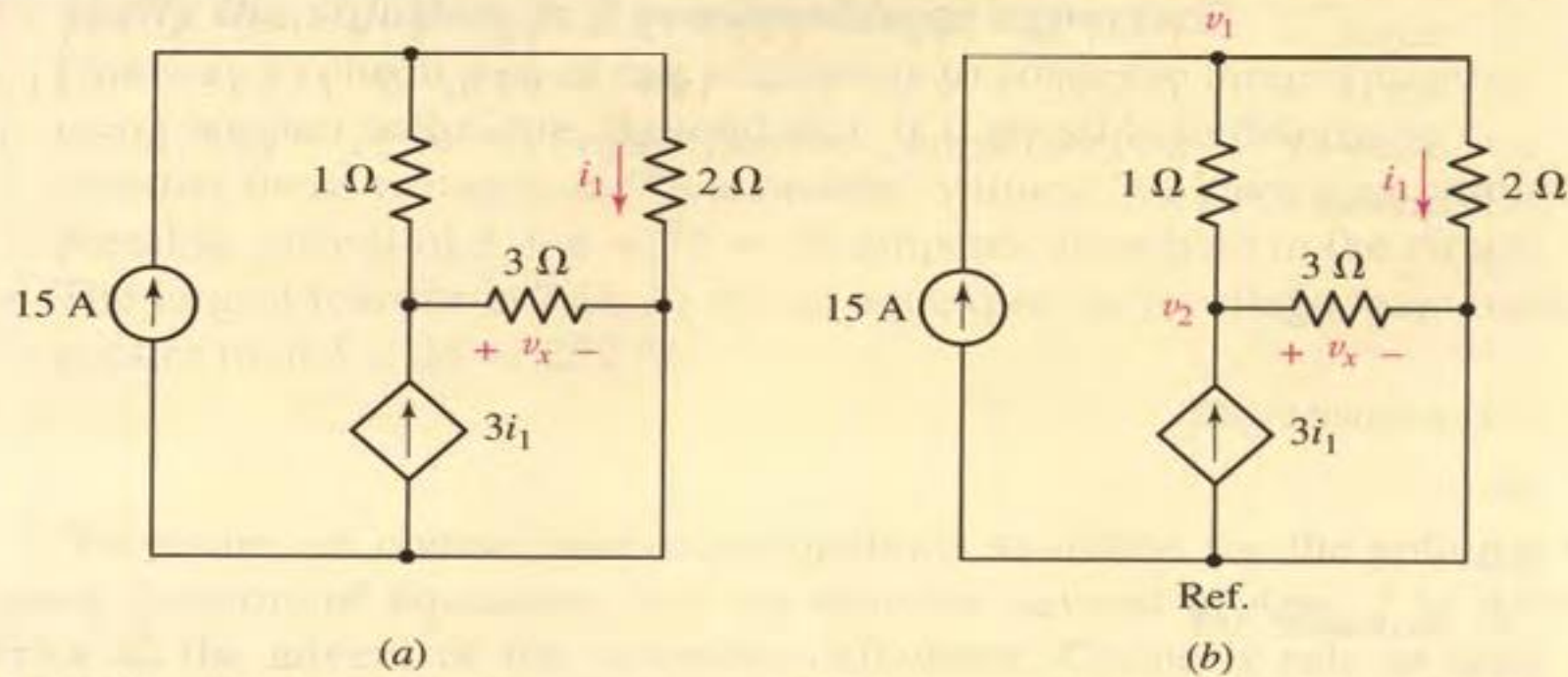Determine the power supplied by the dependent source of Fig. 4.6a.



KCL at node 1

$$15 = \frac{v_1 - v_2}{1} + \frac{v_1}{2}$$

KCL at node 2

$$3i_1 = \frac{v_2 - v_1}{1} + \frac{v_2}{3}$$

$$i_1 = \frac{v_1}{2}$$

After substituting  $i_1$

$$3v_1 - 2v_2 = 30$$

$$-15v_1 + 8v_2 = 0$$

Solving we find  $v_1 = -40$  V,  $v_2 = -75$  V, and  $i_1 = 0.5v_1 = -20$  A.

Power of dependent source is  $(3i_1)(v_2) = (-60)(-75) = 4.5$  kW.