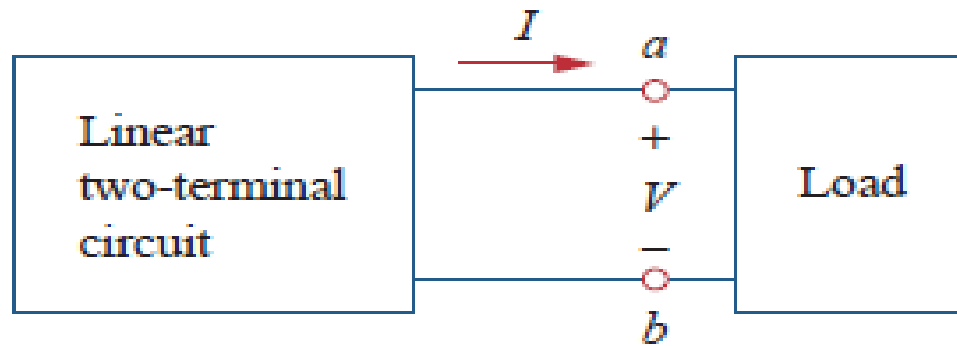



# Chapter 5

## **Circuit Analysis Techniques** **Thevenin's Theorem**


# THÉVENIN'S THEOREM



(a)

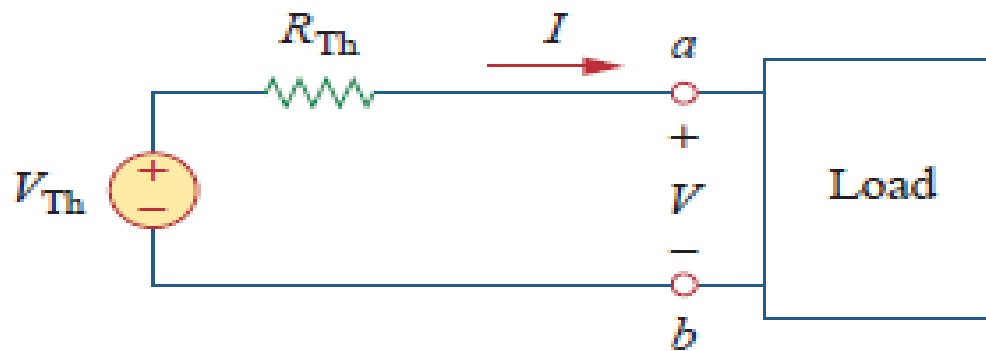


(b)

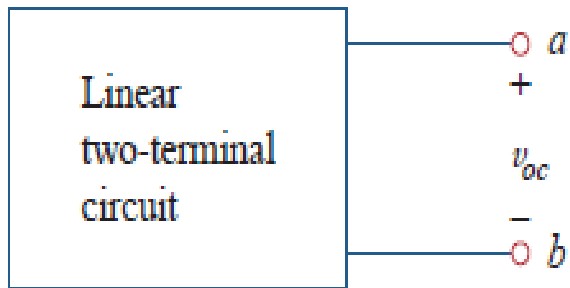


$$V_{Th} = v_{oc}$$

(a)

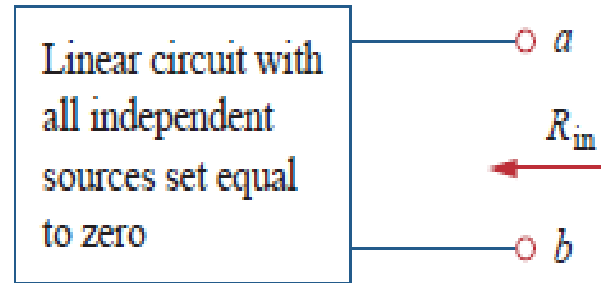


$$R_{Th} = R_{in}$$

(b)

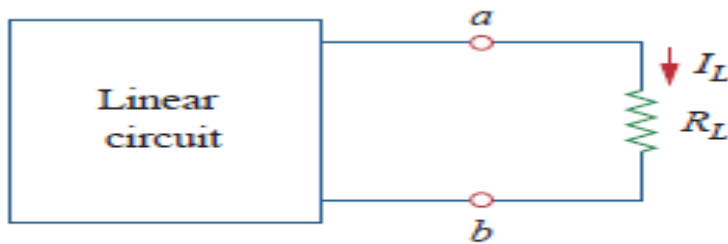

(a)

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

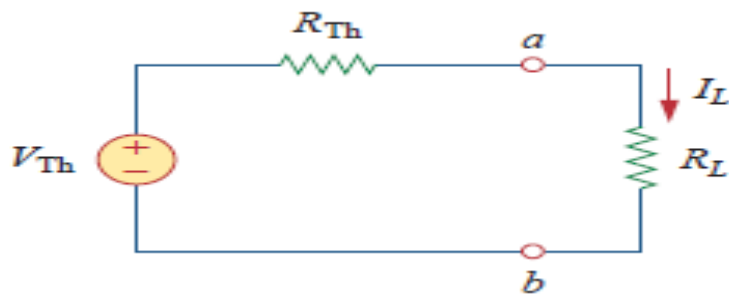

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

Find Thevenin equivalent seen by  $R_L$





$V_{Th}$ : using mesh analysis

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2 \text{ A}$$




$$i_1 = 0.5 \text{ A}$$

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$

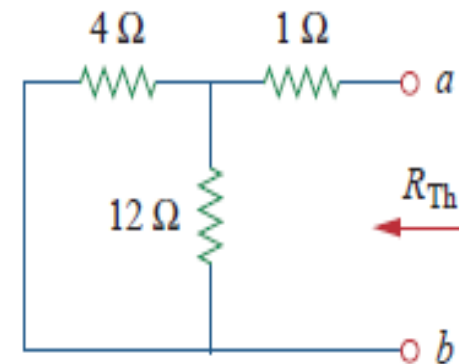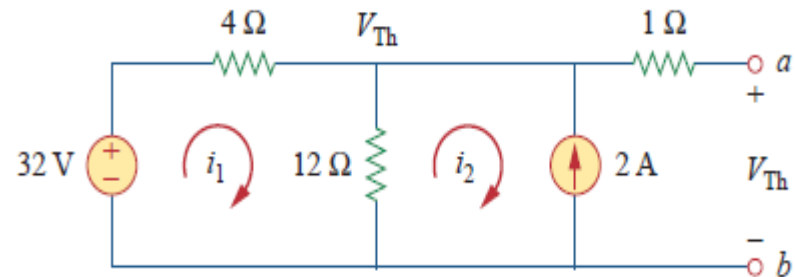
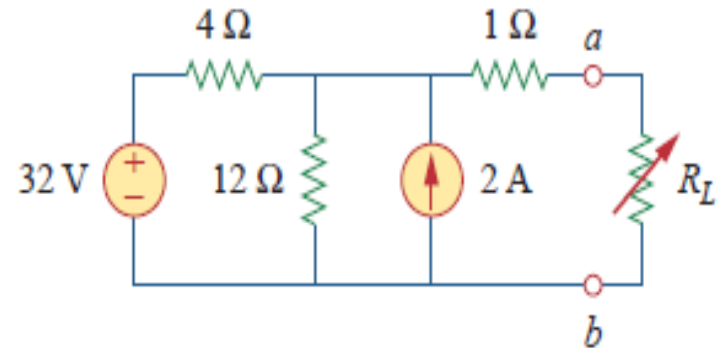
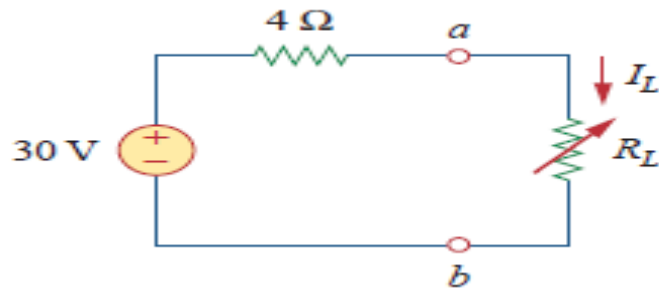
$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$




Find thevenin equivalent seen by  $R_4$

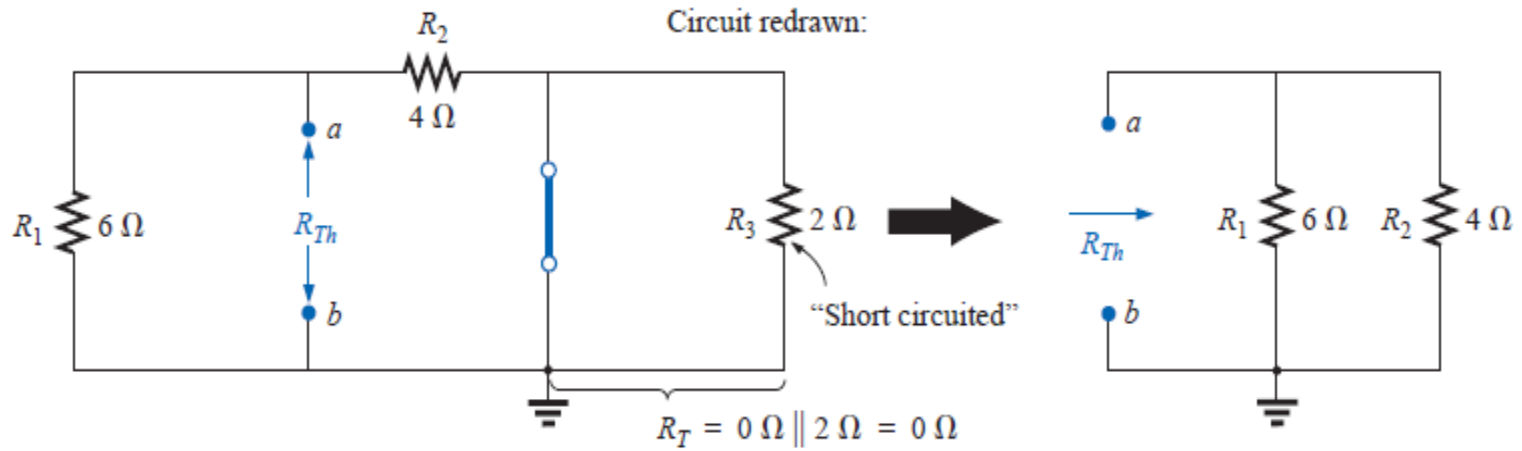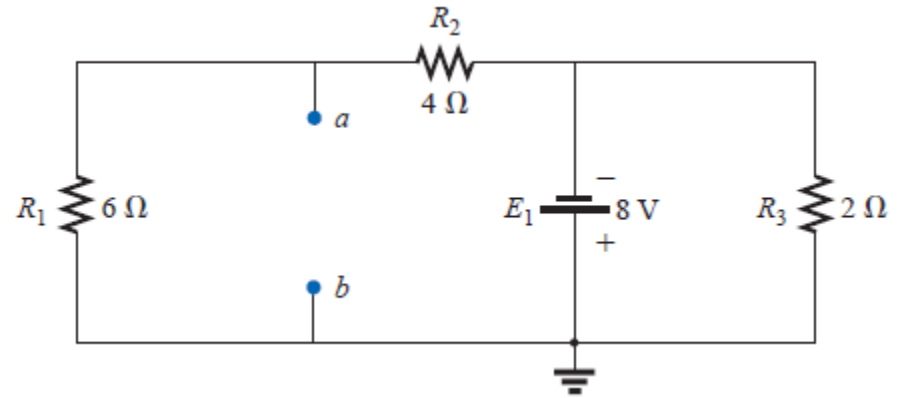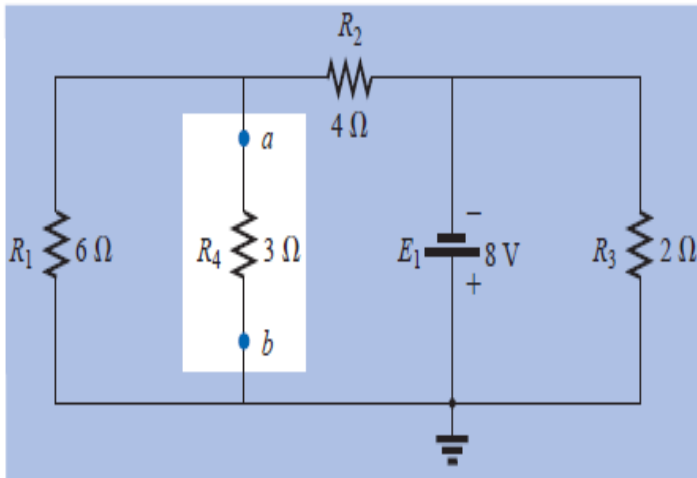

Find Thevenin equivalent seen by  $R_L$

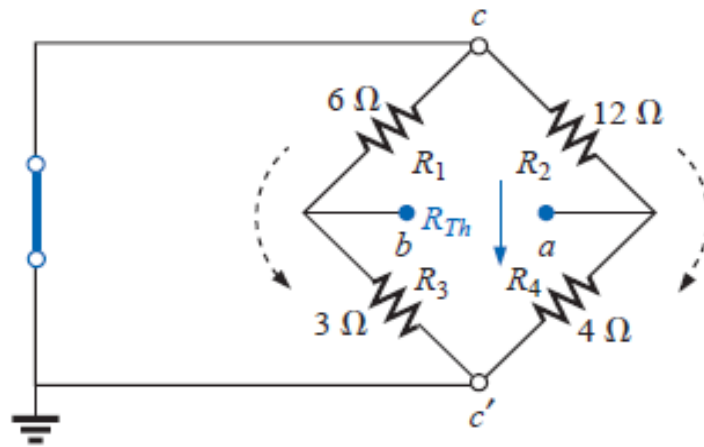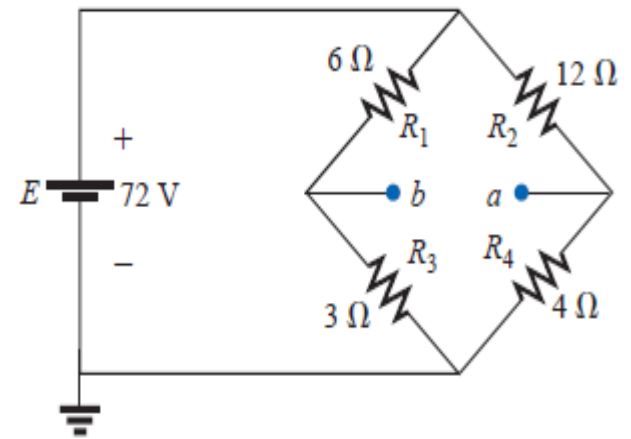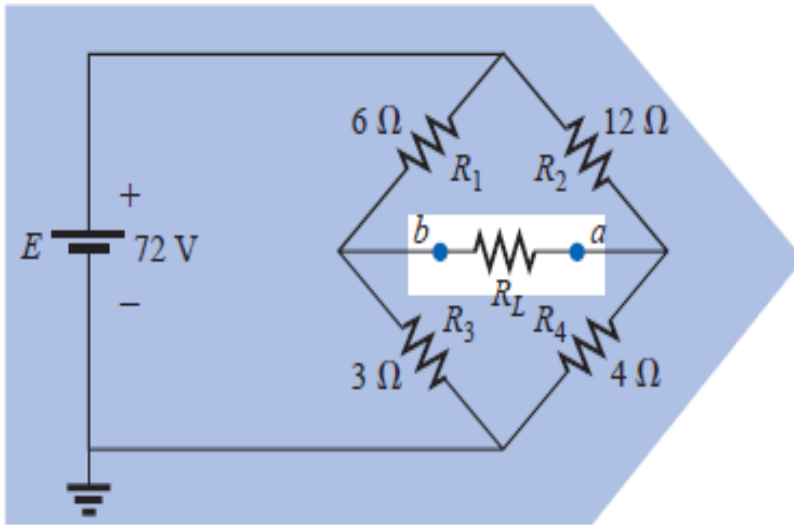

(a)

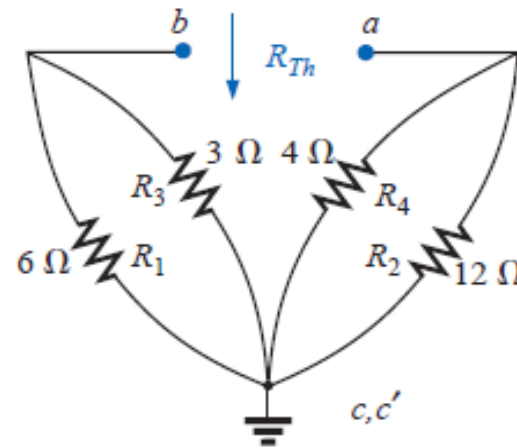

(b)

$$\begin{aligned}
 R_{Th} &= R_{a-b} = R_1 \parallel R_3 + R_2 \parallel R_4 \\
 &= 6 \Omega \parallel 3 \Omega + 4 \Omega \parallel 12 \Omega \\
 &= 2 \Omega + 3 \Omega = 5 \Omega
 \end{aligned}$$

VDR

$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{(6 \Omega)(72 \text{ V})}{6 \Omega + 3 \Omega} = \frac{432 \text{ V}}{9} = 48 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{(12 \Omega)(72 \text{ V})}{12 \Omega + 4 \Omega} = \frac{864 \text{ V}}{16} = 54 \text{ V}$$

$$E_{Th} = V_2 - V_1 = 54 \text{ V} - 48 \text{ V} = 6 \text{ V}$$

