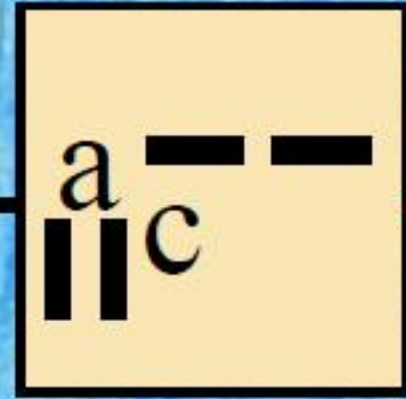


15

## Series and Parallel ac Circuits




## PARALLEL ac CIRCUITS
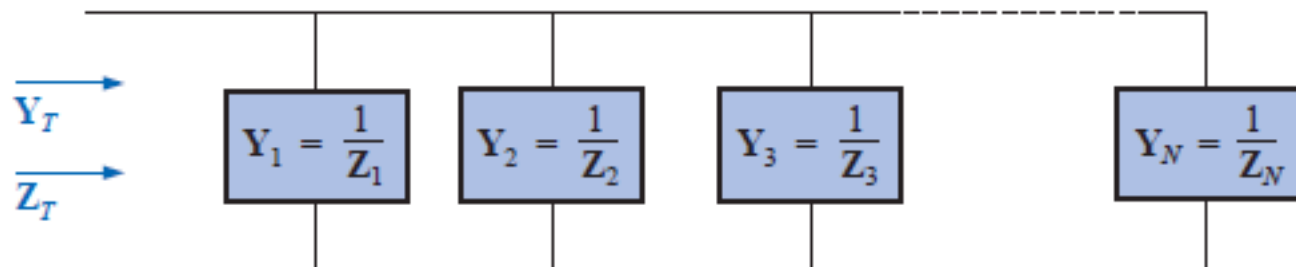
### ADMITTANCE

we define admittance ( $Y$ ) as being equal to  $1/Z$ .

$$Y_T = Y_1 + Y_2 + Y_3 + \dots + Y_N \quad (15.16)$$



$$Y_R = \frac{1}{Z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ$$

$$B_L = \frac{1}{X_L} \quad (\text{siemens, S})$$

$$Y_L = B_L \angle -90^\circ$$

$$Y_C = \frac{1}{Z_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ$$

$$B_C = \frac{1}{X_C} \quad (\text{siemens, S})$$

$$Y_C = B_C \angle 90^\circ$$

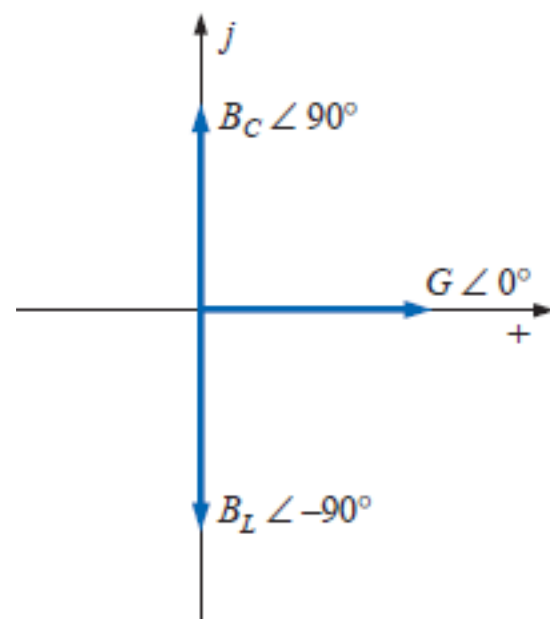


FIG. 15.55

Admittance diagram.

**EXAMPLE 15.12** For the network of Fig. 15.56:

- Find the admittance of each parallel branch.
- Determine the input admittance.
- Calculate the input impedance.
- Draw the admittance diagram.

**Solutions:**

$$\begin{aligned} \text{a. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{20 \Omega} \angle 0^\circ \\ &= 0.05 \text{ S} \angle 0^\circ = 0.05 \text{ S} + j 0 \end{aligned}$$


$$\begin{aligned} \mathbf{Y}_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10 \Omega} \angle -90^\circ \\ &= 0.1 \text{ S} \angle -90^\circ = 0 - j 0.1 \text{ S} \end{aligned}$$

$$\begin{aligned} \text{b. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L = (0.05 \text{ S} + j 0) + (0 - j 0.1 \text{ S}) \\ &= 0.05 \text{ S} - j 0.1 \text{ S} = G - j B_L \end{aligned}$$


$$\begin{aligned} \text{c. } \mathbf{Z}_T &= \frac{1}{\mathbf{Y}_T} = \frac{1}{0.05 \text{ S} - j 0.1 \text{ S}} = \frac{1}{0.112 \text{ S} \angle -63.43^\circ} \\ &= 8.93 \Omega \angle 63.43^\circ \end{aligned}$$

or Eq. (15.17):

$$\begin{aligned} \mathbf{Z}_T &= \frac{\mathbf{Z}_R \mathbf{Z}_L}{\mathbf{Z}_R + \mathbf{Z}_L} = \frac{(20 \Omega \angle 0^\circ)(10 \Omega \angle 90^\circ)}{20 \Omega + j 10 \Omega} \\ &= \frac{200 \Omega \angle 90^\circ}{22.36 \angle 26.57^\circ} = 8.93 \Omega \angle 63.43^\circ \end{aligned}$$

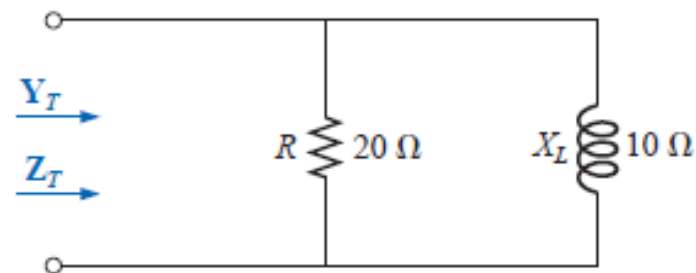

**FIG. 15.56**  
Example 15.12.

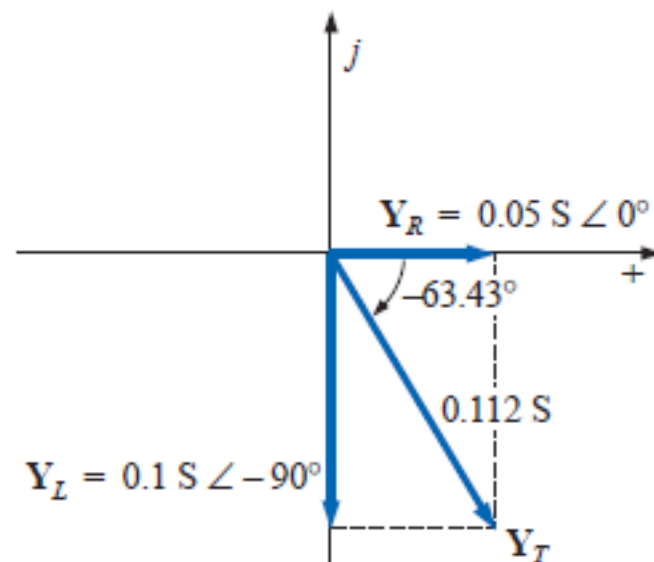

## 15.8 PARALLEL ac NETWORKS


For the representative parallel ac network of Fig. 15.61, the total impedance or admittance is determined as described in the previous section, and the source current is determined by Ohm's law as follows:

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T \quad (15.28)$$

Since the voltage is the same across parallel elements, the current through each branch can then be found through another application of Ohm's law:

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_1} = \mathbf{E}\mathbf{Y}_1 \quad (15.29a)$$

$$\mathbf{I}_2 = \frac{\mathbf{E}}{\mathbf{Z}_2} = \mathbf{E}\mathbf{Y}_2 \quad (15.29b)$$

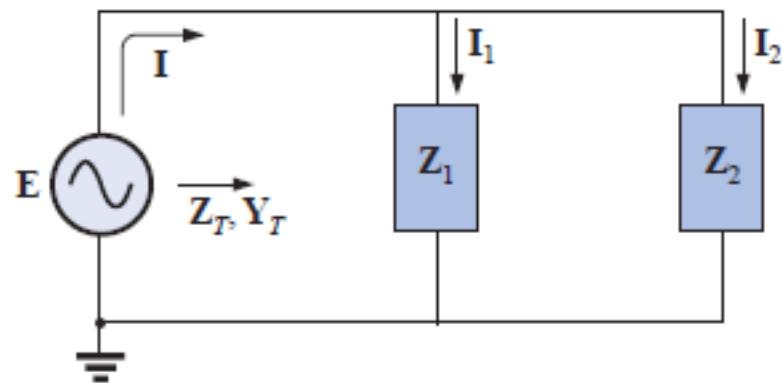

**FIG. 15.61**  
*Parallel ac network.*

Kirchhoff's current law can then be applied in the same manner as employed for dc networks. However, keep in mind that we are now dealing with the algebraic manipulation of quantities that have both magnitude and direction.

$$\mathbf{I} - \mathbf{I}_1 - \mathbf{I}_2 = 0$$

or

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 \quad (15.30)$$

The power to the network can be determined by


$$P = EI \cos \theta_T \quad (15.31)$$

where  $\theta_T$  is the phase angle between  $\mathbf{E}$  and  $\mathbf{I}$ .


Let us now look at a few examples carried out in great detail for the first exposure.

### **R-L**

Refer to Fig. 15.62.

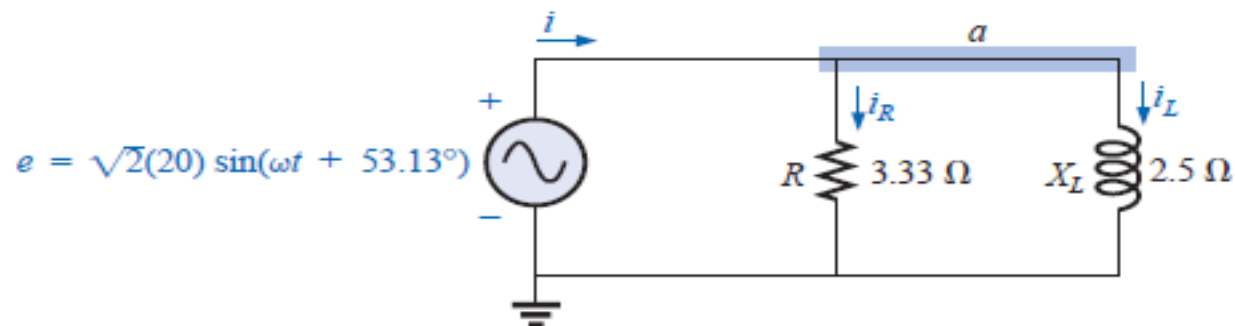

**Phasor Notation** As shown in Fig. 15.63.

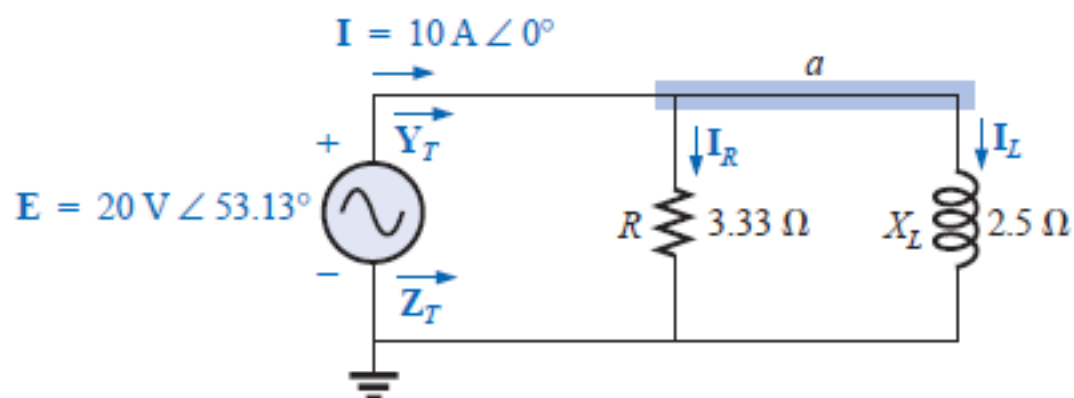


**FIG. 15.63**

*Applying phasor notation to the network of Fig. 15.62.*

**$Y_T$  and  $Z_T$**

$$\begin{aligned}
 Y_T &= Y_R + Y_L \\
 &= G \angle 0^\circ + B_L \angle -90^\circ = \frac{1}{3.33 \Omega} \angle 0^\circ + \frac{1}{2.5 \Omega} \angle -90^\circ \\
 &= 0.3 \text{ S} \angle 0^\circ + 0.4 \text{ S} \angle -90^\circ = 0.3 \text{ S} - j 0.4 \text{ S} \\
 &= 0.5 \text{ S} \angle -53.13^\circ \\
 Z_T &= \frac{1}{Y_T} = \frac{1}{0.5 \text{ S} \angle -53.13^\circ} = 2 \Omega \angle 53.13^\circ
 \end{aligned}$$

*Admittance diagram:* As shown in Fig. 15.64.

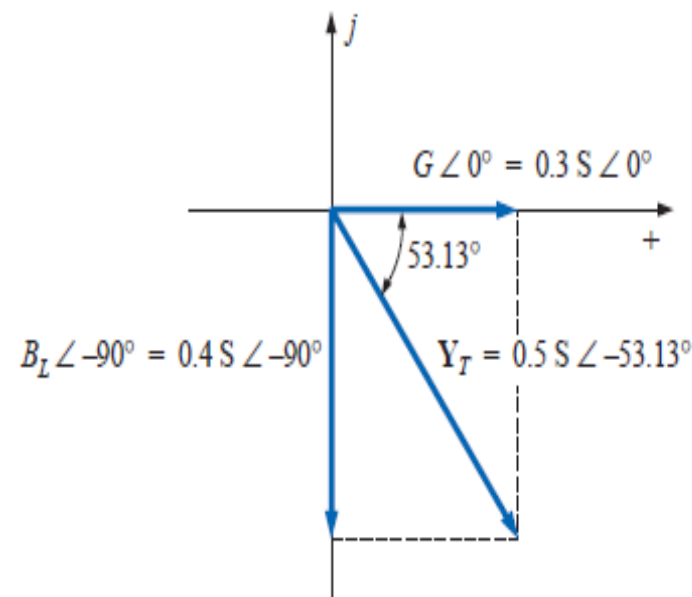

**FIG. 15.64**

I

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T = (20 \text{ V } \angle 53.13^\circ)(0.5 \text{ S } \angle -53.13^\circ) = 10 \text{ A } \angle 0^\circ$$

$\mathbf{I}_R$  and  $\mathbf{I}_L$


$$\begin{aligned} \mathbf{I}_R &= \frac{\mathbf{E} \angle \theta}{R \angle 0^\circ} = (\mathbf{E} \angle \theta)(\mathbf{G} \angle 0^\circ) \\ &= (20 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle 0^\circ) = 6 \text{ A } \angle 53.13^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_L &= \frac{\mathbf{E} \angle \theta}{X_L \angle 90^\circ} = (\mathbf{E} \angle \theta)(\mathbf{B}_L \angle -90^\circ) \\ &= (20 \text{ V } \angle 53.13^\circ)(0.4 \text{ S } \angle -90^\circ) \\ &= 8 \text{ A } \angle -36.87^\circ \end{aligned}$$

*Power:* The total power in watts delivered to the circuit is

$$\begin{aligned} P_T &= EI \cos \theta_T \\ &= (20 \text{ V})(10 \text{ A}) \cos 53.13^\circ = (200 \text{ W})(0.6) \\ &= 120 \text{ W} \end{aligned}$$

or 
$$P_T = I^2 R = \frac{V_R^2}{R} = V_R^2 G = (20 \text{ V})^2 (0.3 \text{ S}) = 120 \text{ W}$$

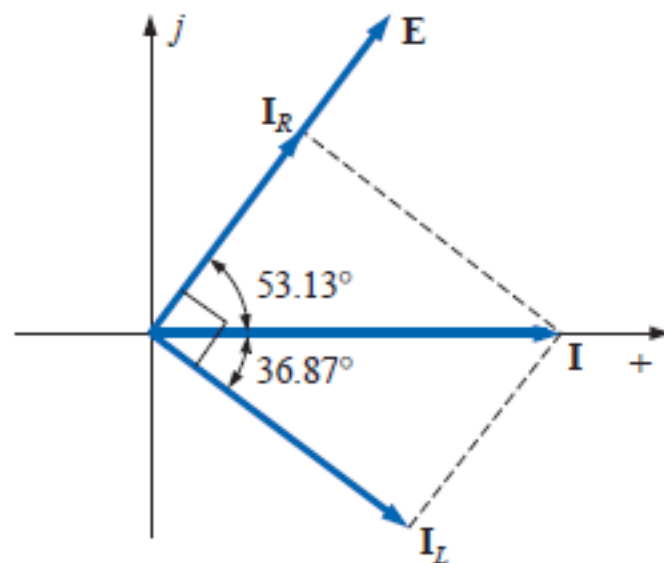

**FIG. 15.65**

*Phasor diagram for the parallel R-L network*

or, finally,

$$\begin{aligned}P_T &= P_R + P_L = EI_R \cos \theta_R + EI_L \cos \theta_L \\&= (20 \text{ V})(6 \text{ A}) \cos 0^\circ + (20 \text{ V})(8 \text{ A}) \cos 90^\circ = 120 \text{ W} + 0 \\&= \mathbf{120 \text{ W}}\end{aligned}$$

*Power factor:* The power factor of the circuit is

$$F_p = \cos \theta_T = \cos 53.13^\circ = \mathbf{0.6 \text{ lagging}}$$

or, through an analysis similar to that employed for a series ac circuit,

$$\cos \theta_T = \frac{P}{EI} = \frac{E^2/R}{EI} = \frac{EG}{I} = \frac{G}{I/V} = \frac{G}{Y_T}$$

and

$$\boxed{F_p = \cos \theta_T = \frac{G}{Y_T}} \quad (15.32)$$


where  $G$  and  $Y_T$  are the magnitudes of the total conductance and admittance of the parallel network. For this case,

$$F_p = \cos \theta_T = \frac{0.3 \text{ S}}{0.5 \text{ S}} = \mathbf{0.6 \text{ lagging}}$$




## CURRENT DIVIDER RULE

$$I_1 = \frac{Z_2 I_T}{Z_1 + Z_2} \quad \text{or} \quad I_2 = \frac{Z_1 I_T}{Z_1 + Z_2}$$

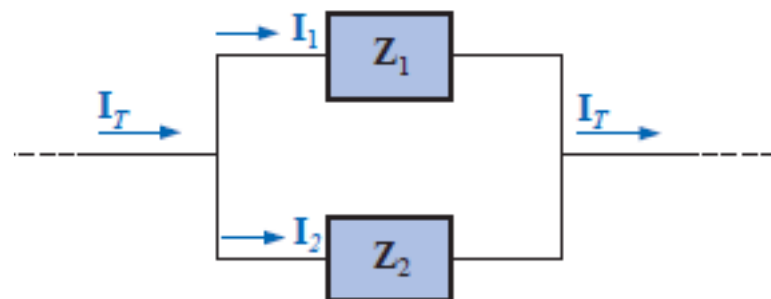

**EXAMPLE 15.16** Using the current divider rule, find the current through each parallel branch of Fig. 15.78.

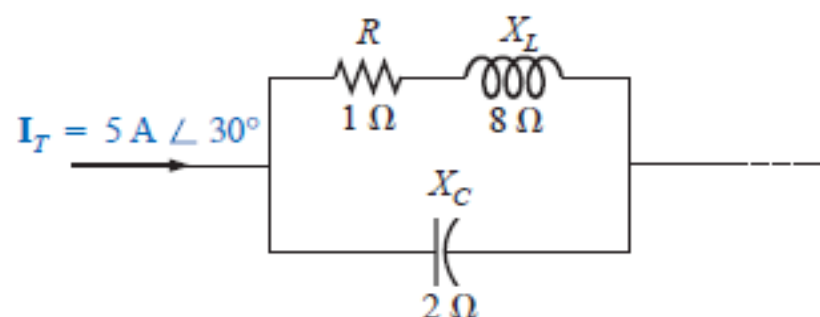

**FIG. 15.78**

*Example 15.16.*

**Solution:**

$$\begin{aligned} I_{R-L} &= \frac{Z_C I_T}{Z_C + Z_{R-L}} = \frac{(2 \Omega \angle -90^\circ)(5 \text{ A} \angle 30^\circ)}{-j2 \Omega + 1 \Omega + j8 \Omega} = \frac{10 \text{ A} \angle -60^\circ}{1 + j6} \\ &= \frac{10 \text{ A} \angle -60^\circ}{6.083 \angle 80.54^\circ} \cong 1.644 \text{ A} \angle -140.54^\circ \end{aligned}$$