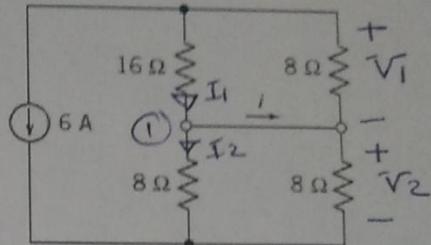


**Question 4: ( 5 marks)**


find i



$$16 \parallel 8 = \frac{16 \times 8}{16+8} = \frac{128}{24} =$$

$$= 5.33 \text{ Ω}$$
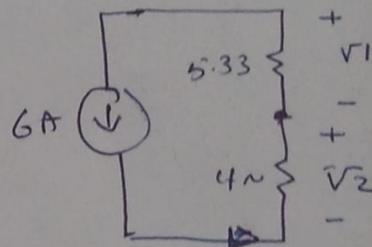
$$8 \parallel 8 = \frac{8 \times 8}{8+8} = 4 \text{ Ω}$$



$$-V_2 = (-6)(4) = -24 \text{ V} \quad (4)$$

$$V_1 = (-6)(5.33) = -31.98 \text{ V} \quad (4)$$

KCL at Node 1

$$I_1 = i + I_2 \approx -2$$

$$I_1 = \frac{V_1}{16} = -\frac{31.98}{16} = \underbrace{-1.9988 \text{ A}}$$

$$I_2 = \frac{V_2}{8} = \frac{-24}{8} = -3 \text{ A}$$

~~\_\_\_\_\_~~

$$-2 = 4 + -3$$

$$i = -2 + 3 = 1 \text{ A}$$

Course's Name : Electric circuits I

Palestine Technical University - Kadoorie

Course's Number : 12110101



Exam's Period : 90 minutes

First

Questions' Number : 4

Exam

Total Mark : 25

Fall 2014

Pages' Number : 4

Instructor's Name : Eng. Muntaser Al-Dabe

Student's Name: .....

Student's Number: .....

Section's Number: .....

Exam's Date :

**Question 1 : ( 6 marks)****Find the following**

- The current  $i_a$  in the  $20\text{-}\Omega$  resistor.
- The voltage  $v_b$  across the  $10\text{-}\Omega$  resistor.
- The current  $i_c$  in the independent voltage source.

$$I_a = \frac{25}{20} = 1.25 \text{ A} \quad \text{--- (2)}$$

KVL

$$-25 + 4I_a - V_b = 0$$

$$-25 + 4(-1.25) - V_b = 0$$


$$-25 + -5 - V_b = 0$$

$$V_b = -30 \quad \text{--- (2)}$$

$$I_{10} = \frac{-30}{10} = -3 \text{ A}$$

KCL at A


$$\begin{aligned} I_c &= I_a + I_{10} \\ &= -1.25 - 3 = -4.25 \text{ A} \end{aligned} \quad \text{--- (2)}$$

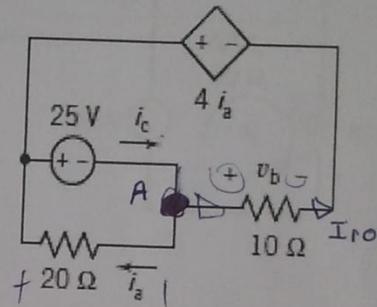

Question 3: (8 marks)

a) (4 marks)

Find  $i_1, i_2, i_3, i_4$

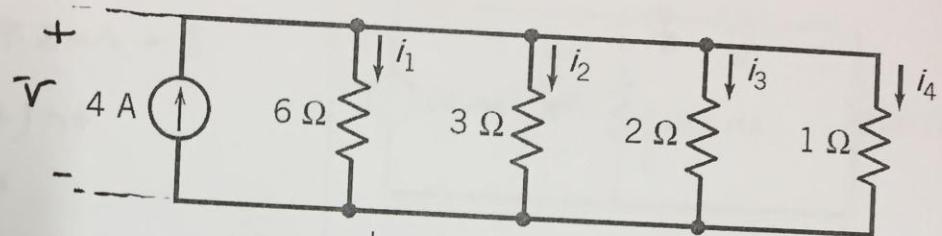

KCL

$$4 = \frac{V}{6} + \frac{V}{3} + \frac{V}{2} + \frac{V}{1}$$

$$4 = \frac{V}{6} + 2\frac{V}{6} + \frac{3V}{6} + 6\frac{V}{6}$$

$$24 = 12V \quad \textcircled{2}$$

$$V = \frac{24}{12} = 2 \text{ volt}$$

$$I_1 = \frac{V}{6} = \frac{2}{6} = 0.333 A \quad \begin{matrix} \frac{1}{2} \\ \frac{1}{3} \end{matrix}$$

$$I_2 = \frac{V}{3} = \frac{2}{3} = 0.666 A \quad \begin{matrix} \frac{2}{3} \\ \frac{1}{2} \end{matrix}$$

$$I_3 = \frac{V}{2} = \frac{2}{2} = 1 A \quad \begin{matrix} \frac{1}{2} \\ 2 \end{matrix}$$

$$I_4 = \frac{V}{1} = \frac{2}{1} = 2 A \quad \begin{matrix} \frac{2}{1} \\ \frac{1}{2} \end{matrix}$$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3} + \frac{1}{2} + \frac{1}{1}$$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{2}{6} + \frac{3}{6} + \frac{6}{6}$$

$$\frac{1}{R_{eq}} = \frac{12}{6} = 2$$

$$R_{eq} = \frac{1}{2} \rightarrow V = 4 \times \frac{1}{2} = 2 \text{ volt}$$

$$I_1 = \frac{2}{6} A$$

$$I_2 = \frac{2}{3} A$$

$$I_3 = \frac{2}{2} = 1 A$$

$$I_4 = \frac{2}{1} = 2 A$$

b) (4 marks)

Find values of R<sub>1</sub> and R<sub>2</sub>

KCL

$$24 \text{ mA} = 19.2 \text{ mA} + I$$

$$I = (24 - 19.2) \text{ mA}$$

$$I = 4.8 \text{ mA}$$

$$R_2 = \frac{0.384}{4.8 \text{ mA}} = 80 \Omega \quad (1)$$

$$V_R = I(80 + 80)$$

$$V_R = (4.8 \text{ mA})(160)$$

$$V_R = 0.768 \text{ V} \quad (2)$$

$$R_1 = \frac{0.768}{19.2 \text{ mA}} = 40 \Omega$$

