

# Chapter 3: SPECIAL-PURPOSE DIODES

## 3-1 THE ZENER DIODE

- A **Zener diode** is a silicon *pn* junction device that is designed for operation in the reverse-breakdown region( set by carefully controlling the doping level).
- A **major application** for zener diodes is **voltage regulation** by providing stable reference voltages for use in power supplies, voltmeters, and other instruments.
- In this section, you will see how the zener diode maintains a nearly constant dc voltage under the proper operating conditions.


After completing this Chapter, you should be able to:

- Describe the characteristics of a zener diode, its operation, equivalent circuits
- Define *temperature coefficient* and power dissipation and derating. to a zener diode
- Interpret zener diode datasheets
- Analyze zener regulation with a variable input voltage and with a variable load
- Discuss zener limiting
- Discuss another special purpose diodes


### Breakdown Characteristics:

- As the reverse voltage ( $V_R$ ) is increased to the breakdown point, the internal zener resistance (zener impedance  $Z_Z$ ), begins to decrease as the reverse current ( $I_R$ ) increases rapidly.
- The zener breakdown voltage ( $V_Z$ ) remains essentially constant although it increases slightly as the zener current,  $I_Z$ , increases.

(a) Zener V-I characteristics

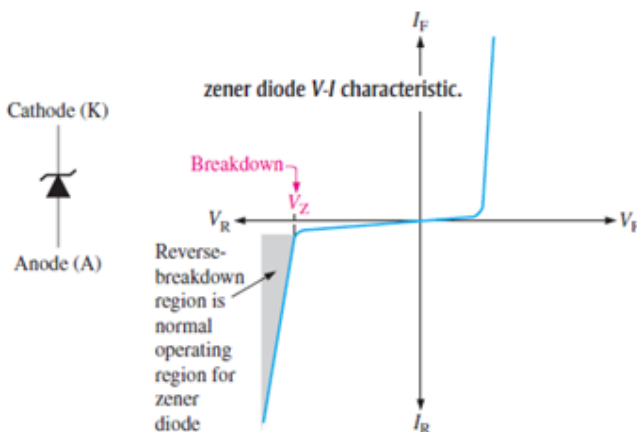

(b) Reverse Characteristic of a Zener

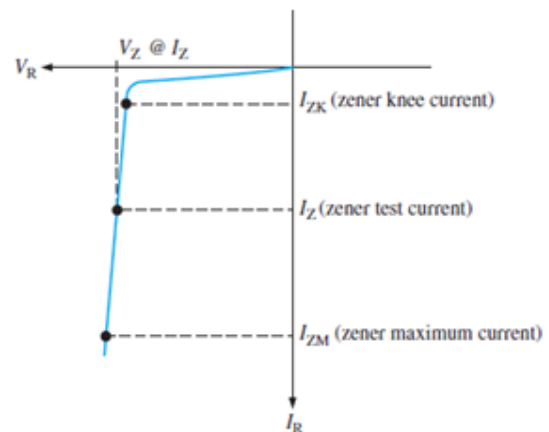

## Zener Breakdown Types

Zener diodes are designed to operate in reverse breakdown. Two types of reverse breakdown in a zener diode:


- **Avalanche effect:** high reverse voltage & available in zeners with breakdown voltages  $> 5\text{ V}$ .
- **Zener breakdown:** low reverse voltages & available in zeners with breakdown voltages  $< 5\text{ V}$ .

## Zener Regulation


- The zener diode maintains a nearly constant voltage across its terminals for values of reverse current ranging from  $I_{ZK}$  to  $I_{ZM}$ .
- There is a maximum current,  $I_{ZM}$ , above which the diode may be damaged due to excessive power
- $V_Z$ , is usually specified on a datasheet at a value of reverse current called the **Zener Test Current**.

## Zener Equivalent Circuits

**Ideal Zener**

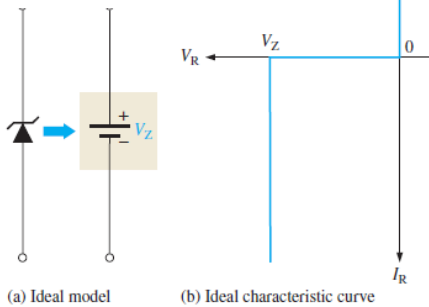


**Practical Zener**

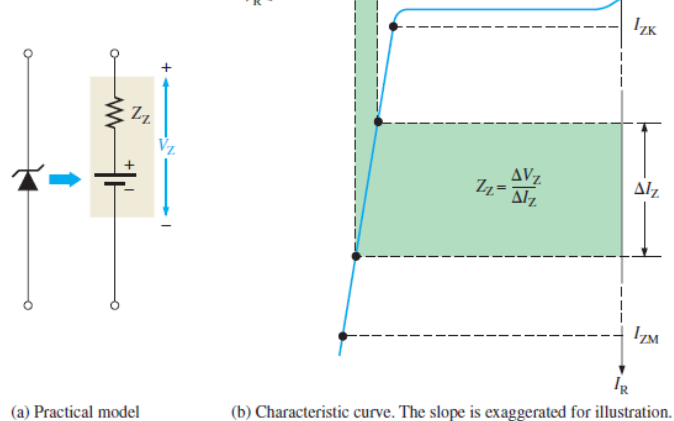
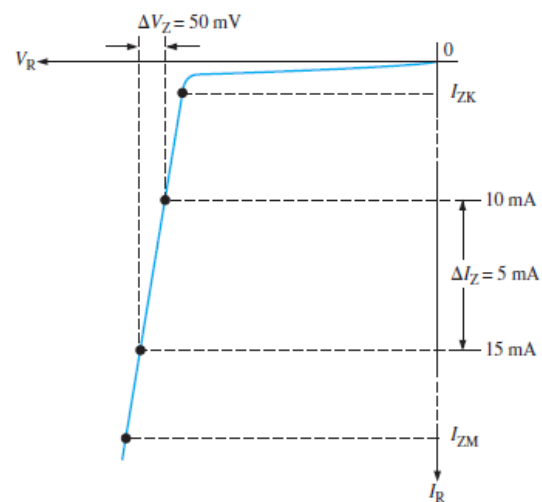
### Example.3.1:

A zener diode exhibits a certain change in  $V_Z$  for a certain change in  $I_Z$  on a portion of the linear characteristic curve between  $I_{ZK}$  and  $I_{ZM}$  as illustrated in the figure. What is the **zener impedance  $Z_Z$** ?



$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{50\text{ mV}}{5\text{ mA}} = 10\ \Omega$$

### Temperature Coefficient (TC):

- The percent change in  $V_Z$  for each degree Celsius change
- **For example:** a **12 V** zener diode with a positive temperature coefficient of **TC= 0.01 (% / C)** will exhibit a **1.2 mV** increase in  $V_Z$  when the junction temperature increases one degree Celsius
- The formula for calculating the change in zener voltage for a given junction temperature change, for a specified temperature coefficient, is:

$$\Delta V_Z = V_Z \times TC \times \Delta T$$

$V_Z$ : @ 25C, **TC**: temp coefficient,  $\Delta T$ : change in temp

- In some cases, the temperature coefficient is expressed in **mV/C** rather than **%/C**, and in this case  $\Delta V_Z$  can be calculated as:

$$\Delta V_Z = TC \times \Delta T$$

#### **EXAMPLE 3-2**

An 8.2 V zener diode (8.2 V at 25°C) has a positive temperature coefficient of 0.05%/°C. What is the zener voltage at 60°C?

**Solution** The change in zener voltage is

$$\begin{aligned}\Delta V_Z &= V_Z \times TC \times \Delta T = (8.2 \text{ V})(0.05\%/^\circ\text{C})(60^\circ\text{C} - 25^\circ\text{C}) \\ &= (8.2 \text{ V})(0.0005/^\circ\text{C})(35^\circ\text{C}) = 144 \text{ mV}\end{aligned}$$

Notice that 0.05%/°C was converted to 0.0005/°C. The zener voltage at 60°C is

$$V_Z + \Delta V_Z = 8.2 \text{ V} + 144 \text{ mV} = 8.34 \text{ V}$$

### Zener Power Dissipation

- **Maximum dc power dissipation  $P_{D(\max)}$ :** maximum power that Zener diodes are specified to operate.
- For example, the 1N746 zener is rated at a  $P_{D(\max)}$  of 500 mW.
- The dc power dissipation is determined by the formula:

$$P_D = V_Z I_Z$$

### Zener Power De-rating

- **Derating** is the operation of a device at less than its rated maximum capability in order to prolong its life.
- The maximum power dissipation of a zener diode is typically specified for temperatures at or below a certain value.
- Above the specified temperature, the maximum power dissipation is reduced according to a **derating factor** expressed in mV/C.
- **The maximum derated power:**

$$P_{D(\text{derated})} = P_{D(\max)} - (\text{mW}/^\circ\text{C})\Delta T$$

**EXAMPLE 3-3**

A certain zener diode has a maximum power rating of 400 mW at 50°C and a derating factor of 3.2 mW/°C. Determine the maximum power the zener can dissipate at a temperature of 90°C.

*Solution*

$$\begin{aligned}P_{D(\text{derated})} &= P_{D(\text{max})} - (\text{mW}/^\circ\text{C})\Delta T \\ &= 400 \text{ mW} - (3.2 \text{ mW}/^\circ\text{C})(90^\circ\text{C} - 50^\circ\text{C}) \\ &= 400 \text{ mW} - 128 \text{ mW} = \mathbf{272 \text{ mW}}\end{aligned}$$