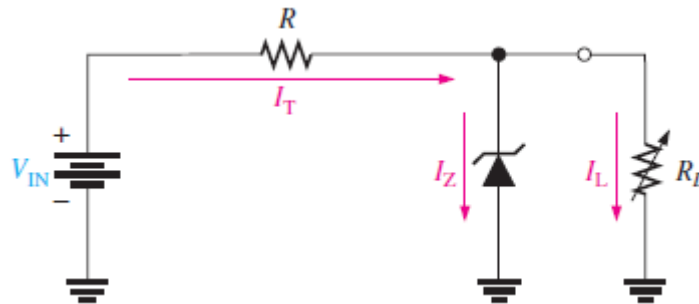


(2) Zener Regulation with a Variable Load

- Zener diode maintains a nearly constant voltage across R_L as long as the zener current is greater than I_{ZK} and less than I_{ZM} .




From No Load to Full Load:

- (a) **No-load condition:** $I_L=0$, all current is through zener.
- (b) When Load is connected:
- I_L remains constant as long as Zener is regulating
 - As R_L : decrease, I_L : increase, I_Z : decrease.
 - Zener continues to regulate until zener current = I_{ZK} and thus I_L is max (**full load condition**).

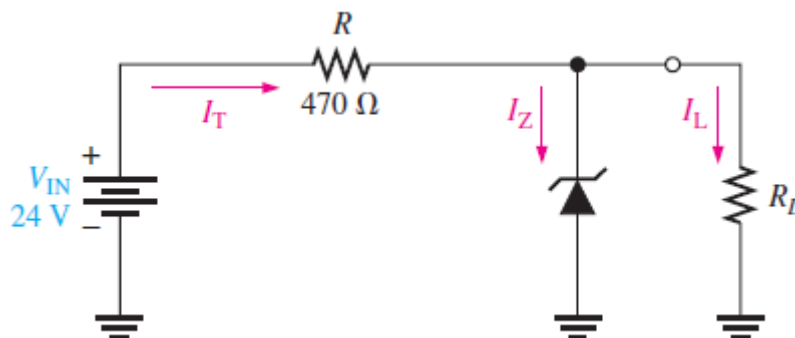EXAMPLE 3-6

Determine the minimum and the maximum load currents for which the zener diode in Figure 3-14 will maintain regulation. What is the minimum value of R_L that can be used? $V_Z = 12\text{ V}$, $I_{ZK} = 1\text{ mA}$, and $I_{ZM} = 50\text{ mA}$. Assume an ideal zener diode where $Z_Z = 0\ \Omega$ and V_Z remains a constant 12 V over the range of current values, for simplicity.



Solution When $I_L = 0 \text{ A}$ ($R_L = \infty$), I_Z is maximum and equal to the total circuit current I_T .

$$I_{Z(\max)} = I_T = \frac{V_{\text{IN}} - V_Z}{R} = \frac{24 \text{ V} - 12 \text{ V}}{470 \Omega} = 25.5 \text{ mA}$$

If R_L is removed from the circuit, the load current is 0 A. Since $I_{Z(\max)}$ is less than I_{ZM} , 0 A is an acceptable minimum value for I_L because the zener can handle all of the 25.5 mA.

$$I_{L(\min)} = 0 \text{ A}$$

The maximum value of I_L occurs when I_Z is minimum ($I_Z = I_{ZK}$), so

$$I_{L(\max)} = I_T - I_{ZK} = 25.5 \text{ mA} - 1 \text{ mA} = 24.5 \text{ mA}$$

The minimum value of R_L is


$$R_{L(\min)} = \frac{V_Z}{I_{L(\max)}} = \frac{12 \text{ V}}{24.5 \text{ mA}} = 490 \Omega$$

Therefore, if R_L is less than 490 Ω , R_L will draw more of the total current away from the zener and I_Z will be reduced below I_{ZK} . This will cause the zener to lose regulation. Regulation is maintained for any value of R_L between 490 Ω and infinity.

► FIGURE 3-15

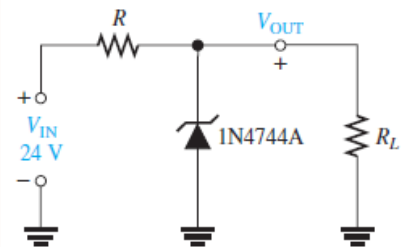EXAMPLE 3-7 For the circuit in Figure 3-15:

- Determine V_{OUT} at I_{ZK} and at I_{ZM} .
- Calculate the value of R that should be used.
- Determine the minimum value of R_L that can be used.



Solution The 1N4744A zener used in the regulator circuit of Figure 3-15 is a 15 V diode. The datasheet in Figure 3-7 gives the following information:
 $V_Z = 15 \text{ V}$ @ $I_Z = 17 \text{ mA}$, $I_{ZK} = 0.25 \text{ mA}$, and $Z_Z = 14 \Omega$.

(a) For I_{ZK} :

$$\begin{aligned} V_{\text{OUT}} &= V_Z - \Delta I_Z Z_Z = 15 \text{ V} - \Delta I_Z Z_Z = 15 \text{ V} - (I_Z - I_{ZK}) Z_Z \\ &= 15 \text{ V} - (16.75 \text{ mA})(14 \Omega) = 15 \text{ V} - 0.235 \text{ V} = 14.76 \text{ V} \end{aligned}$$

Calculate the zener maximum current. The maximum power dissipation is 1 W.

$$I_{ZM} = \frac{P_{D(\max)}}{V_Z} = \frac{1 \text{ W}}{15 \text{ V}} = 66.7 \text{ mA}$$


For I_{ZM} :

$$\begin{aligned} V_{\text{OUT}} &= V_Z + \Delta I_Z Z_Z = 15 \text{ V} + \Delta I_Z Z_Z \\ &= 15 \text{ V} + (I_{ZM} - I_Z) Z_Z = 15 \text{ V} + (49.7 \text{ mA})(14 \Omega) = 15.7 \text{ V} \end{aligned}$$

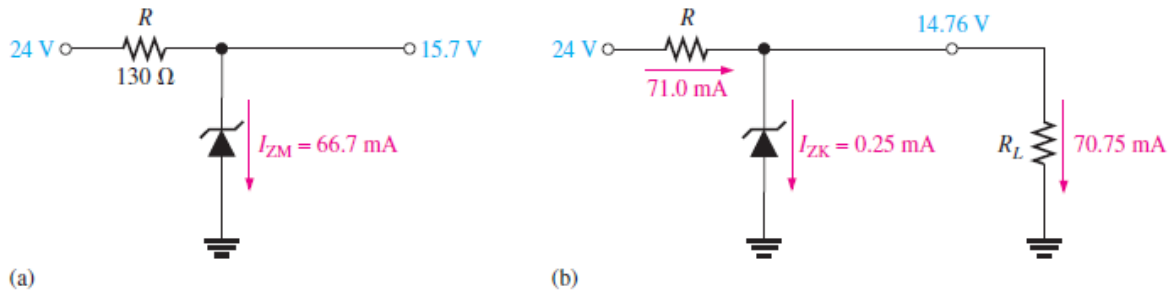- (b) Calculate the value of R for the maximum zener current that occurs when there is no load as shown in Figure 3–16(a).

$$R = \frac{V_{\text{IN}} - V_{\text{OUT}}}{I_{\text{ZK}}} = \frac{24 \text{ V} - 15.7 \text{ V}}{66.7 \text{ mA}} = 124 \Omega$$

$R = 130 \Omega$ (nearest larger standard value).



- (c) For the minimum load resistance (maximum load current), the zener current is minimum ($I_{\text{ZK}} = 0.25 \text{ mA}$) as shown in Figure 3–16(b).

$$I_{\text{T}} = \frac{V_{\text{IN}} - V_{\text{OUT}}}{R} = \frac{24 \text{ V} - 14.76 \text{ V}}{130 \Omega} = 71.0 \text{ mA}$$

$$I_{\text{L}} = I_{\text{T}} - I_{\text{ZK}} = 71.0 \text{ mA} - 0.25 \text{ mA} = 70.75 \text{ mA}$$

$$R_{\text{L}(\text{min})} = \frac{V_{\text{OUT}}}{I_{\text{L}}} = \frac{14.76 \text{ V}}{70.75 \text{ mA}} = 209 \Omega$$