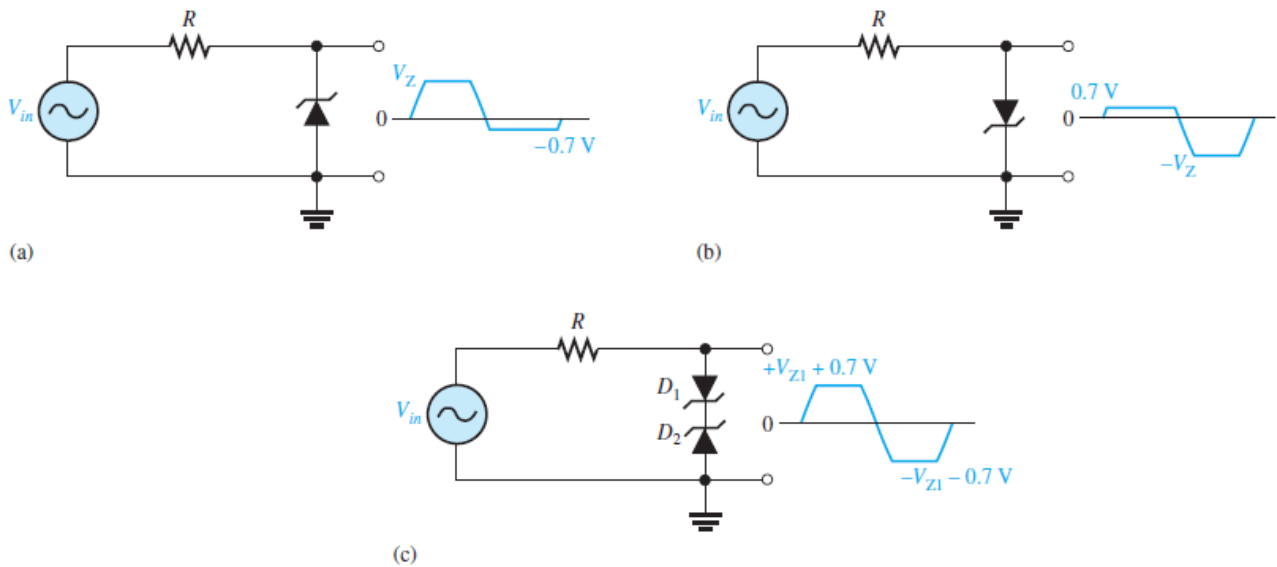


(3) Zener Limiter

In addition to voltage regulation applications, zener diodes can be used in ac applications to limit voltage swings to desired levels.




▲ FIGURE 3-18

Basic zener limiting action with a sinusoidal input voltage.

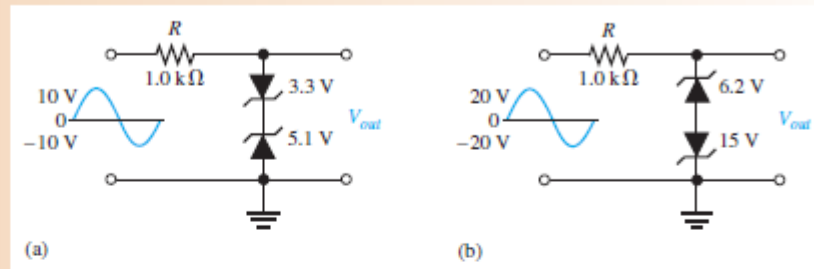
EXAMPLE 3-8

Determine the output voltage for each zener limiting circuit in Figure 3-19.






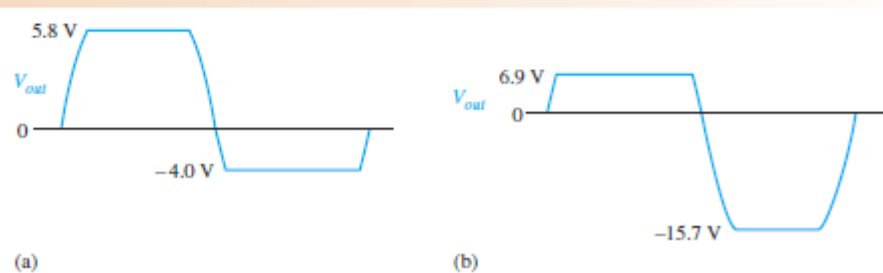

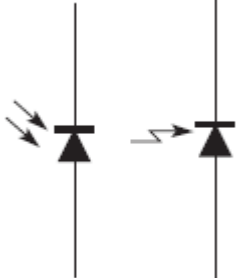
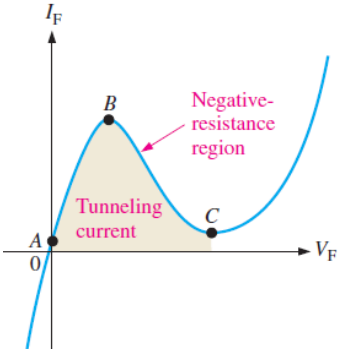
▲ FIGURE 3-19

Solution See Figure 3-20 for the resulting output voltages. Remember, when one zener is operating in breakdown, the other one is forward-biased with approximately 0.7 V across it.



Other Special Purpose Diodes

Diode Name	Description	Applications	Symbol
Varactor Diode	<ul style="list-style-type: none"> The depletion region acts as a capacitor dielectric. The p and n regions are conductive and act as the capacitor plates. Operates in reverse bias As the reverse-bias voltage increases, the depletion region widens, increasing the plate separation, thus decreasing the capacitance. 	Tuning circuits (parallel resonant circuits) in communication systems	
Light Emitting Diode (LED)	<ul style="list-style-type: none"> Operates in forward bias Recombining of electrons with holes release energy as photons (Electroluminescence) Example: GaAs LED which gives IR light. 	<ul style="list-style-type: none"> 7-segment display IR LED in industrial applications LED displays Traffic Lights 	
Photo-Diode	<ul style="list-style-type: none"> Operates in reverse bias When exposed to light, the reverse current increases with the light intensity. 	<ul style="list-style-type: none"> CD players Smoke detectors TV receivers Variable Resistor 	
Laser Diode	<ul style="list-style-type: none"> Operates in forward bias Due to recombination, photons released which strike atoms and cause other photons to be released forming an intense beam of laser light. 	<ul style="list-style-type: none"> CD players Laser printers Fiber optic system 	
Schottky Diode	<ul style="list-style-type: none"> Formed by joining a doped semiconductor region (usually n-type) with a metal When forward biased, the higher energy electrons in the n region are injected into the metal region where they give up their excess energy very rapidly, and a very rapid response to a change in bias occurs. The Schottky is a fast-switching diode (low V_F) 	<ul style="list-style-type: none"> High switching applications Digital circuits 	

<p>PIN Diode</p>	<ul style="list-style-type: none"> • When reverse-biased, the pin diode acts like a nearly constant capacitance. • When forward-biased, it acts like a current-controlled variable resistance. • Contains intrinsic (not doped) semiconductor region. 	<ul style="list-style-type: none"> • Used as a dc-controlled microwave switch. • Modulating device because of changing R. 	
<p>Tunnel Diode</p>	<ul style="list-style-type: none"> • Special characteristic: Negative Resistance. • Heavy doping  <p>A to B: acts as conductor B to C: negative resistance region C: Conventional diode</p>	<ul style="list-style-type: none"> • Useful in oscillator • Useful in microwave amplifiers • Parallel resonant circuit RLC 	