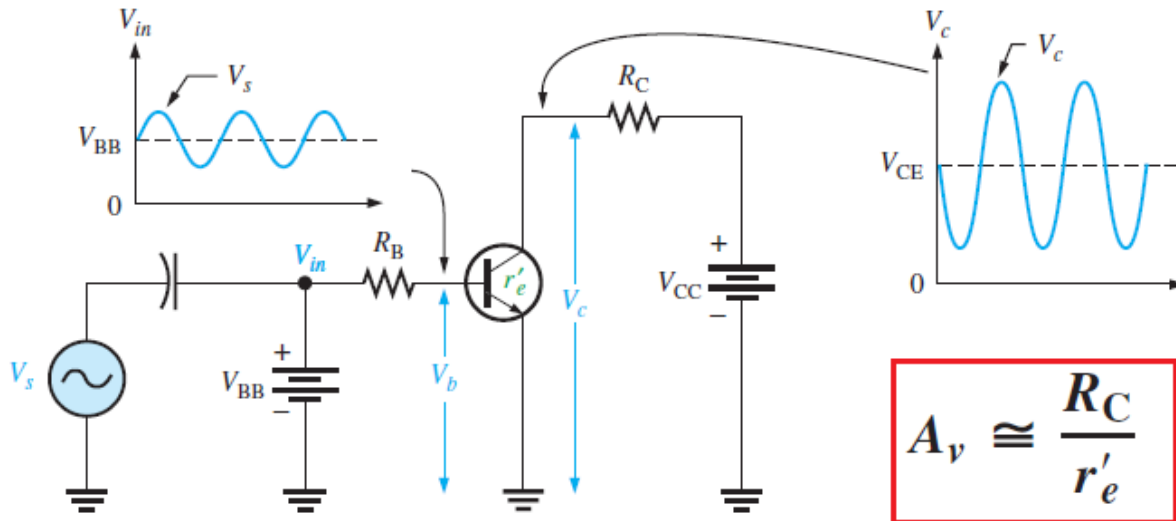


4-4 BJT as an Amplifier


- **Voltage amplification:** a transistor amplifies current because the collector current is equal to the base current multiplied by the Current gain, β .
- The following is the basic transistor amplifier circuit with ac source voltage V_s which is superimposed on the dc bias voltage V_{BB} by capacitive coupling.



EXAMPLE 4-9

Determine the voltage gain and the ac output voltage in Figure 4-22 if $r'_e = 50 \Omega$.

► FIGURE 4-22

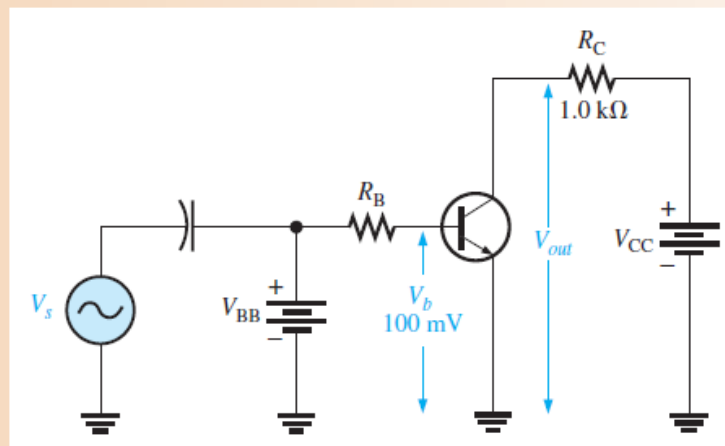

Solution The voltage gain is


$$A_v \cong \frac{R_C}{r'_e} = \frac{1.0 \text{ k}\Omega}{50 \Omega} = 20$$

Therefore, the ac output voltage is

$$V_{out} = A_v V_b = (20)(100 \text{ mV}) = 2 \text{ V rms}$$

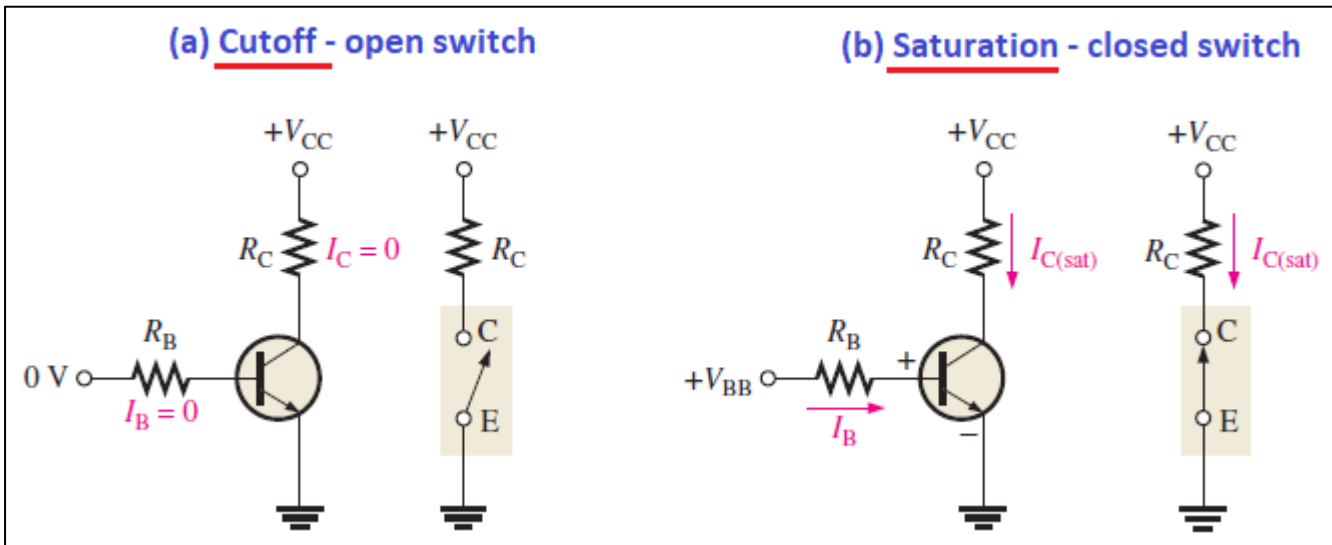4-5: the BJT as a Switch

- When used as an electronic switch, a BJT is normally operated alternately in **cutoff** and **saturation**.



- In part (a):** the transistor is in the cutoff region because the base-emitter junction is reverse-biased. **Ideally** → an open between collector and emitter.
- In part (b),** the transistor is in the saturation region because the base-emitter junction and the base-collector junction are forward-biased and the base current is made large enough to cause the collector current to reach its saturation value. **Ideally** → a short between collector and emitter

<p>■ Conditions in Cutoff</p>	$V_{CE(\text{cutoff})} = V_{CC}$
<p>■ Conditions in Saturation</p>	$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C}$
<p>■ The minimum value of base current needed to produce saturation</p>	
$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta_{DC}}$	