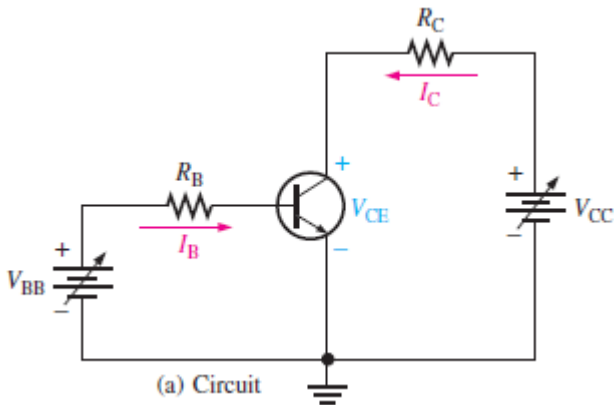


## Collector Characteristic Curves


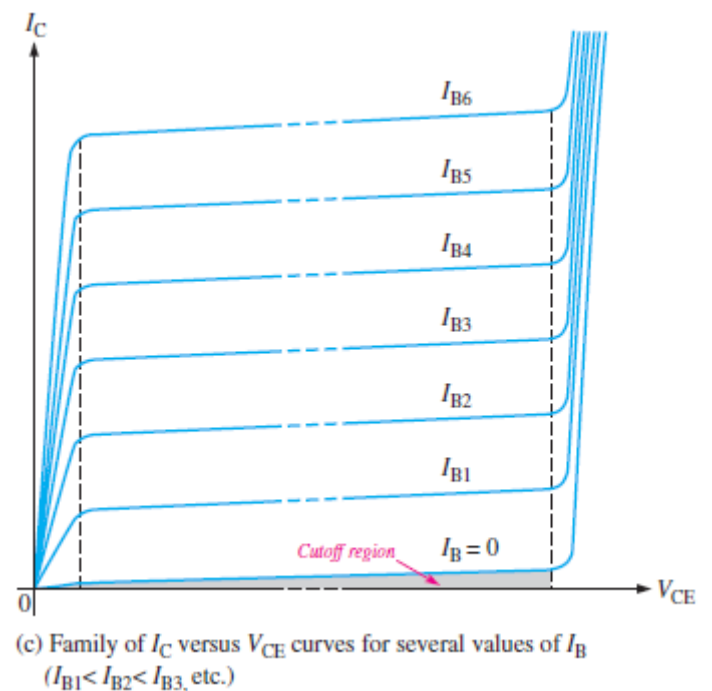


**Figure (b):**

- If  $V_{CC} = 0 \rightarrow$  BE and BC are forwarded  $\rightarrow$  BJT in **Saturation Region**  $\rightarrow I_C$  independent of  $I_B$ .
- **Points A-B:** as  $V_{CC}$  increased,  $V_{CE}$  increased but still  $V_{CE} < 0.7$  and BC is still forwarded. ( $I_C$  still increasing)
- **Points B-C:**  $V_{CE} > 0.7 \rightarrow$  BC: reversed, and BJT in the **Linear region** ( $I_C = \beta_{DC} I_B$ ) and  $V_{CE}$  continues to increase  
**Note:**  $\beta_{DC}$  is dependent on  $I_C$  and Temperature so the curve is not flat.
- **Point C:** BJT in **breakdown region:** at high  $V_{CE}$ , the reversed-biased BC junction breakdown and  $I_C$  increase rapidly.  
**Note:** A transistor should never be operated in this breakdown region.

**Figure (c):**


- A family of collector characteristic curves is produced when  $I_C$  versus  $V_{CE}$  is plotted for several values of  $I_B$ , as illustrated.
- When  $I_B = 0$ , the transistor is in the **cutoff** region although there is a very small collector leakage current as indicated. The amount of collector leakage current for  $I_B = 0$  is exaggerated on the graph for illustration.

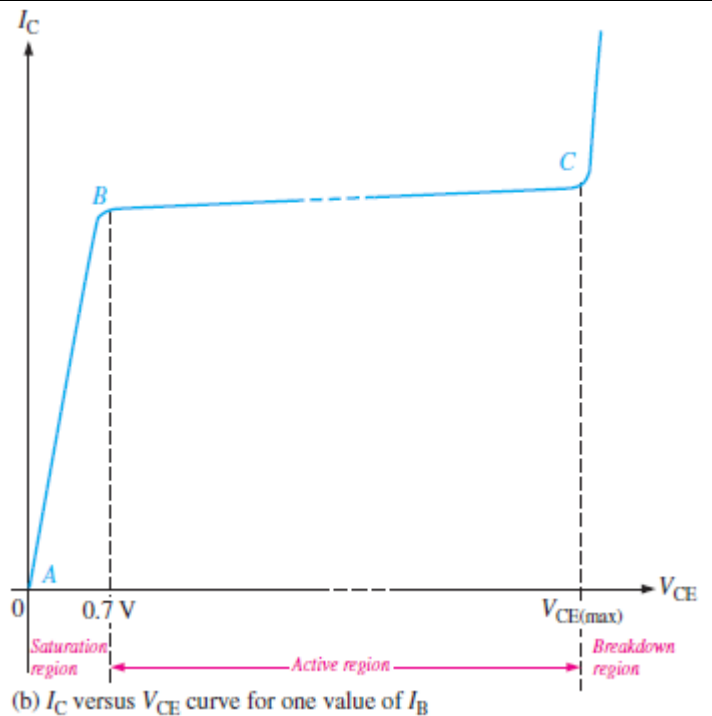

**EXAMPLE 4-3**

Sketch an ideal family of collector curves for the circuit in Figure 4-11 for  $I_B = 5 \mu\text{A}$  to  $25 \mu\text{A}$  in  $5 \mu\text{A}$  increments. Assume  $\beta_{DC} = 100$  and that  $V_{CE}$  does not exceed breakdown.


► **FIGURE 4-11**

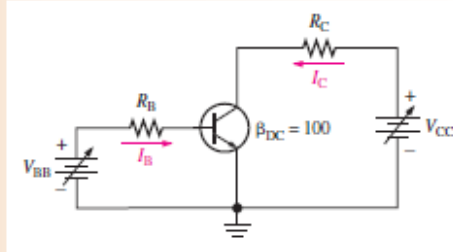

Using the relationship  $I_C = \beta_{DC} I_B$ , values of  $I_C$  are calculated and tabulated in Table 4-1. The resulting curves are plotted in Figure 4-12.


► **TABLE 4-1**

$I_B$	$I_C$
$5 \mu\text{A}$	0.5 mA
$10 \mu\text{A}$	1.0 mA
$15 \mu\text{A}$	1.5 mA
$20 \mu\text{A}$	2.0 mA
$25 \mu\text{A}$	2.5 mA

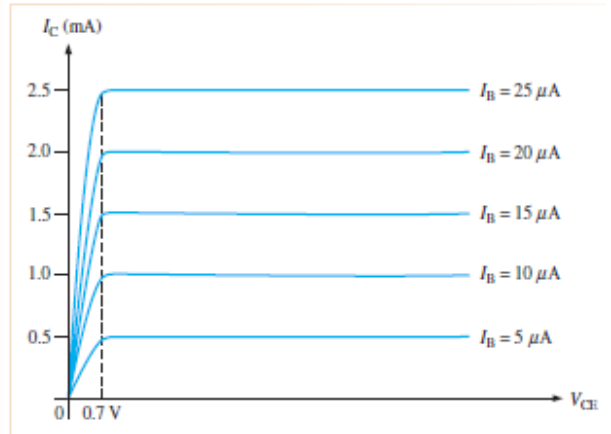

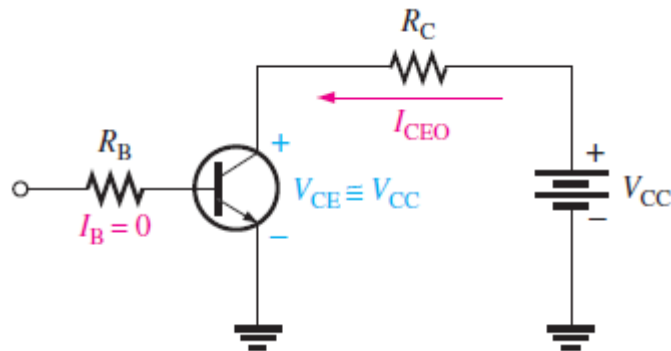
**Cutoff**

- BE and BC junctions are reversed biased
- Collector Leakage Current  $I_{CEO}$  is extremely small and is neglected.



**Saturation**


- As  $I_B$  increases due to increasing  $V_{BB}$ ,  $I_C$  also increases due to the increased voltage drop across  $R_C$ .
- When the transistor reaches saturation,  $I_C$  can increase no further regardless of further increase in  $I_B$ .
- BE and BC junctions are forward biased.
- $I_C = \beta_{DC} I_B$  is no longer valid.

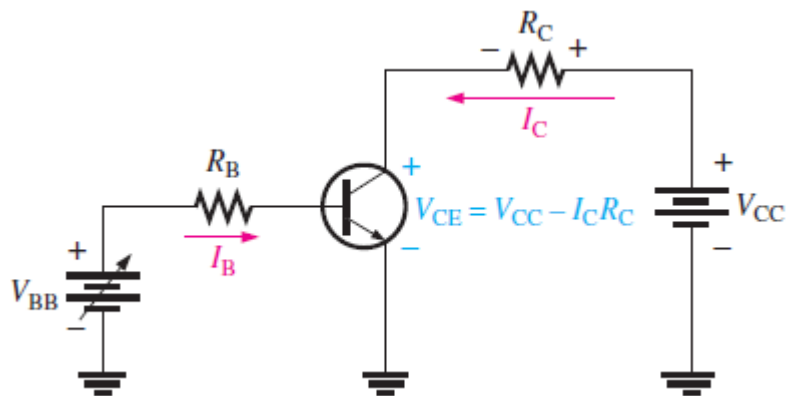

**EXAMPLE 4-4**

Determine whether or not the transistor in Figure 4-16 is in saturation. Assume  $V_{CE(sat)} = 0.2 \text{ V}$ .

► **FIGURE 4-16**

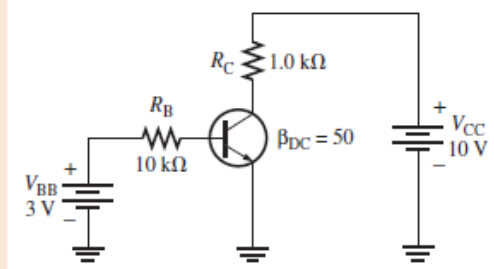

**Solution** First, determine  $I_{C(sat)}$ .

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10 \text{ V} - 0.2 \text{ V}}{1.0 \text{ k}\Omega} = \frac{9.8 \text{ V}}{1.0 \text{ k}\Omega} = 9.8 \text{ mA}$$

Now, see if  $I_B$  is large enough to produce  $I_{C(sat)}$ .


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = \frac{2.3 \text{ V}}{10 \text{ k}\Omega} = 0.23 \text{ mA}$$

$$I_C = \beta_{DC} I_B = (50)(0.23 \text{ mA}) = 11.5 \text{ mA}$$

This shows that with the specified  $\beta_{DC}$ , this base current is capable of producing an  $I_C$  greater than  $I_{C(sat)}$ . Therefore, the **transistor is saturated**, and the collector current value of 11.5 mA is never reached. If you further increase  $I_B$ , the collector current remains at its saturation value of 9.8 mA.
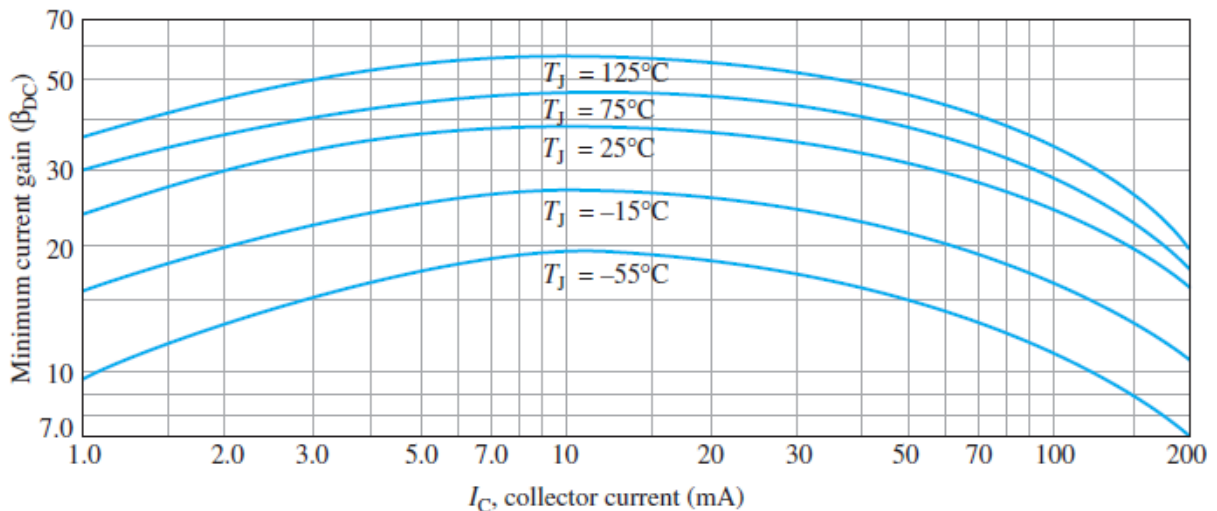
## More about $\beta_{DC}$

The  $\beta_{DC}$  is not truly constant but varies with both **collector current** and with **temperature**.



▲ **FIGURE 4-17**

Variation of  $\beta_{DC}$  with  $I_C$  for several temperatures.