

## Maximum Transistor Rating

- Limitations specified in the datasheet
- Maximum rating are given for:  $V_{CE}$ ,  $I_C$ ,  $P_D$ , ...

### Example:

Power Dissipation maximum ratings

$$P_{D(\max)} = I_C \times V_{CE}$$

- For a given transistor, assume


$$P_{D(\max)} = 500 \text{ mW}$$

$$V_{CE(\max)} = 20 \text{ V}$$

$$I_{C(\max)} = 50 \text{ mA.}$$

- Let us take the following values:

$P_{D(\max)}$	$V_{CE}$	$I_C$
500 mW	5 V	100 mA
500 mW	10 V	50 mA
500 mW	15 V	33 mA
500 mW	20 V	25 mA

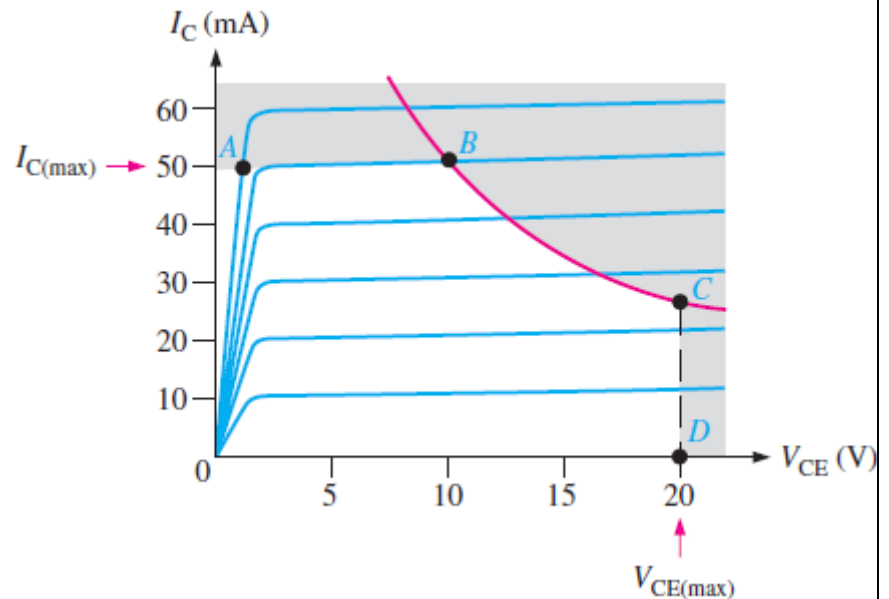

- From these values, the maximum power dissipation curve can be plotted on the collector characteristic curves, as shown. (red)
- The curve shows that this particular transistor cannot be operated in the shaded portion of the graph.

### EXAMPLE 4-5

A certain transistor is to be operated with  $V_{CE} = 6 \text{ V}$ . If its maximum power rating is 250 mW, what is the most collector current that it can handle?


*Solution*

$$I_C = \frac{P_{D(\max)}}{V_{CE}} = \frac{250 \text{ mW}}{6 \text{ V}} = 41.7 \text{ mA}$$

This is the maximum current for this particular value of  $V_{CE}$ . The transistor can handle more collector current if  $V_{CE}$  is reduced, as long as  $P_{D(\max)}$  and  $I_{C(\max)}$  are not exceeded.

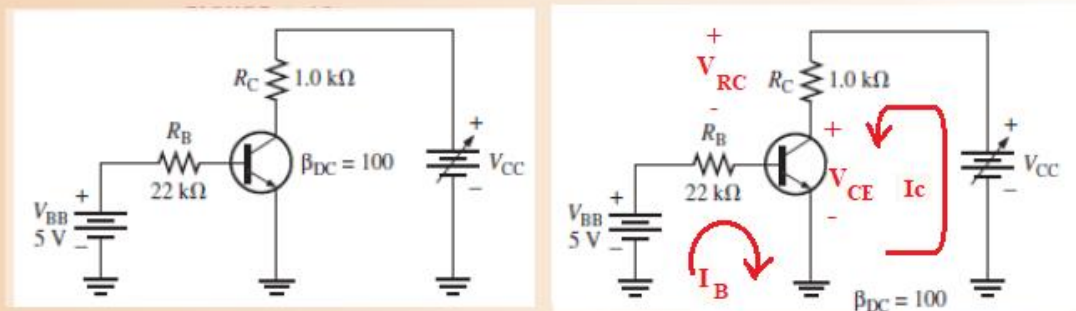**EXAMPLE 4–6**

The transistor in Figure 4–19 has the following maximum ratings:  $P_{D(\max)} = 800 \text{ mW}$ ,  $V_{CE(\max)} = 15 \text{ V}$ , and  $I_{C(\max)} = 100 \text{ mA}$ . Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating. Which rating would be exceeded first?



**Solution** First, find  $I_B$  so that you can determine  $I_C$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{22 \text{ k}\Omega} = 195 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (100)(195 \mu\text{A}) = 19.5 \text{ mA}$$

$I_C$  is much less than  $I_{C(\max)}$  and ideally will not change with  $V_{CC}$ . It is determined only by  $I_B$  and  $\beta_{DC}$ .

The voltage drop across  $R_C$  is

$$V_{R_C} = I_C R_C = (19.5 \text{ mA})(1.0 \text{ k}\Omega) = 19.5 \text{ V}$$

So,

$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 15 \text{ V} + 19.5 \text{ V} = 34.5 \text{ V}$$

$V_{CC}$  can be increased to 34.5 V, under the existing conditions, before  $V_{CE(\max)}$  is exceeded. However, at this point it is not known whether or not  $P_{D(\max)}$  has been exceeded.

$$P_D = V_{CE(\max)} I_C = (15 \text{ V})(19.5 \text{ mA}) = 293 \text{ mW}$$

Since  $P_{D(\max)}$  is 800 mW, it is *not* exceeded when  $V_{CC} = 34.5 \text{ V}$ . So,  $V_{CE(\max)} = 15 \text{ V}$  is the limiting rating in this case. If the base current is removed causing the transistor to turn off,  $V_{CE(\max)}$  will be exceeded first because the entire supply voltage,  $V_{CC}$ , will be dropped across the transistor.

### Derating $P_{D(\max)}$

- $P_{D(\max)}$  is usually specified at  $25^\circ\text{C}$ . For higher temperatures,  $P_{D(\max)}$  is **less**.
- Datasheets often give **derating factors** for determining  $P_{D(\max)}$  at any temperature above  $25^\circ\text{C}$ .

**EXAMPLE 4–7**

A certain transistor has a  $P_{D(\max)}$  of 1 W at  $25^\circ\text{C}$ . The derating factor is  $5 \text{ mW}/^\circ\text{C}$ . What is the  $P_{D(\max)}$  at a temperature of  $70^\circ\text{C}$ ?

**Solution** The change (reduction) in  $P_{D(\max)}$  is

$$\Delta P_{D(\max)} = (5 \text{ mW}/^\circ\text{C})(70^\circ\text{C} - 25^\circ\text{C}) = (5 \text{ mW}/^\circ\text{C})(45^\circ\text{C}) = 225 \text{ mW}$$

Therefore, the  $P_{D(\max)}$  at  $70^\circ\text{C}$  is

$$1 \text{ W} - 225 \text{ mW} = 775 \text{ mW}$$

*Note: an example of a BJT Datasheet is given in Page 189.*