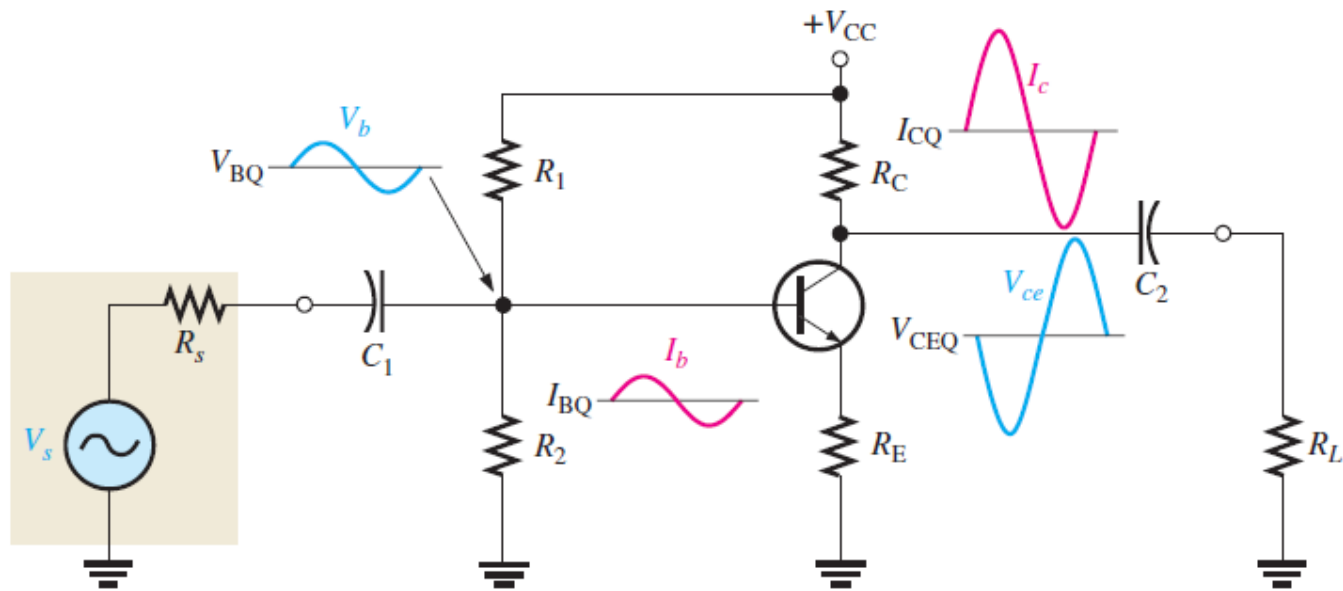


Chapter.6

BJT Amplifiers




◀ FIGURE 6-2

An amplifier with voltage-divider bias driven by an ac voltage source with an internal resistance, R_s .

Amplifier Operation


- ❑ The biasing of a transistor is purely a dc operation. The purpose of biasing is to establish a Q-point about which variations in current and voltage can occur in response to an ac input signal.
- ❑ In applications where small signal voltages must be amplified—such as from an antenna or a microphone—variations about the Q-point are relatively small.
- ❑ Amplifiers designed to handle these small ac signals are often referred to as *small-signal amplifiers*.

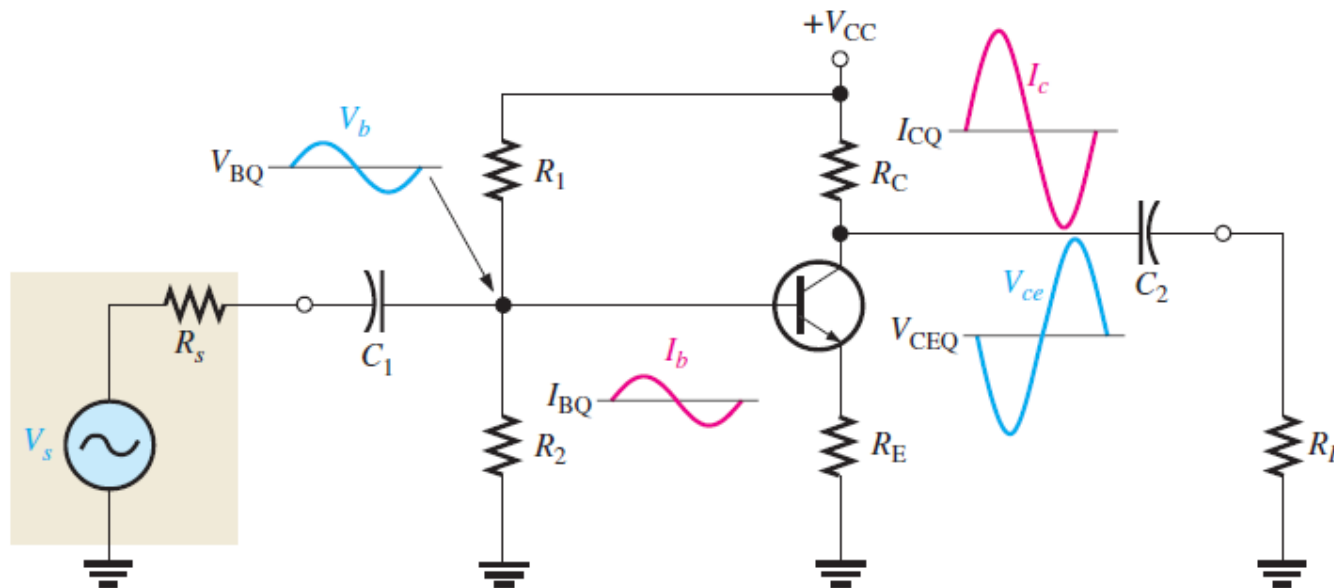

◀ FIGURE 6-2

An amplifier with voltage-divider bias driven by an ac voltage source with an internal resistance, R_s .

AC quantities

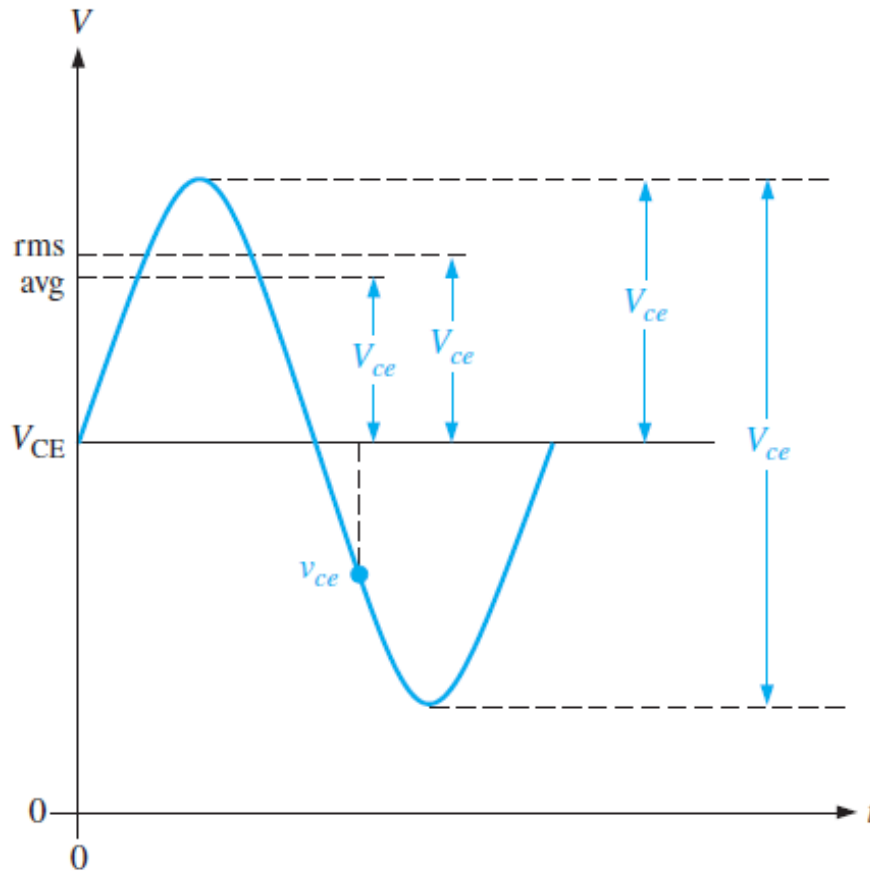

DC $I_C, I_E, V_C,$ and V_{CE}

AC $I_C, I_E, I_b, V_C, V_{ce}$

R_C is the dc collector resistance.

R_c is the ac collector resistance


r'_e internal ac emitter resistance

- ❑ **Vce** can represent **rms**, **average**, **peak**, or **peak-to-peak**
- ❑ **Vce** is in **rms** will be assumed unless stated otherwise.

The Linear Operation

◀ FIGURE 6-2

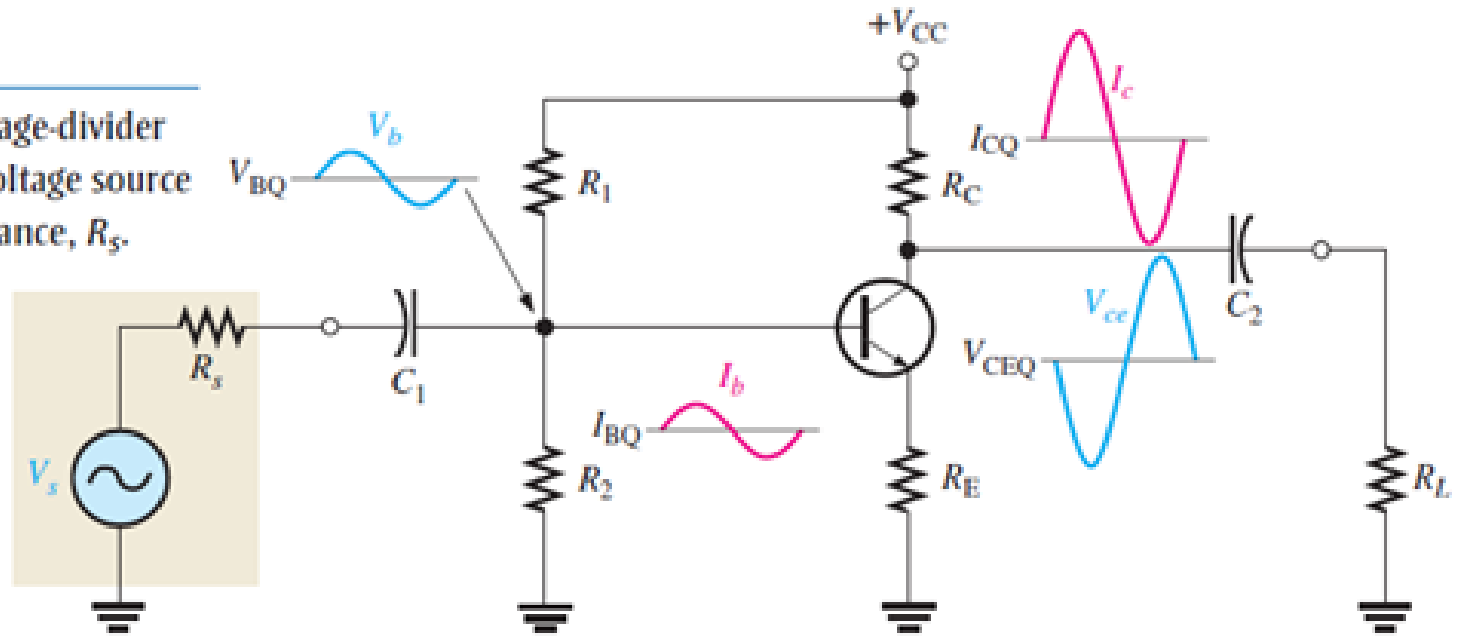An amplifier with voltage-divider bias driven by an ac voltage source with an internal resistance, R_s .




C1 : couple V_s to the base

C2 : couple R_L to the collector

- ❑ **The coupling capacitors:** block dc thus prevent R_s and R_L from changing the dc bias voltages at the base and collector.
- ❑ **Operation:** $V_s \rightarrow V_b$ vary sinusoidally on $V_{BQ} \rightarrow I_b$ vary sinusoidally on $I_{BQ} \rightarrow I_C$ varies sinusoidally on I_{CQ} (in-phase) $\rightarrow V_{ce}$ varies sinusoidally with V_{CE} (out of phase)
- ❑ A transistor produces a **phase inversion** between the base voltage and the collector voltage.

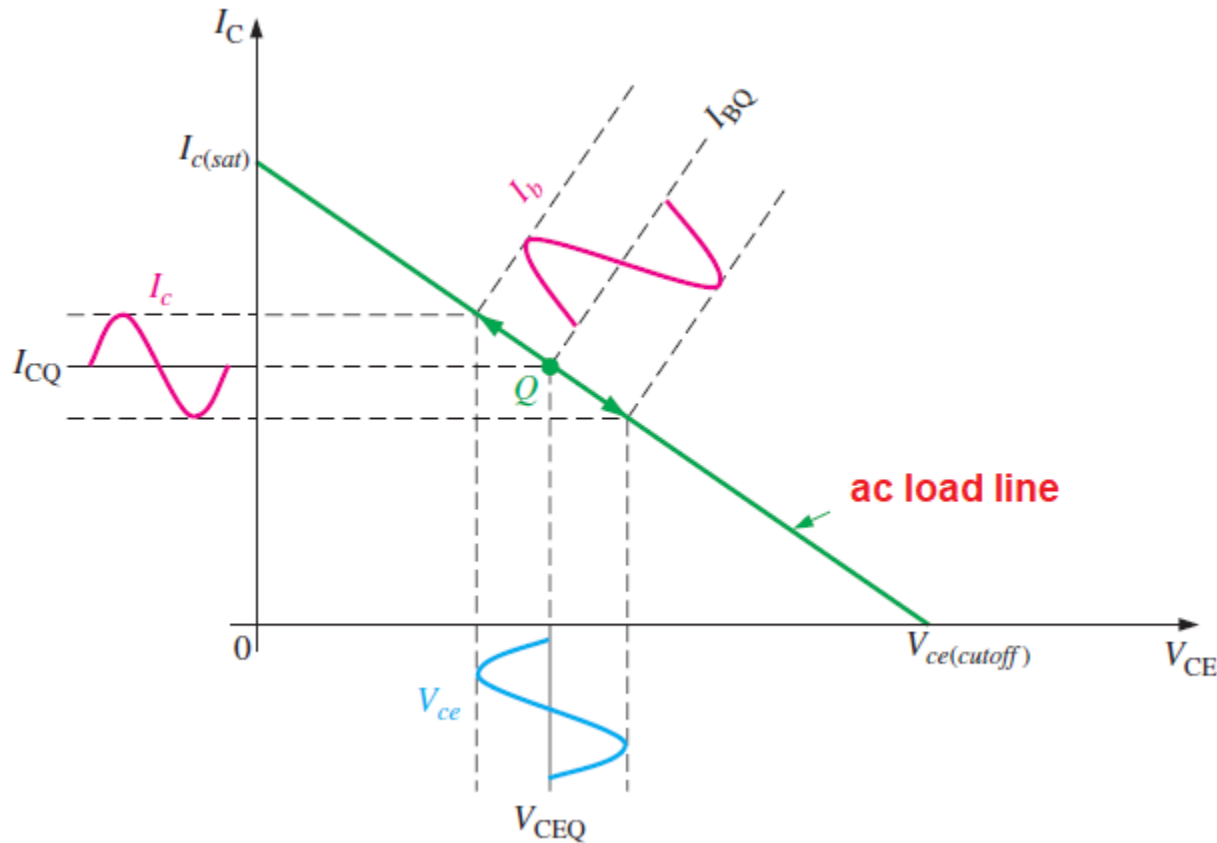Graphical Picture of the Amplifier Operation



◀ FIGURE 6-3

Graphical ac load line operation of the amplifier showing the variation of the base current, collector current, and collector-to-emitter voltage about their dc Q-point values. I_b and I_c are on different scales.


- **Note:** The ac load line differs from the dc load line because the effective ac collector resistance is R_L in parallel with R_C and is less than the dc collector resistance R_C alone.

Graphical Picture of the Amplifier Operation

EXAMPLE 6-1

The ac load line operation of a certain amplifier extends $10\ \mu\text{A}$ above and below the Q-point base current value of $50\ \mu\text{A}$, as shown in Figure 6-4. Determine the resulting peak-to-peak values of collector current and collector-to-emitter voltage from the graph.


► FIGURE 6-4

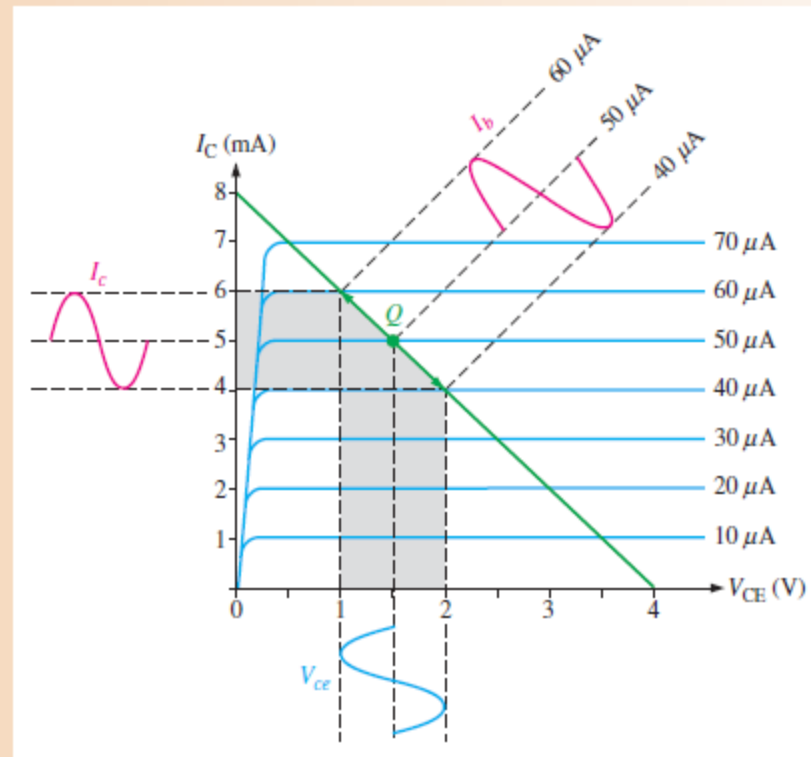


Solution Projections on the graph of Figure 6-4 show the collector current varying from 6 mA to 4 mA for a peak-to-peak value of 2 mA and the collector-to-emitter voltage varying from 1 V to 2 V for a peak-to-peak value of 1 V.

Transistor AC Models

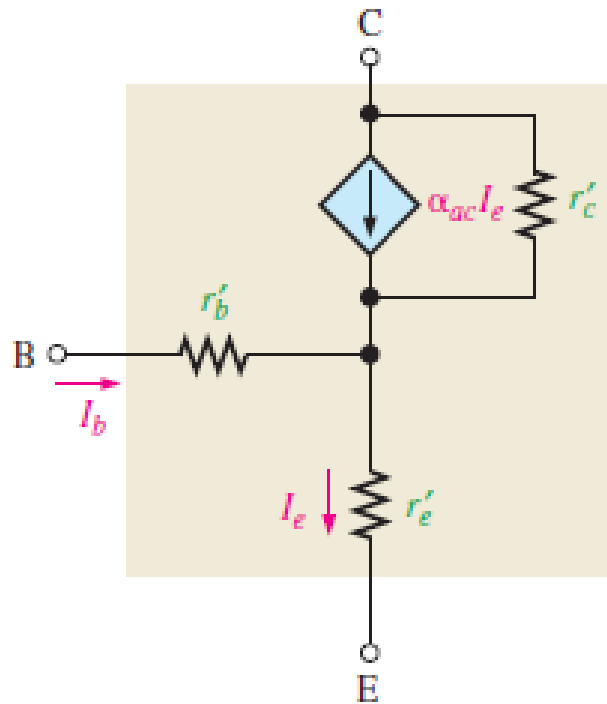- To visualize the operation of a transistor in an amplifier circuit, it is often useful to represent the device by a model circuit that uses various internal transistor parameters to represent its operation.



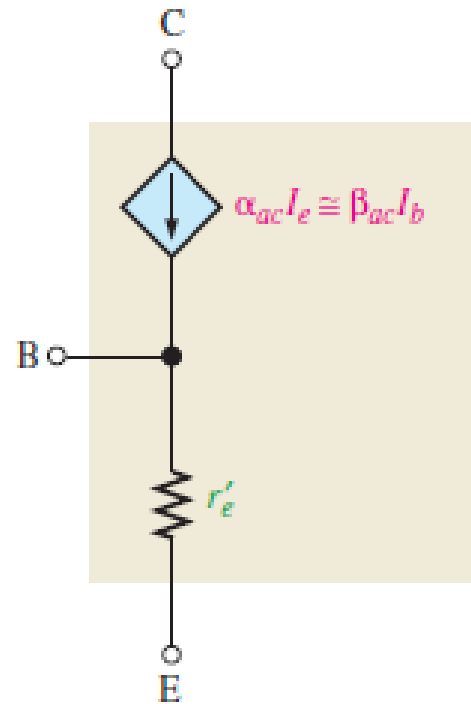(a) Generalized r -parameter model for a BJT



(b) Simplified r -parameter model for a BJT

