
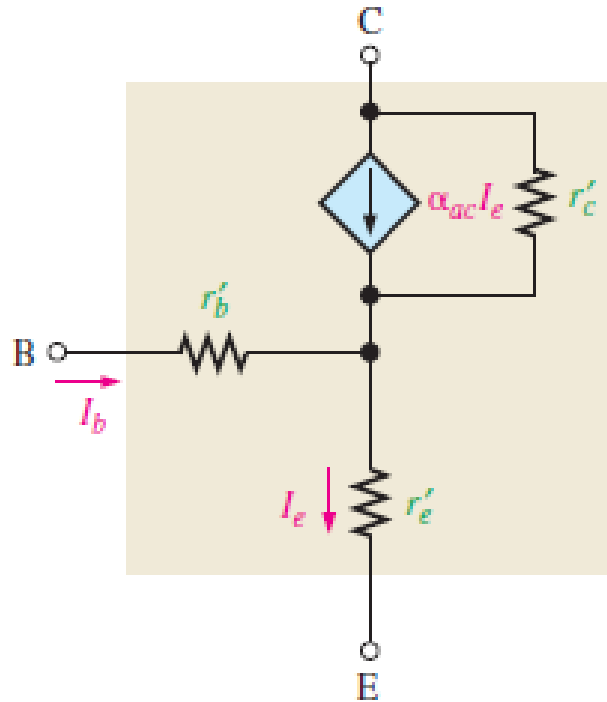


Transistor AC Models

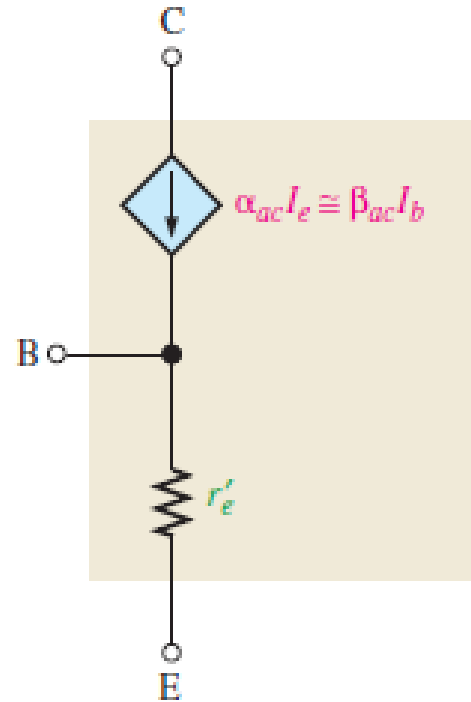
- To visualize the operation of a transistor in an amplifier circuit, it is often useful to represent the device by a model circuit that uses various internal transistor parameters to represent its operation.



(a) Generalized r -parameter model for a BJT



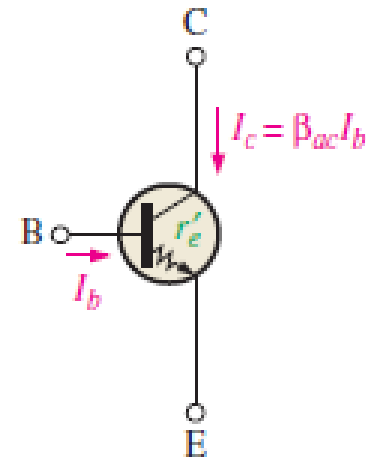(b) Simplified r -parameter model for a BJT



- Transistor models used both : **r- parameters** and **h - parameters**

r - parameters

▼ TABLE 6-1

r parameters.

r PARAMETER	DESCRIPTION
α_{ac}	ac alpha (I_c/I_e)
β_{ac}	ac beta (I_c/I_b)
r'_e	ac emitter resistance
Short << r'_b	ac base resistance
open << r'_c	ac collector resistance

(r'_b) small -> neglect -> short

(r'_c) several hunderd kilohms -> open

$$r'_e \cong \frac{25 \text{ mV}}{I_E} \quad T = 20^\circ\text{C.}$$

h - parameters

- A manufacturer's datasheet typically specifies *h* (hybrid) parameters : *h_i*, *h_r*, *h_f*, and *h_o*

Basic ac *h* parameters.

<i>h</i> PARAMETER	DESCRIPTION	CONDITION
h_i	Input impedance (resistance)	Output shorted
h_r	Voltage feedback ratio	Input open
h_f	Forward current gain	Output shorted
h_o	Output admittance (conductance)	Input open

h parameters for three amplifier configurations.

CONFIGURATION	<i>h</i> PARAMETERS
Common-Emitter	$h_{ie}, h_{re}, h_{fe}, h_{oe}$
Common-Base	$h_{ib}, h_{rb}, h_{fb}, h_{ob}$
Common-Collector	$h_{ic}, h_{rc}, h_{fc}, h_{oc}$

Relationships of *h* Parameters and *r* Parameters

$$\alpha_{ac} = h_{fb}$$


$$\beta_{ac} = h_{fe}$$

$$r'_e = \frac{h_{re}}{h_{oe}}$$


$$r'_c = \frac{h_{re} + 1}{h_{oe}}$$

$$r'_b = h_{ie} - \frac{h_{re}}{h_{oe}}(1 + h_{fe})$$

Comparison between β_{ac} and β_{DC}

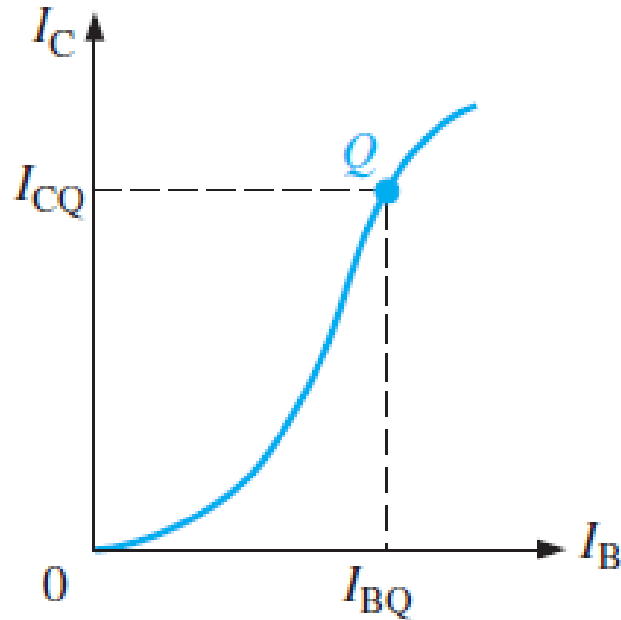

(a) $\beta_{DC} = I_C/I_B$ at Q-point

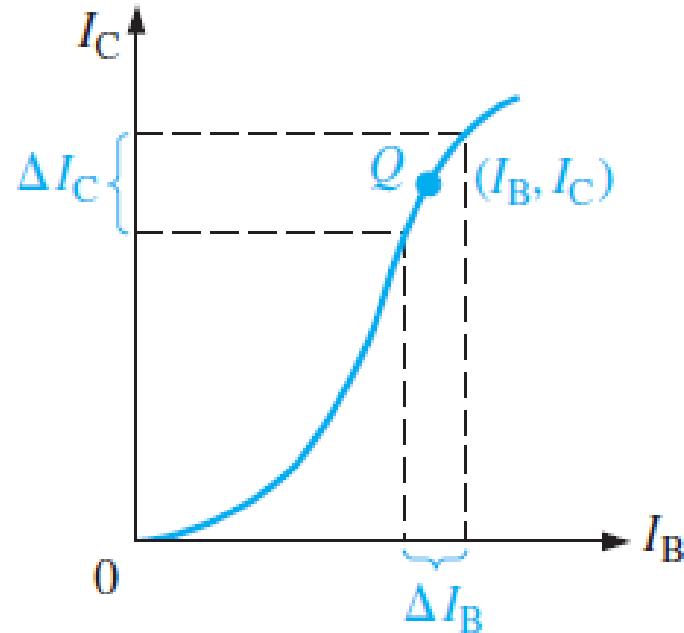


(b) $\beta_{ac} = \Delta I_C/\Delta I_B$

□ For a typical transistor, a graph of I_C versus I_B is nonlinear

□ If you pick a Q-point on the curve and cause the base current to vary an amount ΔI_B then the collector current will vary an amount ΔI_C


Three Amplifier Configurations

The common-emitter

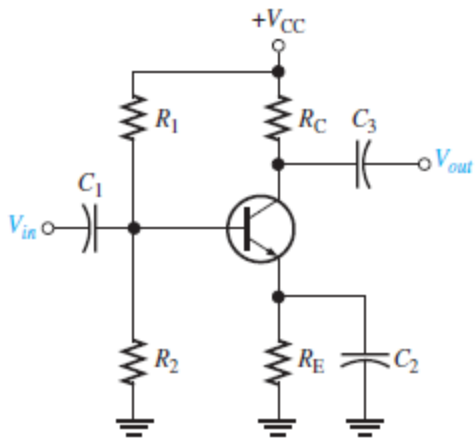


- Input is at the base
- Output is at the collector.
- Emitter is at ac ground
- High voltage gain
- High current gain
- Phase inversion

The common-base

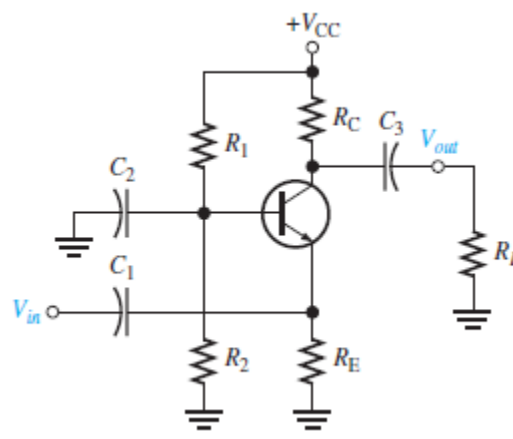

- Input is at the emitter
- Output is at the collector
- Base is at ac ground.
- High voltage gain
- Low input resistance

The common-collector

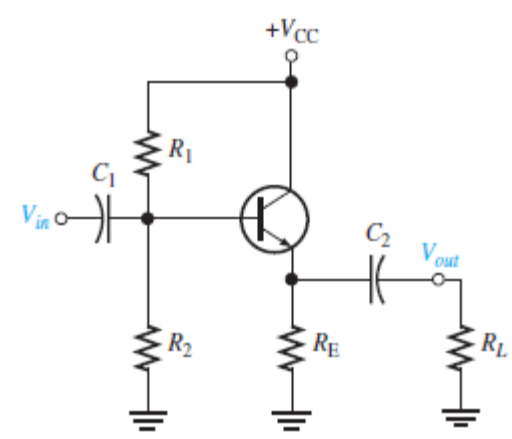


- Input is at the Base
- Output is at the emitter
- Collectors at ac ground.
- Voltage gain ~ 1
- Called also Voltage Follower
- No phase inversion

The Common-Emitter Amplifier

- CE amplifiers exhibit **high voltage gain** and **high current gain**.

▲ FIGURE 6-8

A common-emitter amplifier.

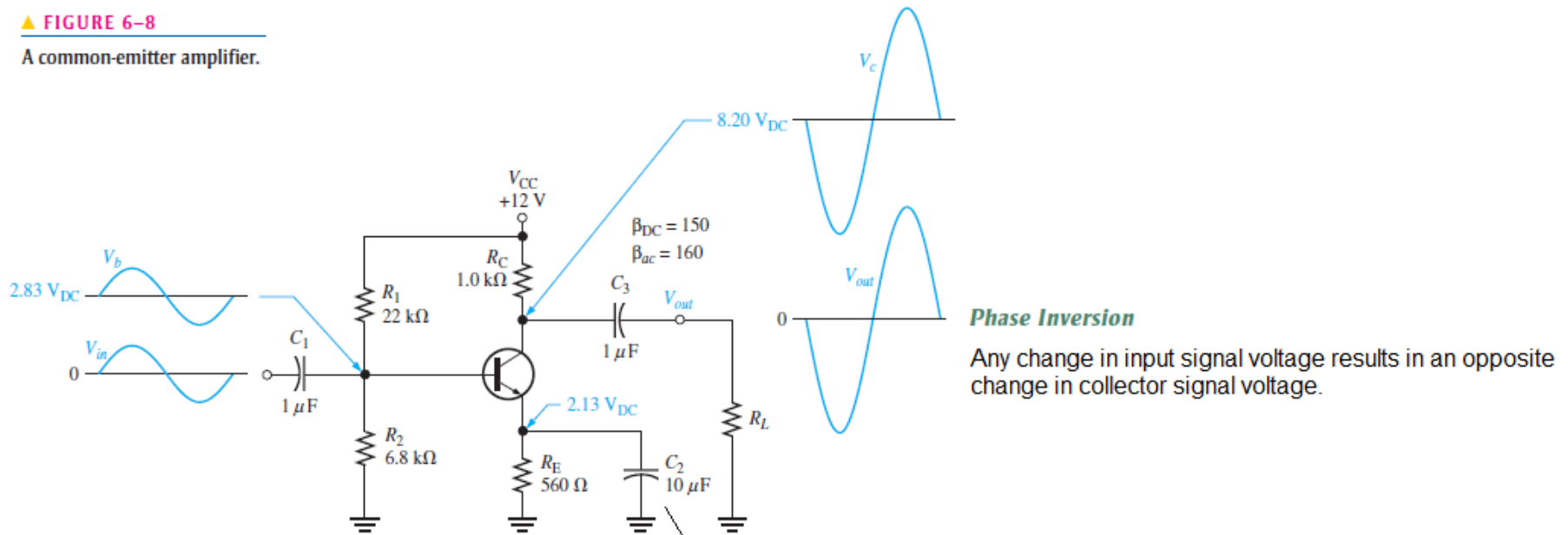

Phase Inversion

Any change in input signal voltage results in an opposite change in collector signal voltage.

C_1, C_3 : coupling capacitors

C_2 : bypass capacitor

There is no signal at the emitter because the bypass capacitor effectively shorts the emitter to ground at the signal frequency.

emitter : common to both input and output signals

The Common-Emitter Amplifier

DC Analysis

- All capacitors - OPEN - due to dc bias.
- Theveninizing the bias circuit and apply KVL to the base emitter circuit

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(6.8 \text{ k}\Omega)(22 \text{ k}\Omega)}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} = 5.19 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{6.8 \text{ k}\Omega}{6.8 \text{ k}\Omega + 22 \text{ k}\Omega} \right) 12 \text{ V} = 2.83 \text{ V}$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{2.83 \text{ V} - 0.7 \text{ V}}{560 \Omega + 34.6 \Omega} = 3.58 \text{ mA}$$

$$I_C \cong I_E = 3.58 \text{ mA}$$


$$V_E = I_E R_E = (3.58 \text{ mA})(560 \Omega) = 2 \text{ V}$$

$$V_B = V_E + 0.7 \text{ V} = 2.7 \text{ V}$$

$$V_C = V_{CC} - I_C R_C = 12 \text{ V} - (3.58 \text{ mA})(1.0 \text{ k}\Omega) = 8.42 \text{ V}$$

$$V_{CE} = V_C - V_E = 8.42 \text{ V} - 2 \text{ V} = 6.42 \text{ V}$$

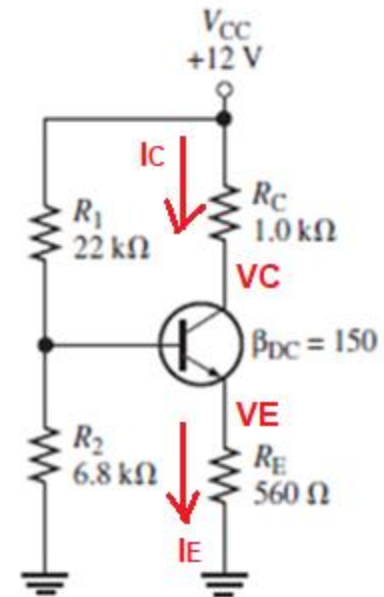Q-Point: ($V_{CEQ} = 6.42 \text{ V}$, $I_{CQ} = 3.58 \text{ mA}$)



▲ **FIGURE 6-9**

DC equivalent circuit for the amplifier in Figure 6-8.