

Exp. No. 6: Kirchhoff's Rules

Objective:

To verify *Kirchhoff's rules* applied to *a two-loop circuit*.

Equipment:

Three carbon resistors ($R_1 = 200$, $R_2 = 300$, and $R_3 = 120$ ohms), two-terminal dc power supply (**5 V and 10 V**), multi-meters, a calculator, and a few connecting wires with alligator clips

Theory:

To solve for unknown currents in multi-loop circuits, we use Kirchhoff's *rules*. There are two rules:

(a) Kirchhoff's Junction Rule or current rule

"The sum of currents going toward a junction is equal to the sum of currents leaving that junction." In other words,

$$\sum \mathbf{I}_{\text{in}} = \sum \mathbf{I}_{\text{out}} \quad (\text{Due to the Conservation of charge})$$

the algebraic sum of currents to and away from a junction is zero.

A junction is a point of connection of 3 or more wires. At the Junction *c* in Fig. 1. I_1 and I_3 leaves Junction *c* and is given a (-) sign. I_2 go toward Junction *c*, it is given (+) sign.

$$\mathbf{I}_3 = \mathbf{I}_1 + \mathbf{I}_2 \quad (1)$$


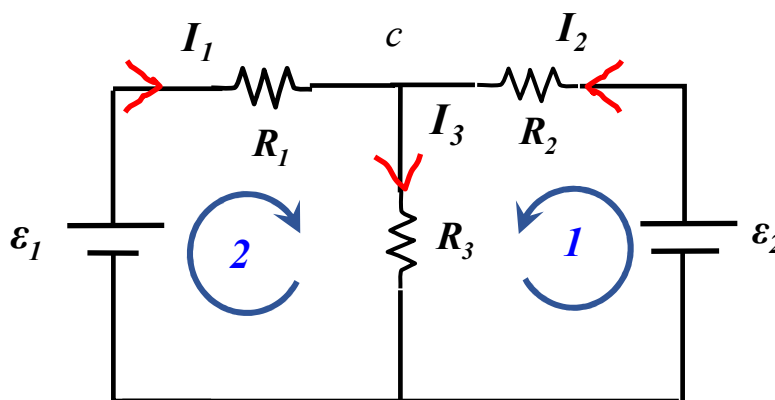


Fig.1: Two-loop Circuit

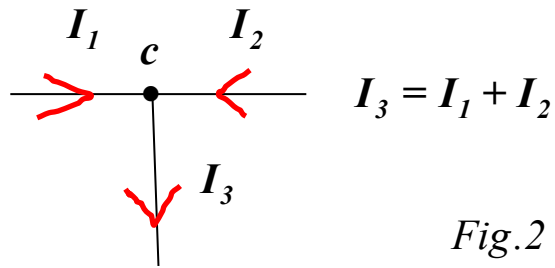(b) Kirchhoff's Loop

Rule

This rule states that **"the sum of voltage jumps and drops across the elements of any closed loop is zero."**



Kirchhoff's Current Rule at the Junction c

$$\sum_{\text{closed loop}} \Delta V = V_{cc} \quad (\text{Conservation of energy})$$

Voltages due to the battery V , we write the voltage across that resistor as the product RI .

1) Rule for Batteries: As we trace a closed loop in either direction, if we go from (-) to (+) **across a battery**, it is a voltage jump and we write $+\mathcal{E}$ for that battery. If we happen to go from (+) to (-) of it, it is a voltage drop and we write it as $-\mathcal{E}$.

2) Rule for Resistors: If we trace in the direction of I , we write $-RI$ (a voltage drop) across resistor R , and if our tracing direction opposes I , we write $+RI$ (a voltage jump) across resistor R .

"**voltage jump**" means **higher voltage**, then write the product RI with a (+) sign. **If our trace direction agrees with the assumed current I** , it is **like losing potential** and the product RI deserves a (-) sign, "**voltage drop**".

For the circuit shown in Figure 1:

For loop (1) $\sum_c V = 0 \quad \mathcal{E}_1 - I_1 R_1 - I_3 R_3 = 0$

$$5 - 200I_1 - 120I_3 = 0 \quad \text{or} \quad 5 = 200I_1 + 120I_3 \quad (1-1)$$

For loop (2) $\mathcal{E}_2 - I_2R_2 - I_3R_3=0$

$$10 - 300I_2 - 120I_3 = 0 \quad \text{or} \quad 10 = 300I_2 + 120I_3 \quad (2-1)$$

$$10 = 300(I_3 - I_1) + 120I_3 \quad 10 = -300I_1 + 420I_3 \quad (2-2)$$

$$I_1 = (5 - 120I_3)/200 \quad (1-2)$$

$$I_2 = (10 - 120I_3)/300 \quad (2-3)$$

$$I_3 = (5 - 120I_3)/200 + (10 - 120I_3)/300$$

$$= 0.025 - 0.6I_3 + 0.033 - 0.4I_3$$

$$\rightarrow 0.058 = 2I_3 \quad \rightarrow I_3 = 0.029 \text{ A} = 29 \text{ mA}$$

$$I_2 = 0.33 - 0.4I_3 \quad I_1 = 0.025 - 0.4I_3$$

Procedure

Construct the two-loop circuit as shown in **Fig. 3**.

Chose R_1 , R_2 , and R_3 . Let $\mathcal{E}_1 = 5V$ and $\mathcal{E}_2 = 5V$.

Measure the **3 different currents** using the ammeter.

Measure the output voltage of batteries and across each resistor record.

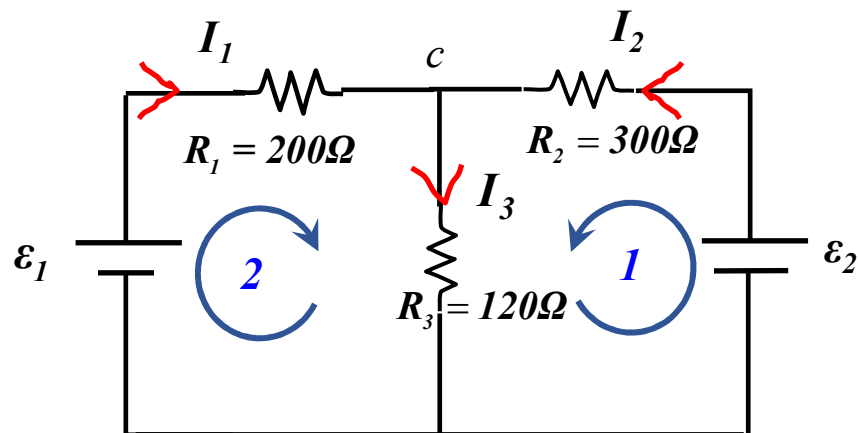


Fig.3: Two-loop Circuit

Experiment No. 6 Kirchhoff's Rules

Name: Day and Date:

Student's No.: Sec:

Partners Names:

Data: $\epsilon_1 = 5V$, $\epsilon_2 = 10 V$

Resistors in Ω	R ₁	R ₂	R ₃
	200 Ω	300 Ω	120 Ω

Currents (A)	I ₁	I ₂	I ₃
Calculated			
Measured via Ammeter			

Q1. Use the **measured values** of currents to prove that $I_3 = I_1 + I_2$.

Voltages (V)	V ₁	V ₂	V ₃
Calculated IR			
Measured via Voltmeter			

Q2. Use the measured values of voltages to prove the closed loop rule $\sum_C \Delta V = 0$. (e.g. is $\epsilon_1 - V_1 - V_3 = 0$ **loop1**) and same for **loop2**.

Q3. In the **Fig.3**. Find the reading of ammeters A₁ and A₂.

