

## Experiment No. 7 AC-Bridge Meter

### Objective:

- (1) To measure unknown capacitance.
- (2) To find out the total impedance for parallel or serial connections.

### Equipment:

- (1) Oscilloscope CRT.
- (2) AC power supply.
- (3) Unknown capacitors.
- (4) The Potentiometer.

### Theory


Measuring a complex impedance with an alternating current (A. C.) is to use some of the types of AC-Bridges, which is an extension of the DC-Wheatstone Bridge.

A generalized diagram for the AC Wheatstone Bridge is shown in Fig. 7.1.

When the voltage across the detector is zero (Detector reads zero), the voltages at both sides of the bridge must be the same. This means that both sides have voltages of the same values for amplitudes and phases. When this balance condition is satisfied (Detector reads zero) it involves two balancing conditions for real and imaginary parts of the complex impedance which must be satisfied simultaneously. Therefore one can use two variable impedances (say for example two capacitances) which can be varied independently the detector reads a minimum value.

When the minimum is achieved, the balance condition for an AC bridge as shown in Fig. 1 is given by

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

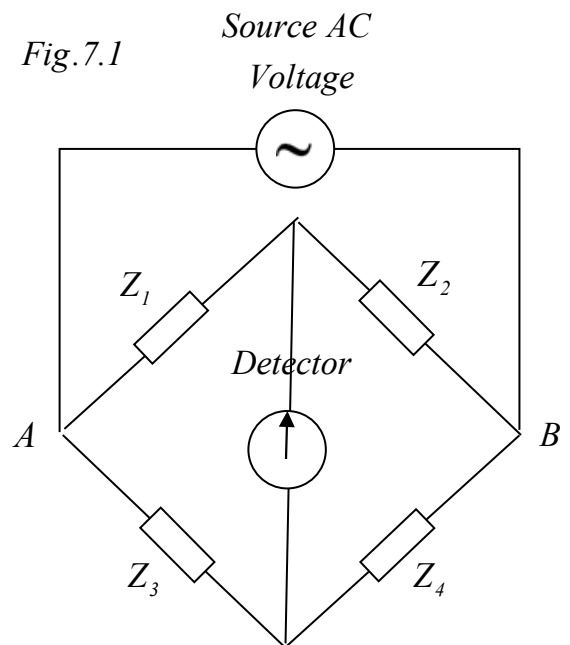

With this equation both balance conditions for real and imaginary parts of the impedances are satisfied simultaneously.

In particular, the AC bridge is used to measure capacitance and the same general balance equation given above can be applied when a balance condition is achieved.

Resistances and capacitances are variable impedances and can be used to reach a balance condition to determine the value of unknown capacitance. This general bridge is shown in fig. 7.2. The unknown capacitor (or condenser)  $C_x$  is represented by the series grouping of  $C_x$  and the standard capacitor  $C_s$  on the same arm. The capacitance value  $C_s$  should be known and well defined. The value of the resistances  $R_1$  and  $R_2$  are variable since they are determined by the two lengths  $L_{AC}$  and  $L_{CB}$  of the wire resistor (cross sectional area is same) when the balance condition is reached,

The Balance condition can be expressed as follows:

$$V_D - V_C = 0$$

For the left branch

$$V_{AD} + V_{DC} + V_{CA} = 0$$

$$V_{AD} + V_{CA} = 0,$$

$$V_{AD} = -V_{CA} = V_{AC}$$

$$I_1 R_{AC} = I_2 Z_x$$

Same for the right branch  $V_{BD} = V_{BC}$

$$I_1 R_{CB} = I_2 Z_s \quad \Rightarrow \quad \frac{I_1 R_{AC}}{I_1 R_{CB}} = \frac{I_2 Z_x}{I_2 Z_s} \quad \text{and} \quad \Rightarrow \quad \frac{R_{AC}}{R_{CB}} = \frac{Z_x}{Z_s}$$

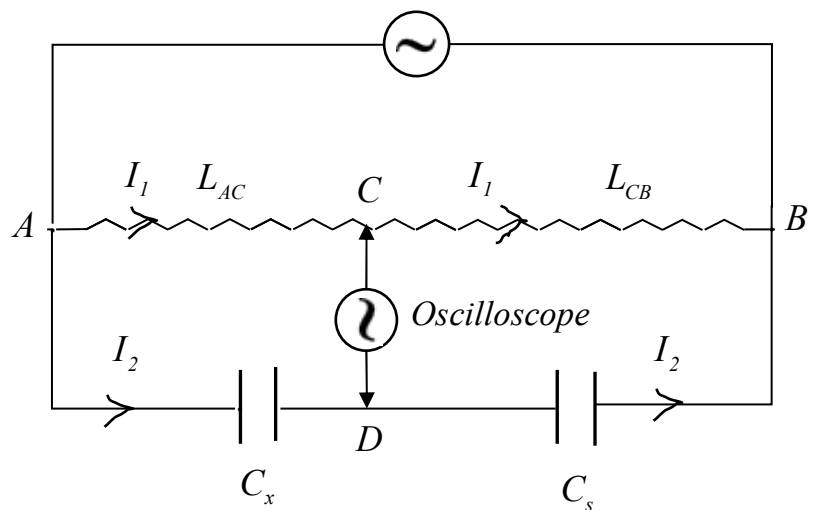


Fig.7.2

$$\Rightarrow \frac{\rho \frac{L_{AC}}{A}}{\rho \frac{L_{CB}}{A}} = \frac{j / \omega C_x}{j / \omega C_s}, \quad \Rightarrow \frac{L_{AC}}{L_{CB}} = \frac{C_s}{C_x} \quad \Rightarrow \quad C_x L_{AC} = C_s L_{CB}$$

$$\boxed{C_x = C_s \frac{L_{CB}}{L_{AC}}}$$

or

$$\boxed{C_s = C_x \frac{L_{AC}}{L_{CB}}}$$

Which determine the unknown capacitance  $C_x$  at the balance condition (which appears as a minimum amplitude at the oscilloscope screen)

## PROCEDURE

- (1) Use the experimental arrangement shown in Figure 7.2 to determine  $C_{x1}$ .
- (2) Adjust the standard capacitance  $C_s = 68 \mu\text{F}$ .
- (3) Record the distance AC when the balance condition is satisfied (signal on the oscilloscope shows minimum zero amplitude)
- (4) Repeat step 3 for  $C_s = 100, 470,$  and  $1000 \mu\text{F}$  and 4 ohms.
- (5) Repeat the procedure for another unknown  $C_{x2}$ .
- (6) Repeat the same measurements for series and parallel capacitance for  $C_{x1}$  and  $C_{x2}$ .
- (7) Tabulate your results in table 4.1.
- (8) Plot on the same graph  $C_s$  versus  $L_{AC} / L_{CB}$ .
- (9) Find the slope for each graph, this will give the value of the corresponding  $C_x$ .

## Experiment No. 7 AC bridge meter

Name: ..... Day and Date: .....

Student's No.: ..... Sec: .....

Partners Names: .....

### Data and Calculation:

C <sub>x1</sub> true value = (            ) μF				C <sub>x2</sub> true value = (            ) μF			
C <sub>s</sub> (μF)	L <sub>AC</sub> (cm)	L <sub>CD</sub> (cm)	$\frac{L_{AC}}{L_{CB}}$	C <sub>s</sub> (μF)	L <sub>AC</sub> (cm)	L <sub>CB</sub> (cm)	$\frac{L_{AC}}{L_{CB}}$
68							
100							
470							
1000							
S <sub>1</sub> = C <sub>x1</sub> =				S <sub>2</sub> = C <sub>x2</sub> =			

C <sub>xs</sub> true value = (            ) μF				C <sub>xp</sub> true value = (            ) μF			
C <sub>s</sub> (μF)	L <sub>AC</sub> (cm)	L <sub>CB</sub> (cm)	$\frac{L_{AC}}{L_{CB}}$	C <sub>s</sub> (μF)	L <sub>AC</sub> (cm)	L <sub>CB</sub> (cm)	$\frac{L_{AC}}{L_{CB}}$
68							
100							
470							
1000							
S <sub>s</sub> = C <sub>xs</sub> =				S <sub>p</sub> = C <sub>xp</sub> =			

**Plot C<sub>s</sub> vs. L<sub>AC</sub> / L<sub>CB</sub> on the same graph below for each values and determine the slope of each line.**

**(1) From your graph determine each value of C<sub>x</sub> = S.**

**(2) Find the percentage error for each value of C<sub>x</sub> for:**

**C<sub>x1</sub>:**

**C<sub>x2</sub>:**

**C<sub>xs</sub>:**

**C<sub>xp</sub>:**

**(3) Show from your values of slopes that C<sub>xp</sub> = C<sub>x1</sub> + C<sub>x2</sub> and  $\frac{1}{C_{xs}} = \frac{1}{C_{x1}} + \frac{1}{C_{x2}}$ .**

