



Question 1 : (8 marks)

Using nodal analysis find power of 28 v voltage source

$V_1 = -28$ *ans 1*

$V_3 = 4$ *ans 1*

KCL at Node 2 *ans 1*

$\frac{V_2}{8} + \frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{4} = 0$

$\frac{V_2}{8} + \frac{V_2}{10} - \frac{V_1}{10} + \frac{V_2}{4} - \frac{V_3}{4} = 0$

$V_2 \left[\frac{1}{8} + \frac{1}{10} + \frac{1}{4} \right] = +\frac{V_1}{10} + \frac{V_3}{4}$

$V_2 \left[\frac{5}{40} + \frac{4}{40} + \frac{10}{40} \right] = \frac{-28}{10} + \frac{4}{4}$

$V_2 \left[\frac{19}{40} \right] = -2.8 + 1$ *ans 2*

$V_2 \times 19 = -1.8 \times 40$

$V_2 \times 19 = -72$


$V_2 = \frac{-72}{19} = -3.79 \text{ volt}$

power of 28 volt

$P_{28} = -(28)(I_s)$ *ans 1*

KCL at 1 *ans 1*

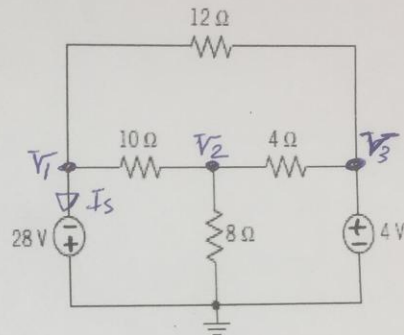$I_s + \frac{V_1 - V_2}{10} + \frac{V_1 - V_3}{12} = 0$



$I_s = - \left[\frac{-28 + 3.79}{10} + \frac{-28 - 4}{12} \right]$

$I_s = - \left[-2.421 + -2.667 \right]$ *ans 1*

$I_s = - \left[-5.088 \right] = 5.088 \text{ A}$

$P_{28} = -(28)(5.088) = -142.46 \text{ watt}$


Question 2: (8 marks)

Find power of dependent source, using mesh analysis

$I_1 = 4(I_2 + 1)$
 $I_1 = 4I_2 + 4$
 $-I_1 + 4I_2 + 4 = 0$

$I_1 = 4I_a$
 $I_3 = -1A$
 $I_a = I_2 - I_3$
 $I_a = I_2 + 1$

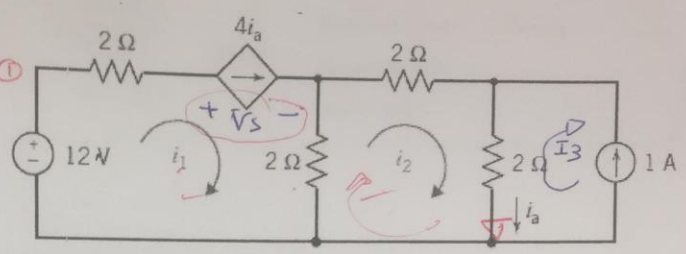$I_1 = 4I_a$ --- ①
 $I_3 = -1A$ --- ②
 $I_a = I_2 - I_3 = I_2 + 1$
 $I_1 = 4(I_2 + 1)$
 $I_1 = 4I_2 + 4$ --- ③



KVL at mesh 2

$2(I_2 - I_1) + 2I_2 + 2(I_2 - I_3) = 0$
 $-2I_1 + 6I_2 - 2I_3 = 0$
 $-2I_1 + 6I_2 + 2 = 0$ --- ③

sub ② in ③

$-2(4I_2 + 4) + 6I_2 + 2 = 0$
 $-8I_2 - 8 + 6I_2 + 2 = 0$
 $-2I_2 - 6 = 0$
 $-2I_2 = 6$
 $I_2 = -\frac{6}{2} = -3A$

$I_1 = 4I_a$
 or $I_1 = 4I_2 + 4$
 $I_a = I_2 + 1 = -3 + 1 = -2A$
 $I_1 = 4(-2) + 4 = -8 + 4 = -4A$

Power of dependent source

$P_{dep} = (V_s)(4I_a)$

KVL at mesh 1

$-12 + 2I_1 + V_s + 2(I_1 - I_2) = 0$
 $-12 + 2(-8) + V_s + 2(-8 + 3) = 0$
 $-12 - 16 + V_s + 2(-5) = 0$
 $-28 + V_s - 10 = 0$
 $V_s = 28 + 10 = 38 \text{ volt}$
 $P_{dep} = (38)(4)(-2) = -304$

Question 3: (9 marks)

Using nodal analysis find power of element? check your results?

From super node

$$\bar{V}_2 - \bar{V}_1 = 16 \quad \text{①} \rightarrow \bar{V}_2 = 16 + \bar{V}_1$$

KCL at super node

$$\frac{\bar{V}_1 - 0}{20} + \frac{\bar{V}_2 - 0}{40} = 4 \quad \text{②}$$

$$2\bar{V}_1 + \bar{V}_2 = 160$$

$$2\bar{V}_1 + 16 + \bar{V}_1 = 160$$

$$3\bar{V}_1 = 160 - 16$$

$$3\bar{V}_1 = 144$$

$$\bar{V}_1 = \frac{144}{3} = 48 \text{ volt}$$

$$\bar{V}_2 = 16 + 48 = 64 \text{ volt}$$


$$\boxed{\begin{array}{l} \bar{V}_1 = 48 \text{ V} \\ \bar{V}_2 = 64 \text{ V} \end{array}}$$

$$P_{20\Omega} = \frac{\bar{V}_1^2}{20} = \frac{48^2}{20} = 115.2 \text{ W}$$

$$P_{40\Omega} = \frac{\bar{V}_2^2}{40} = \frac{64^2}{40} = 102.4 \text{ W}$$

$$P_{4A} = -4 \times \bar{V}_2 = -4 \times 64 = -256 \text{ W}$$
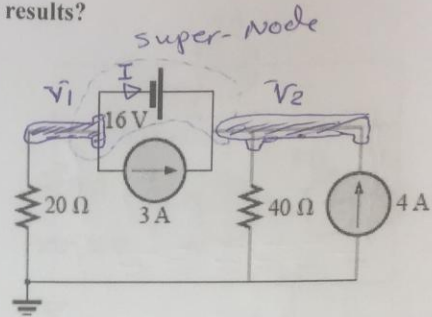
$$P_{3A} = (3)(\bar{V}_1 - \bar{V}_2) = (3)(48 - 64) \\ = 3 \times -16 = -48 \text{ W}$$



$$P_{16V} = -16 \times I$$

KCL at ①

$$3 + \frac{\bar{V}_1}{20} + I = 0$$

$$I = -\left(3 + \frac{\bar{V}_1}{20}\right)$$

$$I = -\left(3 + \frac{48}{20}\right) = -5.4 \text{ A}$$

$$P_{16V} = -16 \times -5.4 = 86.4 \text{ W}$$

$$\sum P_i = 0 \quad \text{check}$$

$$= 115.2 + 102.4 - 256 - 48 + 86.4 \\ = \text{Zero}$$

$$\bar{V}_1 = 48 \text{ V} \quad \text{--- ①}$$

$$\bar{V}_2 = 64 \text{ V} \quad \text{--- ①}$$

$$P_{20\Omega} = 115.2 \text{ W} \quad \text{--- ①}$$

$$P_{40\Omega} = 102.4 \text{ W} \quad \text{--- ①}$$

$$P_{4A} = -256 \text{ W} \quad \text{--- ①}$$

$$P_{3A} = -48 \text{ W} \quad \text{--- ①}$$

$$P_{16V} = 86.4 \text{ W} \quad \text{--- ①}$$

End of Questions

Question 2: (8 marks)

Using mesh analysis find power of 3 A current source

$I_3 = 8 \text{ A}$ (1)

From super-mesh

$I_2 - I_1 = 3 \rightarrow I_2 = 3 + I_1$ (1)

KVL ab super mesh

$-20 + 4I_1 + 6(I_1 - I_3) + 8(I_2 - I_3) + 1 \cdot I_2 = 0$

$10I_1 + 9I_2 - 14I_3 = 20$ (1)

$10I_1 + 9(3 + I_1) - 14 \times 8 = 20$

$19I_1 + 27 - 112 = 20$

$19I_1 - 85 = 20$

$19I_1 = 20 + 85$


$19I_1 = 105$

$I_1 = \frac{105}{19} = 5.526 \text{ A}$

$I_2 = 3 + 5.526 = 8.526 \text{ A}$

$I_1 = 5.526 \text{ A}$	(1)
$I_2 = 8.526 \text{ A}$	(1)
$I_3 = 8 \text{ A}$	(1)

$P_{3A} = (3)(V_3)$

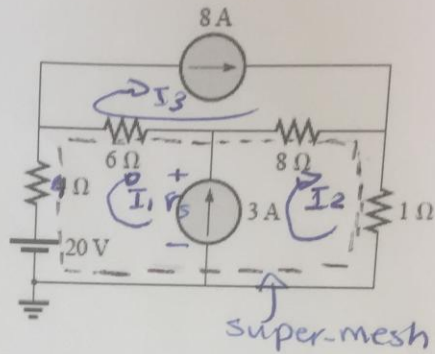

KVL ab loop 1

$-20 + 4I_1 + 6(I_1 - I_3) + V_3 = 0$

$-20 + 10I_1 - 6I_3 + V_3 = 0$

$-20 + 10(5.526) - 6 \times 8 + V_3 = 0$

$-20 + 55.26 - 48 + V_3 = 0$

$-12.74 + V_3 = 0$ (1)

$V_3 = 12.74 \text{ volt}$ (1)

$P_{3A} = -3 \times 12.74 = -38.22 \text{ W}$