



Question 1 : (6 marks)

Find values of R and b

$$v_1 = 4, \quad v_2 = 0, \quad v_3 = -6$$

$$i_a = \frac{v_2 - v_1}{40} = \frac{0 - 4}{40} = -0.1 \text{ A}$$

KCL at 2

$$i_a + b i_a + \frac{v_2 - v_3}{20} = 0$$

$$-0.1 + b(-0.1) + \frac{0 + 6}{20} = 0$$

$$-0.1 + b(-0.1) + 0.3 = 0$$

$$-0.1b + 0.2 = 0$$

$$-0.1b = -0.2$$

$$b = \frac{-0.2}{-0.1} = 2$$

KCL at G

$$\frac{v_3}{R} + \frac{v_1}{10} + b i_a = 0$$

$$\frac{-6}{R} + \frac{4}{10} + 2(-0.1) = 0$$


$$\frac{-6}{R} + 0.4 - 0.2 = 0$$

$$\frac{-6}{R} + 0.2 = 0$$


$$\frac{-6}{R} = -0.2$$

$$6 = 0.2 \cdot R$$

$$R = \frac{6}{0.2} = 30 \Omega$$

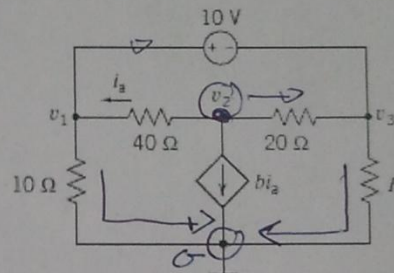

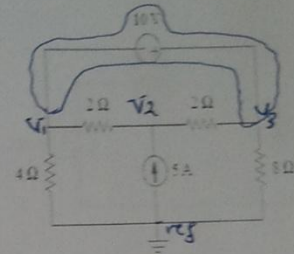Question 1: (7 marks)
Using nodal analysis, find the power of the current source



$$V_3 - V_1 = 10 \quad \text{--- ①}$$

$$\boxed{V_3 = 10 + V_1} \quad \text{--- x --- ②}$$

KCL at Node 2

$$5 = \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} \quad \text{--- ③}$$

$$10 = V_2 - V_1 + V_2 - V_3$$

$$10 = 2V_2 - V_1 - V_3$$

$$10 = 2V_2 - V_1 - (10 + V_1)$$

$$10 = 2V_2 - V_1 - 10 - V_1$$

$$20 = 2V_2 - 2V_1$$

$$20 = 2(V_2 - V_1)$$

$$10 = V_2 - V_1 \quad V_2 = 10 + V_1$$

$$\boxed{V_1 = V_2 - 10} \quad \text{--- ** --- ④}$$

KCL at super Node (1+3)

$$+ \frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_3 - V_2}{2} + \frac{V_3}{8} = 0 \quad \text{--- ⑤}$$

$$\frac{2V_1}{8} + \frac{4(V_1 - V_2)}{8} + \frac{4(V_3 - V_2)}{8} + \frac{V_3}{8} = 0$$

$$2V_1 + 4V_1 - 4V_2 + 4V_3 - 4V_2 + V_3 = 0$$

$$6V_1 - 8V_2 + 5V_3 = 0 \quad \text{--- ⑥}$$

$$6V_1 - 8(10 + V_1) + 5(10 + V_1) = 0 \quad \text{--- ⑦}$$

$$6V_1 - 80 - 8V_1 + 50 + 5V_1 = 0$$

$$3V_1 - 30 = 0$$

$$3V_1 = 30$$

$$3V_1 = 30$$

$$V_1 = \frac{30}{3} = 10 \text{ V} \quad \text{--- ⑧}$$

$$V_2 = 10 + V_1 = 10 + 10 = 20 \text{ V} \quad \text{--- ⑨}$$

$$P = -5 \times 20$$

$$= -100 \text{ W}$$

$$= -100 \text{ W} \quad \text{--- ⑩}$$

Question 4: (7 marks)
 Find nodal voltages V_1 , V_2 and V_3

$V_2 - V_1 = 8$ --- (1) a.k.a (1)

$V_3 - V_1 = 12$ --- (2) a.k.a (1)

→ $V_2 = 8 + V_1$
 → $V_3 = 12 + V_1$
 KCL at ref.

$\frac{V_1}{4} + \frac{V_2}{10} + \frac{V_3}{5} = 0$ --- (3) a.k.a (2)

→ $V_1 = -5.82$ volt --- (1) a.k.a

→ $V_2 = 2.18$ volt a.k.a (1)

→ $V_3 = 6.18$ volt a.k.a (1)

